

ESC201: INTRODUCTION TO ELECTRONICS

MODULE 3: FREQUENCY DOMAIN ANALYSIS




Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur

Frequency Response


$$V_c = V_s \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_s \frac{1}{j\omega RC + 1} H(\omega)$$

$$V_c(\omega) = V_s(\omega)H(\omega)$$
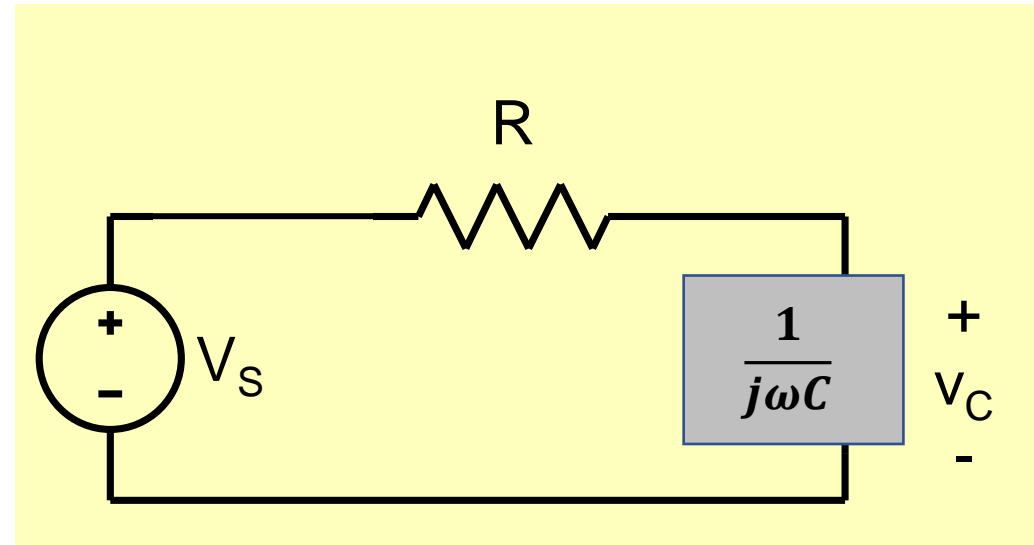
$$H(\omega) = \frac{V_c(\omega)}{V_s(\omega)}$$




Transfer function of RC

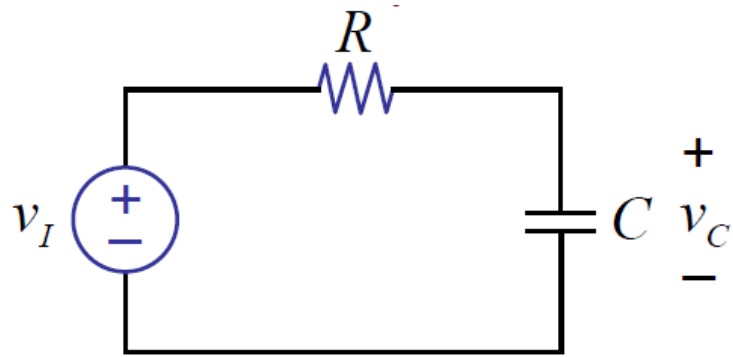

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

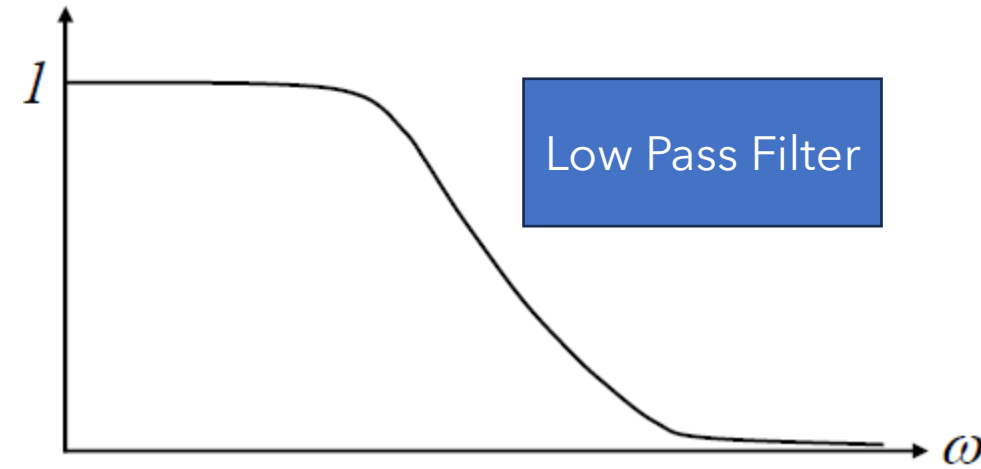

$$G = \frac{V_2}{V_1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega CR)$$


At low ω ~ 1

$\sim 0^\circ$

At high ω $\sim \frac{1}{\omega}$


$\sim -90^\circ$

Bode Plot

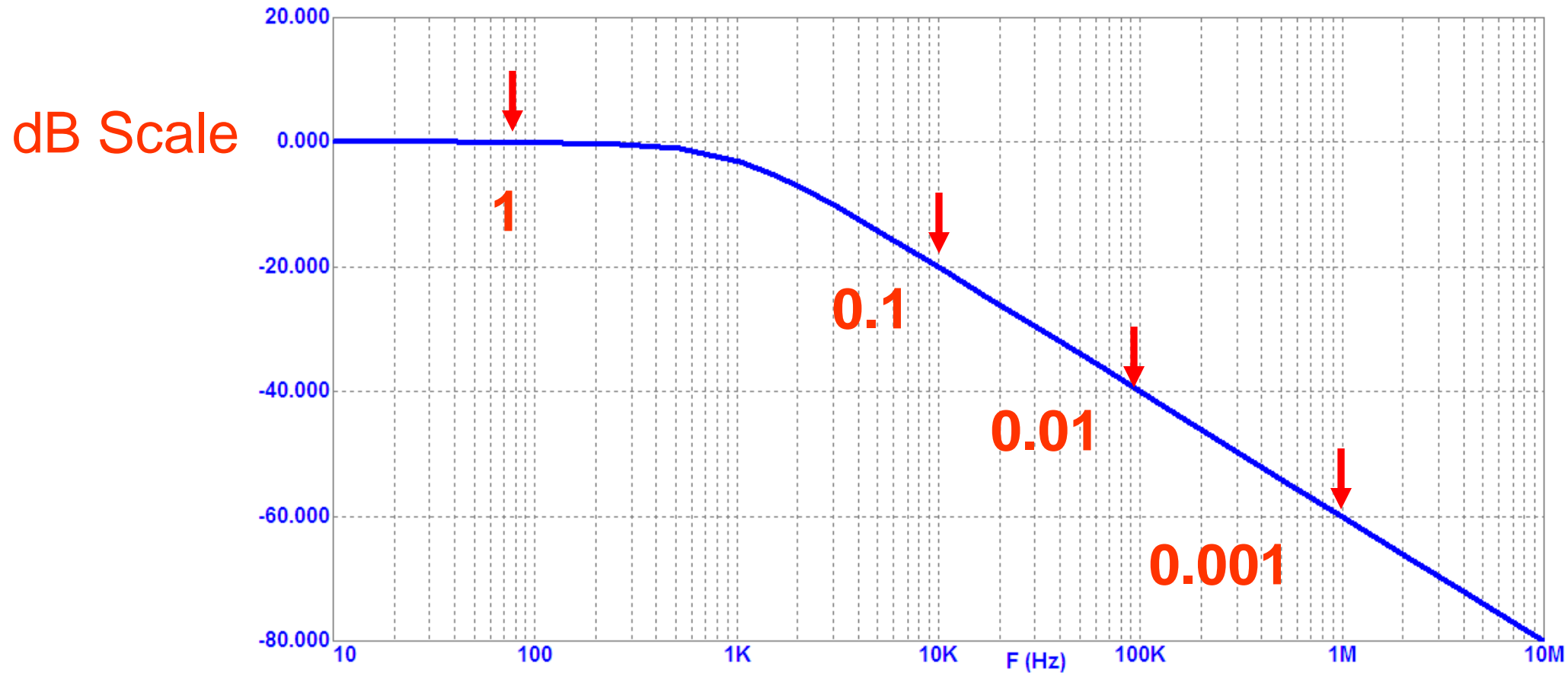

A plot of the decibel magnitude of transfer function versus frequency using a logarithmic scale for frequency is called a **Bode plot**

Plotting RC transfer function

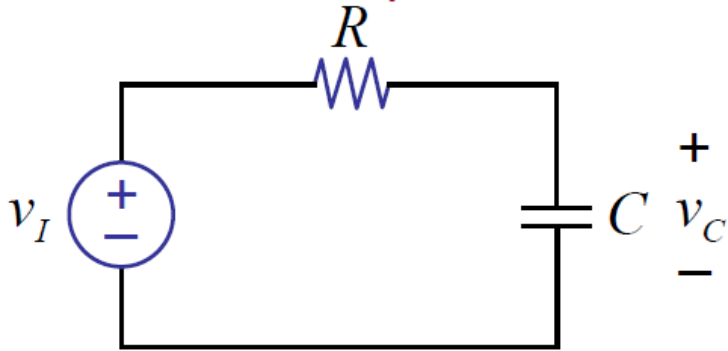

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega CR)$$

$$\omega \ll \omega_{3dB}$$

$$\omega \gg \omega_{3dB}$$


$$|H|_{dB} = -20 \log_{10} \sqrt{1 + (\omega RC)^2}$$

$$\omega = \frac{1}{RC} \quad \omega_{dB} \quad \Rightarrow \quad |H(j\omega)| = \frac{1}{\sqrt{1 + (1)^2}} = \frac{1}{\sqrt{2}} = -3dB$$

$$|H|_{dB} = -20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2}$$

$$|H|_{dB} \approx -20 \log_{10}(1) = 0$$

$$|H|_{dB} \approx -20 \log_{10} \left(\frac{\omega}{\omega_{3dB}} \right)$$

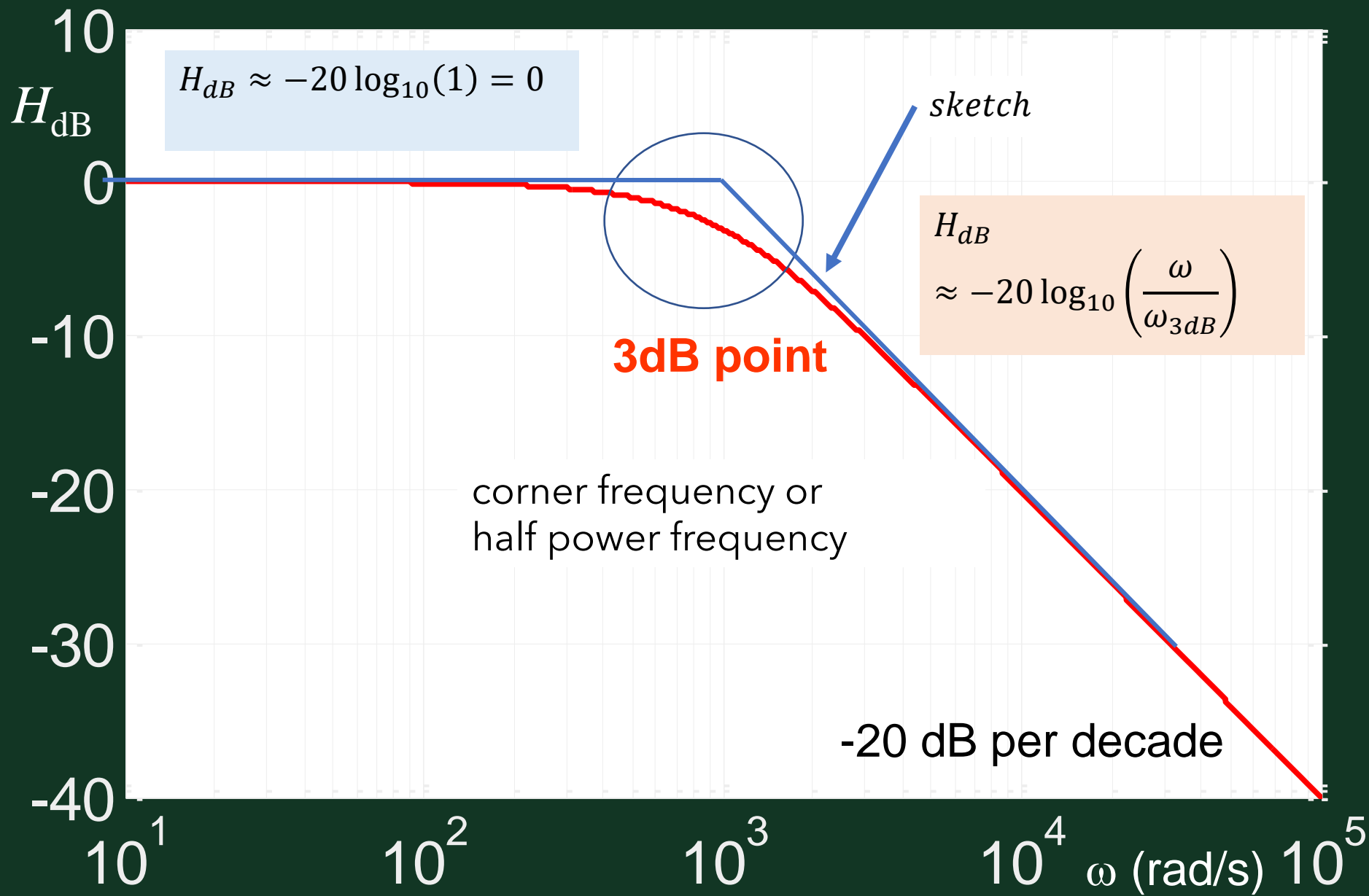

$$H_{dB} = -20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_{3dB}} \right)^2}$$

$$\omega_{3dB} = \frac{1}{RC} = 10^3$$

ω	H_{dB}
ω_{3dB}	0
$10 \omega_{3dB}$	-20
$100 \omega_{3dB}$	-40

20dB/ decade
decrease



$$\sim H \propto \frac{c}{\omega}$$

$$H(dB) \propto -20 \log \omega/c$$

Relationship between time constant and 3dB frequency

$$H_{dB} = -20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_{3dB}} \right)^2}$$

$$\omega_{3dB} = \frac{1}{RC}$$

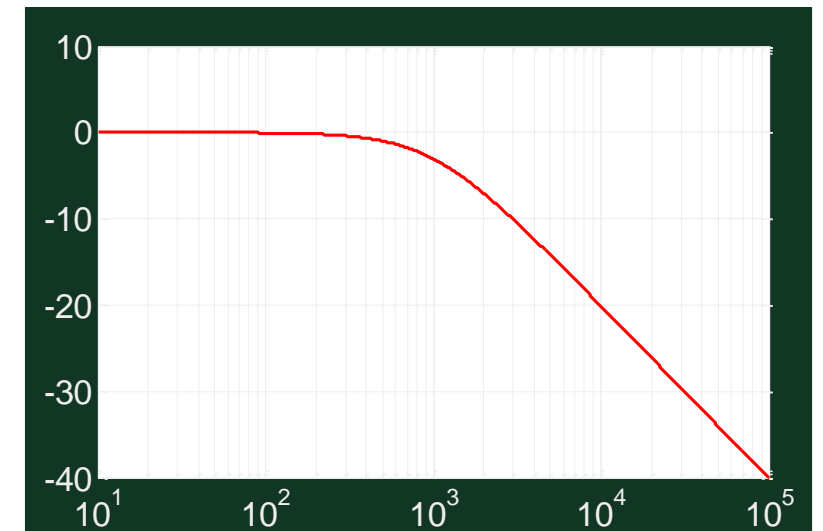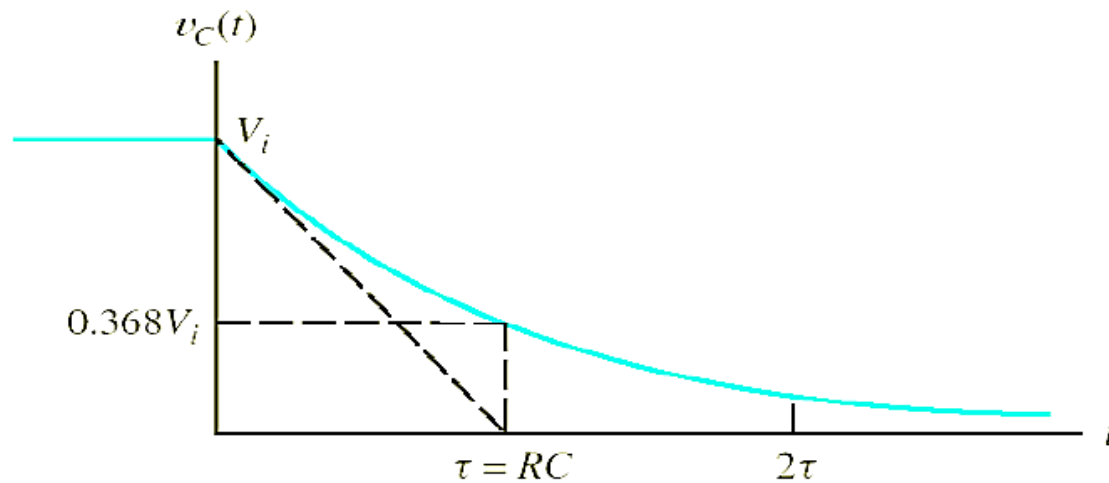


Phase plot

$$\phi(\omega) = -\tan^{-1}(\omega/\omega_o)$$

$$\omega \rightarrow 0, \phi \rightarrow 0 \quad \omega \rightarrow \infty, \phi \rightarrow -90^\circ$$
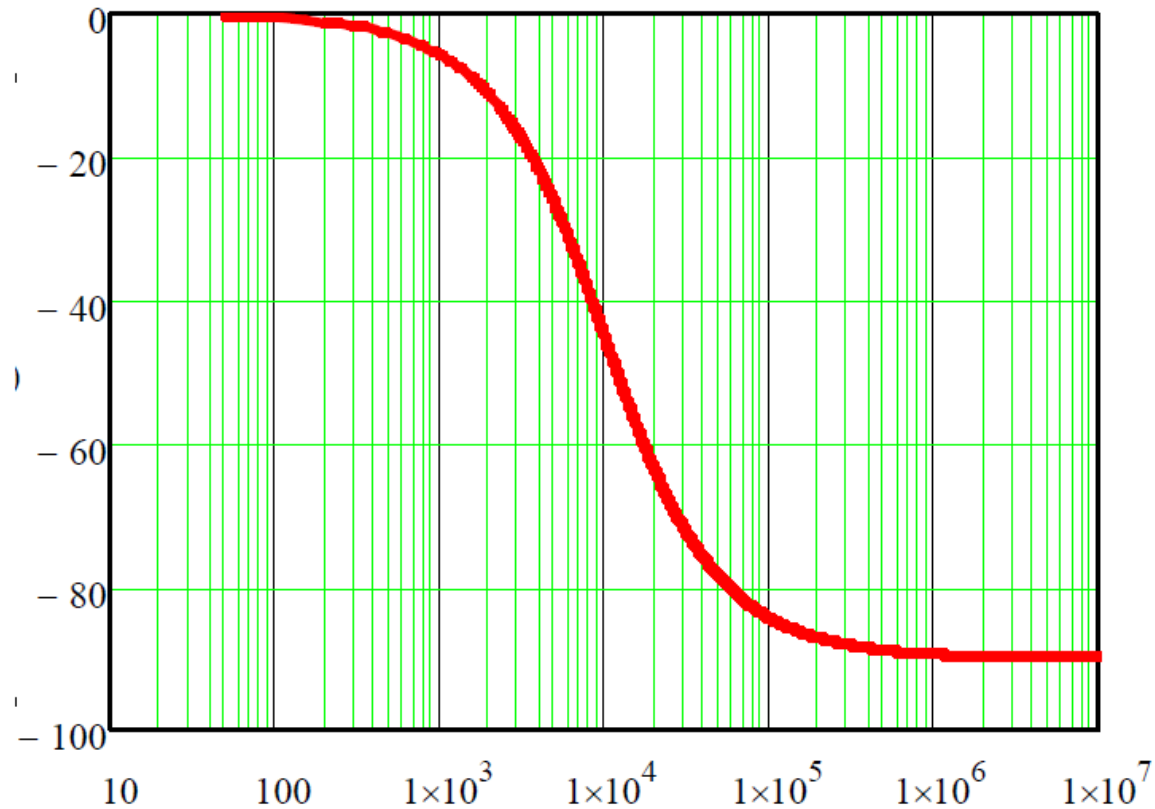
$$\omega = \omega_o, \phi \rightarrow -45^\circ$$




Sketching Bode Plots

$$H(j\omega) = \frac{10}{1 + j\omega 10^{-3}}$$


$$\omega_{3dB} = 10^3$$

$$H_{dB} = 20 - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{10^3}\right)^2}$$

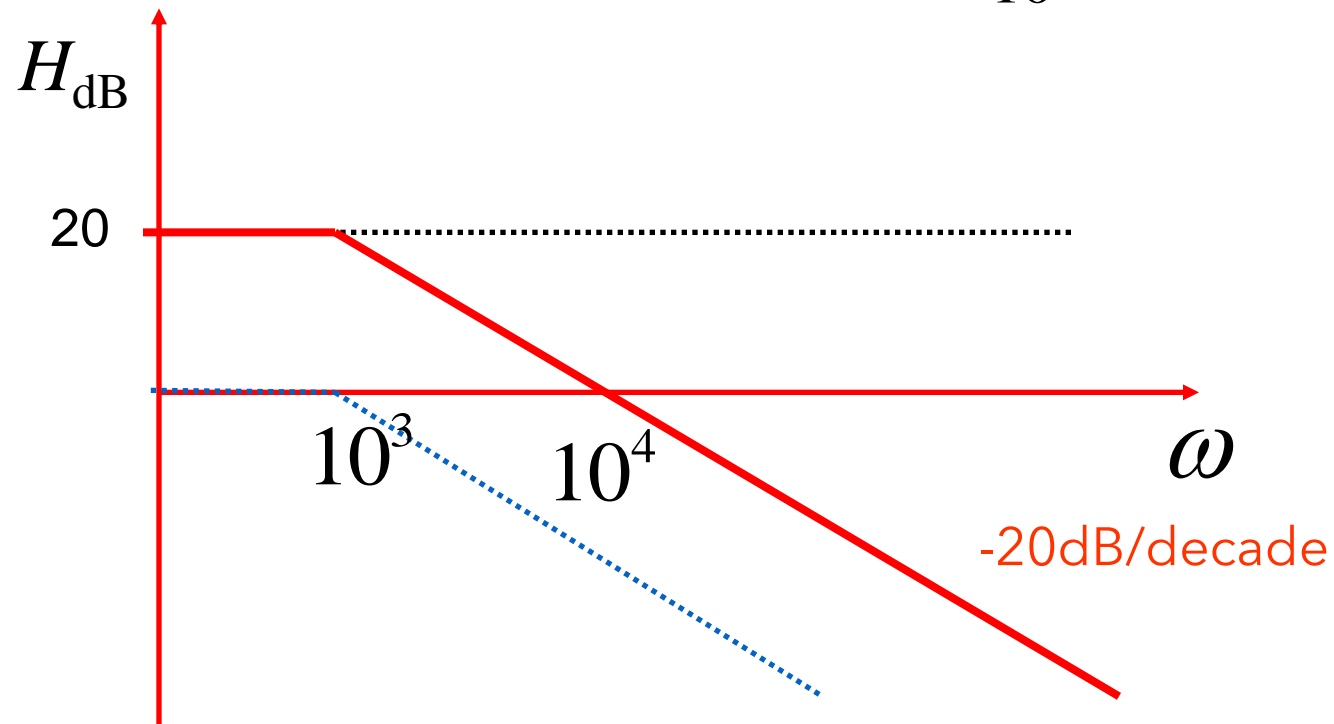$\omega \ll 10^3 : 0dB$
 $\omega \gg 10^3 : -20 \log_{10} \frac{\omega}{10^3}$



Sketching Bode plots

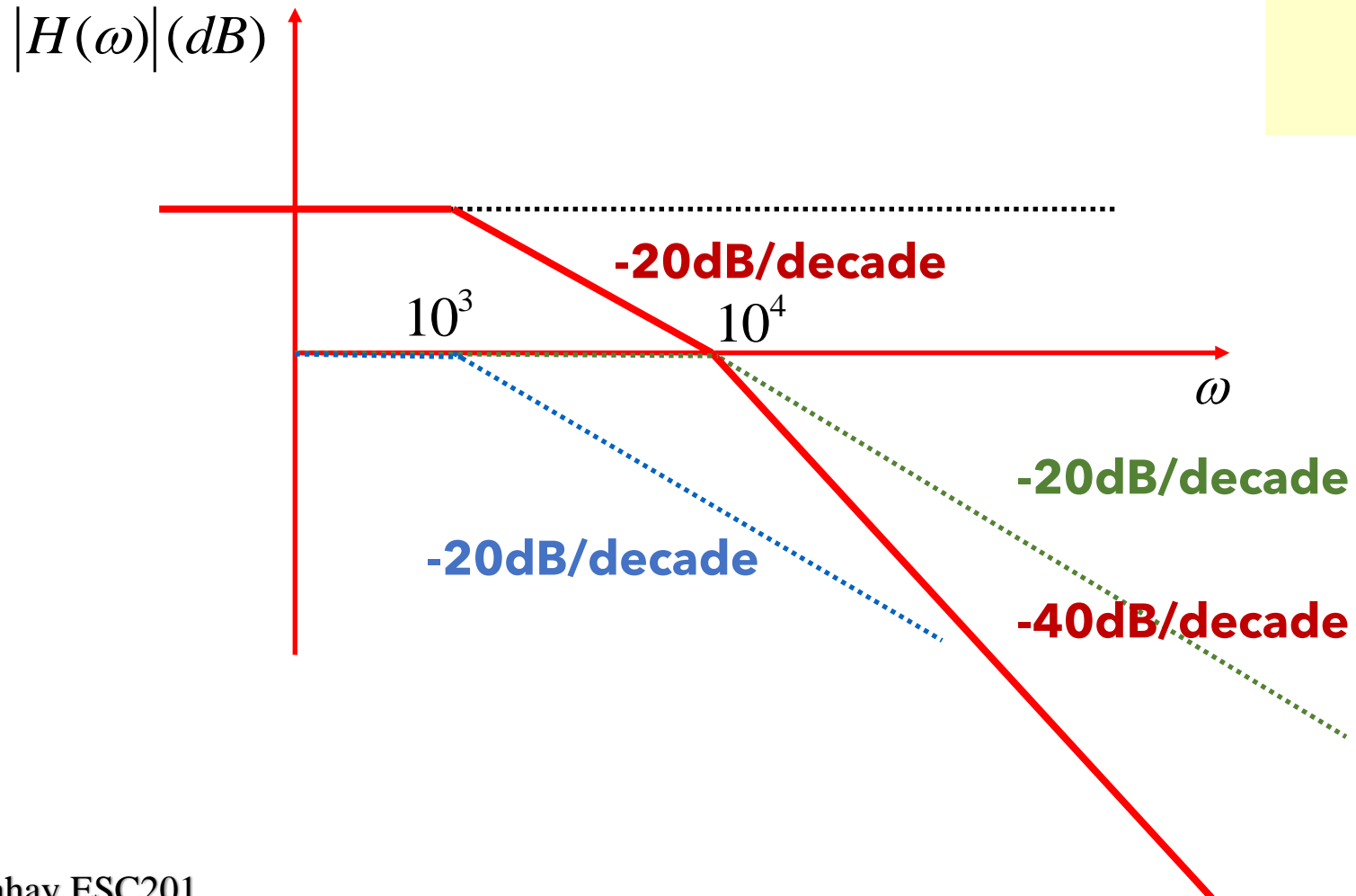


$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}}$$

Phase plot

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}}$$

$$\begin{aligned} \omega \rightarrow 0, \phi \rightarrow 0 & \quad \omega \rightarrow \infty, \phi \rightarrow -90^\circ \\ \omega = \omega_0, \phi \rightarrow -45^\circ \end{aligned}$$
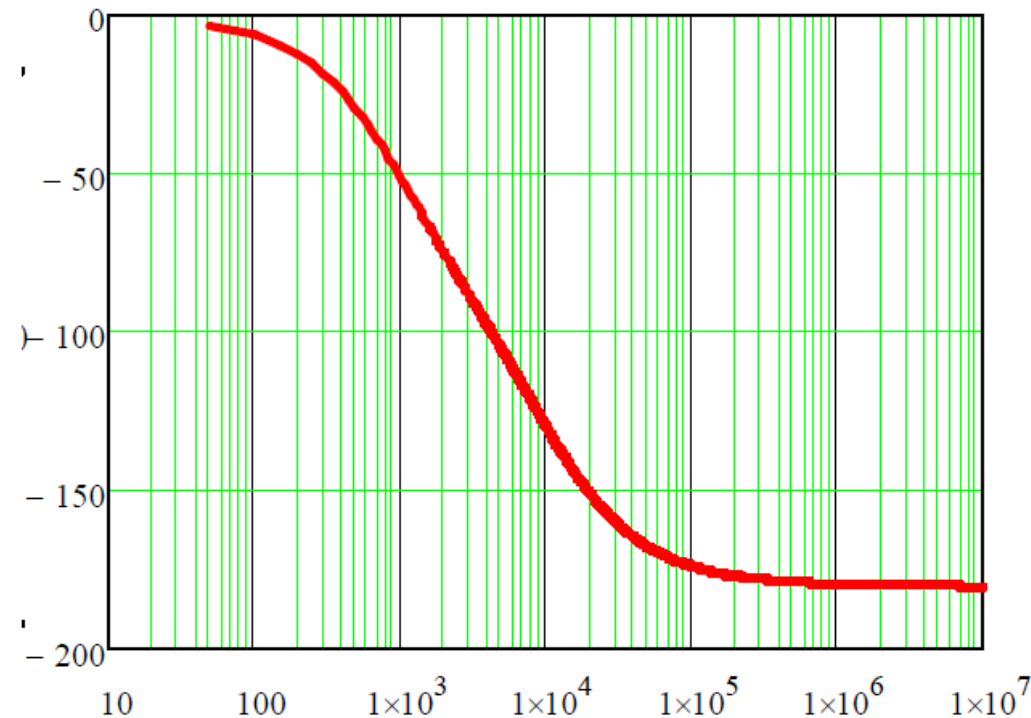
$$\varphi(\omega) = -\tan^{-1}(\omega/10^3) - \tan^{-1}(\omega/10^4)$$




Sketching Bode plots

$$H(\omega) = \frac{10}{1 + j\frac{\omega}{10^3}} \times \frac{1}{1 + j\frac{\omega}{10^4}} \times \frac{1}{1 + j\frac{\omega}{10^5}}$$

$$20\text{Log}_{10}(|H(\omega)|) = 20 - 20\text{log}_{10}\sqrt{1 + \left(\frac{\omega}{10^3}\right)^2} - 20\text{log}_{10}\sqrt{1 + \left(\frac{\omega}{10^4}\right)^2} - 20\text{log}_{10}\sqrt{1 + \left(\frac{\omega}{10^5}\right)^2}$$

$|H(\omega)| (dB)$

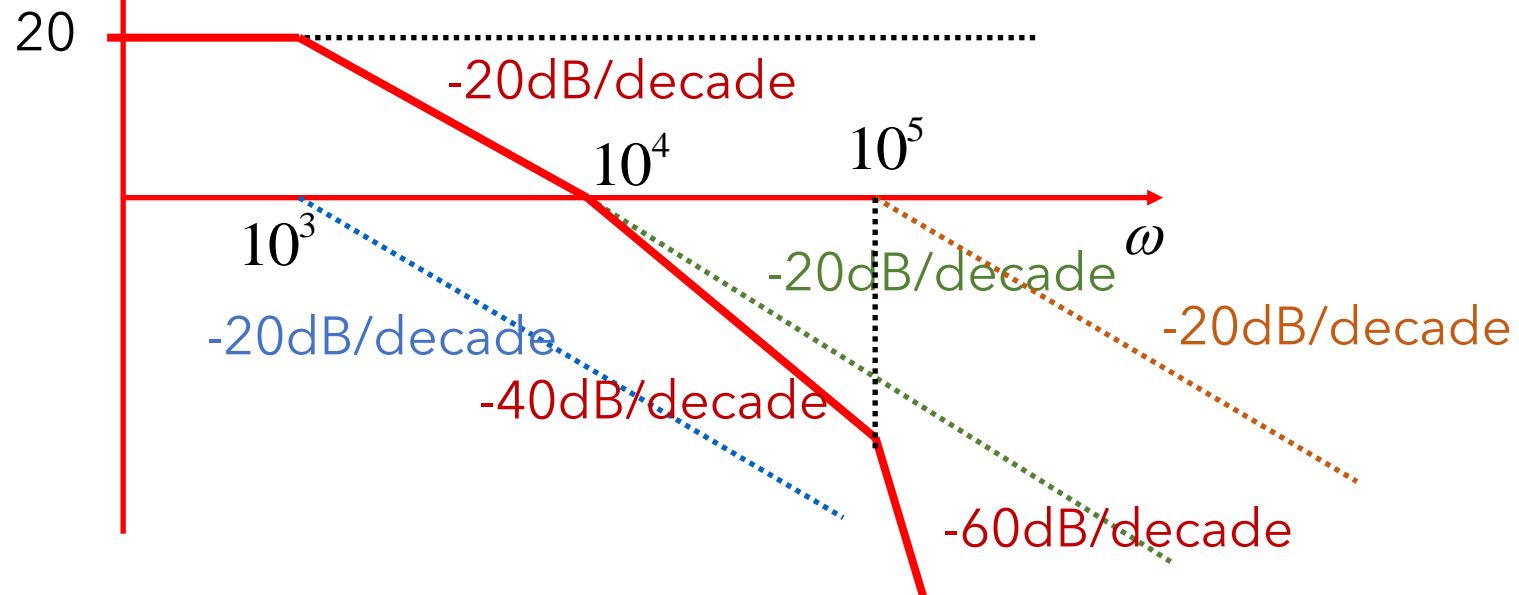


Sketching Bode Plot

$$H(\omega) = (j\omega)^N$$


In dB scale

$$20\log_{10}(|H(\omega)|) = 20N \log_{10}(\omega)$$

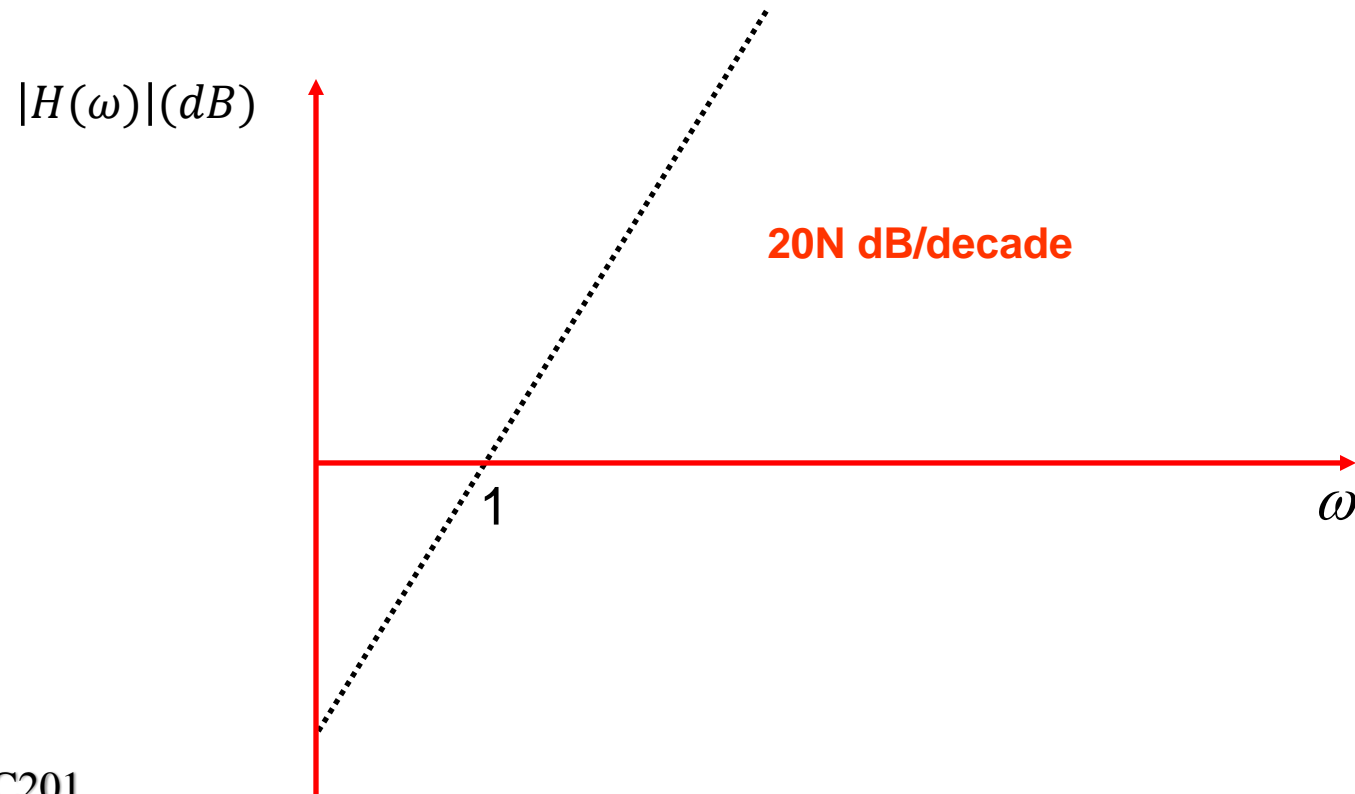

Sketching Bode Plot


$$20\text{Log}_{10}(|H(\omega)|) = 20\log_{10}\left(\frac{\omega}{\omega_{3dB}}\right) - 20\log_{10}\sqrt{1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2}$$

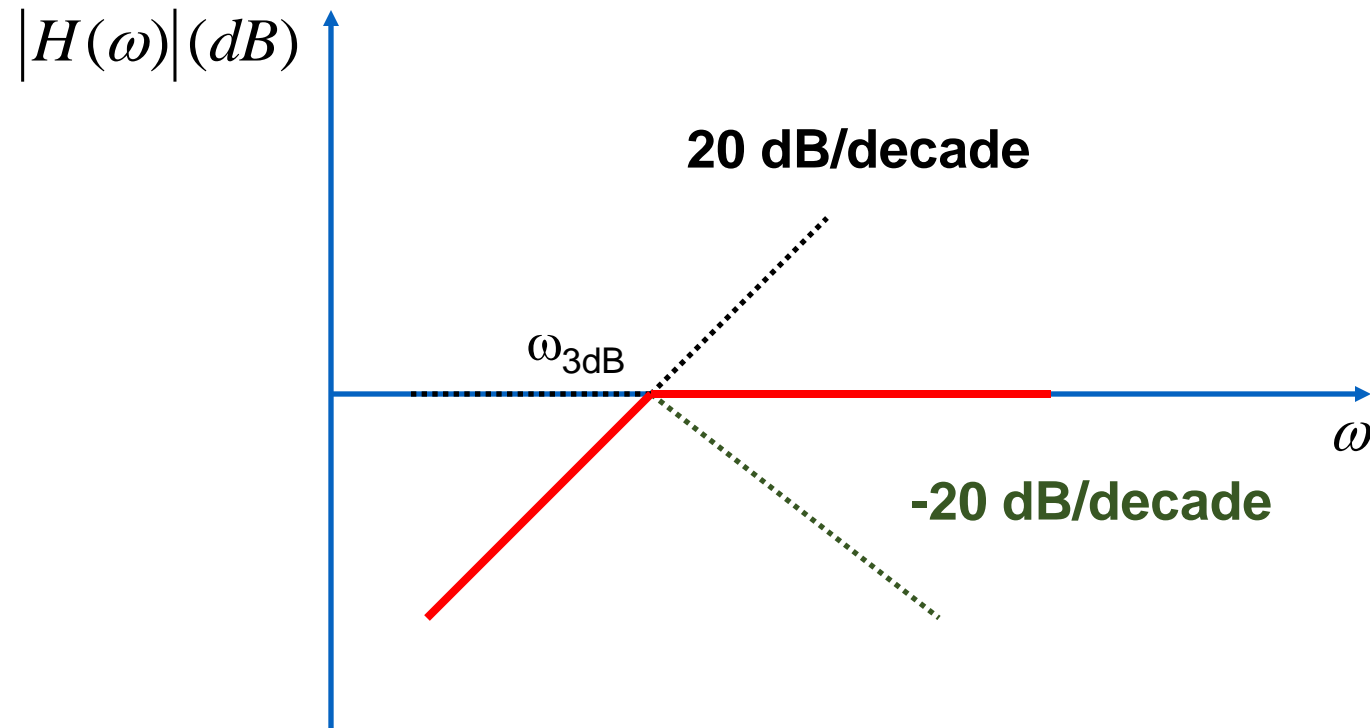

High Pass Filter


Bode Plot
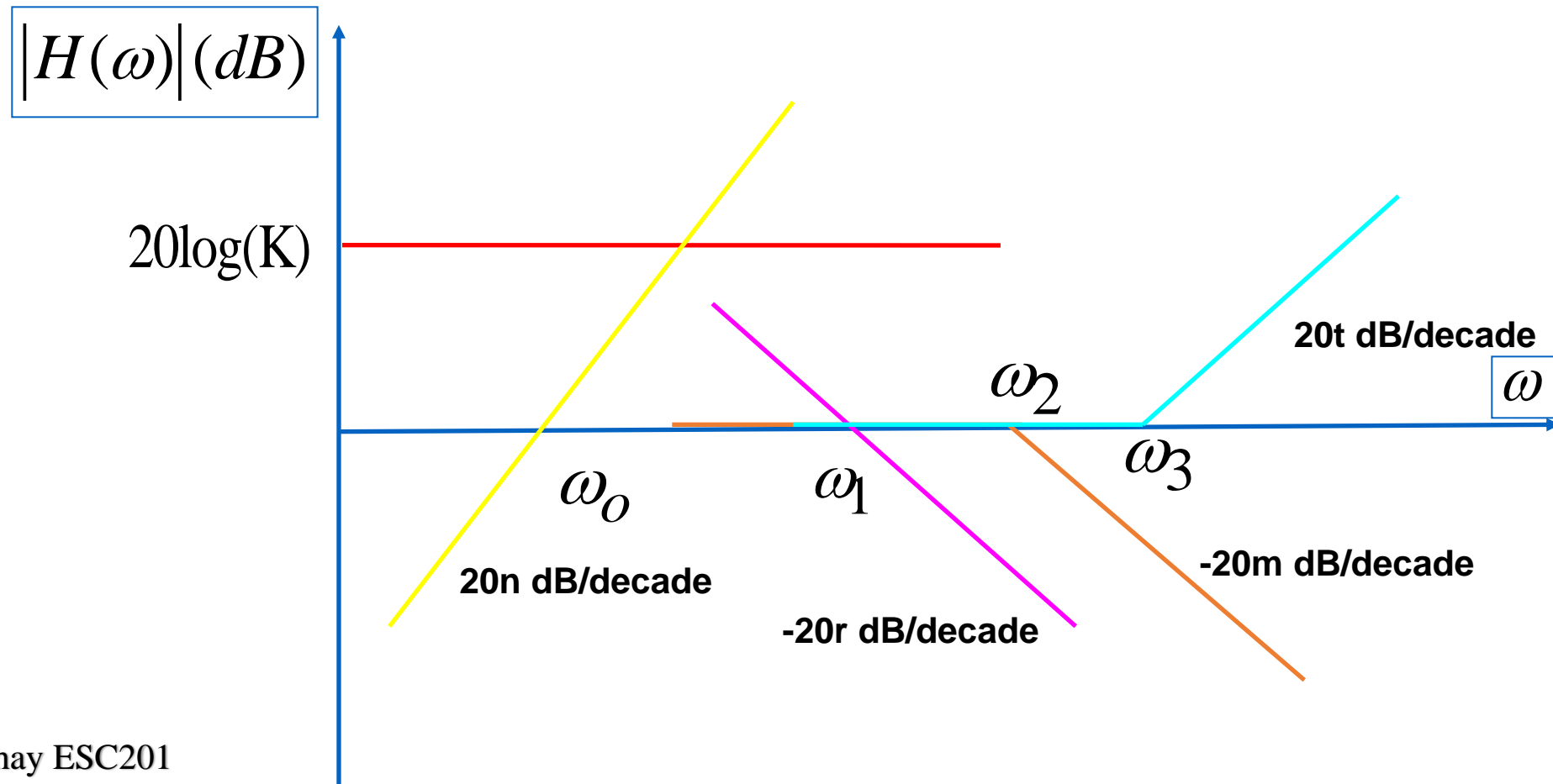
$$H(\omega) = K \times j(\omega / \omega_o)^n \times \frac{1}{j(\omega / \omega_1)^r} \times \frac{1}{\{1 + j(\omega / \omega_2)\}^m} \times \{1 + j(\omega / \omega_3)\}^t$$





Bode Plot

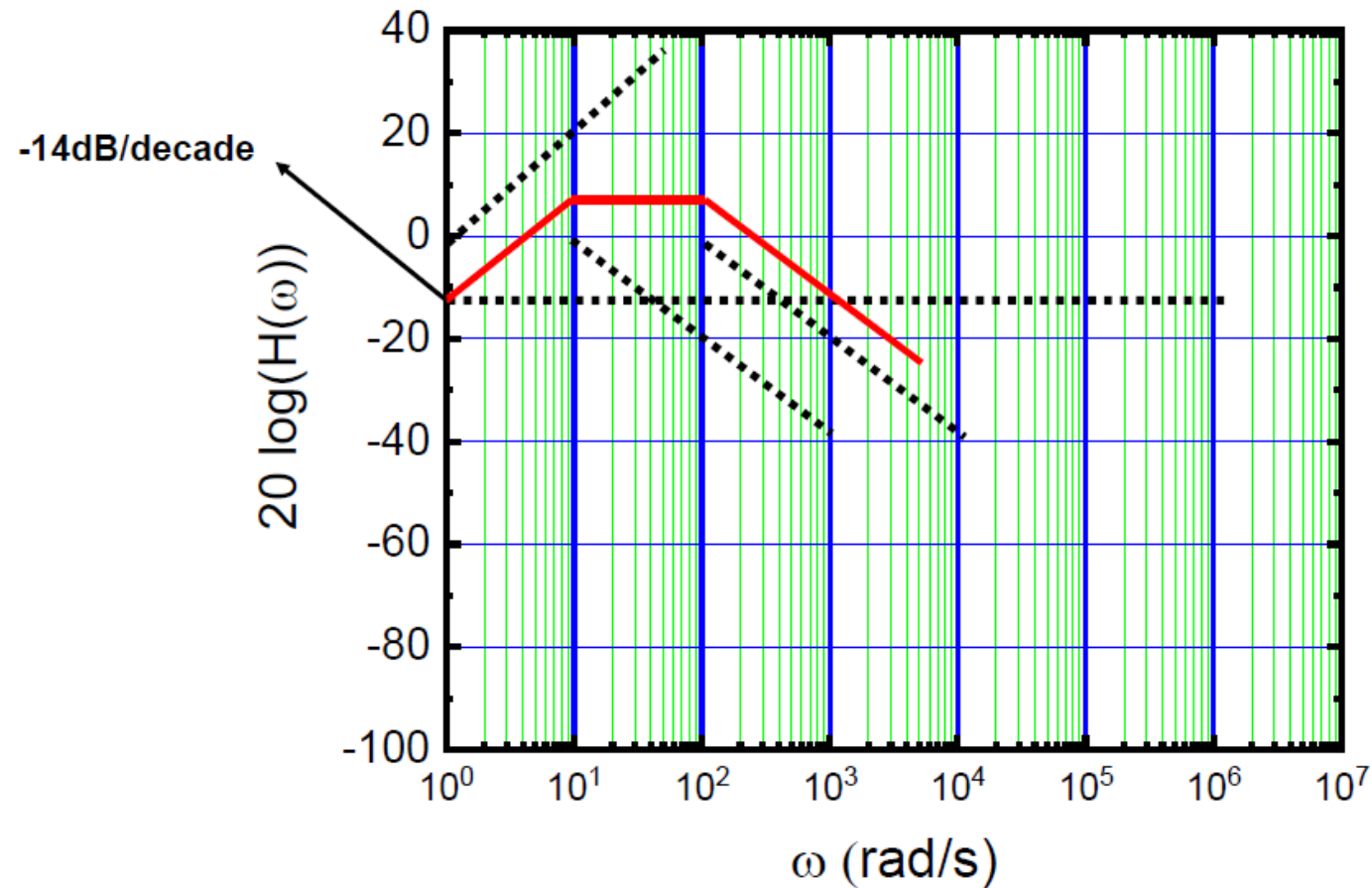
$$H(\omega) = 200 \times j\omega \times \frac{1}{10 + j\omega} \times \frac{1}{100 + j\omega} = 0.2 \times j\omega \times \frac{1}{1 + j\frac{\omega}{10}} \times \frac{1}{1 + j\frac{\omega}{100}}$$




Recall Example

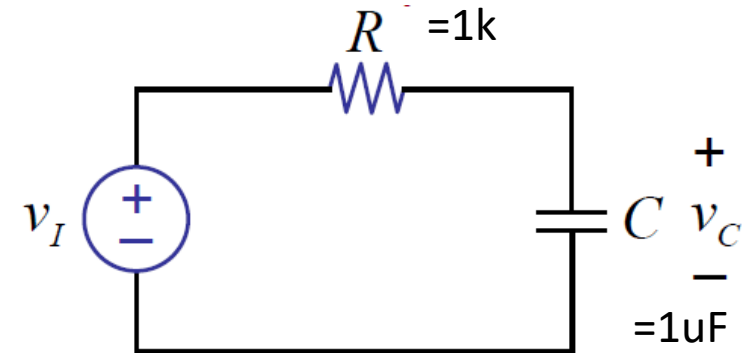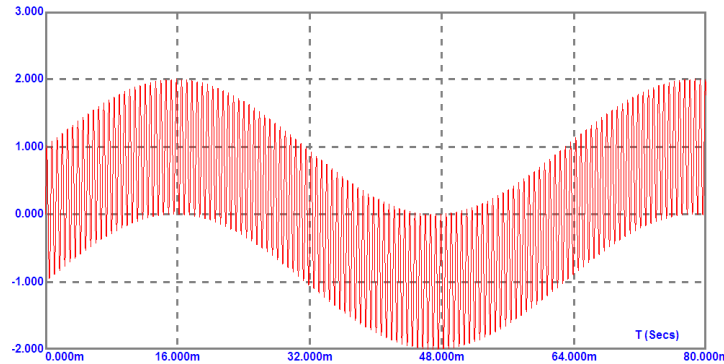




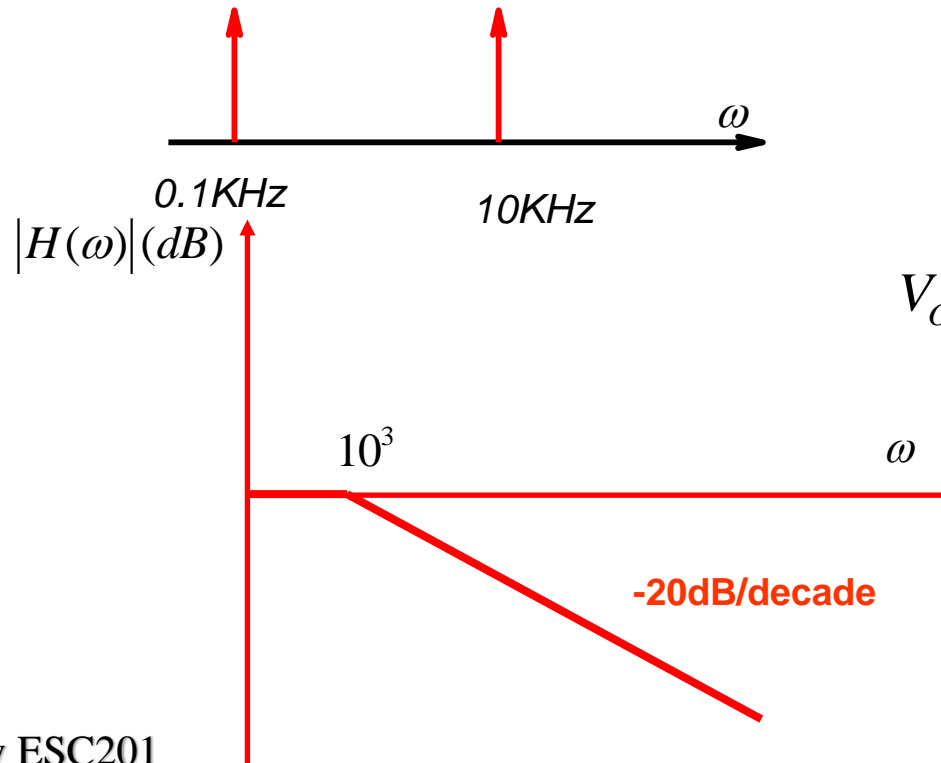
$$H(\omega) = \frac{1}{1 + j\omega 10^{-3}} = \frac{1}{1 + j\frac{\omega}{10^3}}$$



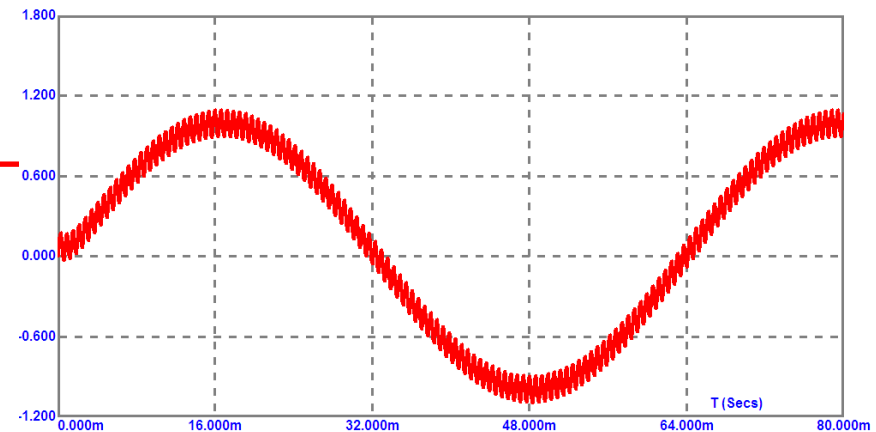
$$V_o(t) = 1\sin(100t) + 0.1\sin(10^4 t)$$



Example: low pass filter...

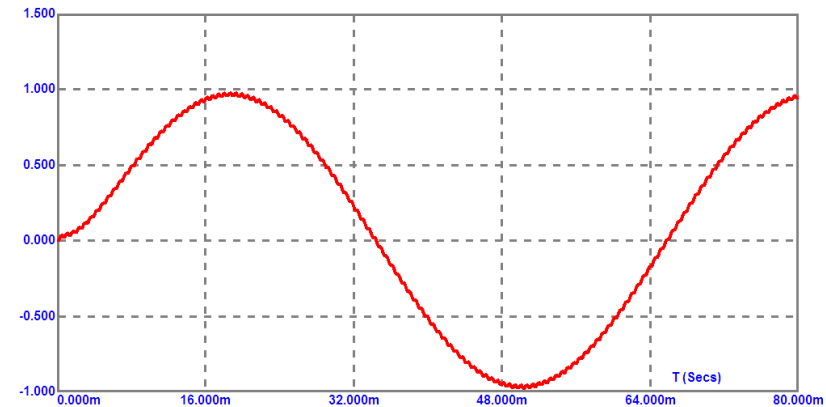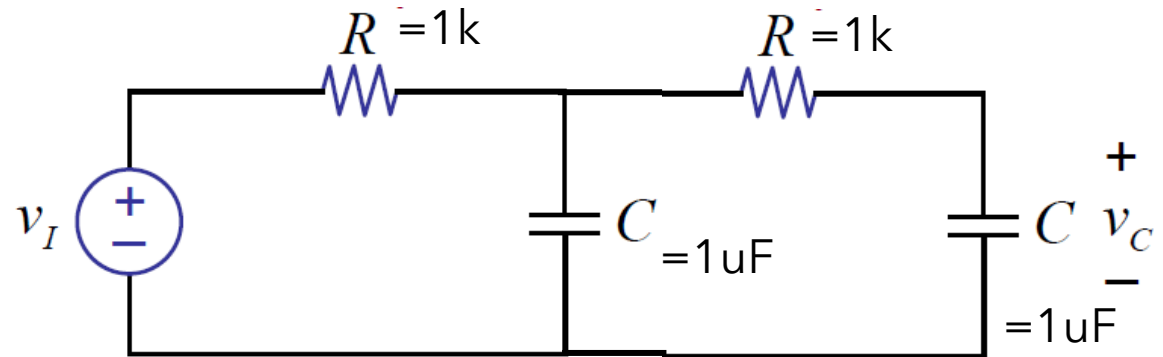
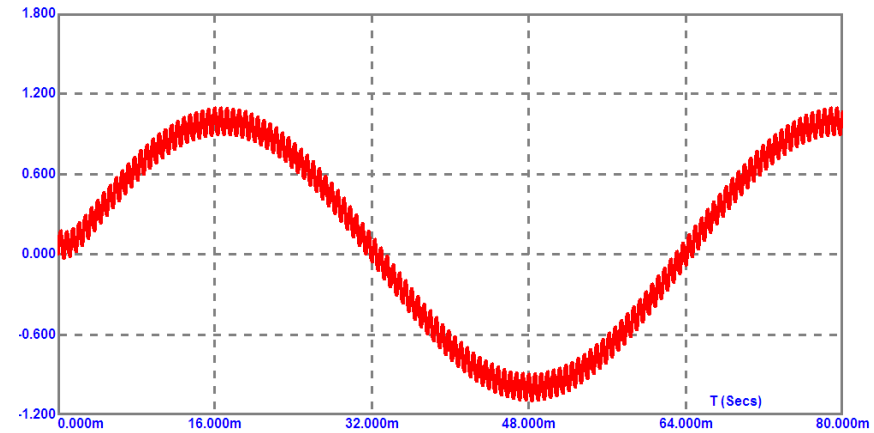
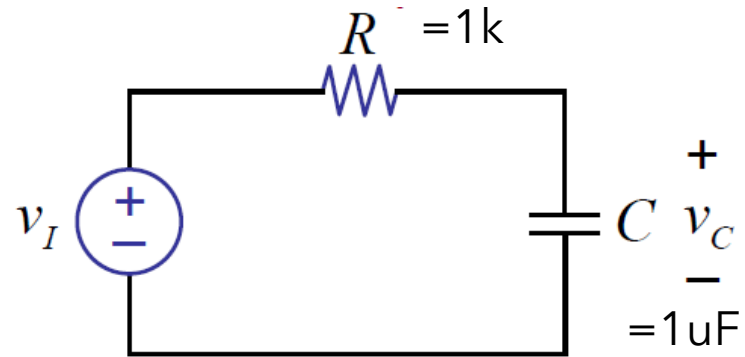


Analysis of two-stage RC

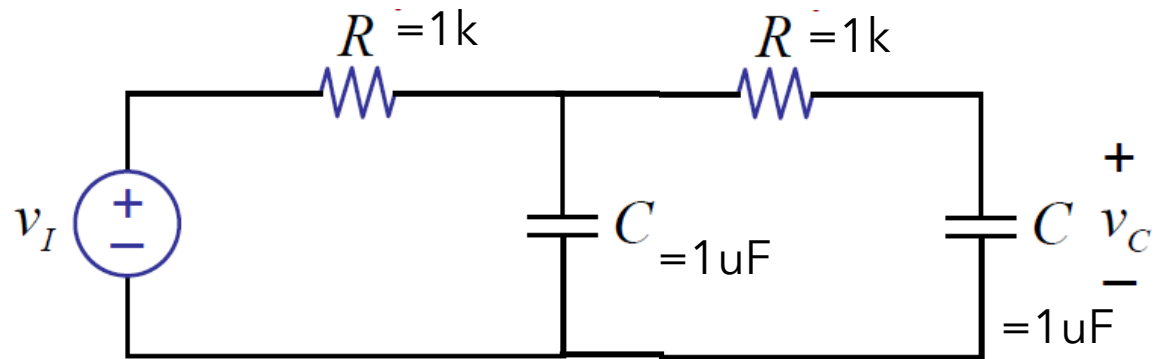

$$\begin{aligned} H(\omega) &= \frac{\left(R + \frac{1}{j\omega C}\right) \parallel \frac{1}{j\omega C}}{R + \left(R + \frac{1}{j\omega C}\right) \parallel \frac{1}{j\omega C}} \times \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \\ &= \frac{1}{1 - \omega^2 R^2 C^2 + 3j\omega RC} \\ &\approx \frac{1}{1 + 3j\omega RC} \times \frac{1}{1 + \frac{j\omega RC}{3}} \end{aligned}$$

Example: low pass filter...

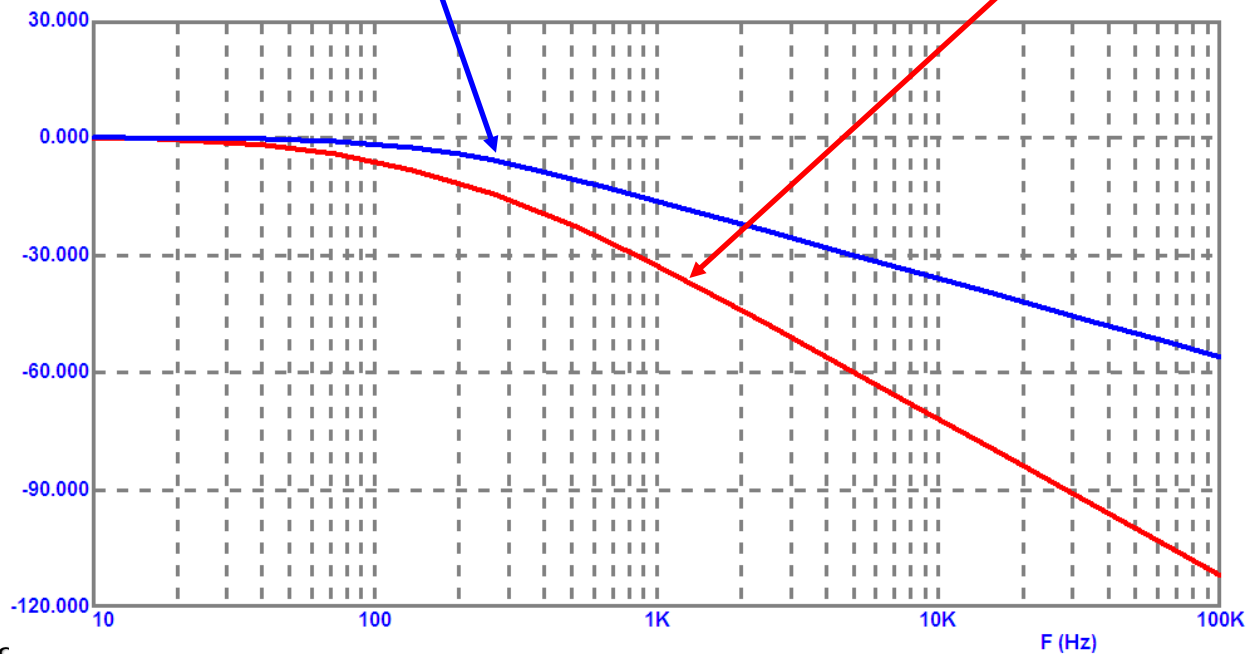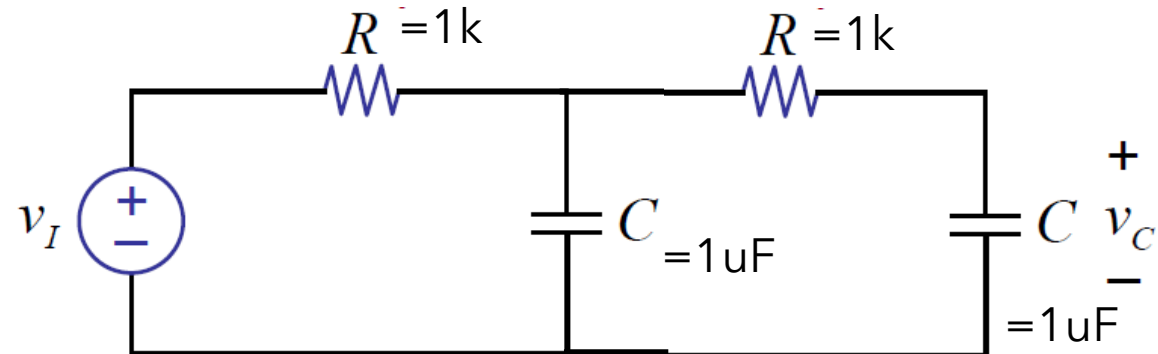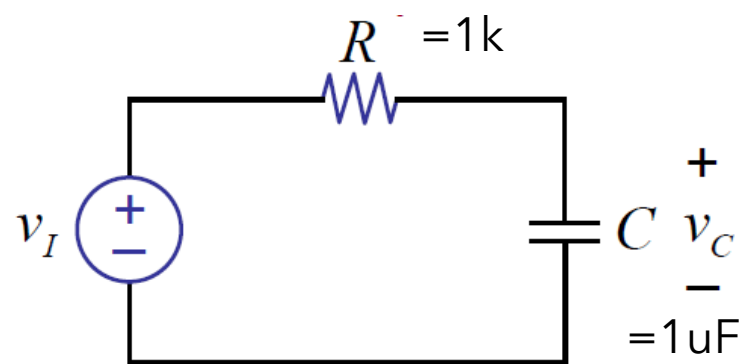

-20dB/decade

-40dB/decade

Adding more RC stages, makes the characteristics sharper

