


# ESC201: INTRODUCTION TO ELECTRONICS

## MODULE 3: FREQUENCY DOMAIN ANALYSIS







Dr. Shubham Sahay,  
Assistant Professor,  
Department of Electrical Engineering,  
IIT Kanpur

# MQ-2

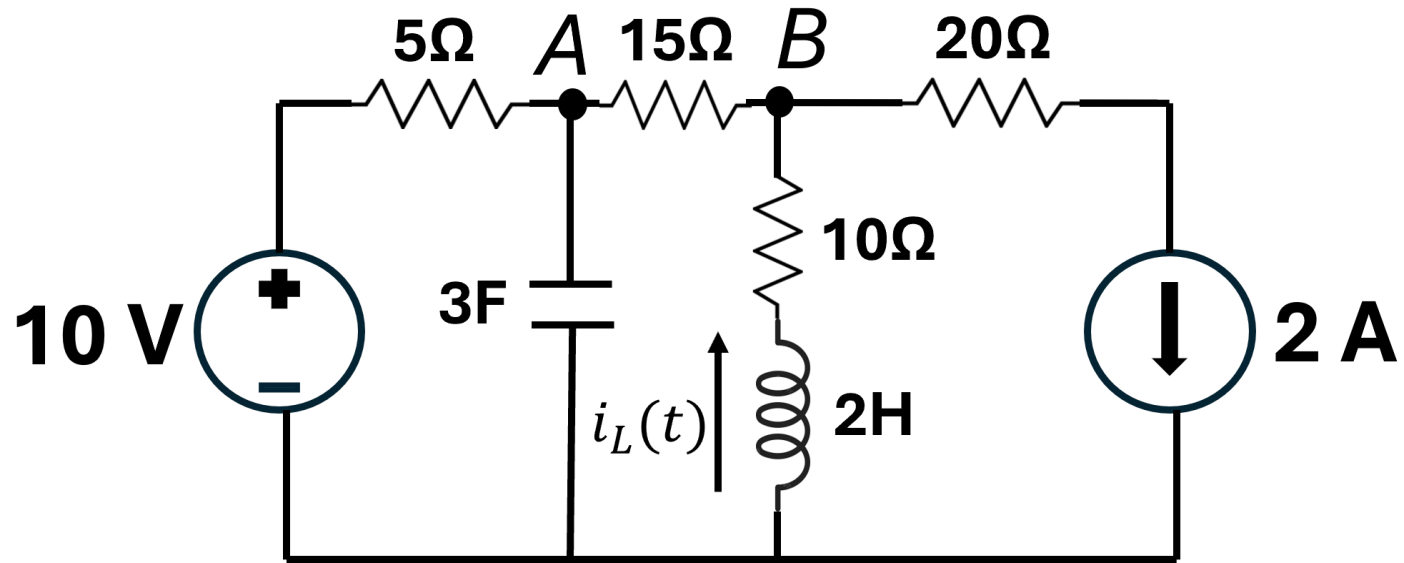


# Why Sinusoidal Steady-state Response

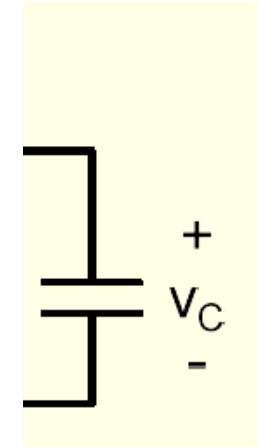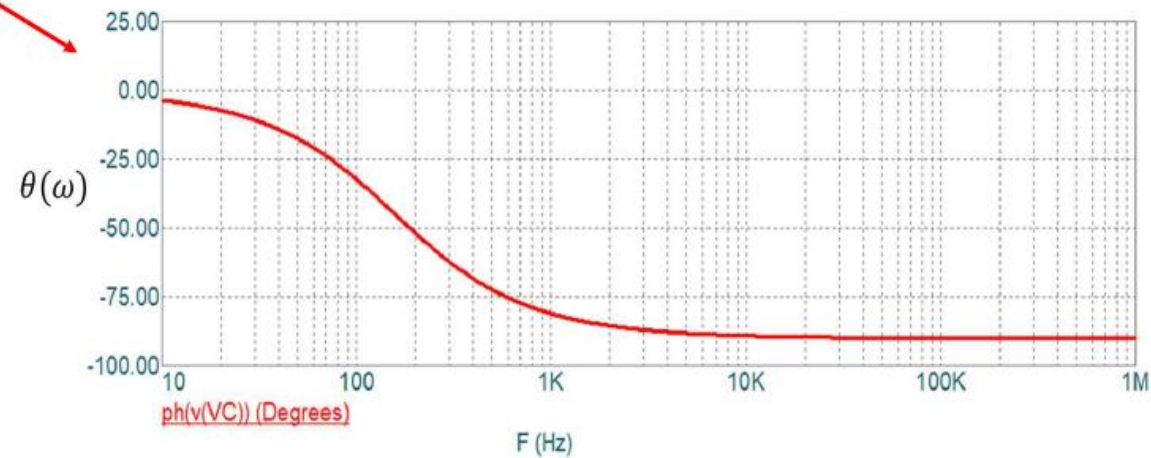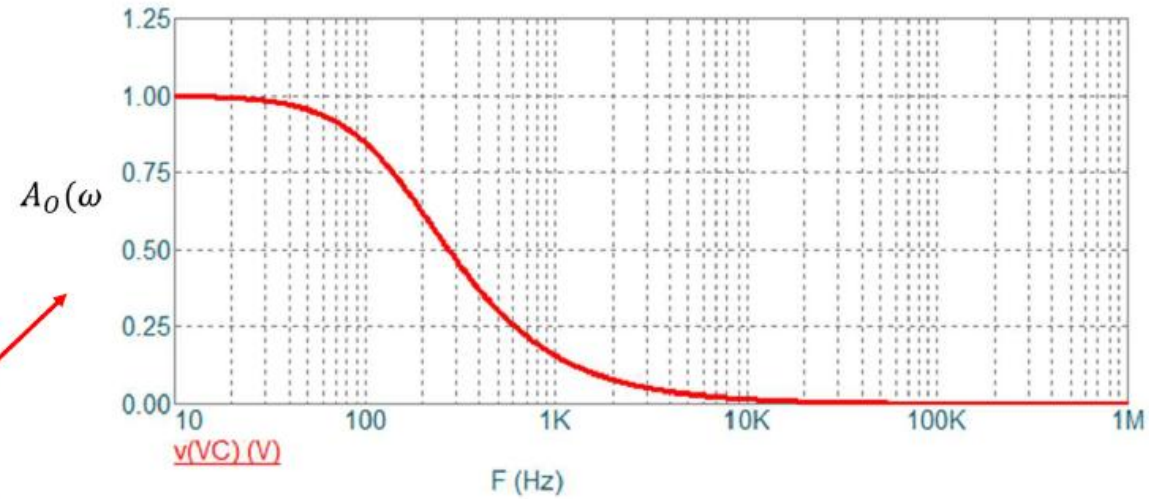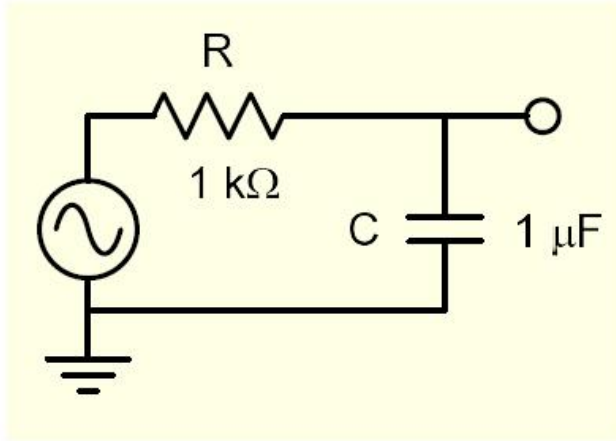

system


# Domain Transformation and Solution

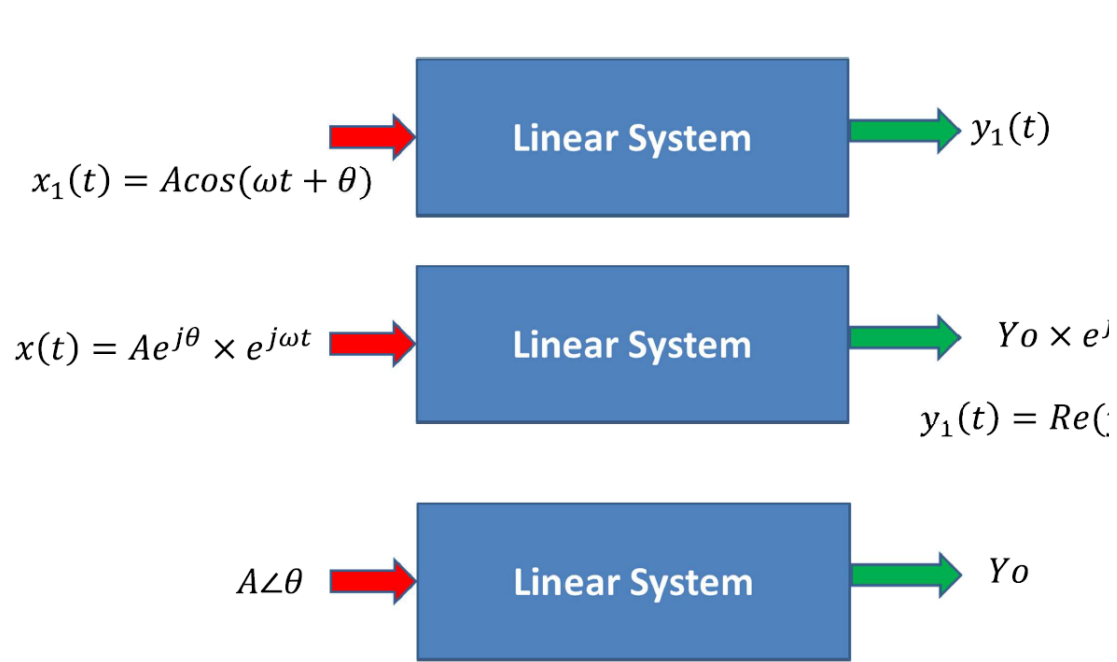


Current through the inductor lags the voltage by 90°

$$V_L = j\omega L \times I_L$$

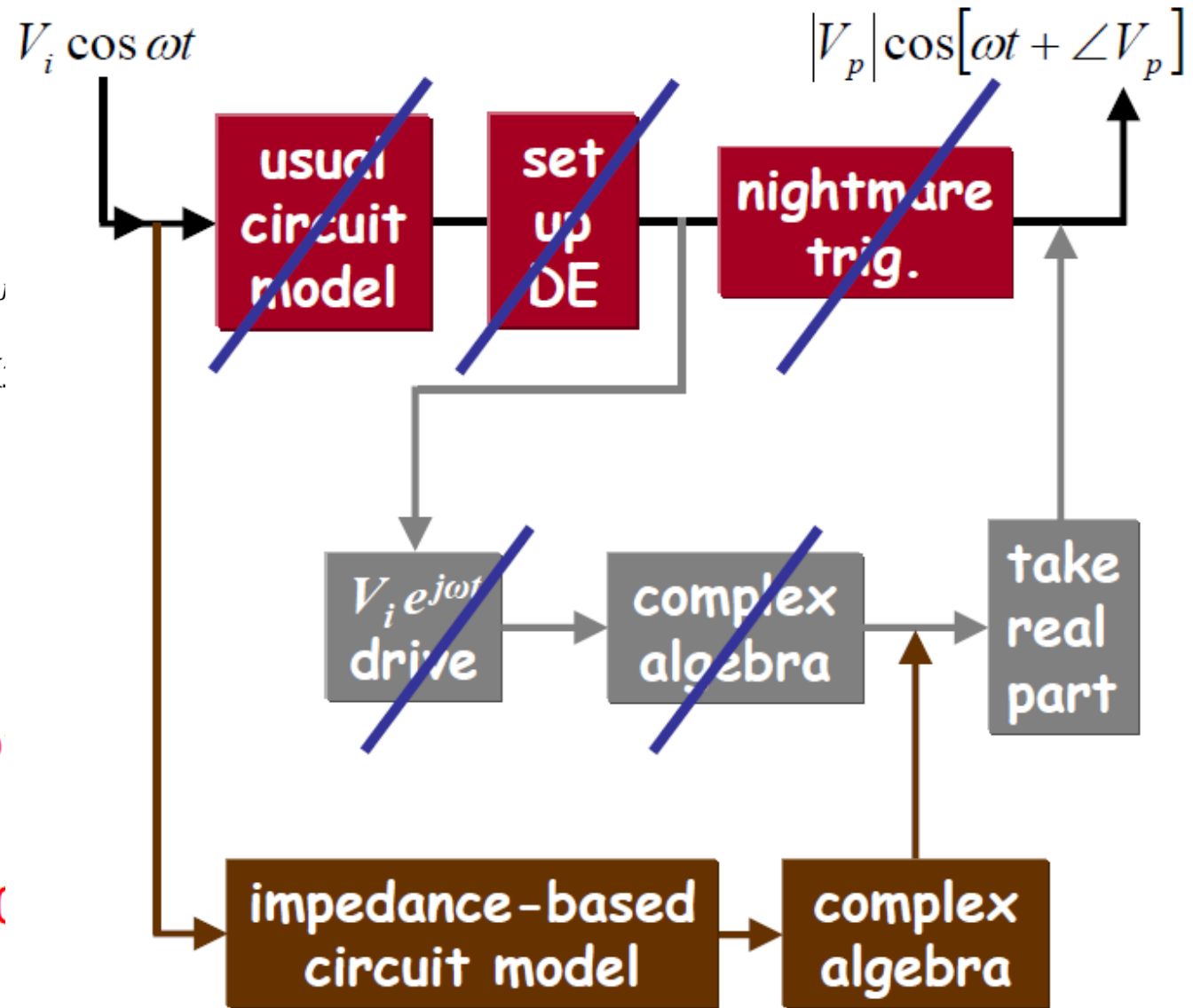
In a capacitor, current leads voltage by 90°




# Big Picture

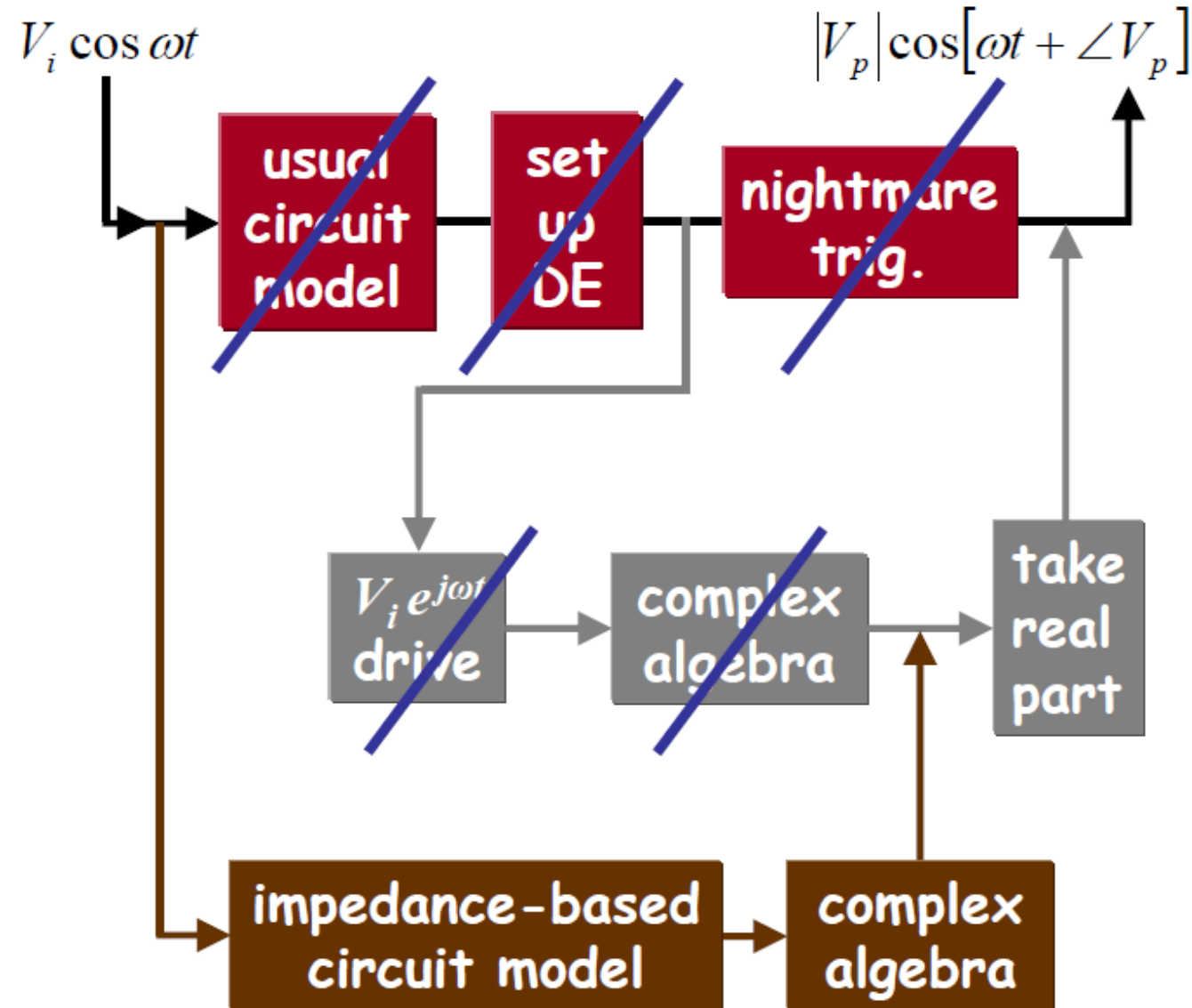

# Series-parallel operations

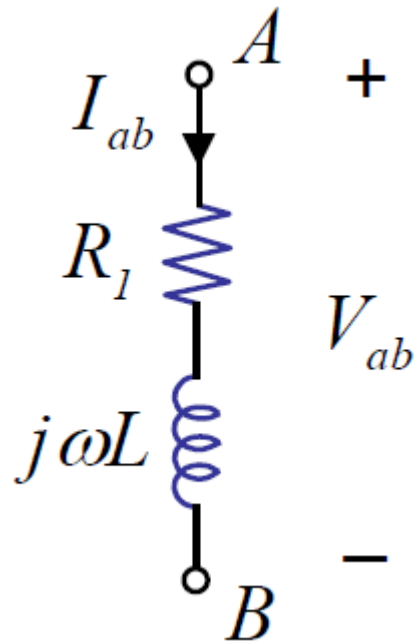


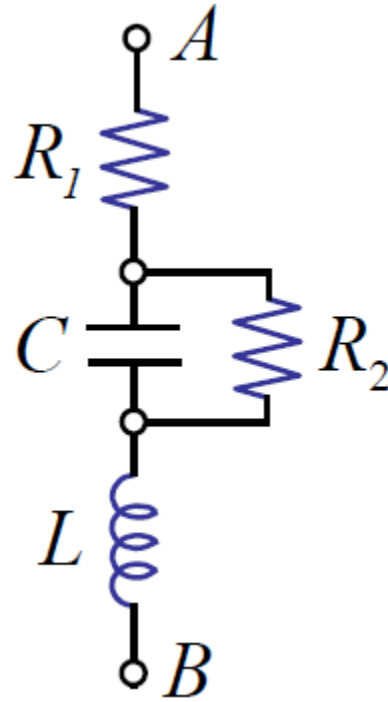
$$Z_{AB} = \frac{V_{ab}}{I_{ab}} = R_1 + j\omega L$$



$$\begin{aligned} Z_{AB} &= R_1 + Z_C \parallel R_2 + Z_L \\ &= R_1 + \frac{Z_C R_2}{Z_C + R_2} + Z_L \\ &= R_1 + \frac{R_2}{1 + j\omega C R_2} + j\omega L \end{aligned}$$
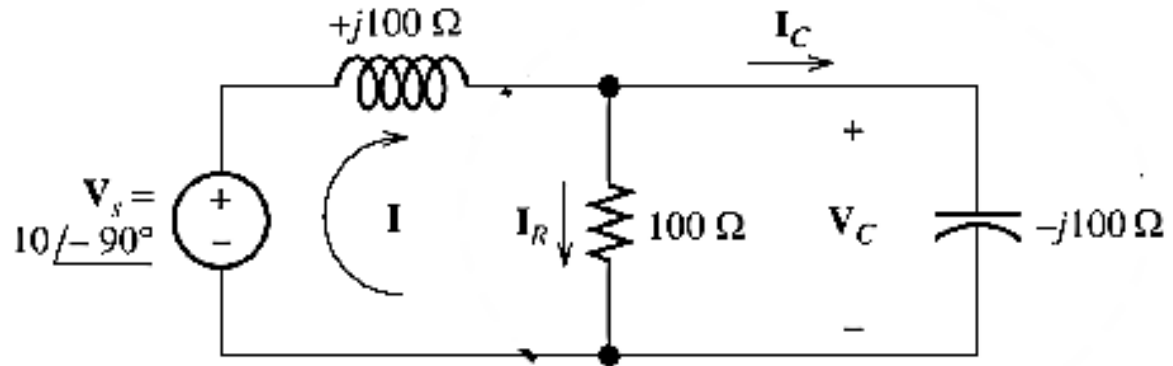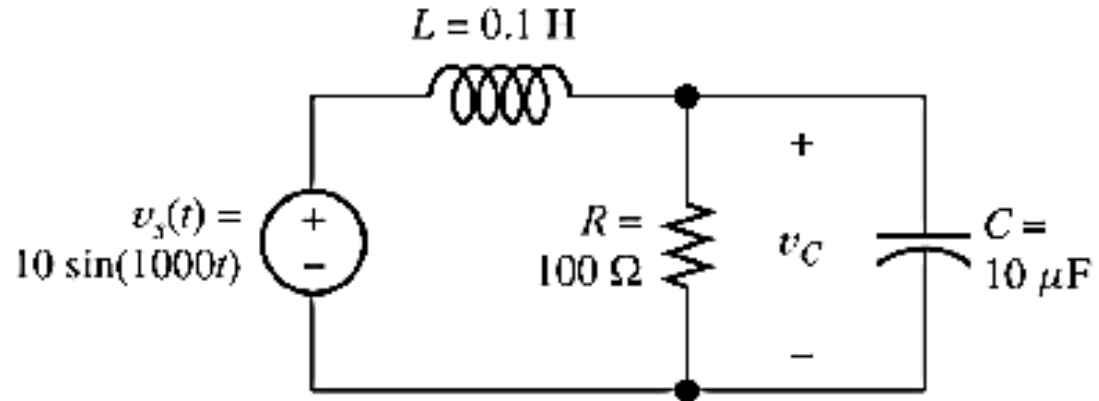
# Example

Find the voltage across capacitor in steady state




$$V_C = V_s \frac{Z_{RC}}{100j + Z_{RC}}$$

$$V_C = 10 \angle -90^\circ \frac{50 - 50j}{100j + 50 - 50j} = -10V$$

$$v_C(t) = -10 \cos(1000t)$$

$$\frac{1}{Z_{RC}} = \frac{1}{100} + \frac{1}{-j100}$$



$$Z_{RC} = 50 - 50j$$

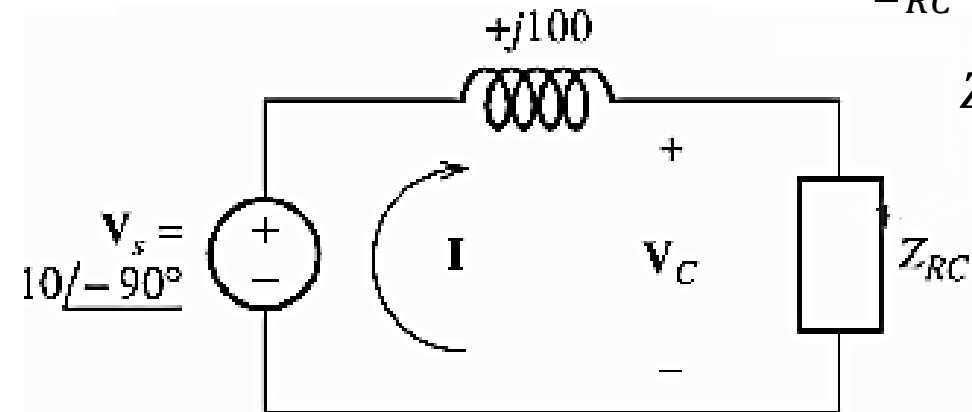


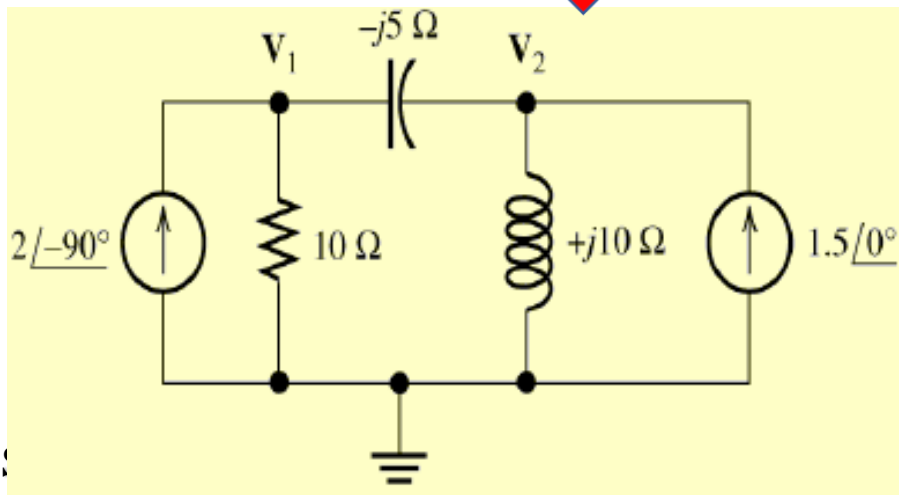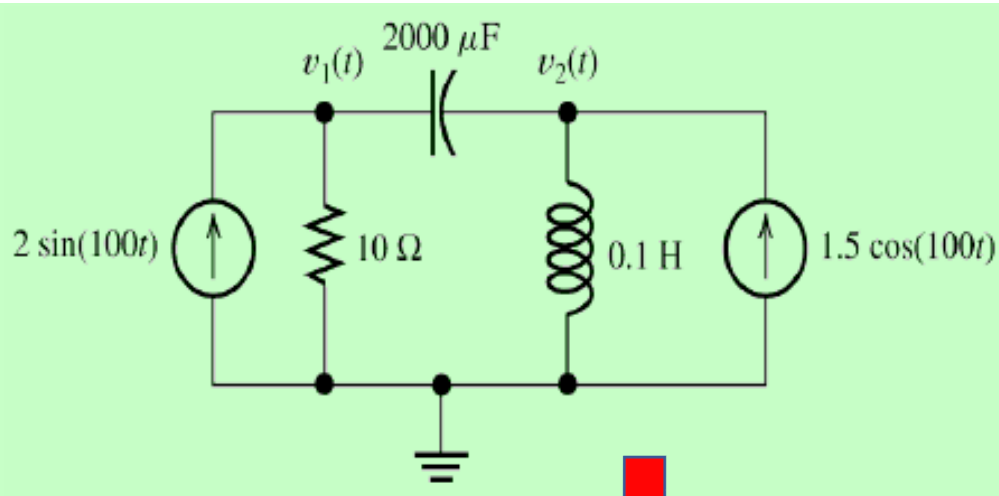
# Example 2

Use nodal analysis to find  $v_1(t)$  in steady state



$$\frac{V_1}{10} + \frac{V_1 - V_2}{-j5} = 2 \angle -90^\circ$$
$$(0.1 + j0.2)V_1 - j0.2V_2 = -j2$$



$$\frac{V_2}{j10} + \frac{V_2 - V_1}{-j5} = 1.5 \angle 0^\circ$$
$$-j0.2V_1 + j0.1V_2 = 1.5$$

$$V_1 = 16.1 \angle 29.7^\circ$$

$$v_1(t) = 16.1 \cos(100t + 29.7^\circ)$$



# Mesh Analysis

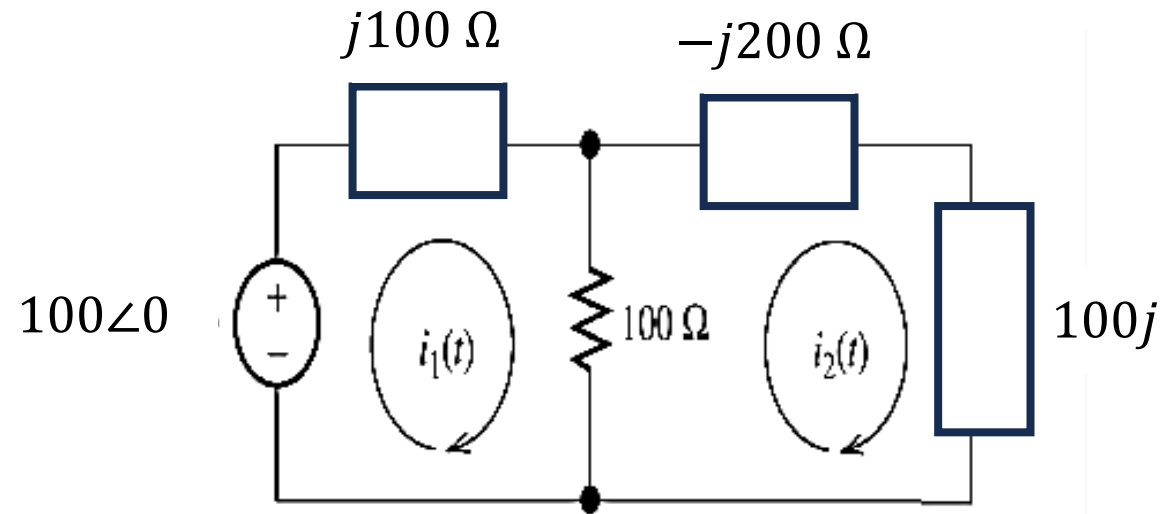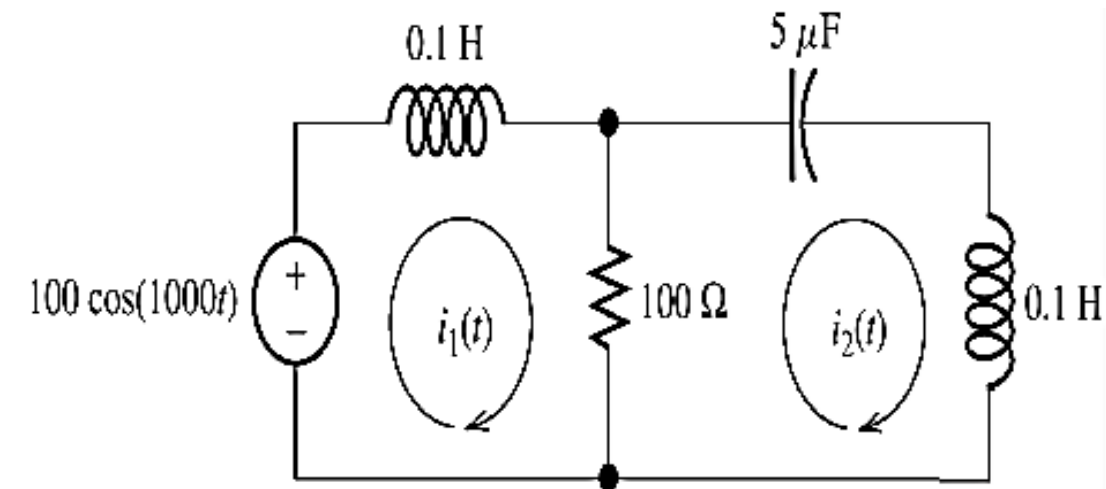

$$j100I_1 + 100(I_1 - I_2) = 100$$


$$(100 + j100)I_1 - 100I_2 = 100$$

$$-j200I_2 + j100I_2 + 100(I_2 - I_1) = 0$$

$$-100I_1 + (100 - j100)I_2 = 0$$


$$I_1 = 1.414 \angle -45^\circ \text{ A and } I_2 = 1 \angle 0^\circ \text{ A}$$
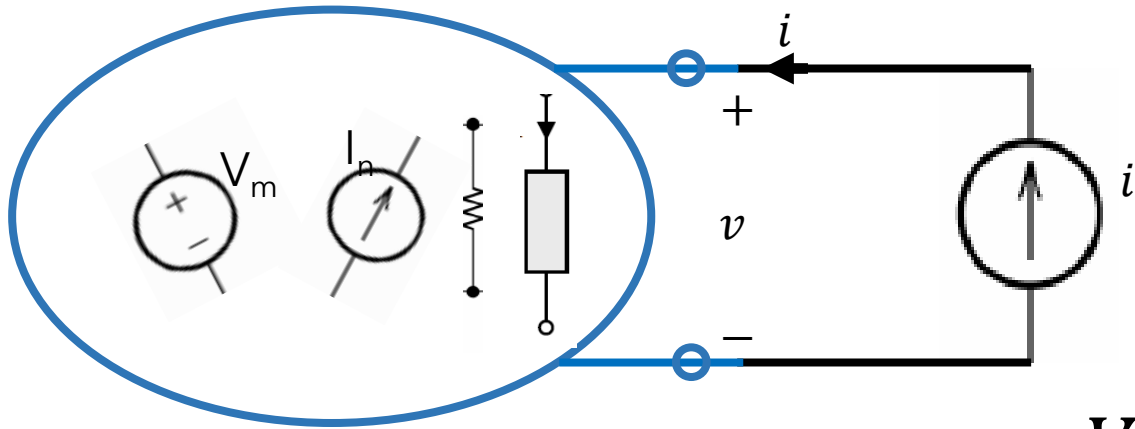
# Thevenin/Norton Equivalent with Impedances




$$V = V_{TH} + Z_{TH}i$$

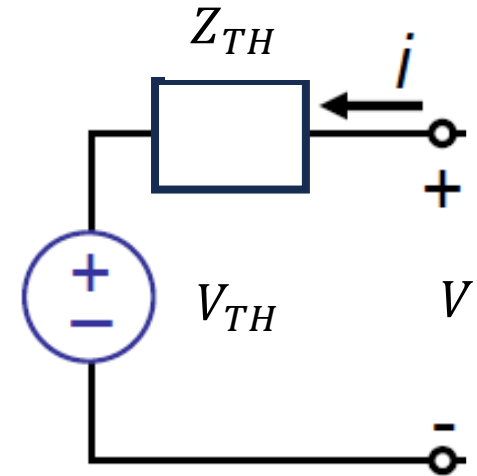Can be modeled as a phasor voltage source in series with an impedance!




$$I = \frac{V}{Z_{TH}} - I_N$$

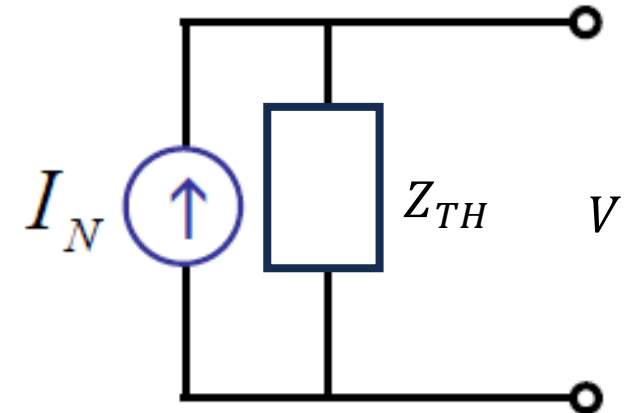Can be modeled as a phasor current source in parallel with an impedance!




# Example

Find the Thevenin/Nortan Equivalent

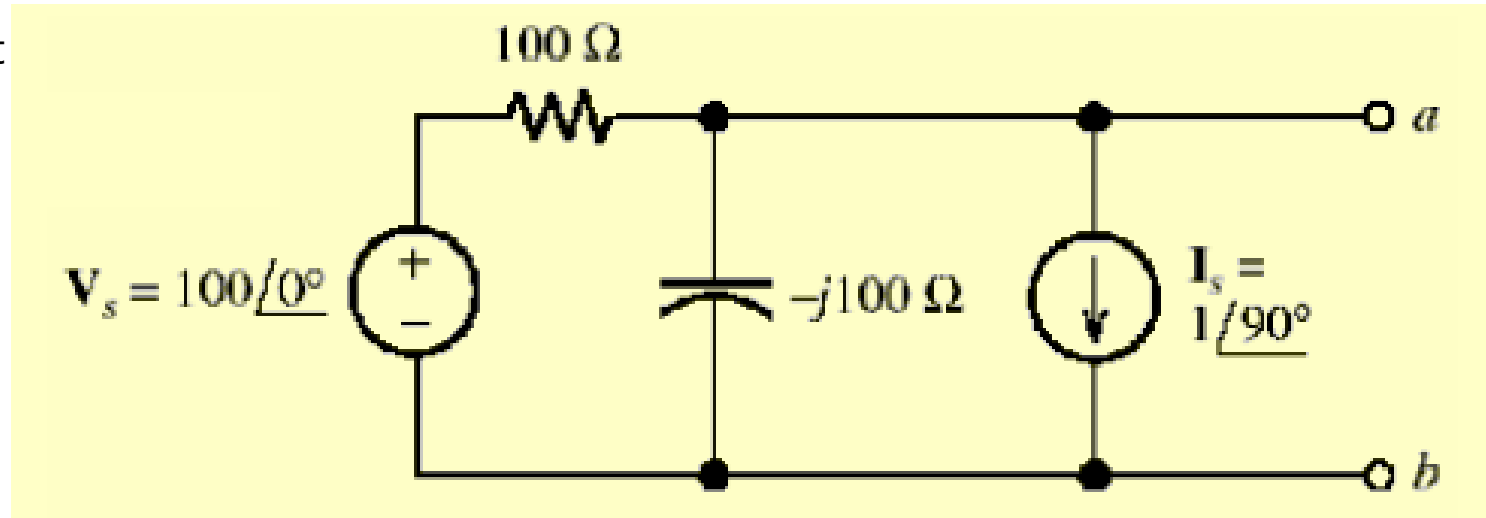

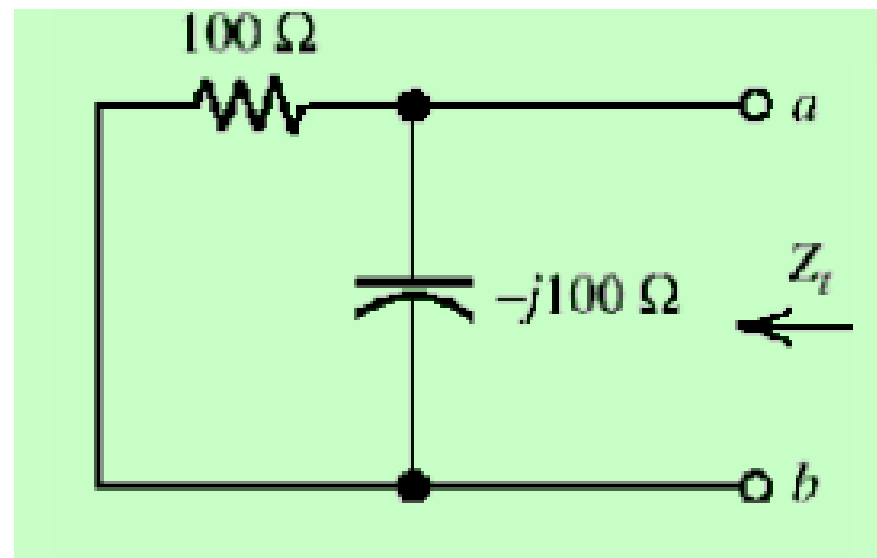
Thevenin Impedance: All sources to be zeroes



$$\frac{1}{Z_{TH}} = \frac{1}{100} + \frac{1}{-j100}$$

$$Z_{TH} = (50 - 50j)\Omega$$

# Example

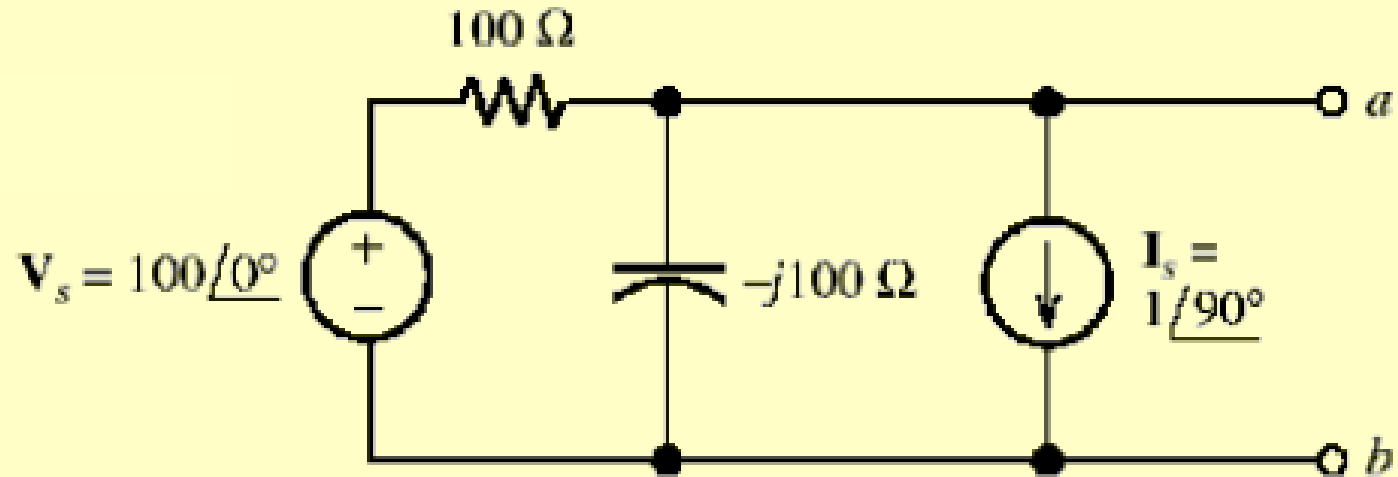


Nortan Current: Short circuit the terminals


$$\begin{aligned} I_{sc} &= I_R - I_s = \frac{100\angle 0^\circ}{100} - 1\angle 90^\circ \\ &= 1 - j = 1.414\angle -45^\circ \end{aligned}$$

Thevenin Voltage
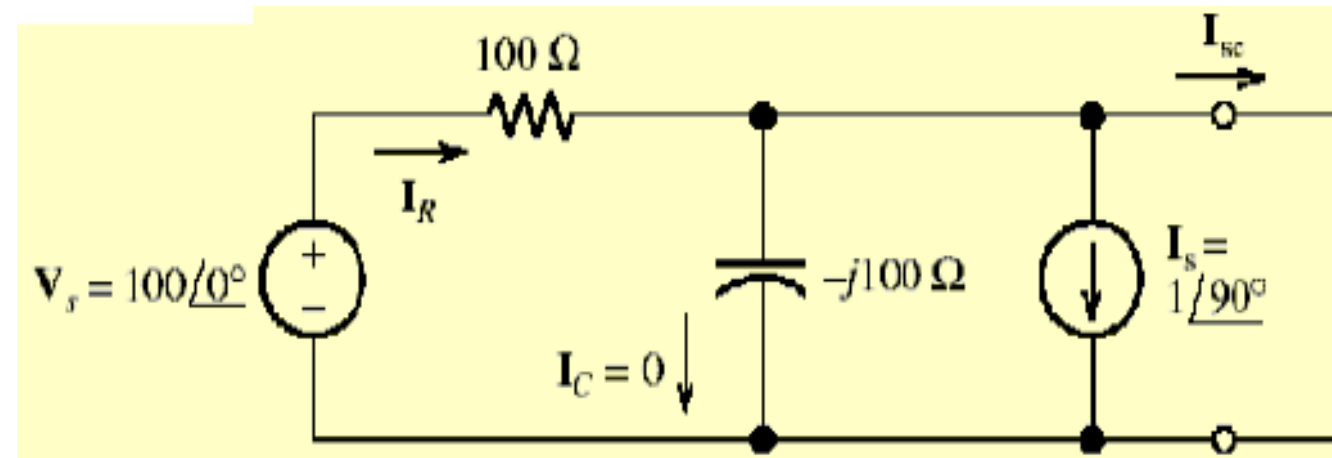
$$V_{TH} = I_{SC} Z_{TH} = 100\angle -90^\circ \text{ V}$$


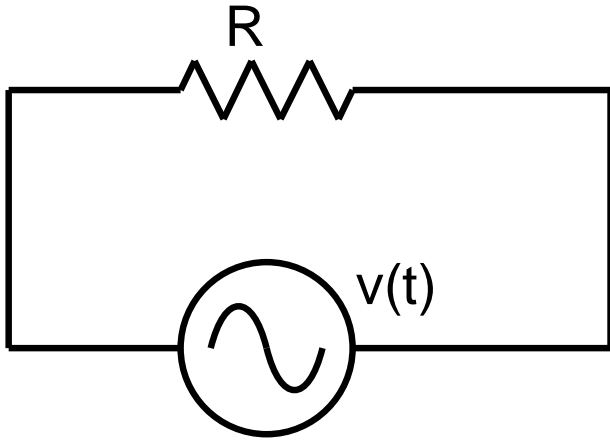
# Power dissipation with sinusoidal Voltage




$$p_{avg} = \frac{\frac{1}{T} \int_0^T v(t)^2 dt}{R}$$

$$p_{avg} = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

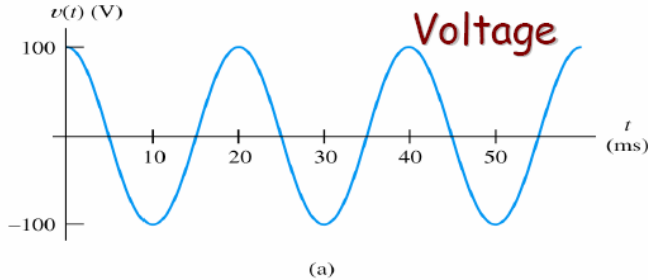

(a)

$$p_{avg} = I_{rms}^2 R$$


$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

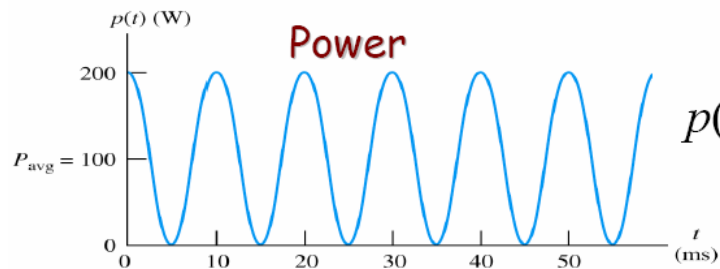

$$p(t) \quad p(t) = v(t)i(t) = \frac{v(t)^2}{R}$$

$$p(t) = 200 \cos^2 100\pi t \text{ W}$$

# Average power in Inductor

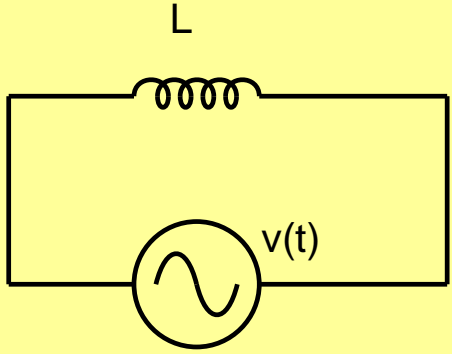




$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$


$$\begin{aligned} p(t) &= v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t) \\ &= \frac{V_m I_m}{2} \sin(2\omega t) \end{aligned}$$

$$p_{avg} = 0$$

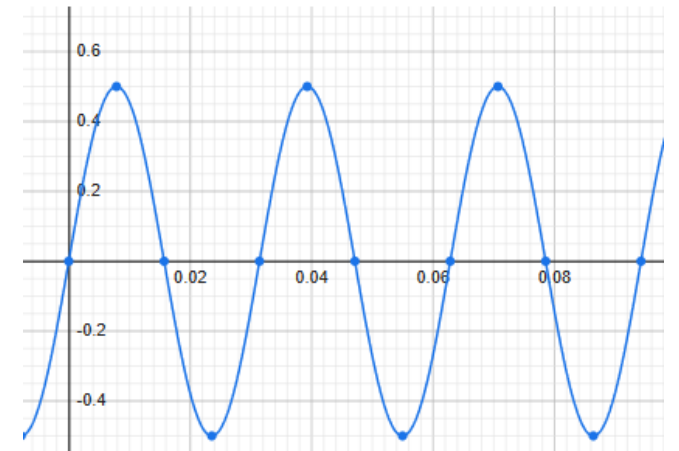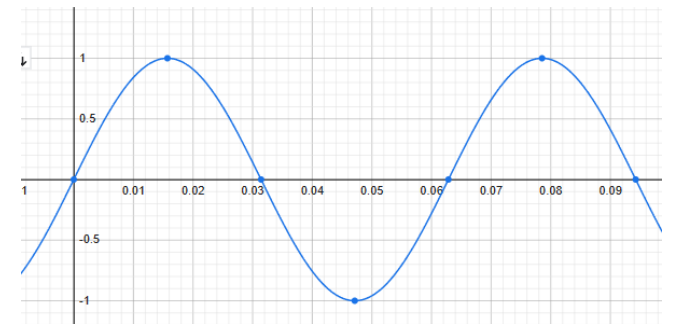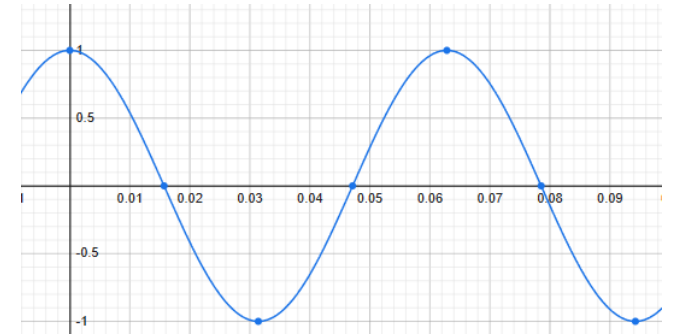Average power absorbed by inductor is zero



# Average power in Capacitor

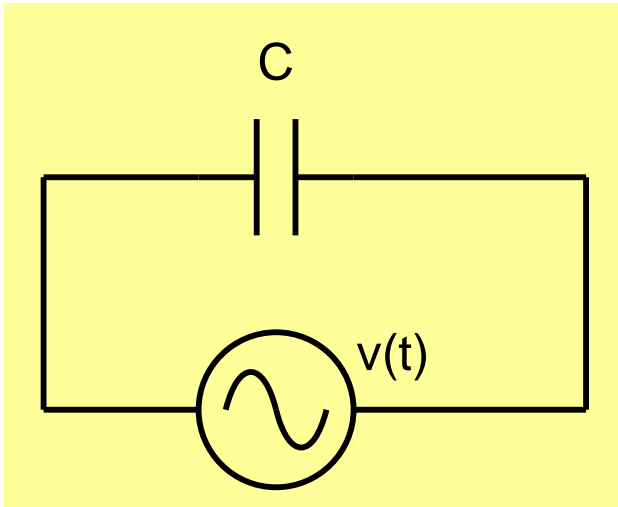

$$p(t) = v(t)i(t) = -V_m I_m \cos(\omega t) \sin(\omega t)$$


$$= -\frac{V_m I_m}{2} \sin(2\omega t)$$

$$p_{avg} = 0$$

Average power absorbed by capacitor is zero




# Inductive and Capacitive loads

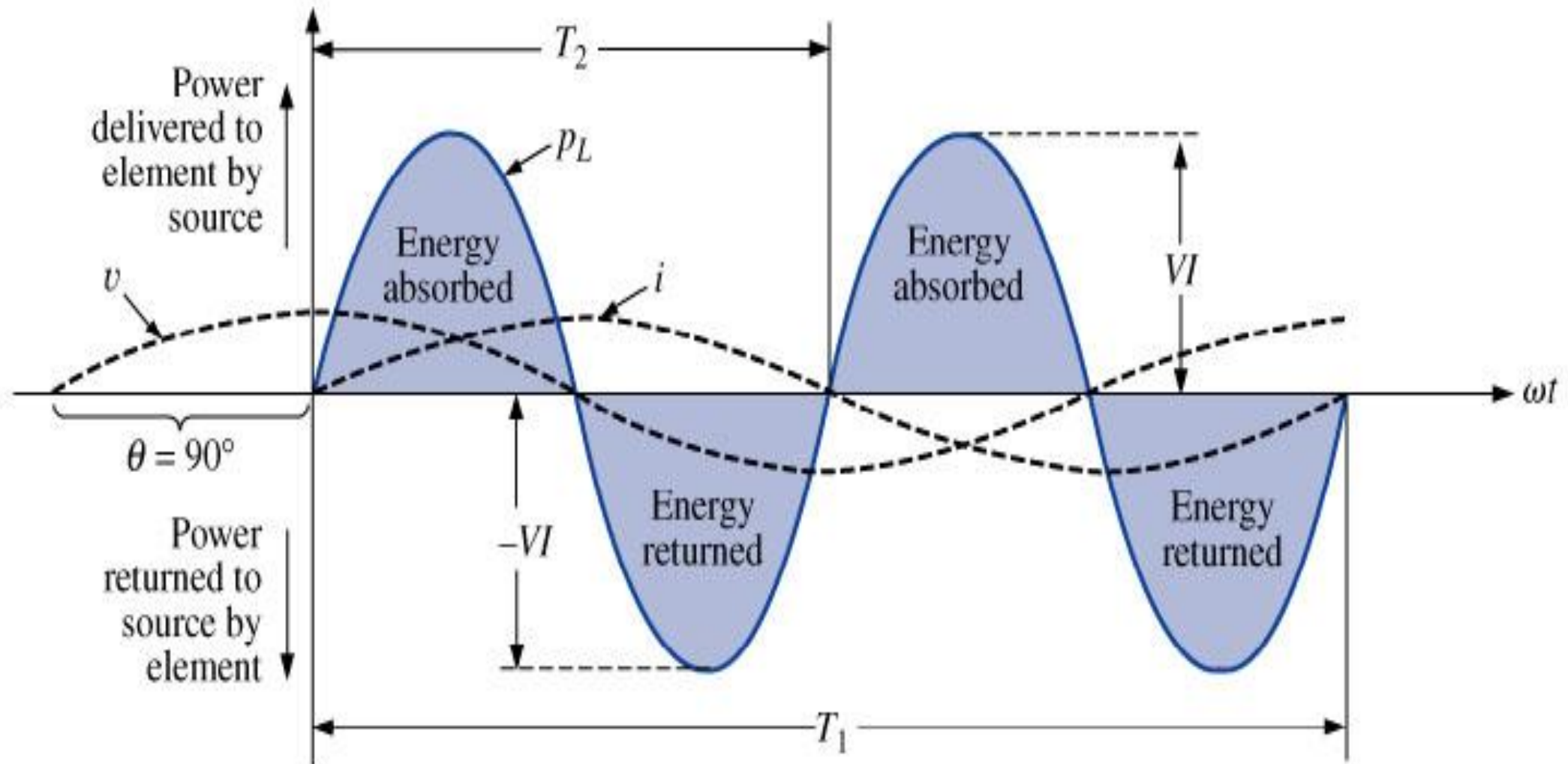

# Average Power in Circuits with Impedances

$$I = \frac{V}{Z} = \frac{V_m \angle 0^\circ}{|Z| \angle \theta} = I_m \angle -\theta$$

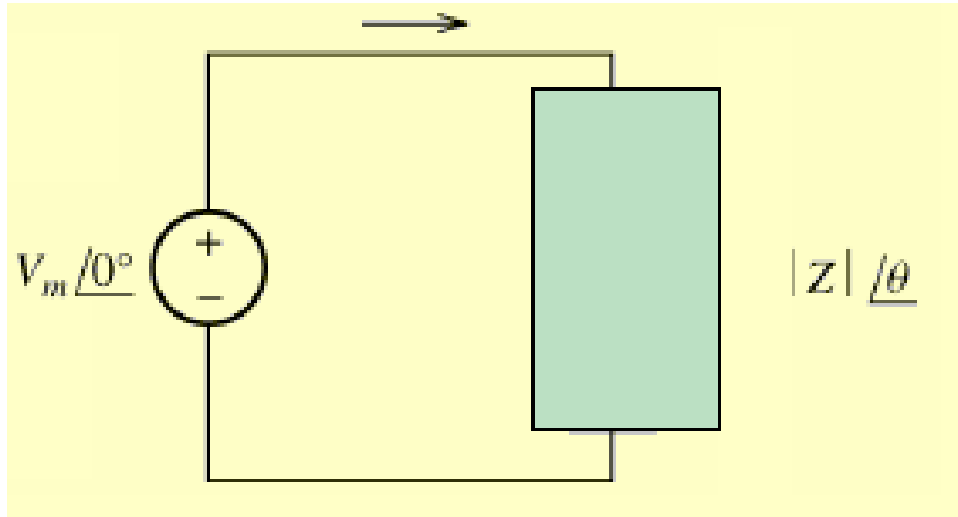

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$\frac{1}{T} \int_0^T \cos \omega t \cos \omega t + \theta \, dt = \frac{1}{2} \cos \theta$$

$$p_{avg} = \frac{1}{T} \int_0^T v(t) i(t) \, dt$$

$$p_{avg} = \frac{1}{T} \int_0^T V_m \cos(\omega t) I_m \cos(\omega t - \theta) \, dt$$

$$p_{avg} = V_m I_m \frac{1}{2} \cos \theta = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \theta$$

$$p_{avg} = V_{rms} I_{rms} \cos \theta$$

**Power factor**


$$I_m = \frac{V_m}{|Z|}$$

$$I_{rms} = \frac{V_{rms}}{|Z|}$$

$$\text{PF} = 1: R$$

$$\text{PF} = 0: L \text{ or } C$$

# Example

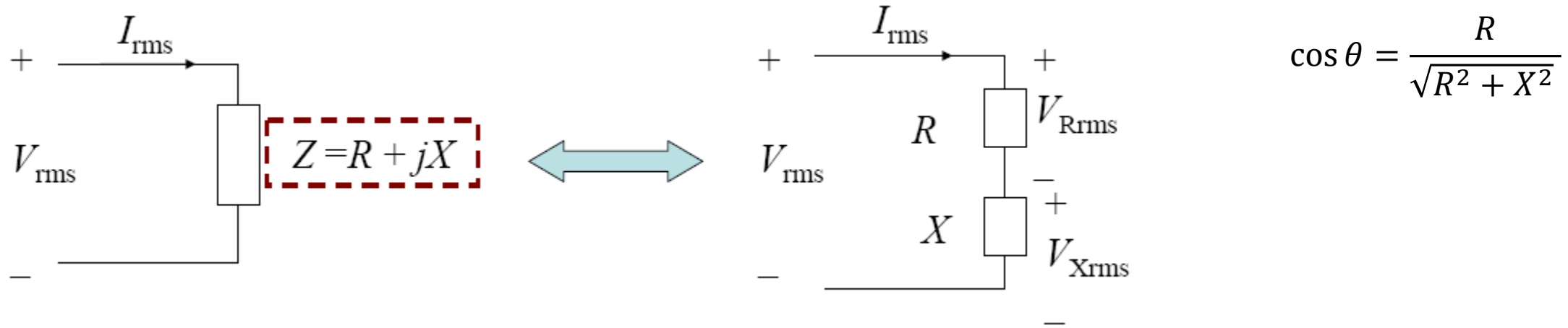

Average power consumed by  $Z$


$$\begin{aligned} p_{avg} &= V_{rms} I_{rms} \cos \theta = I_{rms} |Z| I_{rms} \frac{R}{\sqrt{R^2 + X^2}} \\ &= I_{rms}^2 R = \frac{V_{R,rms}^2}{R} \end{aligned}$$

RMS Voltage  
across  $R$

=Average power consumed by  $R$
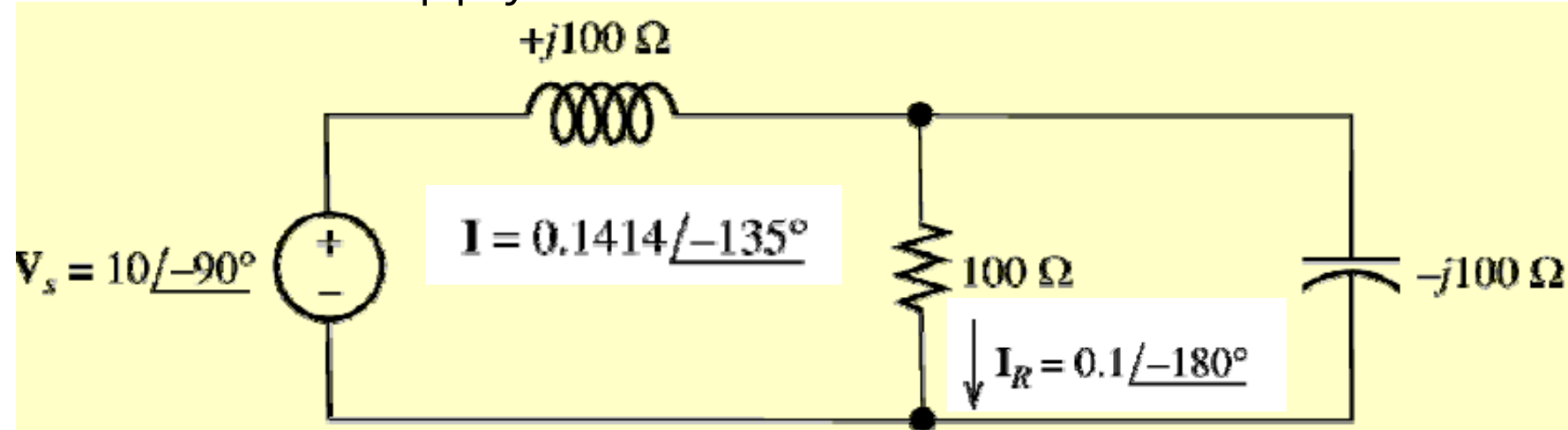
# Example

Find the average power drawn from the supply.



$$P = V_{rms} I_{rms} \cos(\theta)$$

$$V_{rms} = \frac{|V_s|}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.071V$$

$$\begin{aligned} P &= V_{rms} I_{rms} \cos(\theta) \\ &= 7.071 \times 0.1 \times \cos(45^\circ) \\ &= 0.5 \text{ W} \end{aligned}$$



$$I_{rms} = \frac{|I|}{\sqrt{2}} = \frac{0.1414}{\sqrt{2}} = 0.1A$$

Where is this power dissipated?


$$I_{Rrms} = \frac{0.1}{\sqrt{2}} = 0.071$$

$$P = I_{Rrms}^2 \times R = 0.5W$$

# Charge for reactive power?

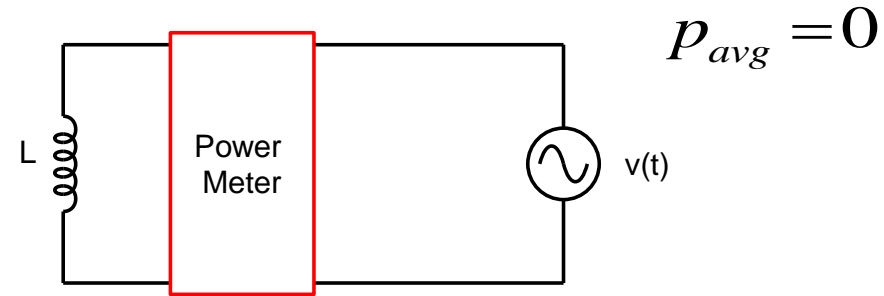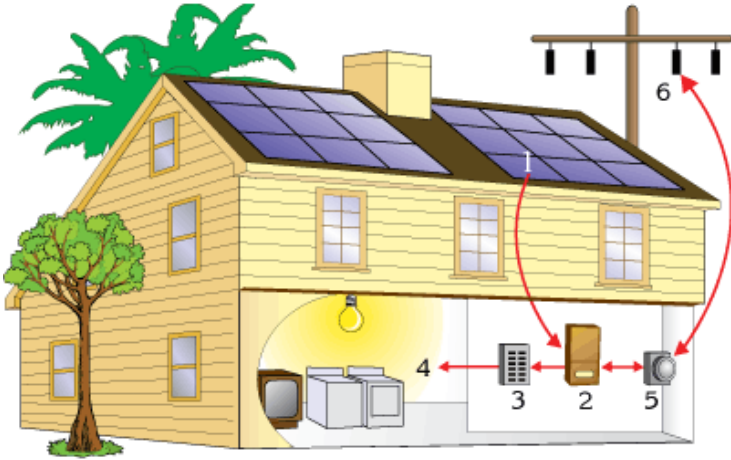

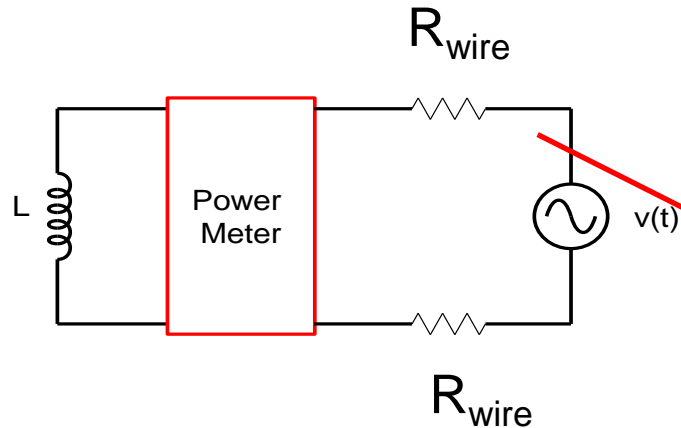Should a power company charge a person even though power consumed is zero?



Power is dissipated  
There is a cost for generation of this power.

# Average & reactive power

Average power:  $P = V_{\text{rms}} I_{\text{rms}} \cos \theta$

Reactive power:  $Q = V_{\text{rms}} I_{\text{rms}} \sin \theta$

(Volt Amperes Reactive (VAR))


Apparant power:  $V_{\text{rms}} I_{\text{rms}}$ , Units: volt-amperes (VA)

$$\begin{aligned} P^2 + Q^2 &= V_{\text{rms}}^2 I_{\text{rms}}^2 \cos^2(\theta) + V_{\text{rms}}^2 I_{\text{rms}}^2 \sin^2(\theta) \\ &= (V_{\text{rms}} I_{\text{rms}})^2 \\ &= (\text{Apparant power})^2 \end{aligned}$$

$$\text{Apparant power} = \sqrt{P^2 + Q^2}$$

- No average power is consumed in a pure inductive/capacitive load
- But reactive power has current associated with it and causes loss of power in transmission lines
- Power companies charge their industrial customers for reactive power.

# Apparent Power

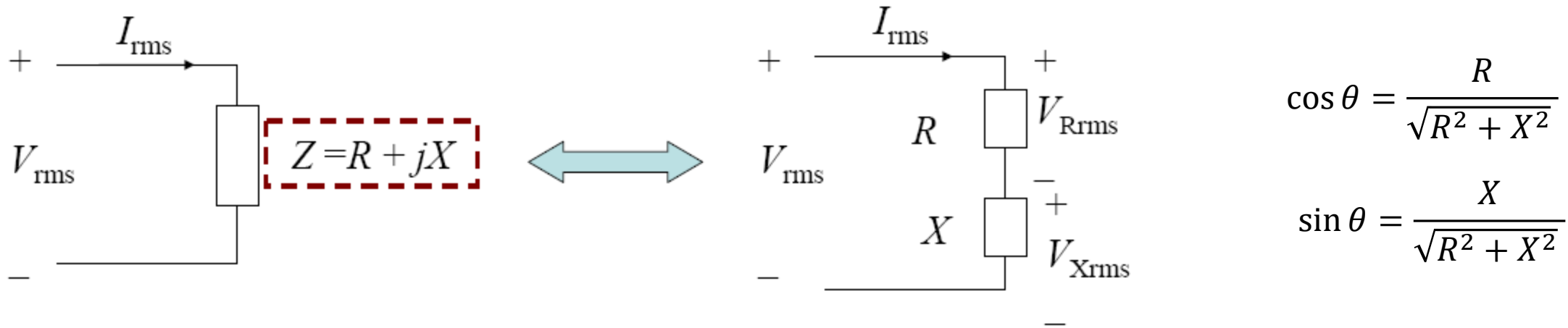

Reactive power

$$q_{avg} = V_{rms} I_{rms} \sin \theta = I_{rms} |Z| I_{rms} \frac{X}{\sqrt{R^2 + X^2}}$$


$$= I_{rms}^2 X = \frac{V_{X,rms}^2}{X}$$

RMS Voltage  
across  $X$

= Reactive power at  $X$


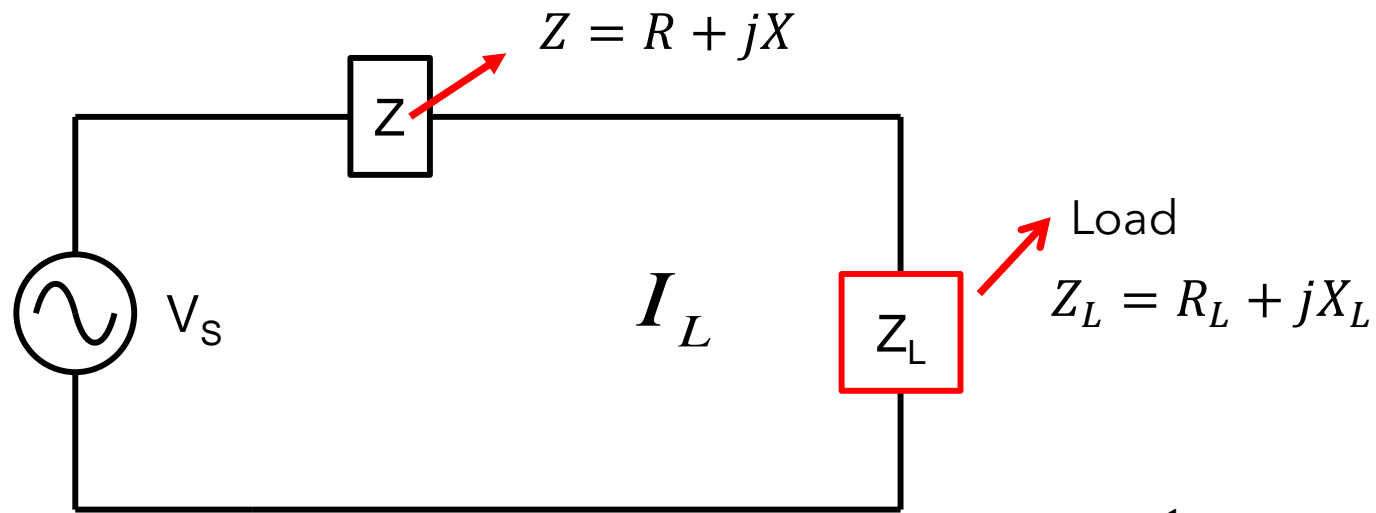
# Maximum power transfer for sinusoidal input



$$I_L = \frac{V_s}{R + R_L + j(X + X_L)}$$

$$I_{L,rms} = \frac{1}{\sqrt{2}} \frac{V_s}{|R + R_L + j(X + X_L)|}$$

$$P_L = \frac{1}{2} \frac{V_s^2}{(R + R_L)^2 + (X + X_L)^2} R_L$$

To maximize  $P_L$

$$X_L = -X$$

$$R_L = R$$

$$Z_L = \bar{Z}$$

$$P_L = \frac{1}{2} \frac{V_s^2}{(R + R_L)^2} R_L$$

$$P_L = \frac{1}{8} \frac{V_s^2}{R}$$