

# ESC201: INTRODUCTION TO ELECTRONICS


## MODULE 3: FREQUENCY DOMAIN ANALYSIS





Dr. Shubham Sahay,  
Assistant Professor,  
Department of Electrical Engineering,  
IIT Kanpur
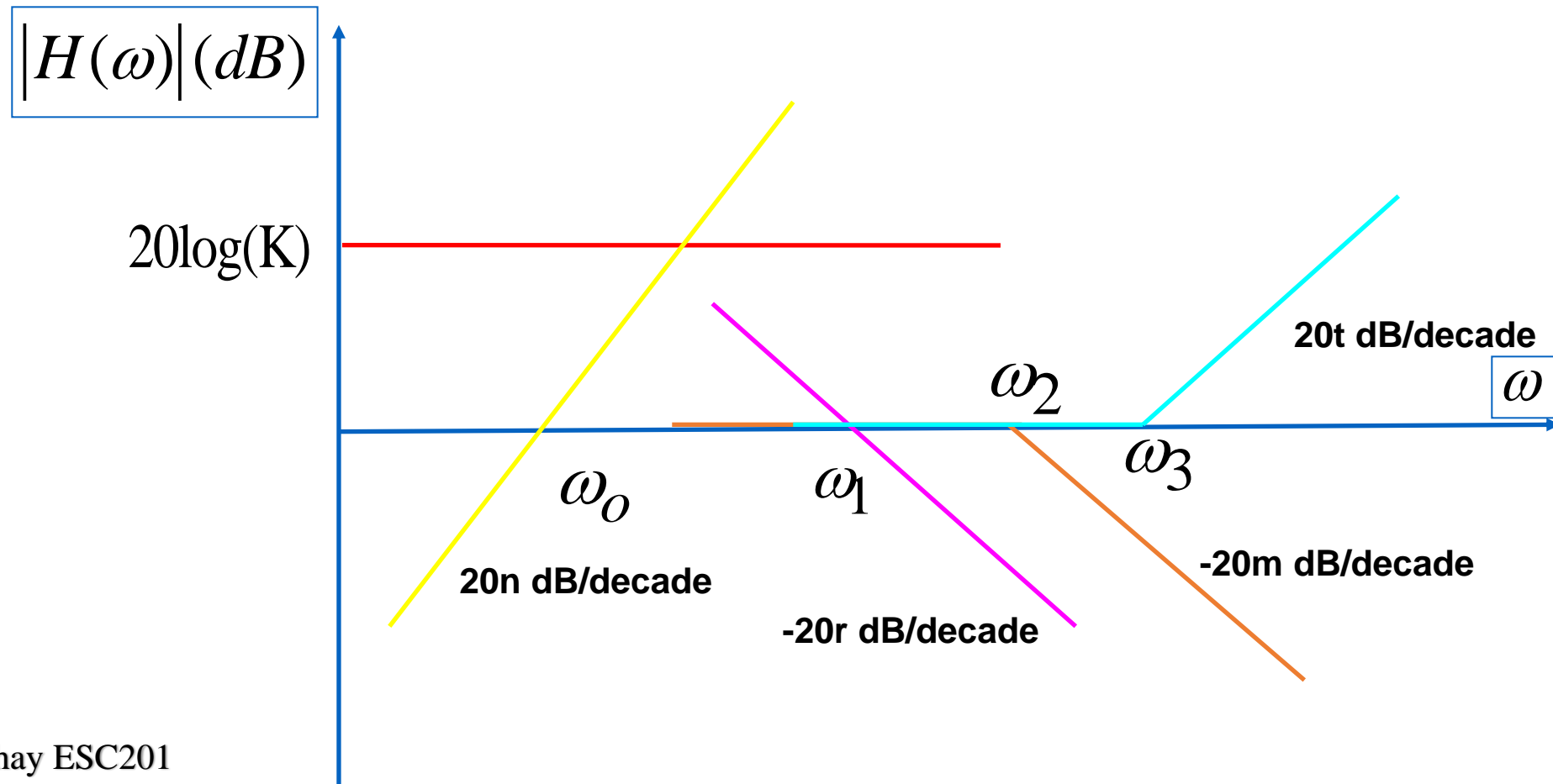
# Bode Plot


$$H(\omega) = K \times j(\omega / \omega_o)^n \times \frac{1}{j(\omega / \omega_1)^r} \times \frac{1}{\{1 + j(\omega / \omega_2)\}^m} \times \{1 + j(\omega / \omega_3)\}^t$$




# Recall Example

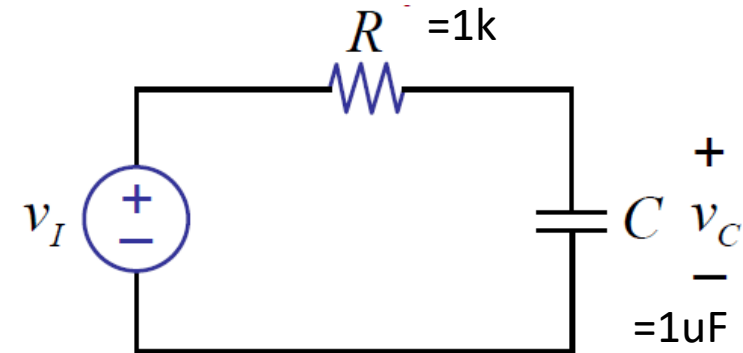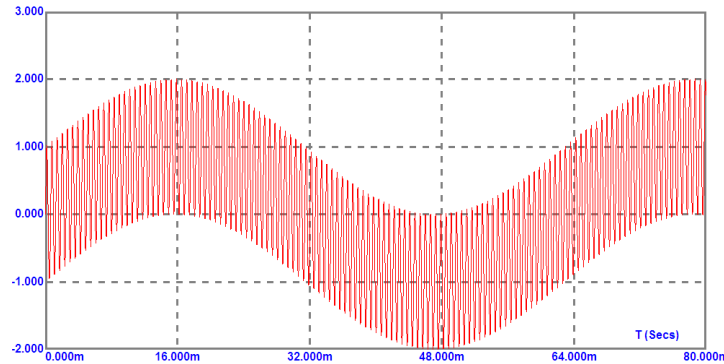




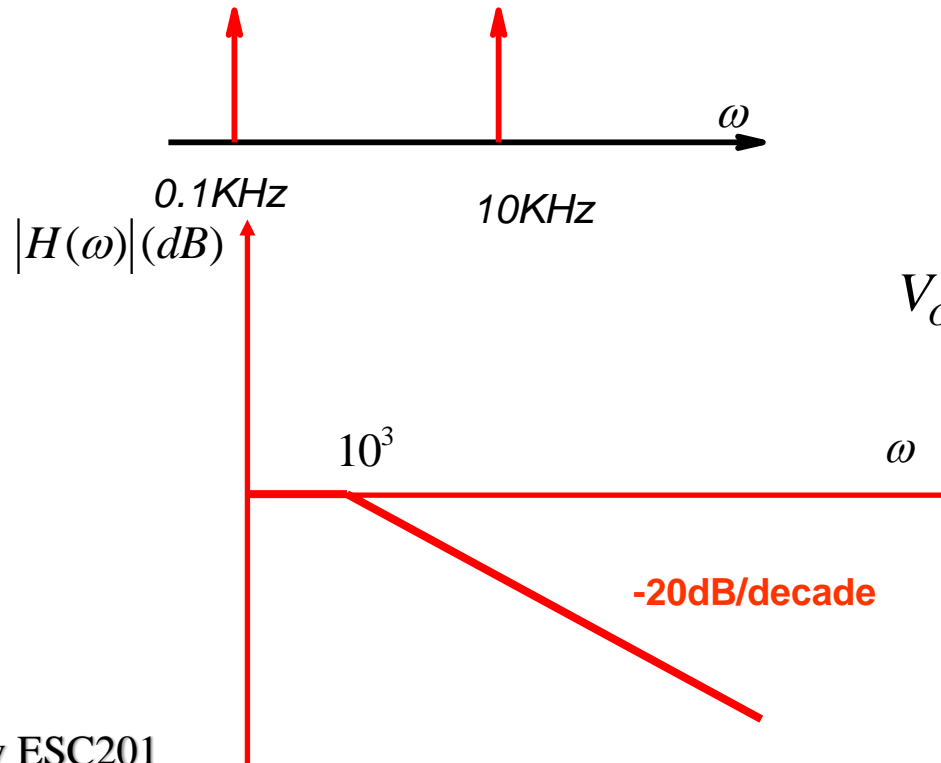
$$H(\omega) = \frac{1}{1 + j\omega 10^{-3}} = \frac{1}{1 + j\frac{\omega}{10^3}}$$



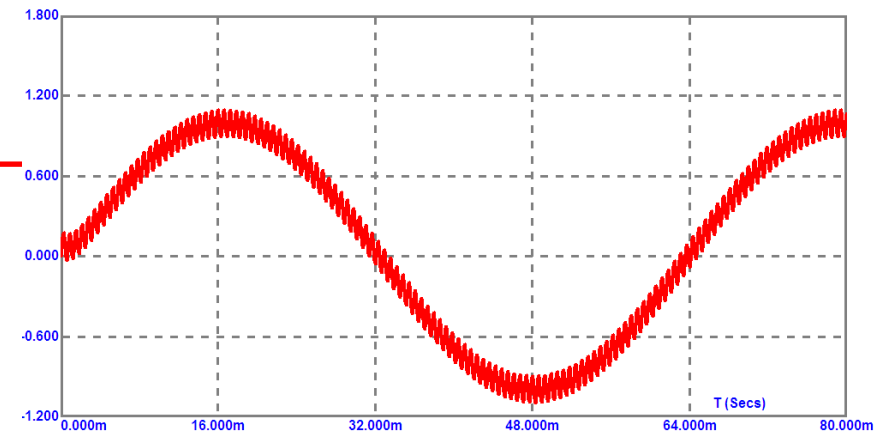
$$V_o(t) = 1\sin(100t) + 0.1\sin(10^4 t)$$



# Example: low pass filter...

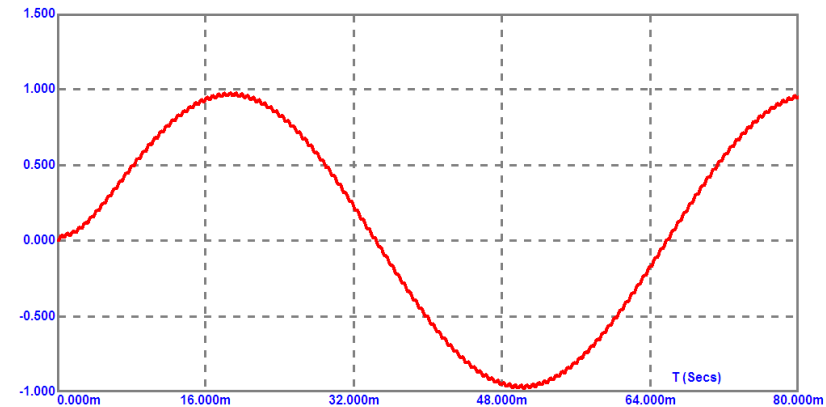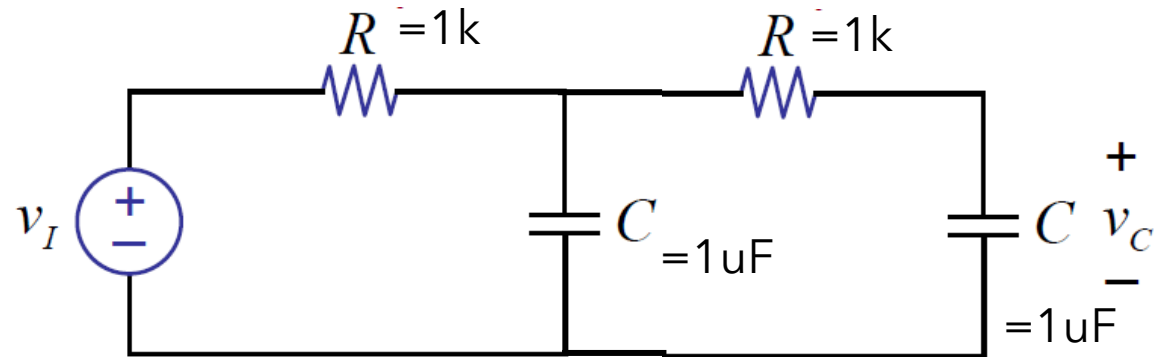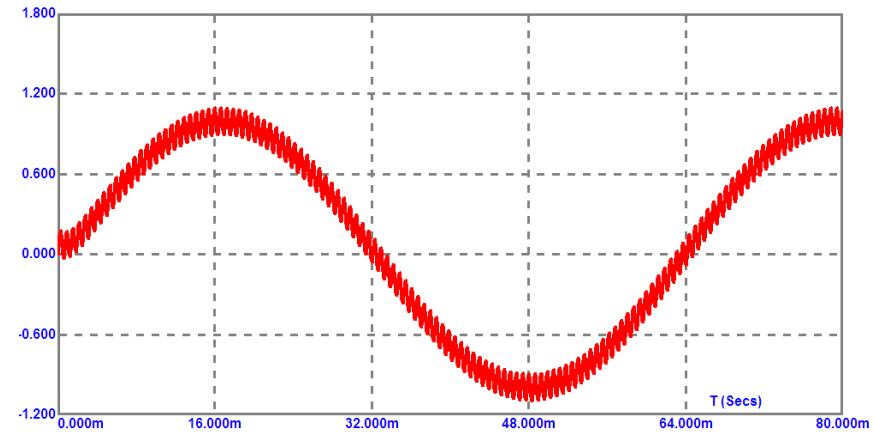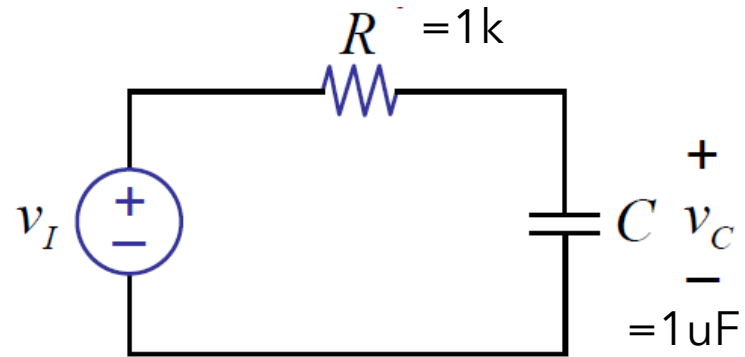


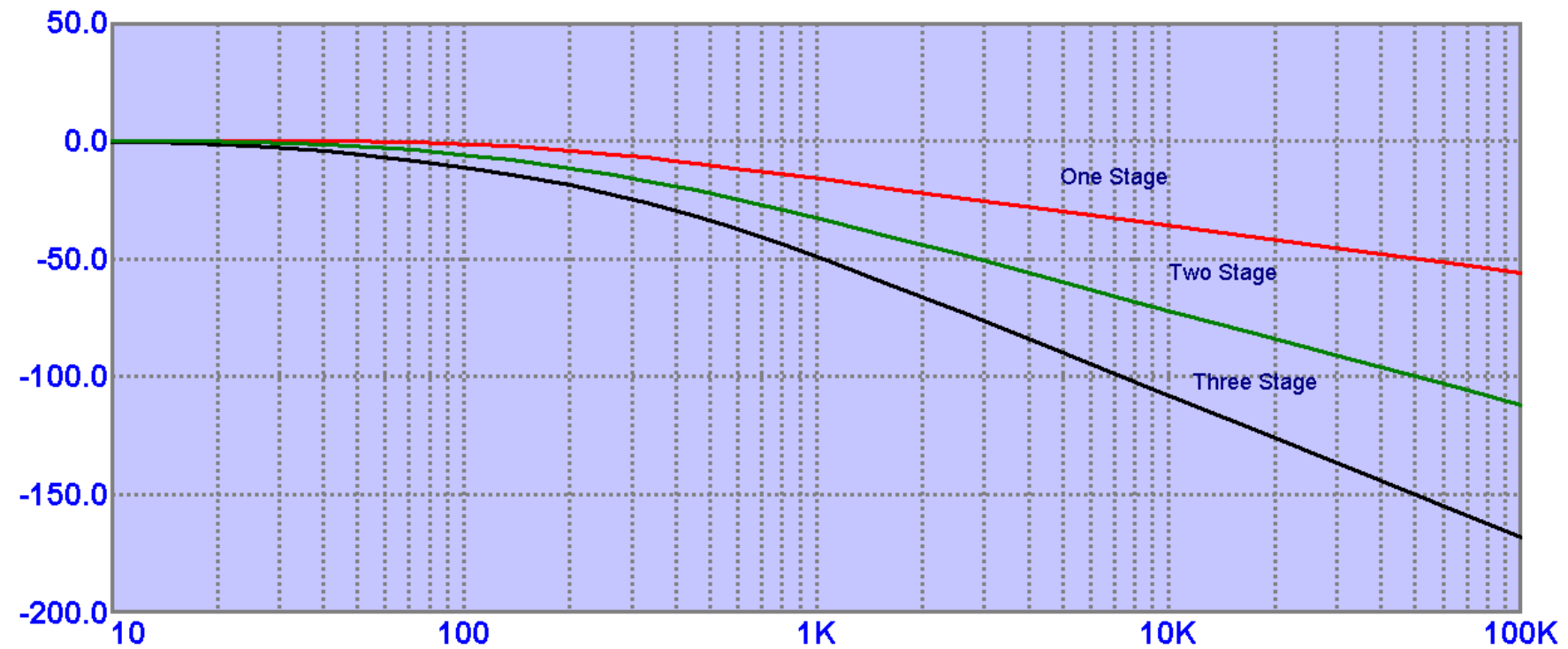Adding more RC stages, makes the characteristics sharper






# Filters

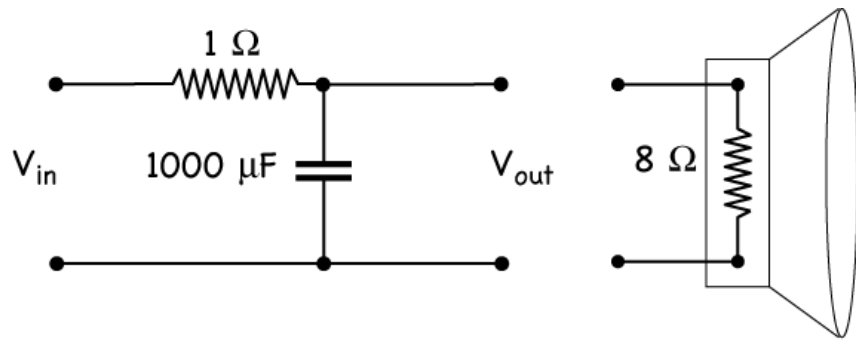

Low-Pass Audio Filter




Removing Noise from Images

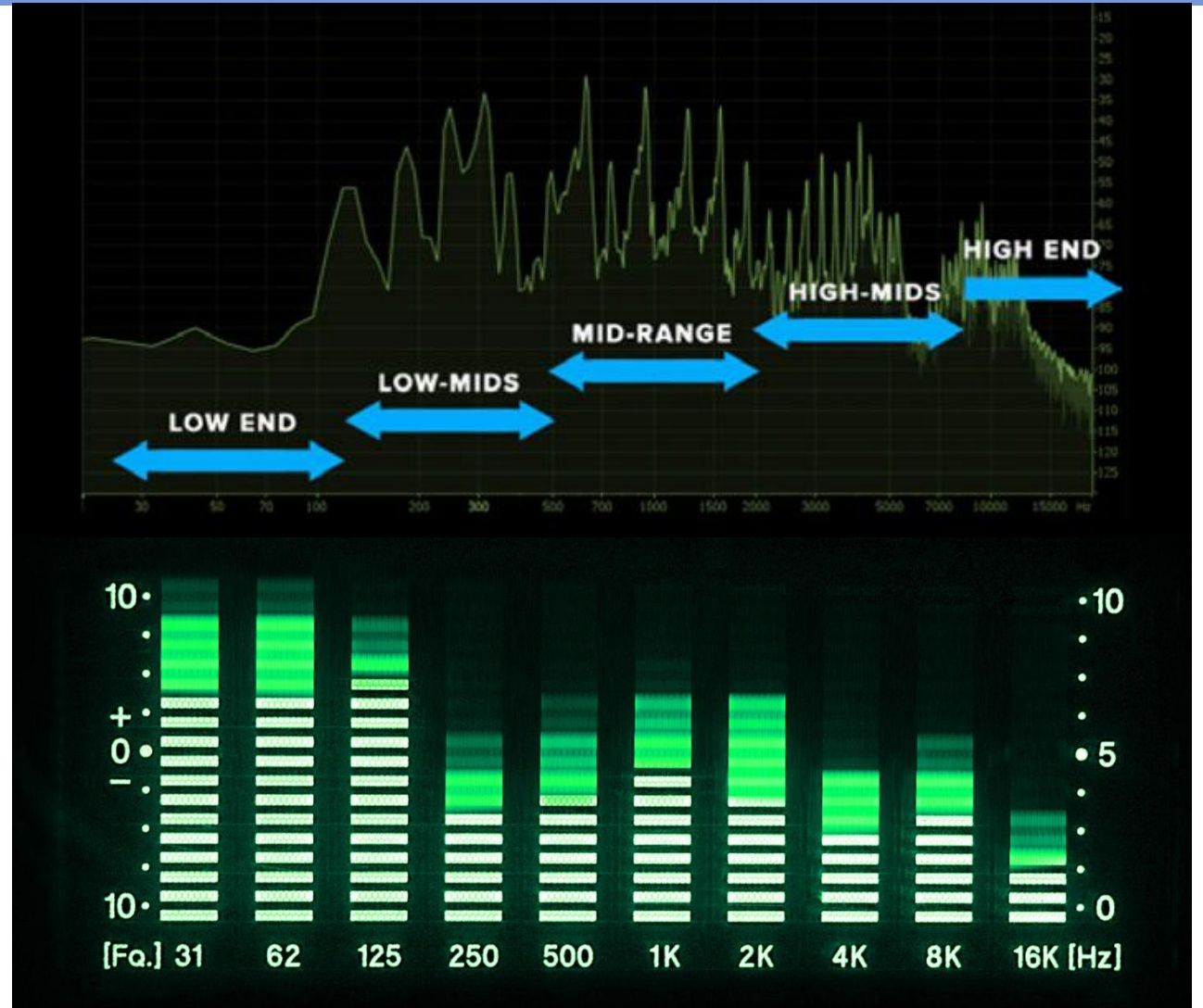

Equalization of Sound




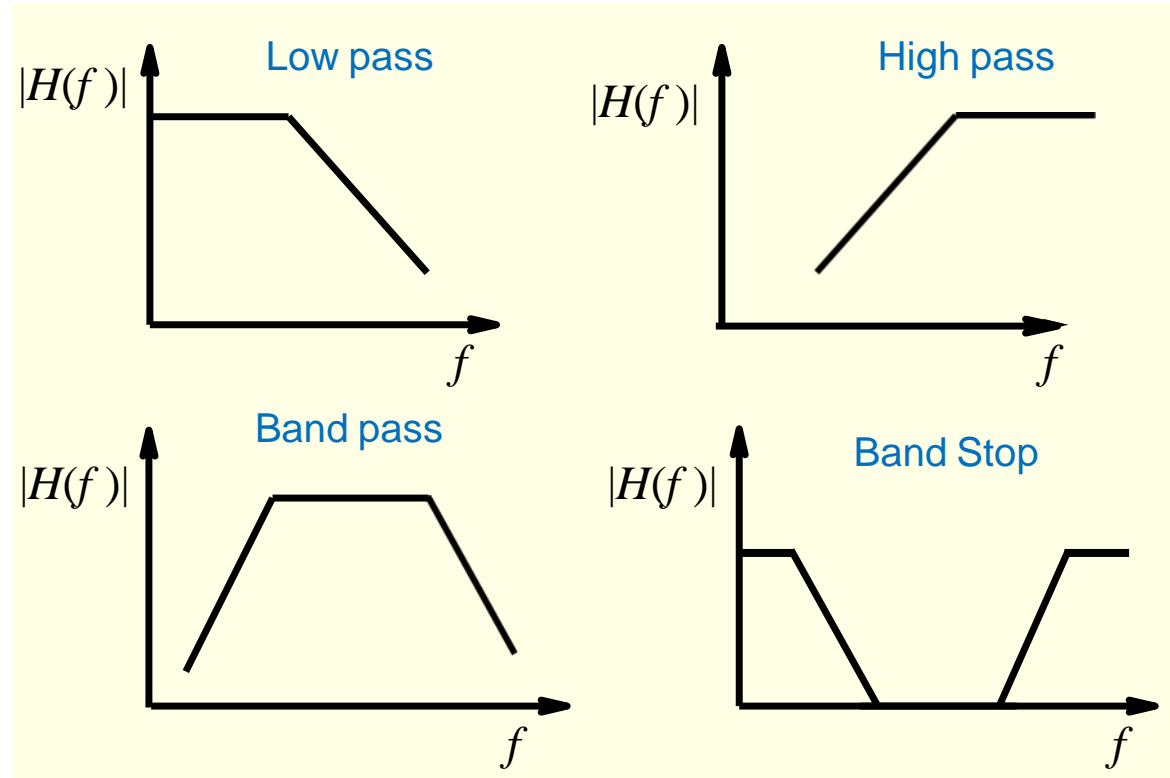
# Filters for Electrical Signals

**Filter** – pass / amplify signal in a band of frequency and reject / attenuate the remaining



- Many practical applications in electronics and electrical systems
- Tuning radios, cleaning up communication signals, removing higher frequencies from power systems, ... + many other areas


# RC Filters

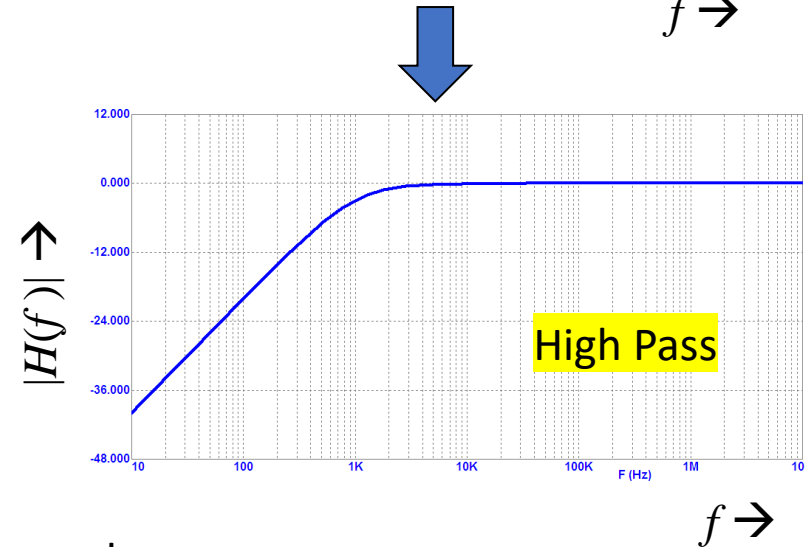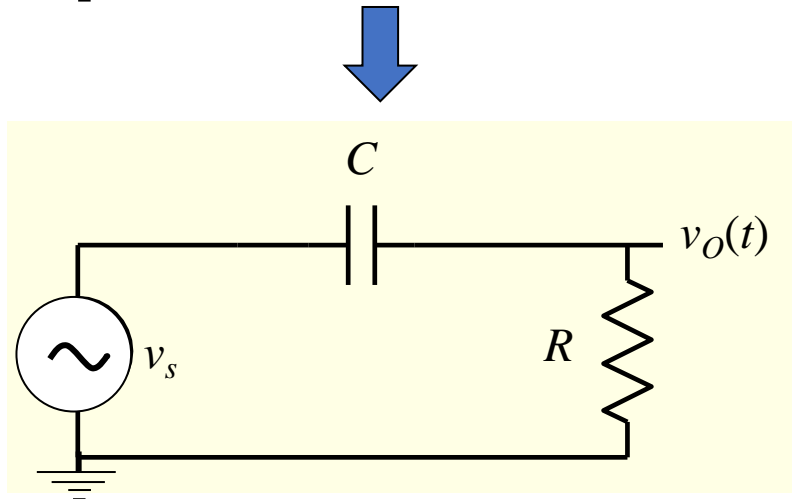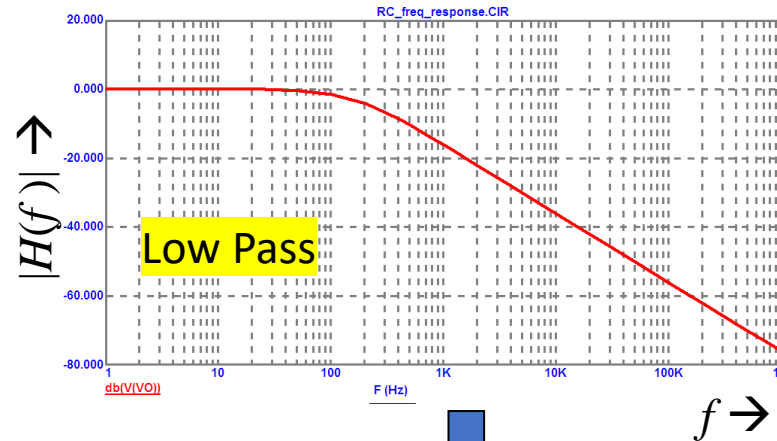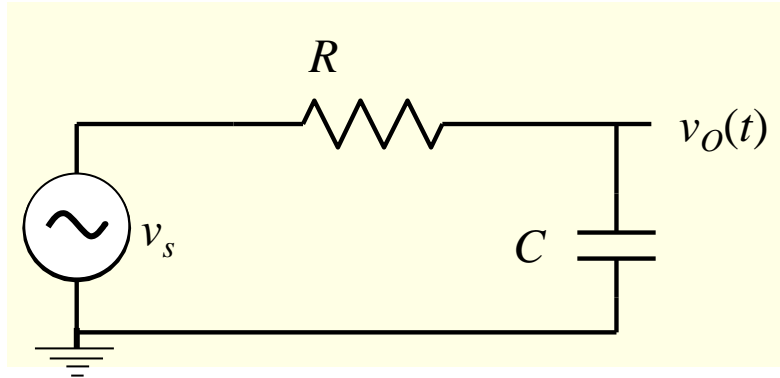


- Capacitor and resistor positions are swapped
- Low pass becomes high pass filter!
- In both cases  $\omega_{3dB} = (R \cdot C)^{-1} \rightarrow f_{3dB} = (2\pi \cdot R \cdot C)^{-1}$



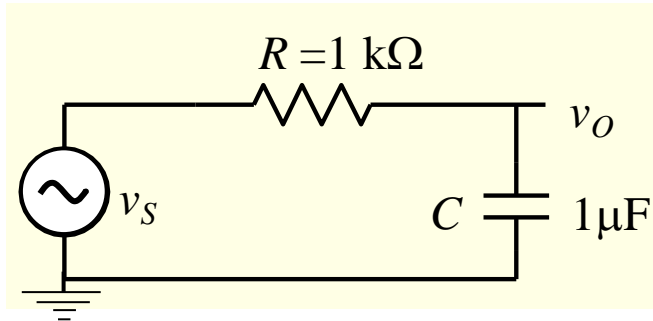
# Single Capacitor Circuit $\omega_{3dB}$


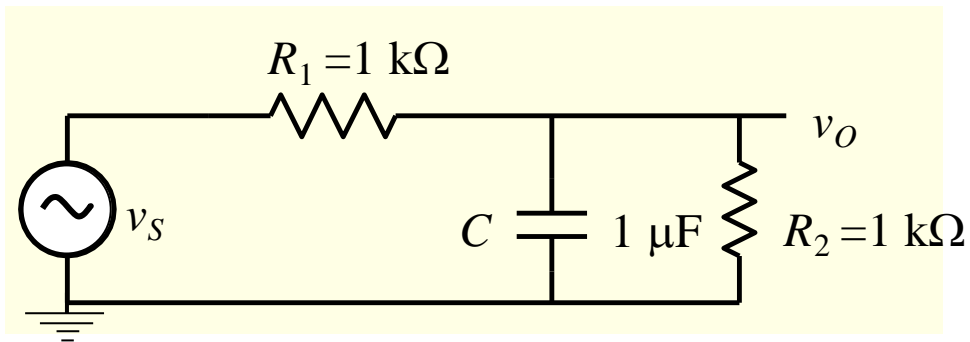
$$\omega_{3dB} = \frac{1}{RC} = 10^3 \text{ rad / s}$$



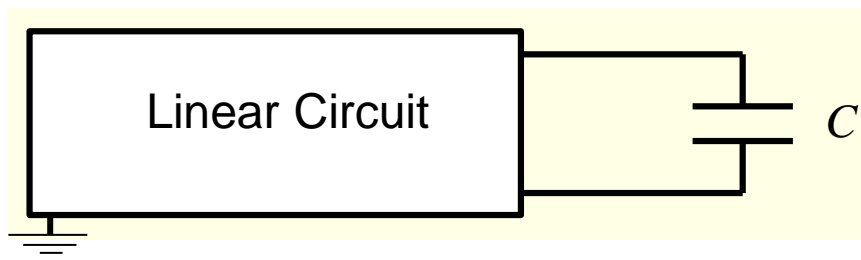
$$\omega_{3dB} = \frac{1}{R_1 \parallel R_2 C}$$



$$\omega_{3dB} = \frac{1}{\tau} = \frac{1}{R_{eq} C}$$


Find Thévenin resistance across the capacitance to find  $R_{eq}$  in time constant

# Asymptotic Behaviour

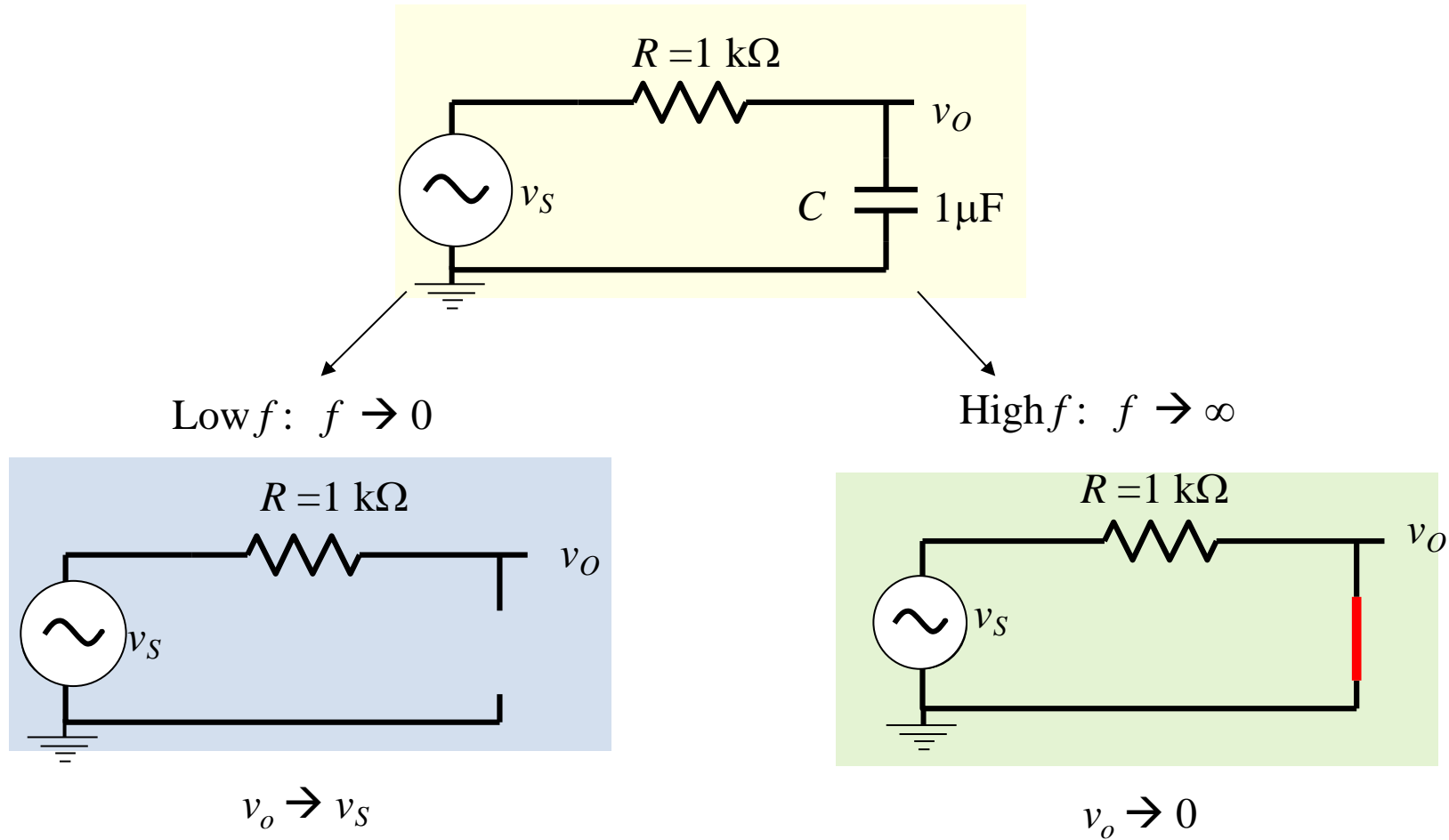


Clear hints of a low-pass filter behaviour!
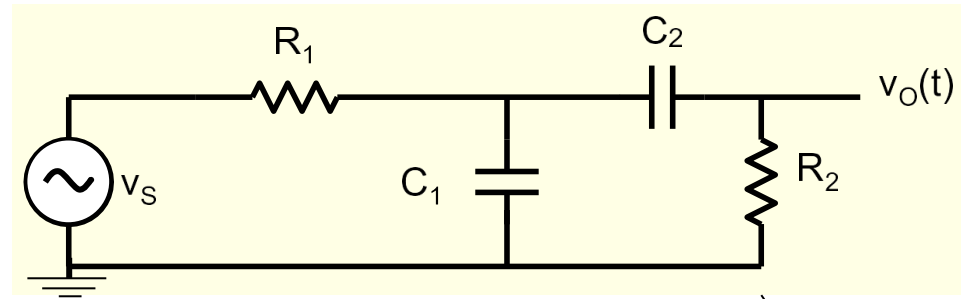
# Circuit Attenuating High and Low Frequency




Low  $f$ :  $f \rightarrow 0$


High  $f$ :  $f \rightarrow \infty$

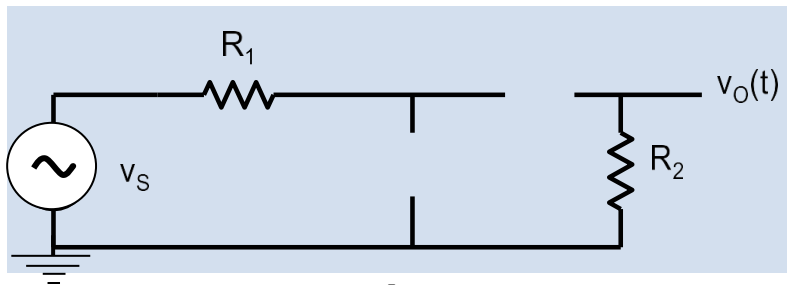

$v_o \rightarrow 0$



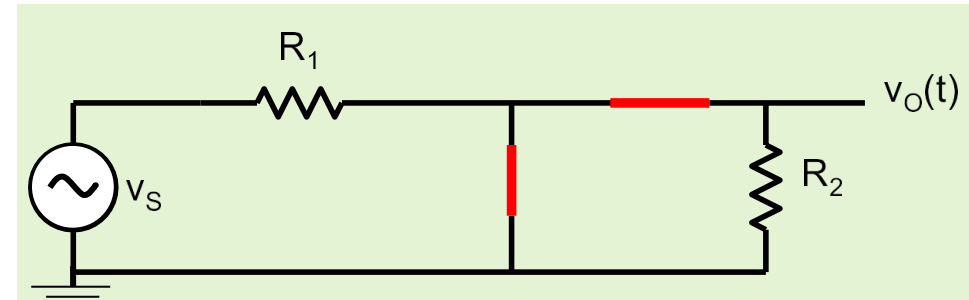


$v_o \rightarrow 0$

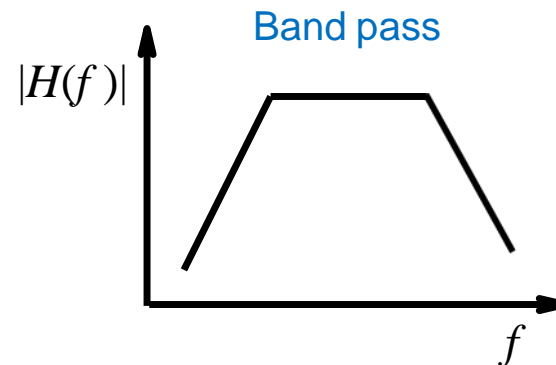

Could this be a bandpass filter?



# A Bandpass Filter

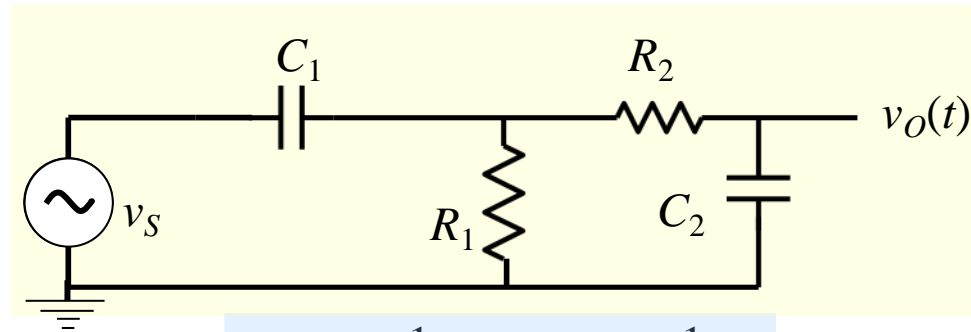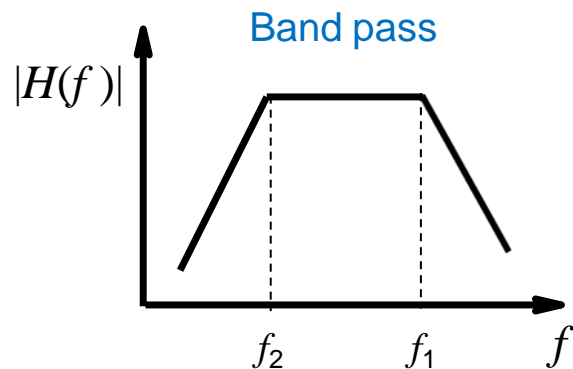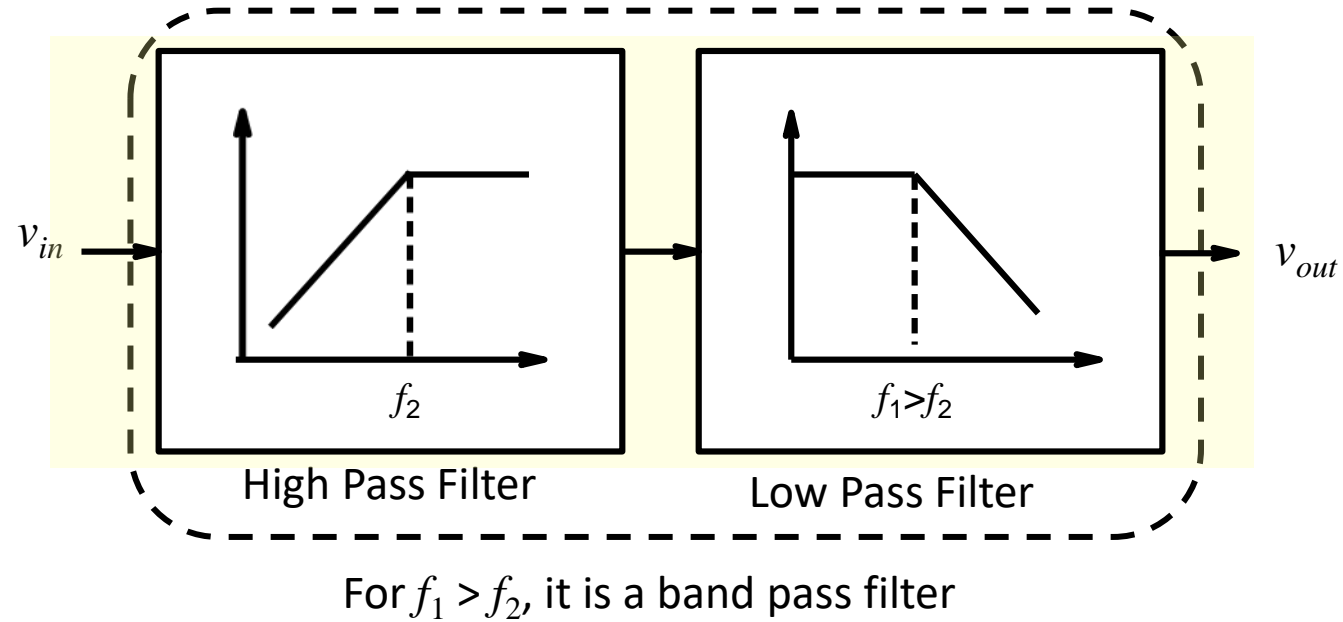


$$f_2 \cong \frac{1}{2\pi R_1 C_1} ; f_1 \cong \frac{1}{2\pi R_2 C_2}$$
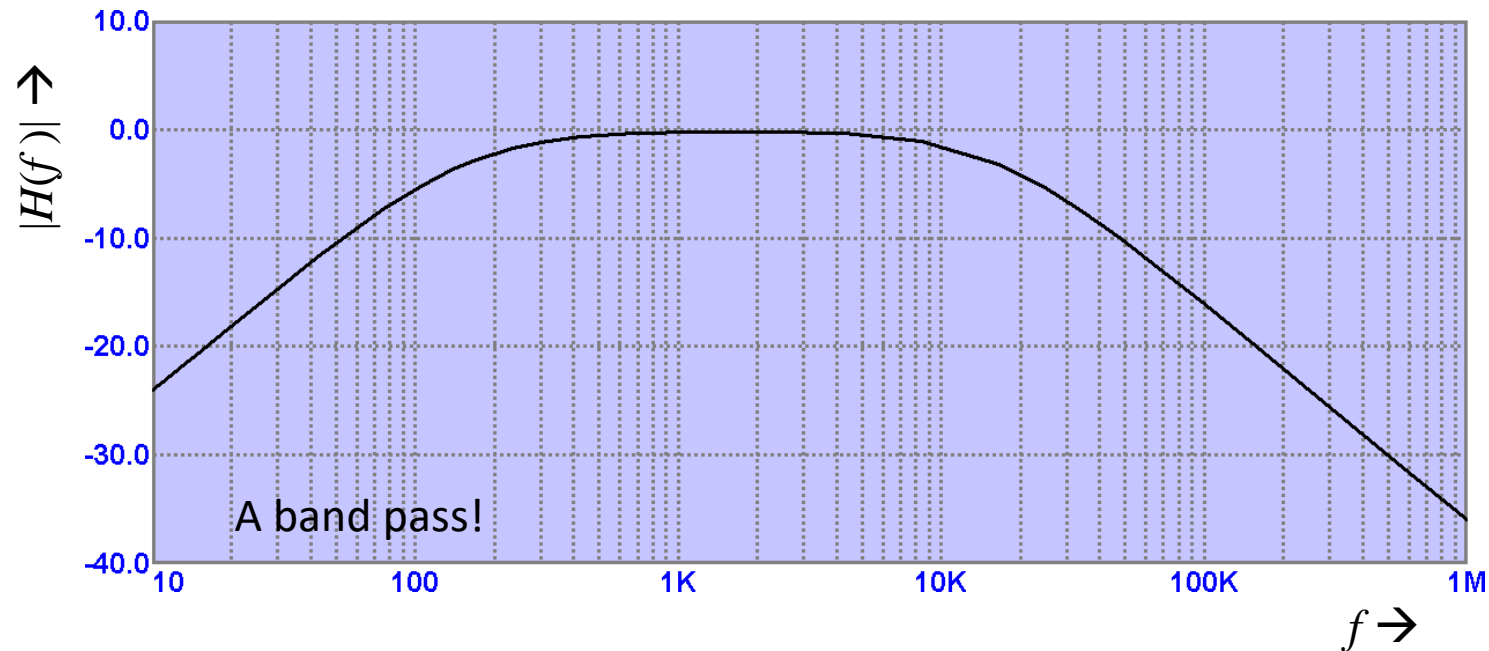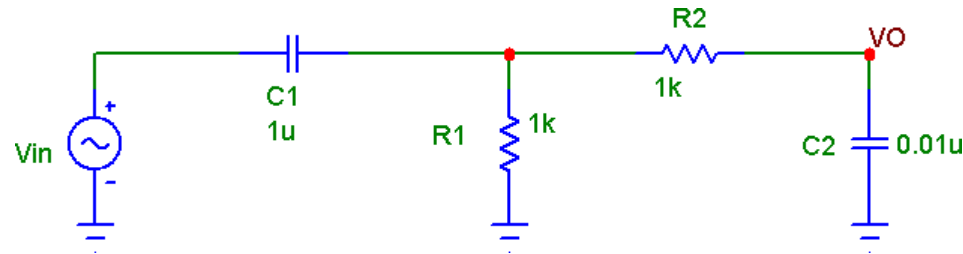
## Example: Band Pass filter


$$f_2 \cong \frac{1}{2\pi R_1 C_1} ; f_1 \cong \frac{1}{2\pi R_2 C_2}$$



# Band Stop Filter

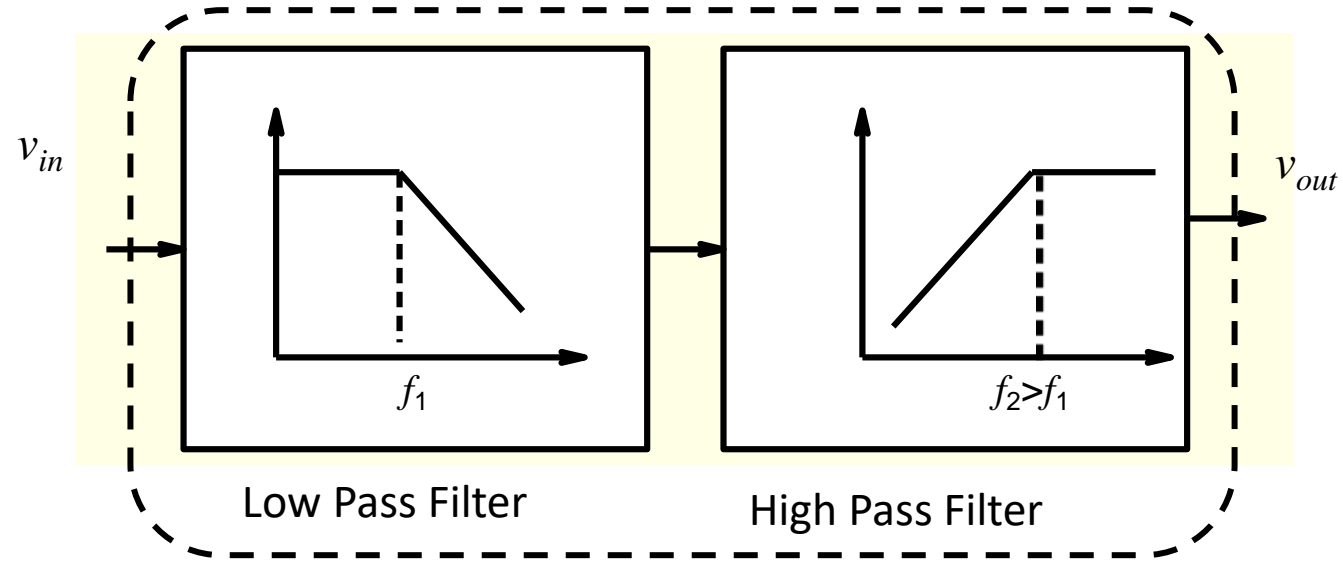

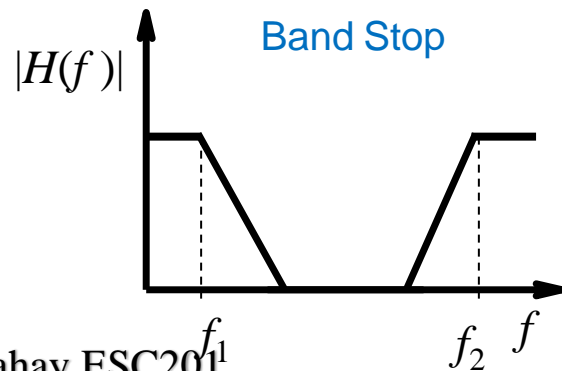For  $f_1 < f_2$ , it is a band pass filter




Will this work?



Well, it does work if designed properly!




## Example: Band Stop filter

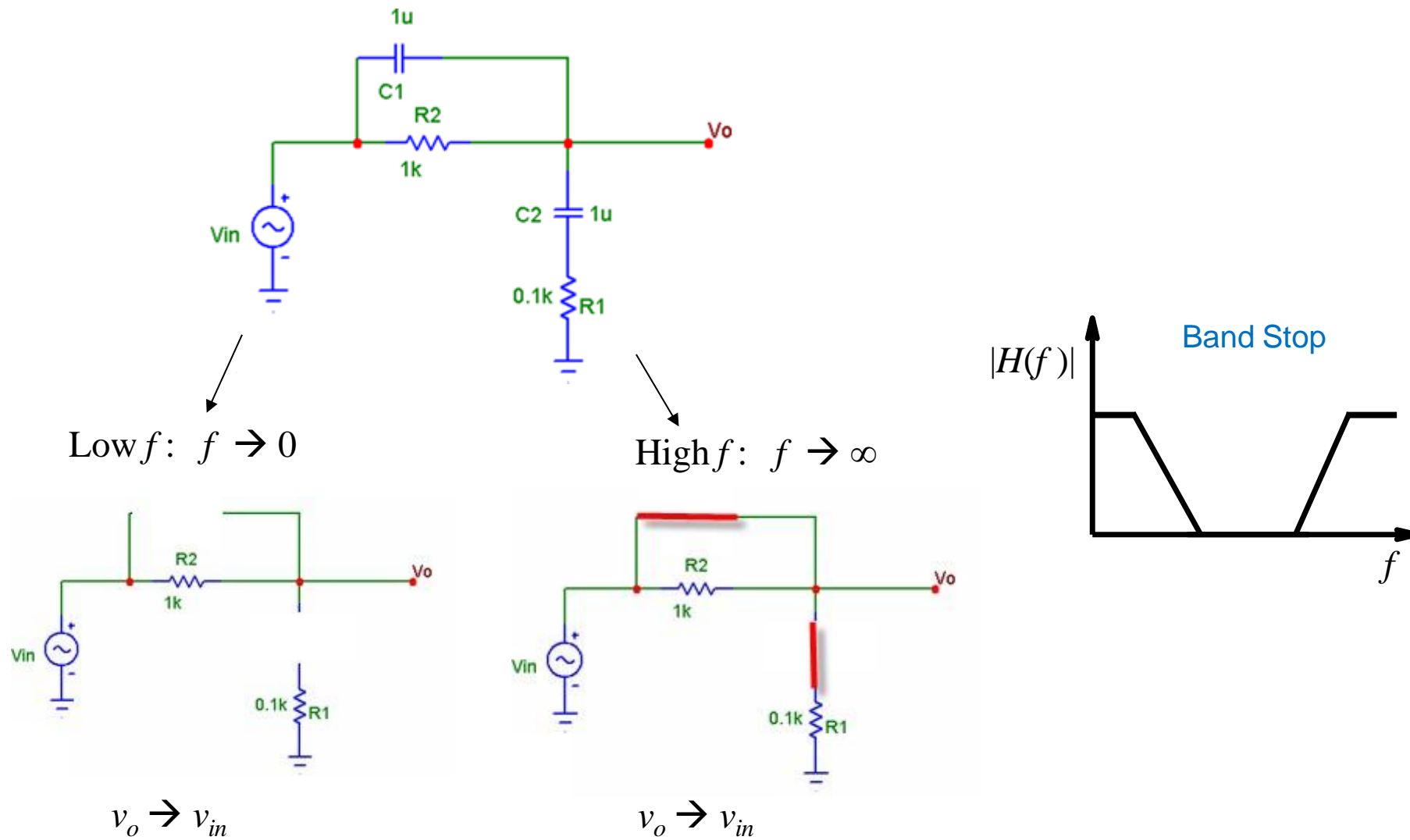

Example: Band Stop filter (continued)

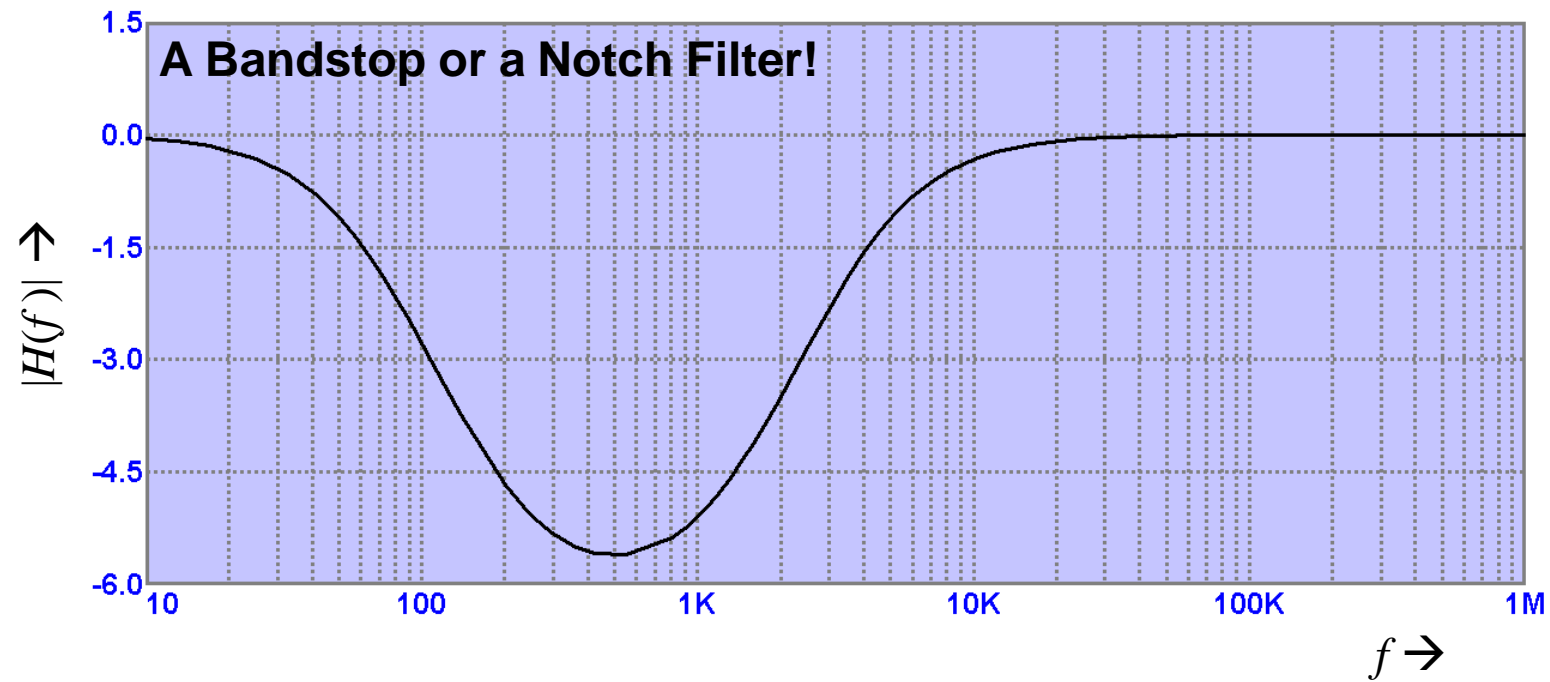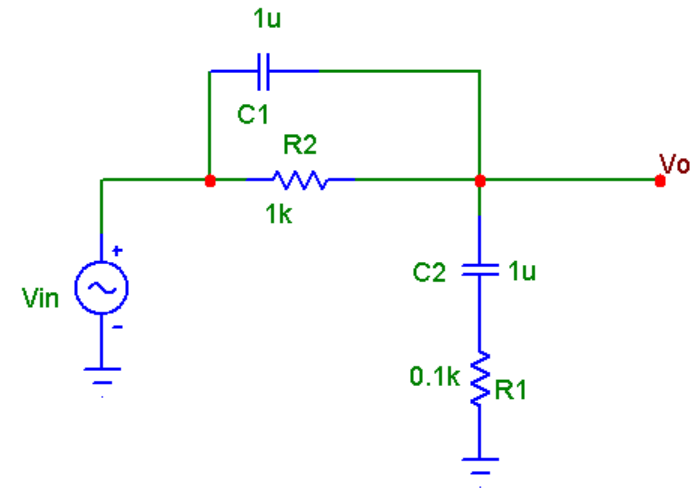


# RL High Pass Filters

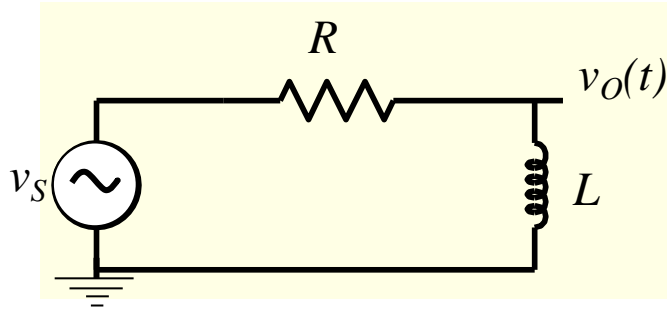


$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$

$$H(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j(\omega / \omega_{3dB})}{1 + j(\omega / \omega_{3dB})}$$

$$\omega_{3dB} = \frac{R}{L}$$

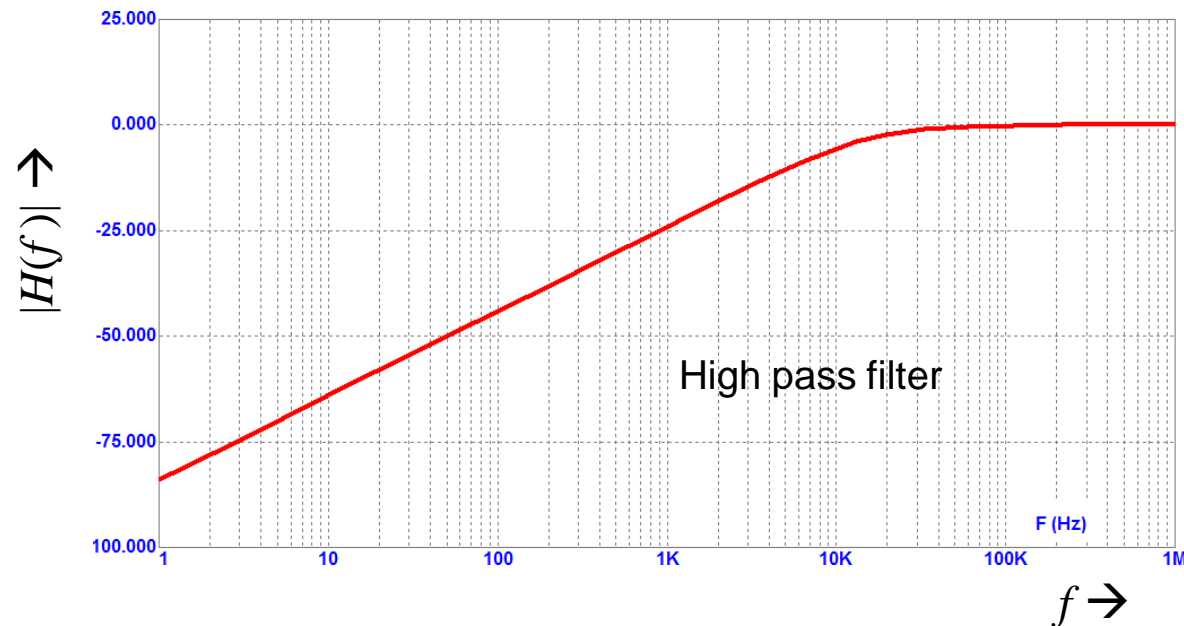


# RL Low Pass Filters

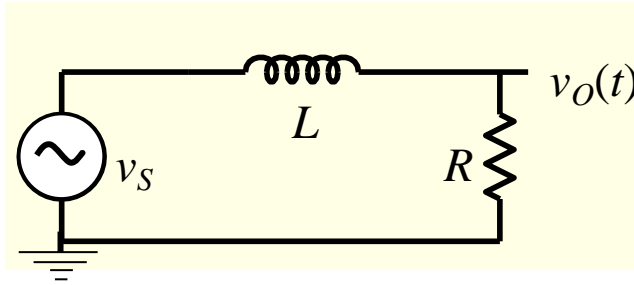

$$H(\omega) = \frac{V_O(\omega)}{V_S(\omega)}$$

$$H(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j(\omega / \omega_{3dB})}$$


$$\omega_{3dB} = \frac{R}{L}$$

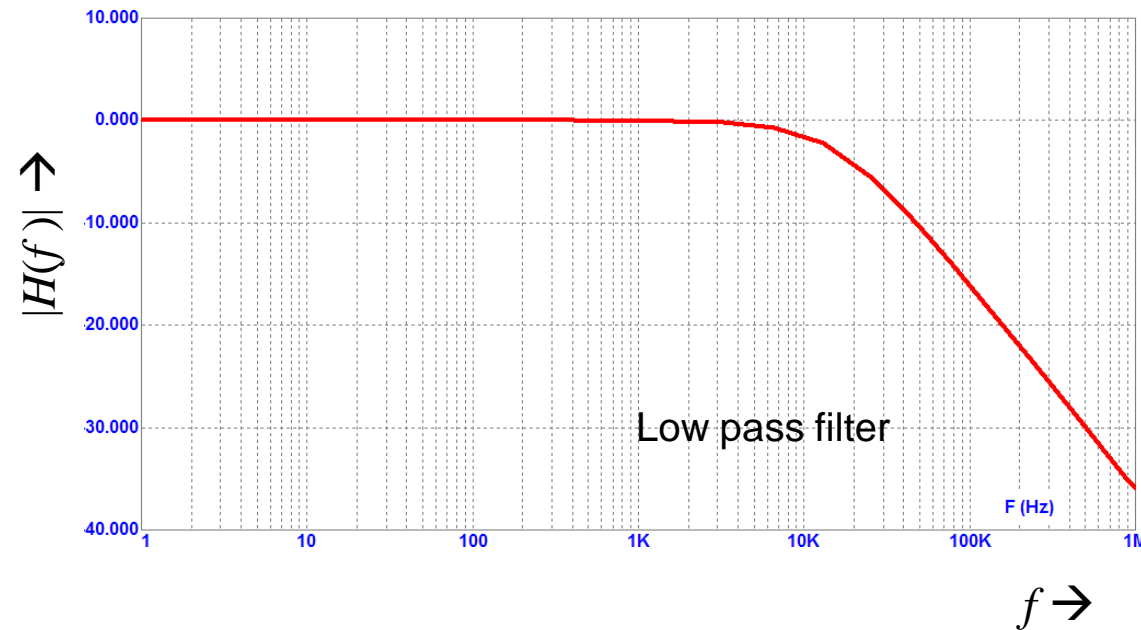

# FM Radio

Different radio channels are separated by very narrow frequency interval.

For example  
MHz) or Re

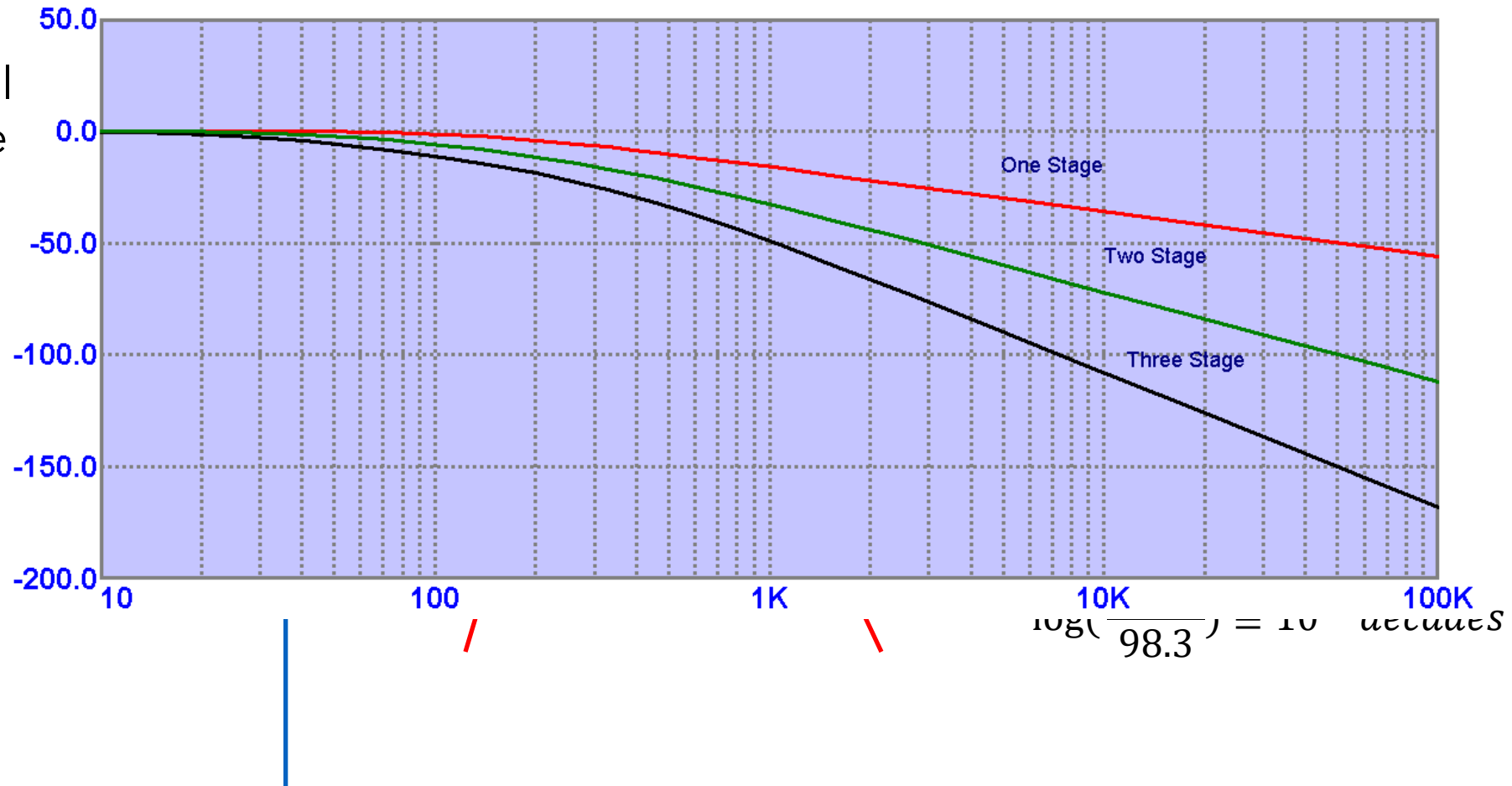

# Resonance

- Every system has its own natural frequency of oscillation.





- If you apply an external stimulus at natural frequency: System exhibits an extremely large response



# RLC Circuit

$$\frac{V_r}{V_i} = \frac{R}{j\omega L + \frac{1}{j\omega C} + R}$$

$$\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

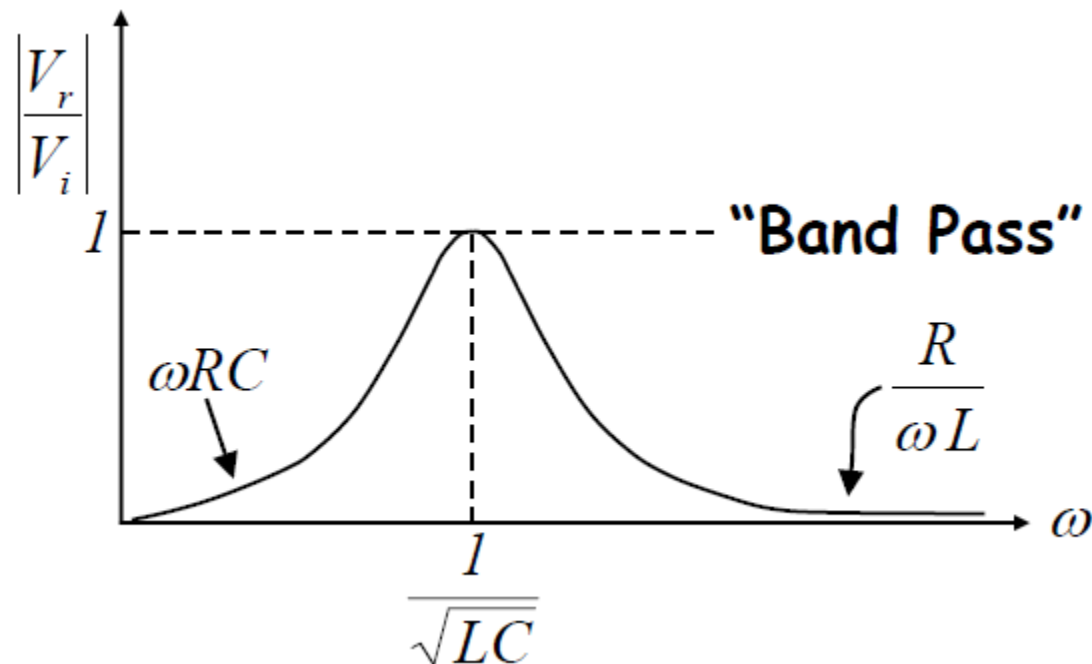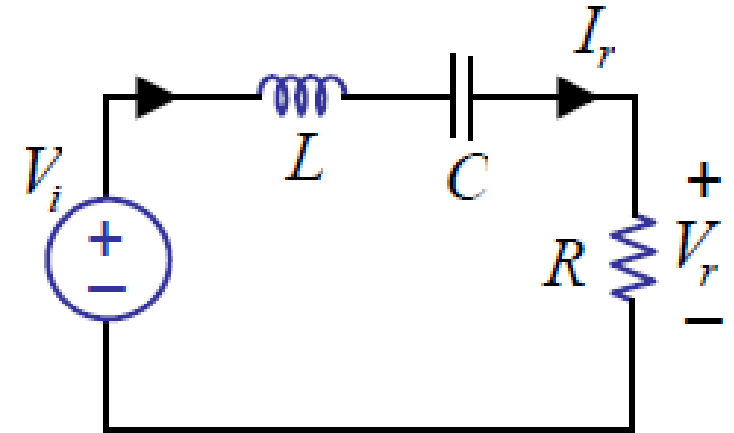

Observe:

$$\text{Low } \omega: \approx \omega RC$$

$$\text{High } \omega: \approx \frac{R}{\omega L}$$

$$\omega\sqrt{LC} = 1: \approx 1$$

# Series Resonant Circuit

$$I_r = \frac{V_i}{Z_{eq}} \quad Z_{eq} = R + j\omega L - j\frac{1}{\omega C}$$


Resonance is a condition in which capacitive and inductive reactance cancel each other to give rise to a purely resistive circuit

$$j\omega_o L - j\frac{1}{\omega_o C} = 0$$

$$\Rightarrow \omega_o = \frac{1}{\sqrt{LC}} \quad \text{Resonant frequency} \quad f_o = \frac{1}{2\pi\sqrt{LC}}$$



$$Z_{eq} = R$$

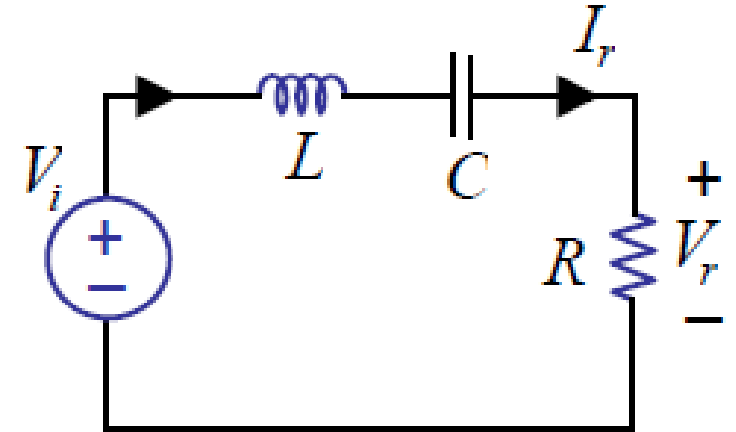Current and voltage are in phase (power factor is unity)!



$$|I_r(\omega)| = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

# Series Resonant Circuit

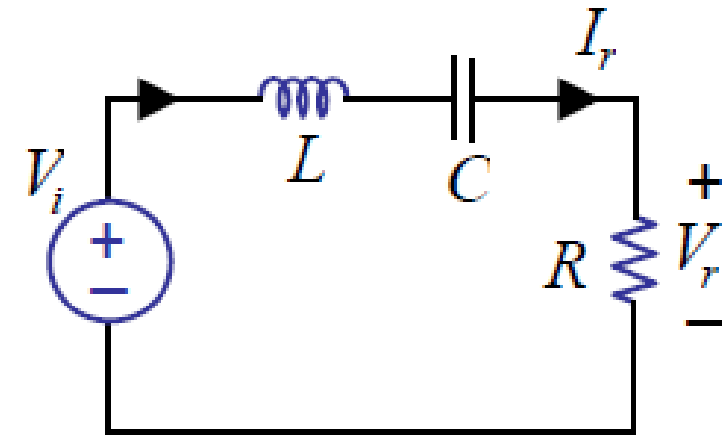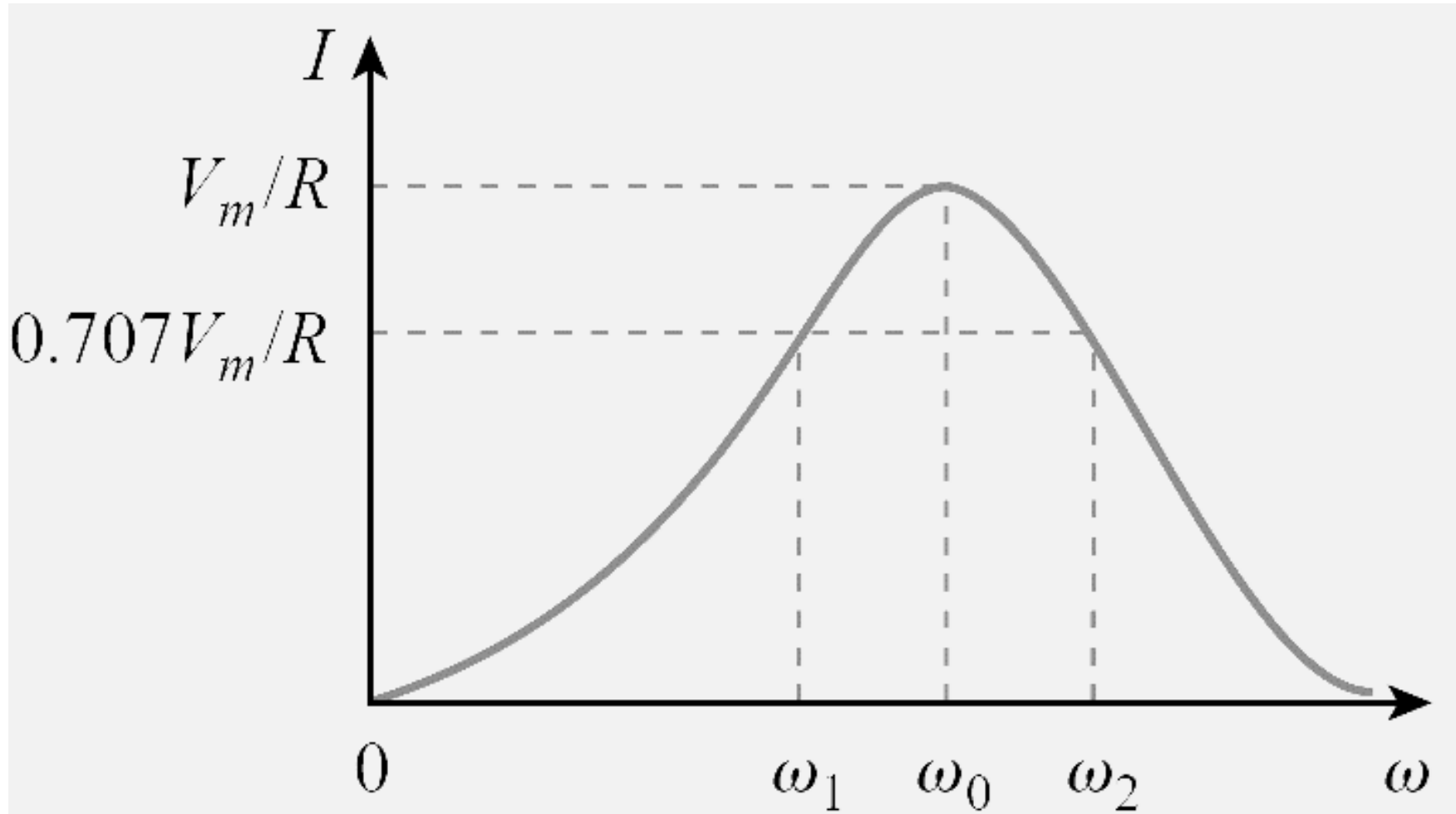

$\omega_1$  and  $\omega_2$  are called half-power frequencies


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# Half-power Frequency

$$|I(\omega)| = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

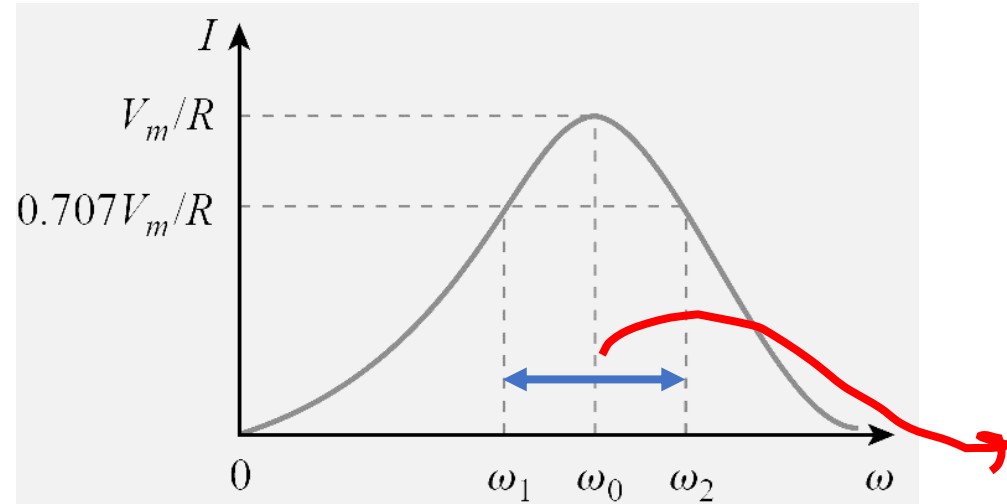$\omega_1$  and  $\omega_2$   
half-power frequencies



$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\Delta\omega = \omega_2 - \omega_1 = \frac{R}{L}$$

Bandwidth

$$|I(\omega_1)| = \frac{V_m}{\sqrt{R^2 + (\omega_1 L - \frac{1}{\omega_1 C})^2}} = \frac{V_m}{\sqrt{2}R}$$

$$|I(\omega_2)| = \frac{V_m}{\sqrt{R^2 + (\omega_2 L - \frac{1}{\omega_2 C})^2}} = \frac{V_m}{\sqrt{2}R}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$Q = \frac{\omega_0}{\Delta\omega}$$


Quality Factor

$$Q = \frac{\sqrt{L}}{\sqrt{C}R}$$


# RLC Circuit

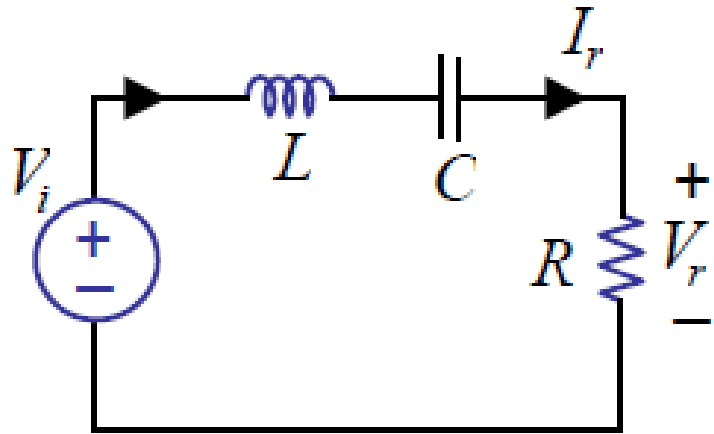

$$|V_o(\omega)| = |V_I| \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

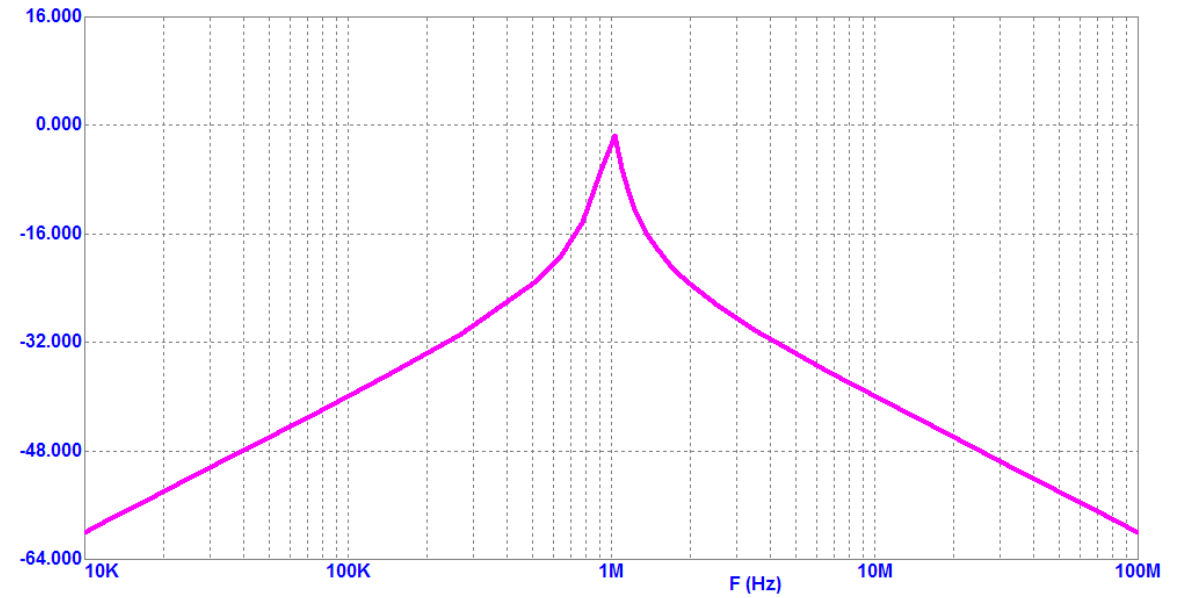

# Bandwidth & Quality Factor

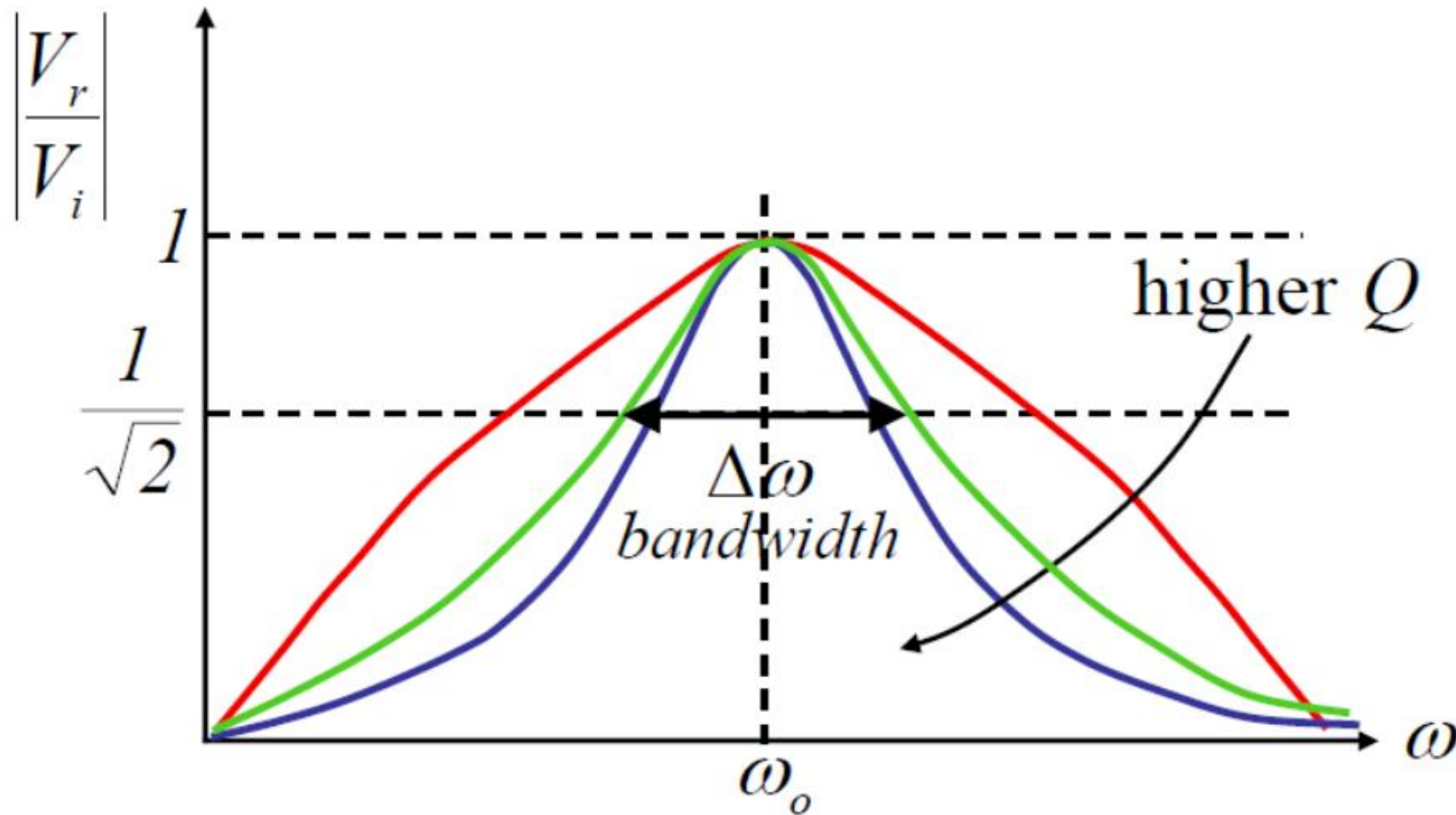

$$Q = \frac{\omega_0}{\Delta\omega}$$

Quality Factor


$Q$  represents sharpness of resonance

For high  $Q$  circuits:

$$\omega_1 \simeq \omega_0 - \frac{B}{2}, \quad \omega_2 \simeq \omega_0 + \frac{B}{2}$$



# Parallel Resonance

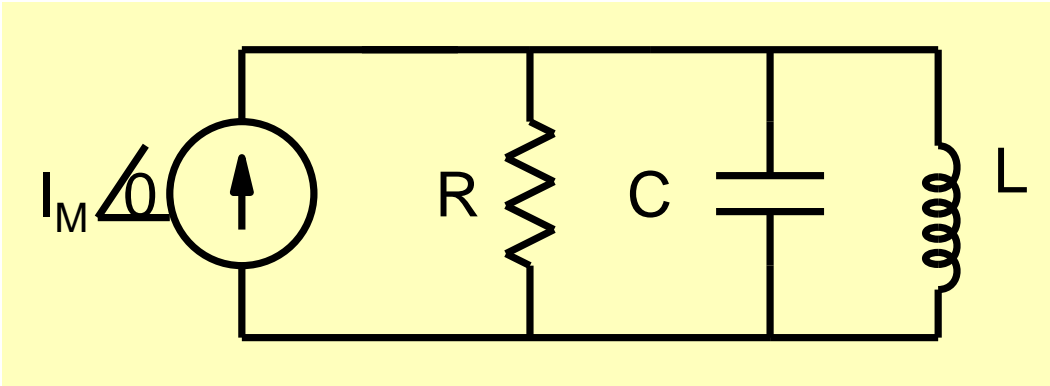


$$Y_{eq} = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$$

Resonant frequency:


$$j\omega_o C - j\frac{1}{\omega_o L} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{LC}}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$Z_{eq} = R$$

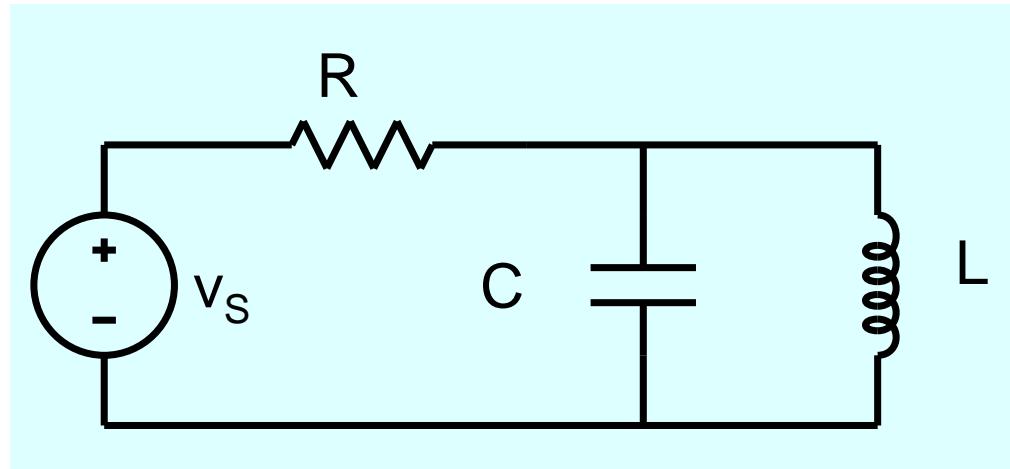

# Example

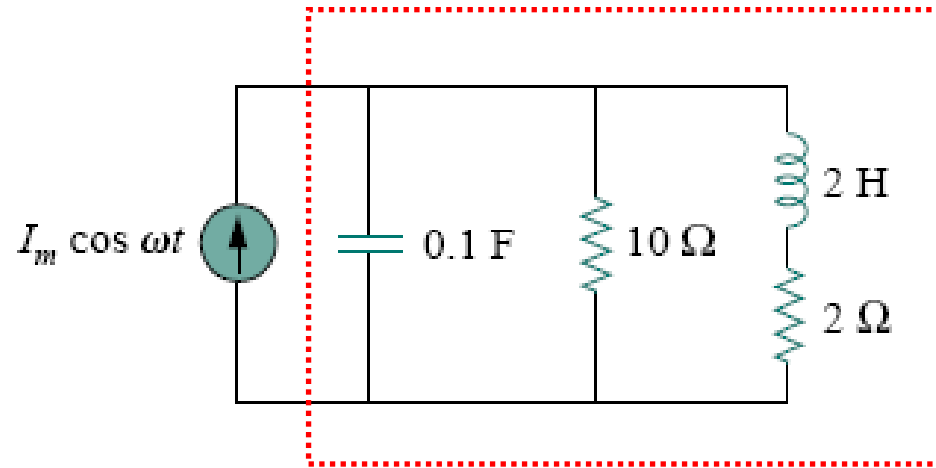

**What is the resonant frequency ?**

$$\mathbf{Y} = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance,  $\text{Im}(\mathbf{Y}) = 0$


$$\omega_0 0.1 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0 \quad \Rightarrow \quad \omega_0 = 2 \text{ rad/s}$$

$$f_o = \frac{\omega_o}{2\pi}$$

# RLC Circuit

$$|V_o(\omega)| = |V_I| \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$|V_o(\omega)| = \frac{1}{\sqrt{1 + Q^2 \left( \frac{\omega^2}{\omega_0^2} - 1 \right)^2}}$$

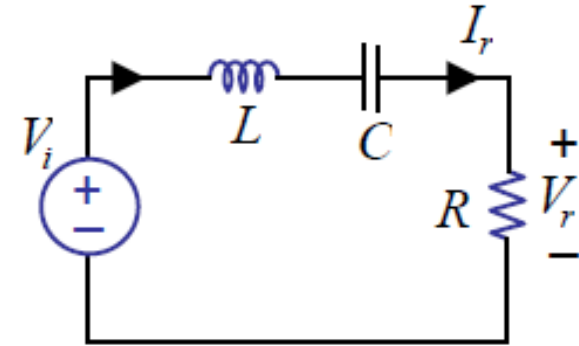

For  $\omega = \omega_0$ ,  $V_o = 1$  so the signal simply passes through !

How much  $Q$  do we need to pass 450KHz but reject 460KHz by 60dB?

$$\omega_0 = 2\pi \times 450 \times 10^3 = 2.827 \times 10^6 \text{ rad} / \text{s}$$

$$\omega = 2\pi \times 460 \times 10^3 = 2.89 \times 10^6 \text{ rad} / \text{s}$$

For an attenuation of -60dB or  $10^{-3}$  at  $\omega$ :

$$Q = \frac{1000}{(460/450)^2 - 1} = 23000$$

This is a large value of  $Q$ !

# RLC Filters

