

ESC201: INTRODUCTION TO ELECTRONICS

MODULE 5: AMPLIFIERS




Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur



Difference Amplifier

An amplifier that is:

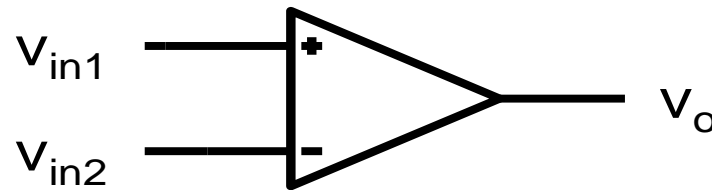- sensitive to difference in input voltages; and
- insensitive to what is common.



$$v_{id} = v_{in1} - v_{in2}$$

$$v_{ic} = \frac{v_{in1} + v_{in2}}{2}$$

$$v_o = A_d v_{id} + A_{cm} v_{ic}$$


A_d : Differential mode gain

A_{cm} : Common mode gain

$$A_d \gg A_{cm}$$

$$\text{Common Mode Rejection Ratio: } CMRR = \frac{A_d}{A_{cm}}$$


Ideal Operational Amplifier

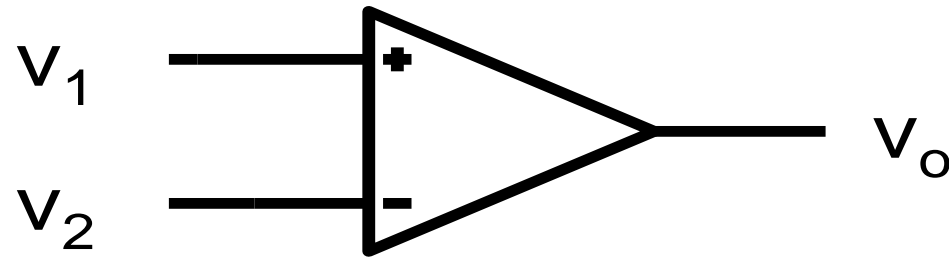

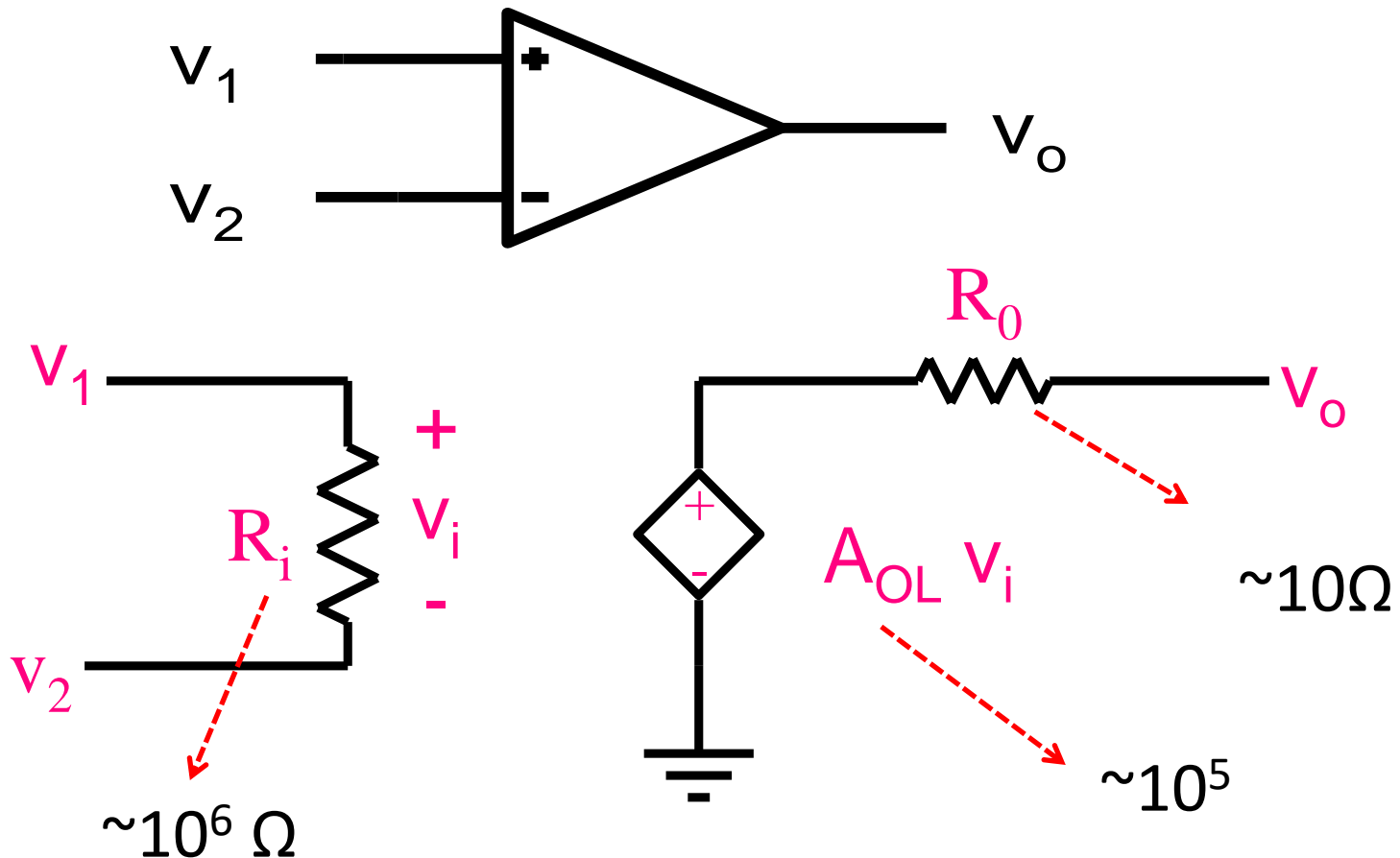1. Infinite Differential-mode voltage gain
2. Infinite Common mode Rejection ratio
3. Infinite Input Resistance
4. Zero output Resistance
5.




Equivalent Circuit Model

A simple equivalent circuit model of an op-amp




This assumes very high CMRR


Simulation Results

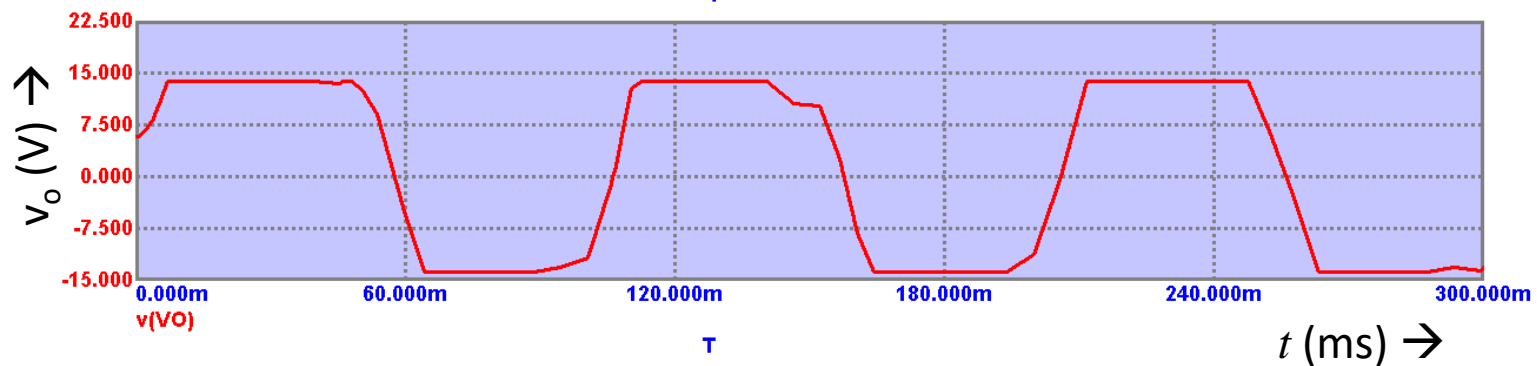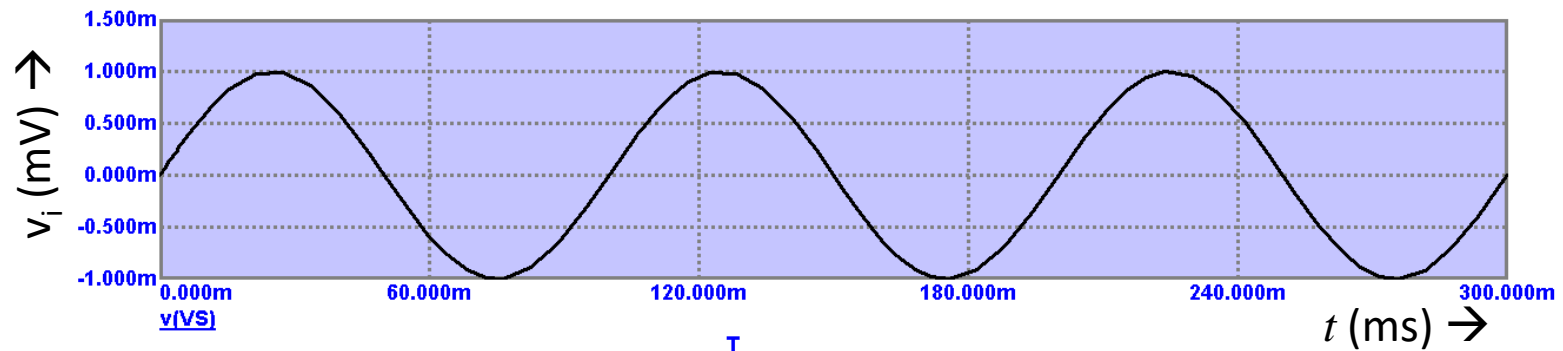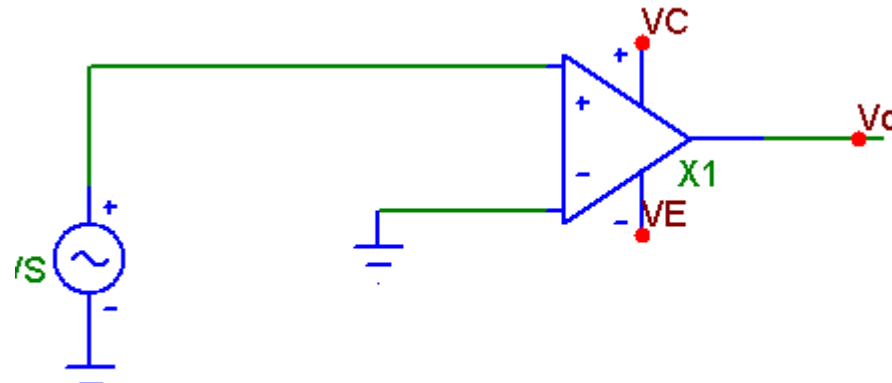

Negative and Positive Feedback

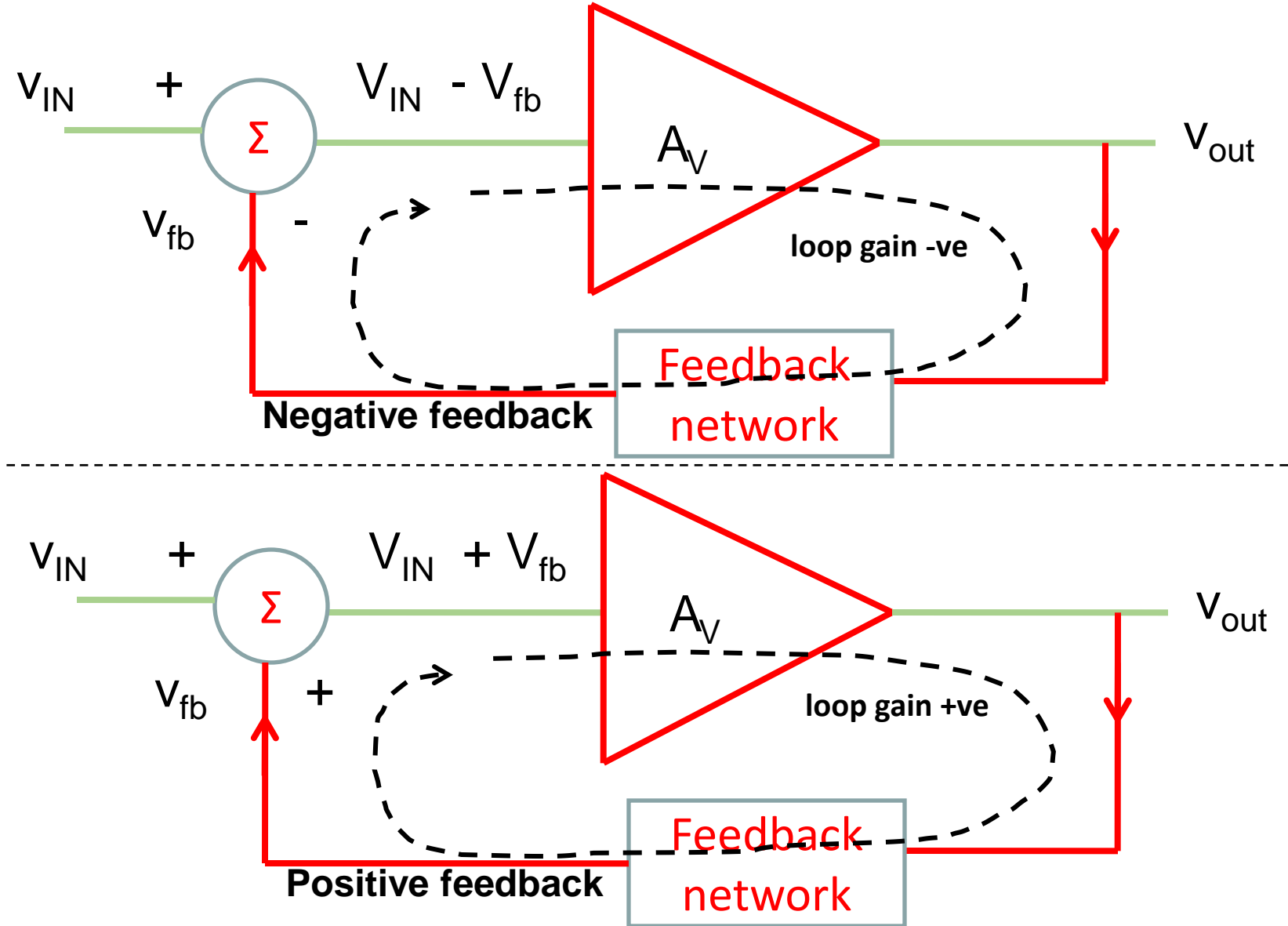




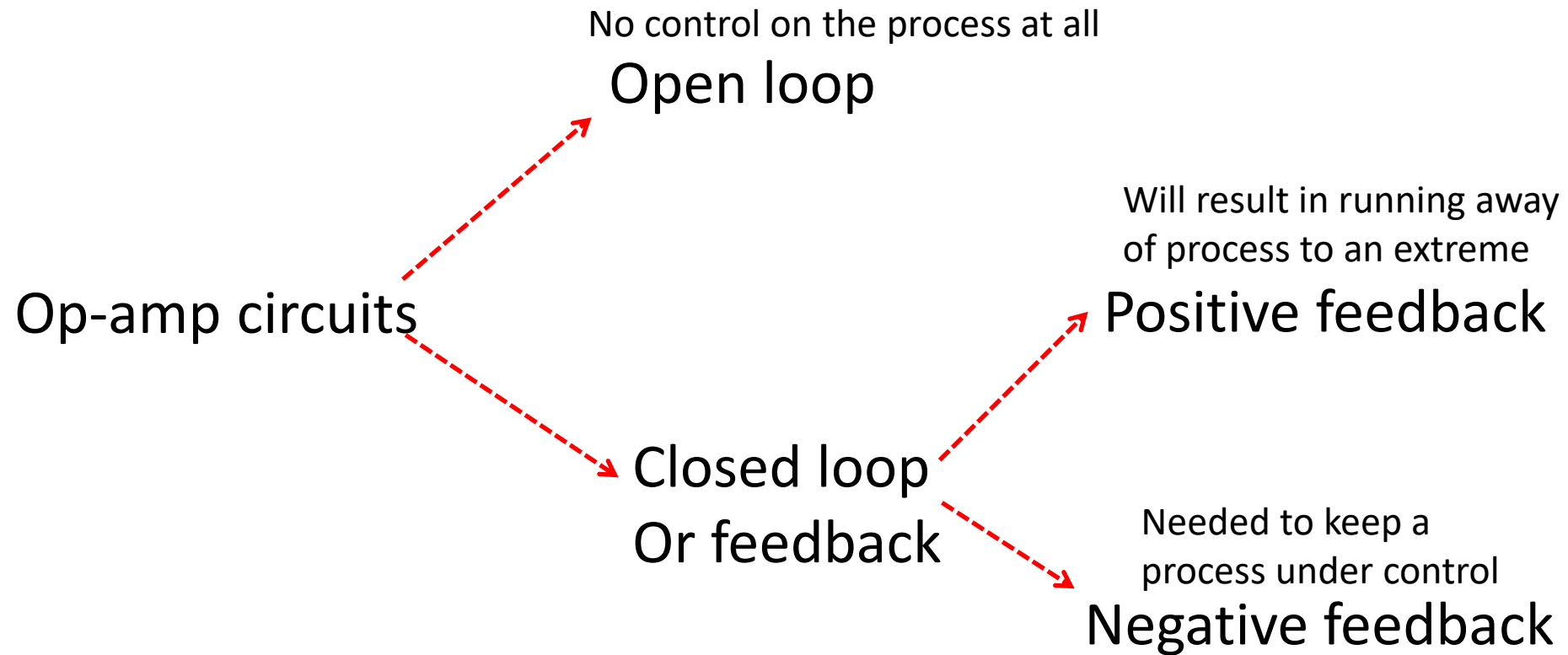
Op-amp Circuit Classification by Feedback




Most Op-amp Circuits employ negative feedback

Note: The classification and behaviour is true for all systems in this universe!

Inverting amplifier

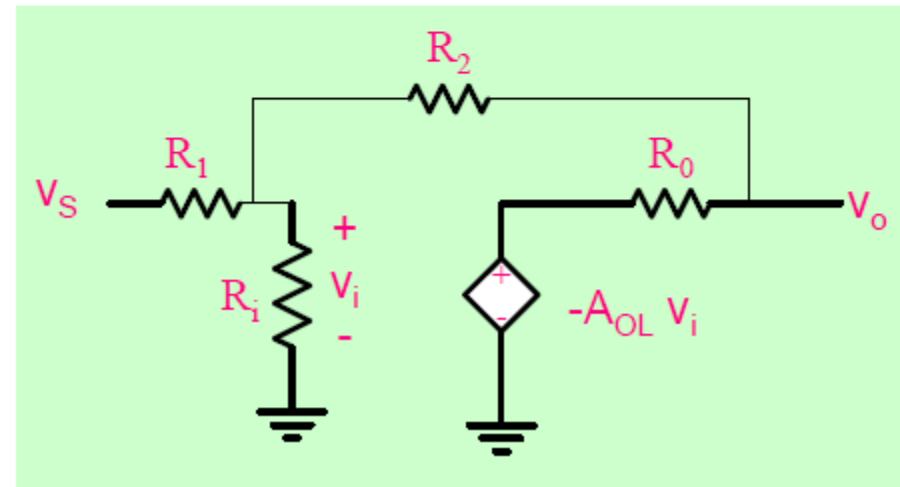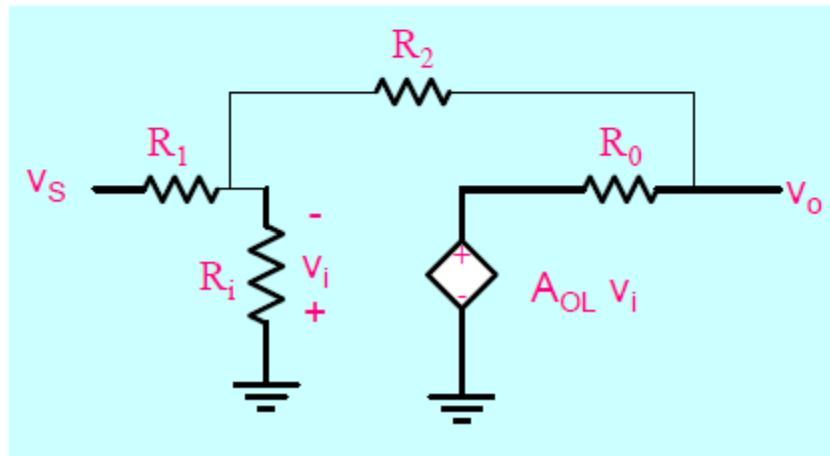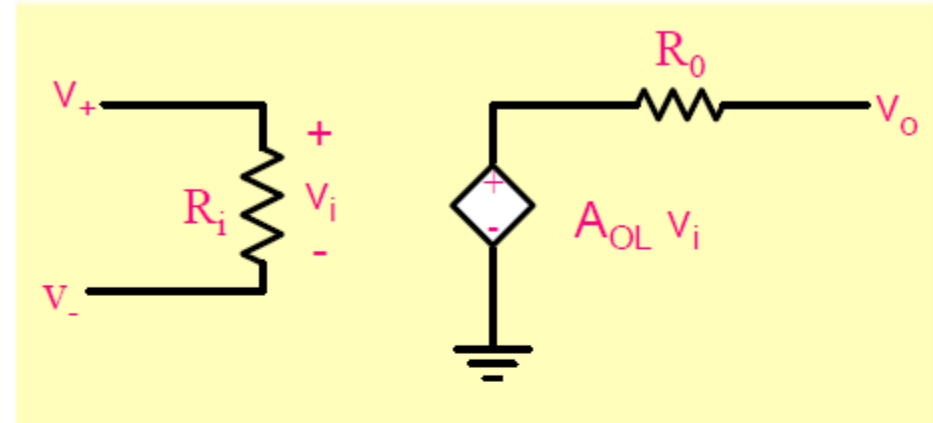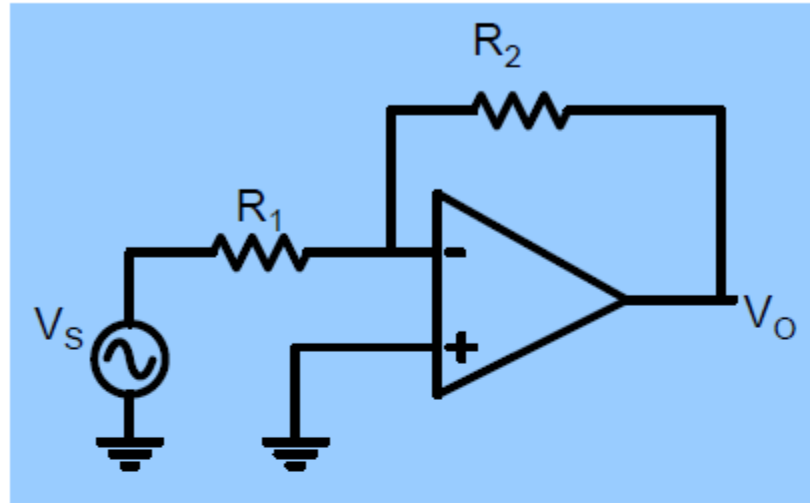

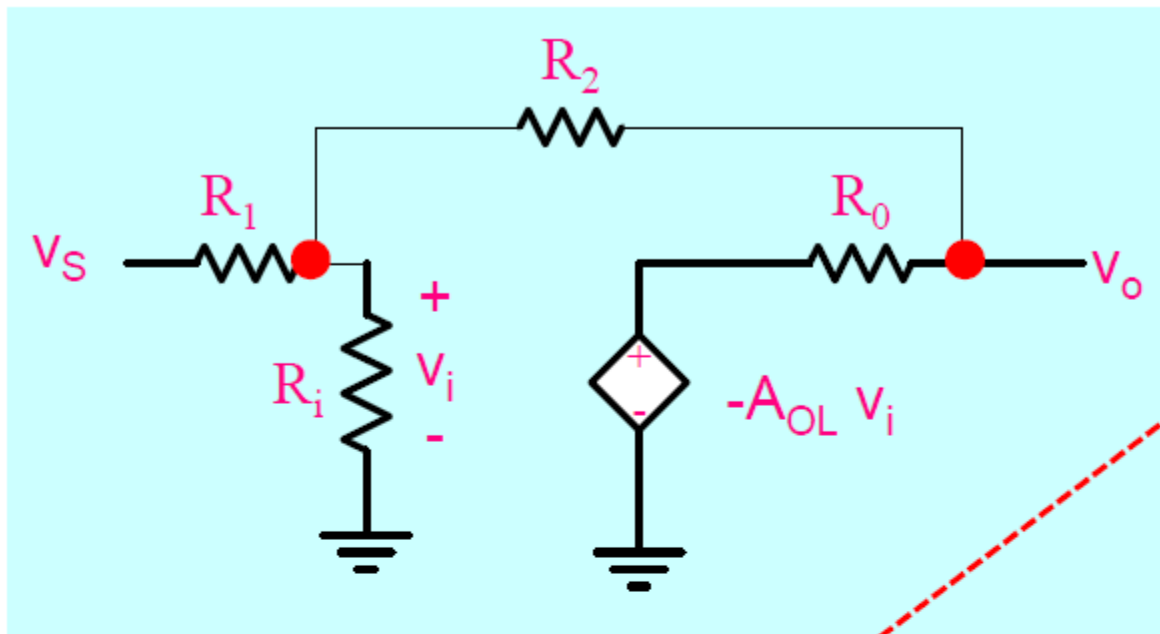

Nodal Analysis

$$\frac{v_S - v_i}{R_1} = \frac{v_i}{R_i} + \frac{v_i - v_o}{R_2} \quad (1)$$

$$\frac{-A_{OL}v_i - v_o}{R_o} = \frac{v_o - v_i}{R_2} \quad (2)$$


$$\frac{v_S}{R_1} = -\frac{v_o}{R_2} + v_i \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right) \quad (3)$$

$$\text{As } A_{OL} \rightarrow \infty \quad v_i \rightarrow 0$$

$$v_i = v_o \frac{\frac{1}{R_o} + \frac{1}{R_2}}{\frac{-A_{OL}}{R_o} + \frac{1}{R_2}} \quad (4)$$

This is called the **Virtual Ground** property

Inverting Amplifier

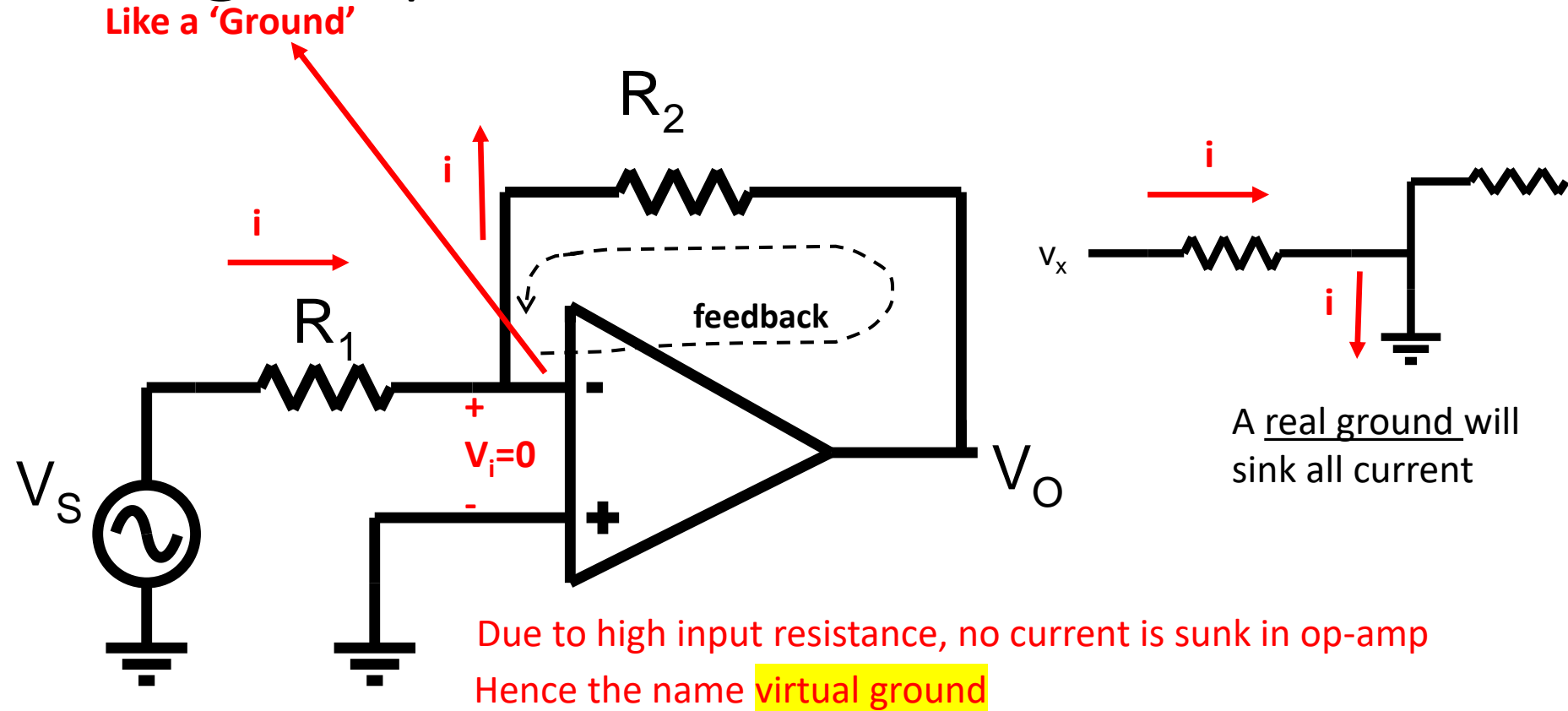


Under negative feedback with high gain

Op-amp input is a nullator: no current/no voltage: open circuit and short circuit at the same time!

Op-amp output is a norator: can supply any value of current and voltage

Virtual Ground Property

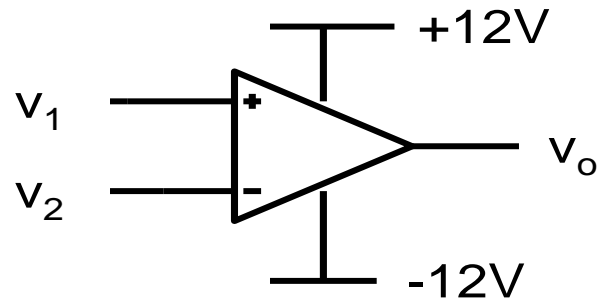

for op-amp connected in negative feedback

$$v_1 \cong v_2$$


In an op-amp with **negative feedback**, the voltage of the inverting terminal is equal to the voltage of the non-inverting terminal if the **gain of the op-amp is sufficiently high**

This property **does not** hold under certain conditions such as

- ☐ open loop,
- ☐ positive feedback
- ☐ or if the op-amp is saturated.

Input of an Op-amp is a Nullator

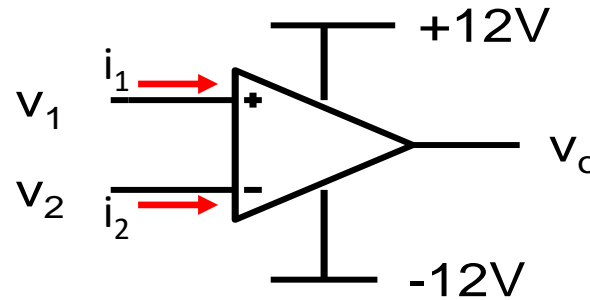For an ideal op-amp circuits under negative feedback



With negative feedback:


1. $v_1 \approx v_2$
(as in a short circuit)

2. $i_1 \approx 0; i_2 \approx 0$
(as in an open circuit)

The op-amp input appears to have properties of short and open circuit simultaneously !
Its behaviour approaches that of a nullator!

Output of an Op-amp is a Norator

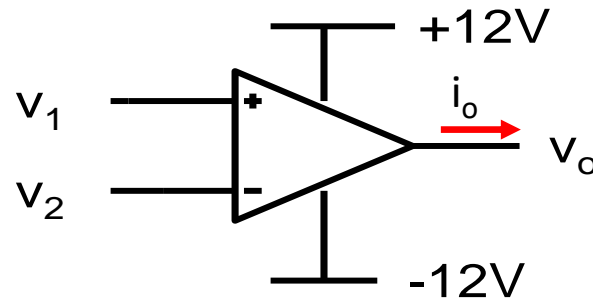For an ideal op-amp circuits under negative feedback




With negative feedback:

1. v_o can take any voltage between the supply voltages (as in an open circuit)
2. i_o can supply any current needed - up to a value. (as in a short circuit)

At the output side op-amp appears to be like a short and an open circuit simultaneously !
Its behaviour approaches that of a norator!

Inverting Amplifier

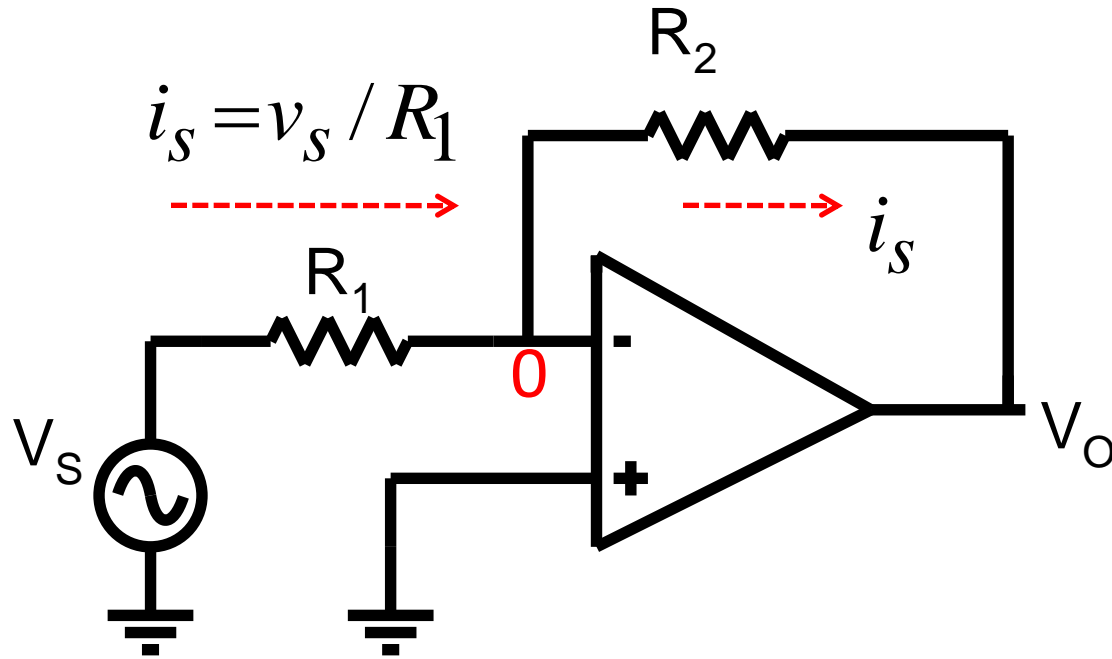
Re-analyze inverting amplifier with the concepts discussed



$$\frac{0 - v_O}{R_2} = i_S = \frac{v_S}{R_1}$$

$$\frac{v_O}{v_S} = -\frac{R_2}{R_1}$$

Non-Inverting Amplifier

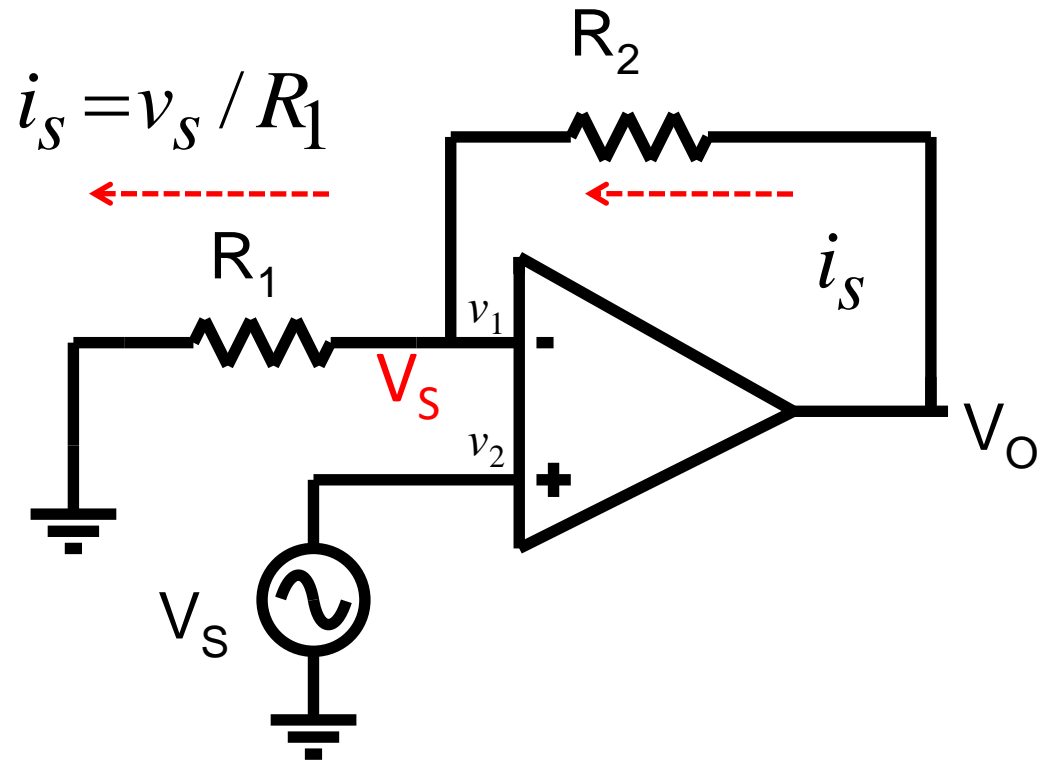


1. $v_1 = v_2$

2. $i_1 = i_2 = 0$


$$\frac{v_O - v_S}{R_2} = i_S = \frac{v_S}{R_1}$$

$$\frac{v_O}{v_S} = 1 + \frac{R_2}{R_1}$$


Examples

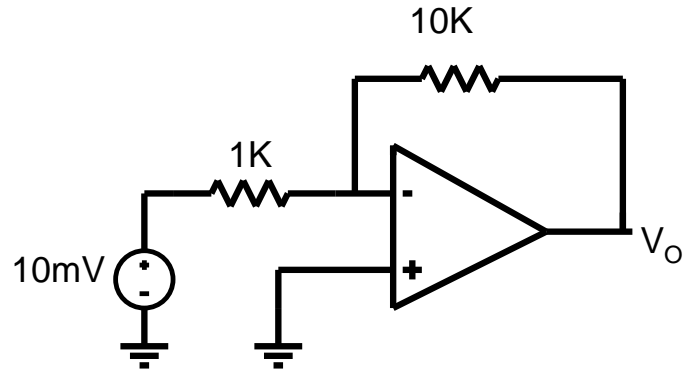
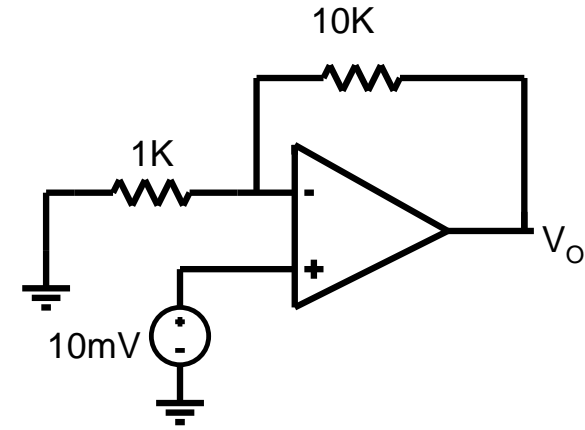
$$\frac{v_o}{v_S} = -\frac{R_2}{R_1} \Rightarrow v_o = -100mV$$


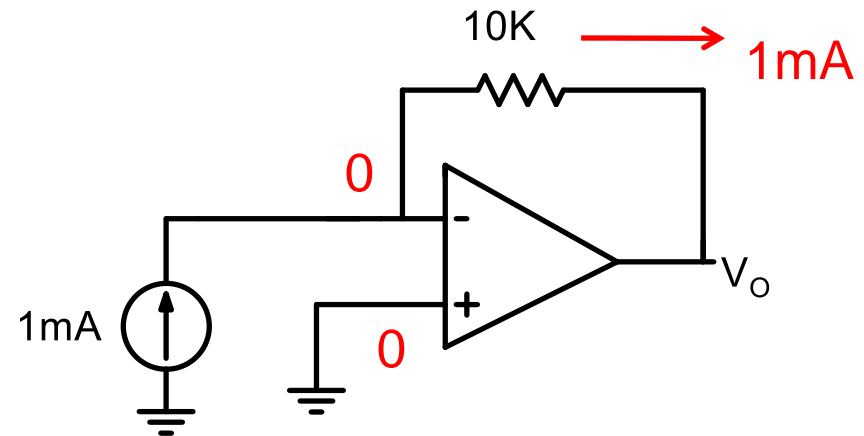
$$\frac{v_o}{v_S} = 1 + \frac{R_2}{R_1} \Rightarrow v_o = 110mV$$




$$\frac{0 - v_o}{10K} = 1mA \quad v_o = -10V$$

Op-amp with Negative Feedback

- We have seen we can build
 - Inverting amplifiers
 - Noninverting amplifiers
- We will see that we can build
 - Adders
 - Subtractors
 - Weighted adders and subtractors
- And further
 - Integrator, differentiator
 - Log amplifier, antilog amplifier
 - Multiplier
 - Temperature sensor,
 - And much more!

Adder

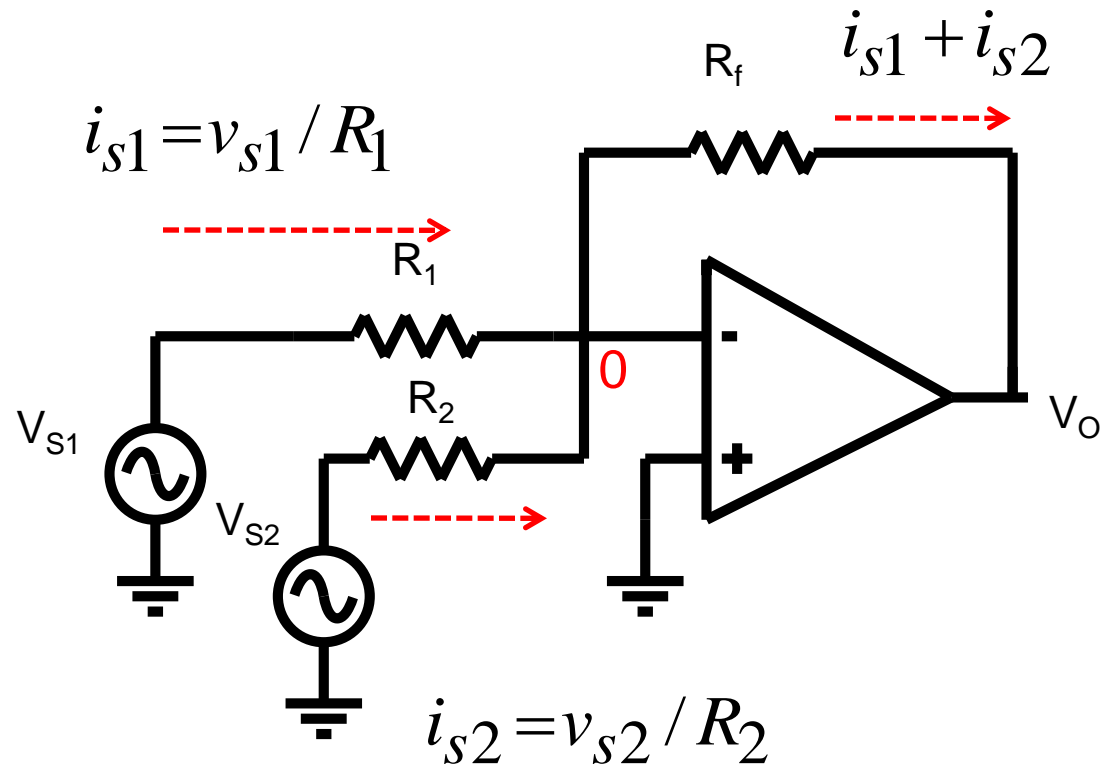


$$\frac{0 - v_o}{R_f} = i_{s1} + i_{s2} = \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2}$$

$$v_o = -\left(\frac{R_f}{R_1} v_{s1} + \frac{R_f}{R_2} v_{s2}\right)$$

$$\text{For } R_1 = R_2 = R \quad v_o = -\frac{R_f}{R} (v_{s1} + v_{s2})$$


Adder: Alternative Analysis

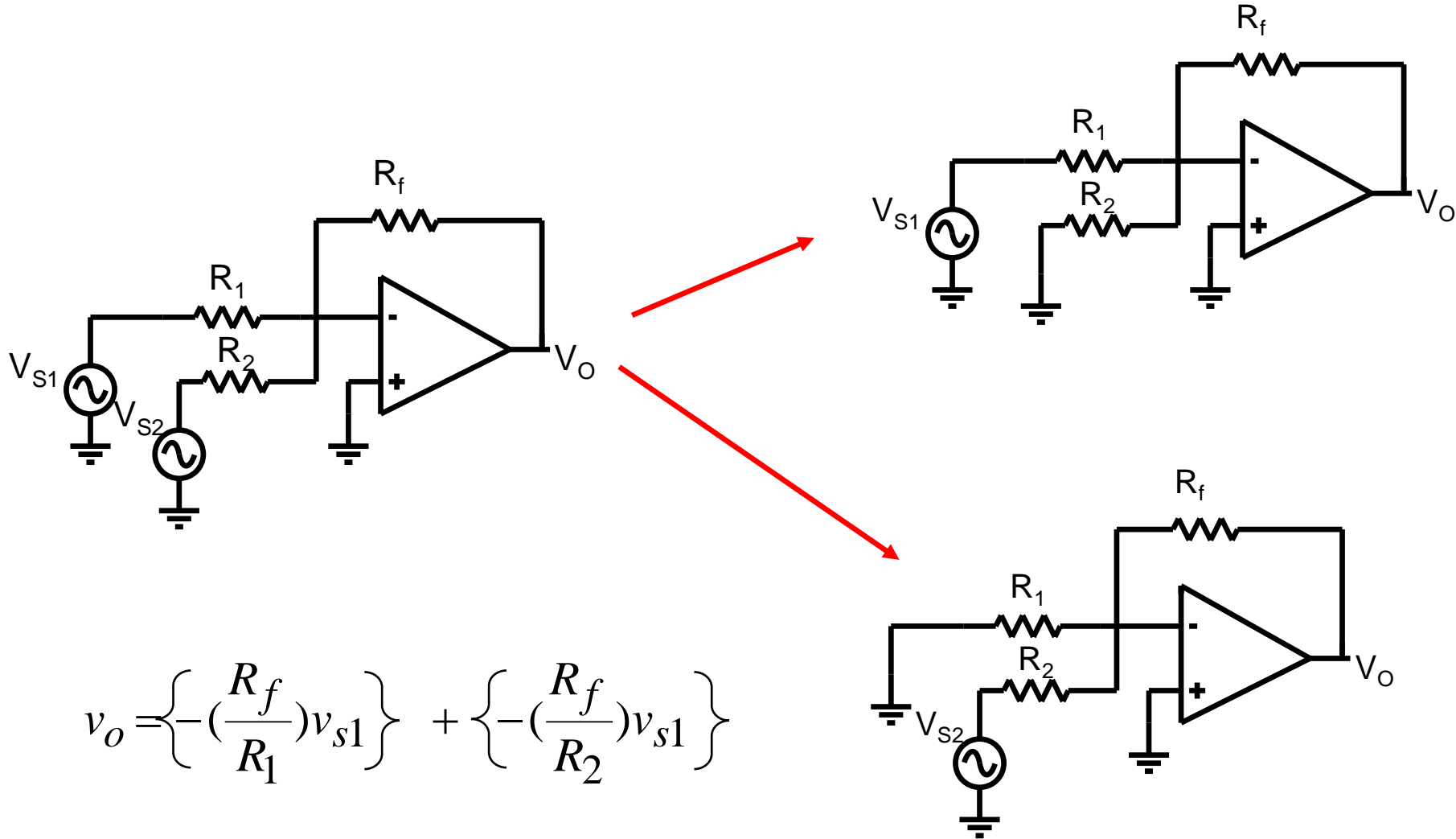


Design Example 1

Design a circuit that would generate the following output given three input voltages v_{s1} , v_{s2} and v_{s3} .

$$v_o = -10v_{s1} - 4v_{s2} - 5v_{s3}$$

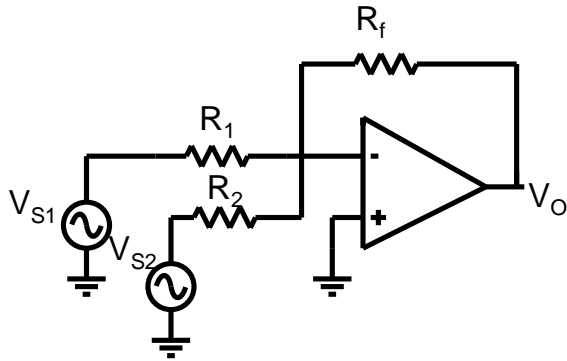
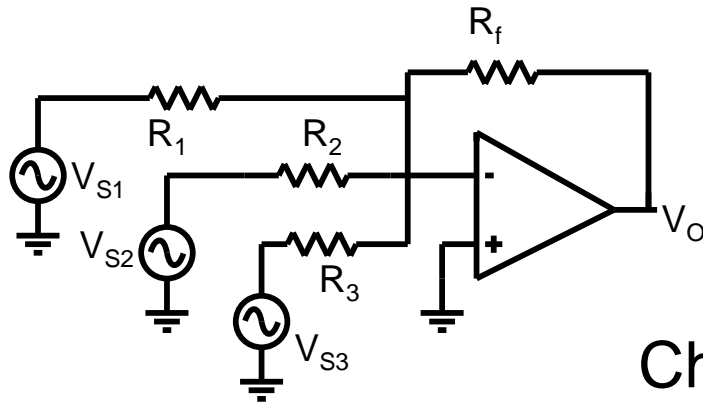
$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2}$$



$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2} - \frac{R_f}{R_3}v_{s3}$$


Choose : $R_f = 10 \text{ k}\Omega \quad \Rightarrow R_1 = 1 \text{ k}\Omega$

$\Rightarrow R_2 = 2.5 \text{ k}\Omega \quad \Rightarrow R_3 = 2 \text{ k}\Omega$

Design Example 2

Design a circuit that would generate the following output given two input voltages v_{s1} and v_{s2} .

$$v_o = 10v_{s1} + 4v_{s2}$$

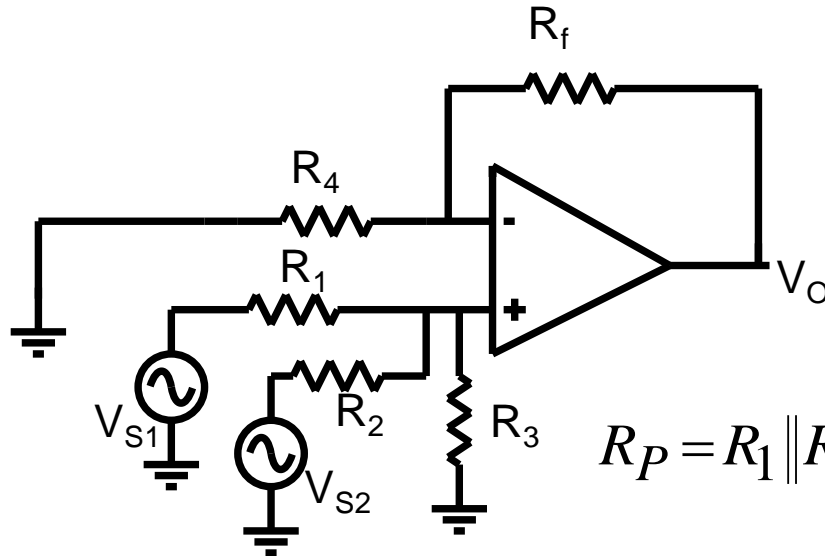

$$v_o = \left(\frac{R_p}{R_1} v_{s1} + \frac{R_p}{R_2} v_{s2} \right) \times \left(1 + \frac{R_f}{R_4} \right)$$


$$R_p = R_1 \parallel R_2 \parallel R_3$$

The voltage at the non-inverting terminal due to each signal has to be evaluated - it is a voltage divider configuration for each of the supply considered separately.


Voltage contribution by i^{th} source to input node: $v_i \cdot (R_p / R_i)$

Why don't you give it a try and design the circuit?

Cascading Circuits

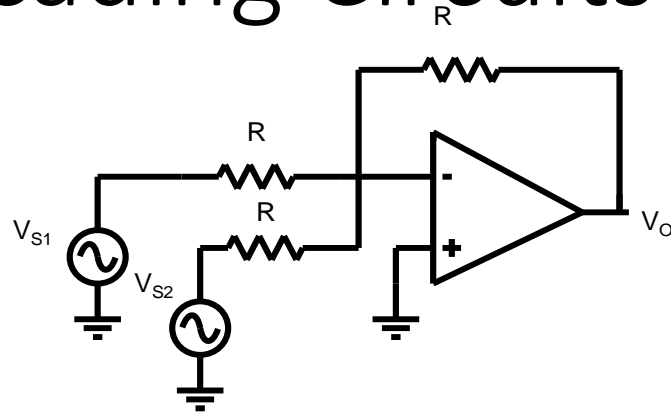

$$v_o = -(v_{s1} + v_{s2})$$

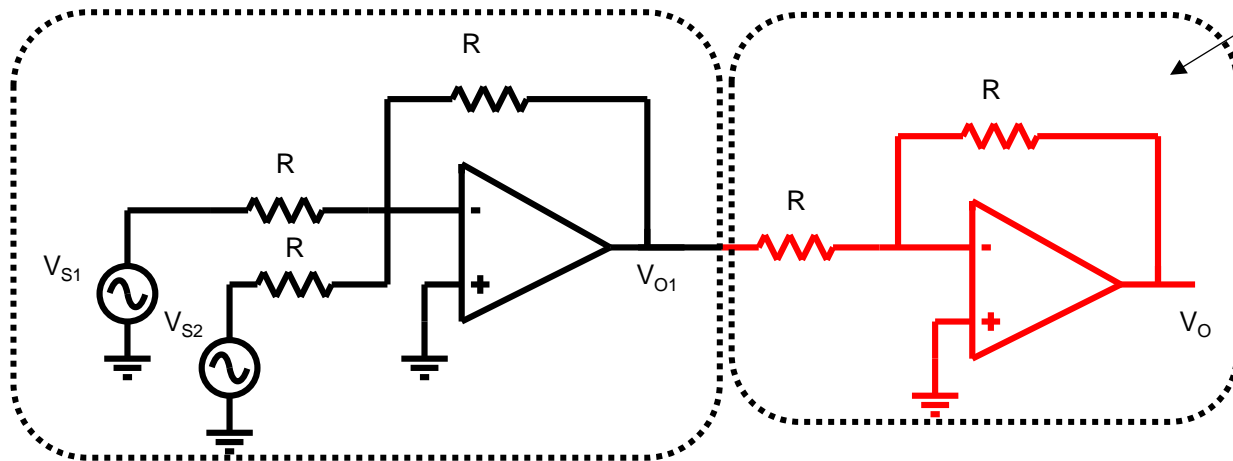


$$v_{o1} = -(v_{s1} + v_{s2})$$

$$v_o = -v_{o1} \quad \Rightarrow \quad v_o = (v_{s1} + v_{s2})$$

Have we made some assumption here ?

When does the assumption hold?

Example 1

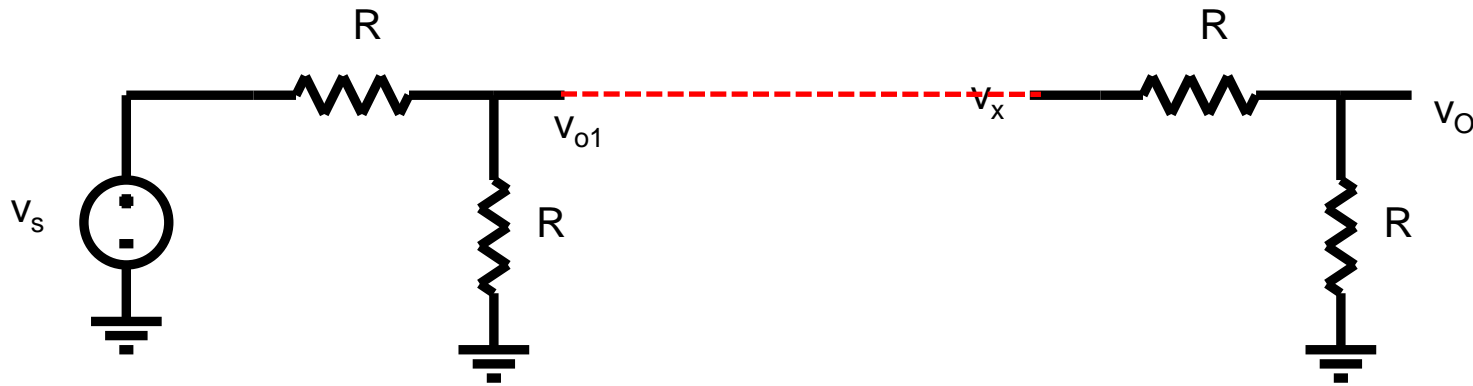

$$\frac{v_{o1}}{v_s} = 0.5$$

$$\frac{v_o}{v_x} = 0.5$$

Connect the two circuits.


$$v_{o1} = v_x$$

$$\frac{v_o}{v_x} = \frac{v_o}{v_{o1}} = 0.5$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_{o1}} \times \frac{v_{o1}}{v_s} = 0.5 \times 0.5 = 0.25$$


Is this indeed true? When can this be valid even as an approximation?

BUT

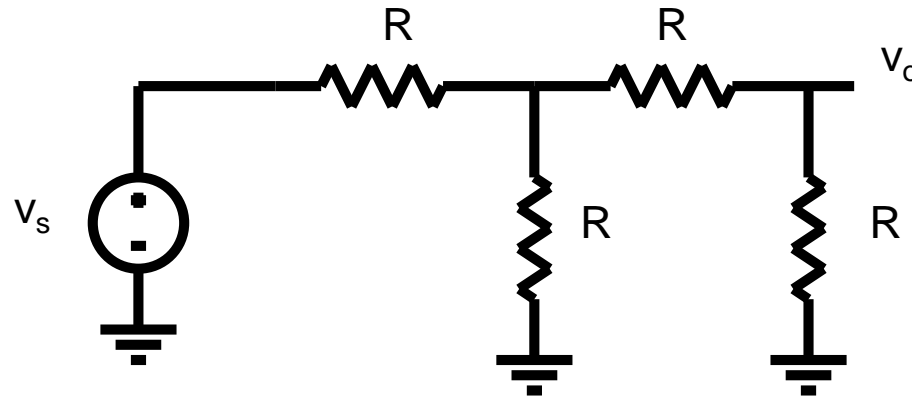

$$\frac{v_o}{v_s} = 0.2$$

Where is the error ?

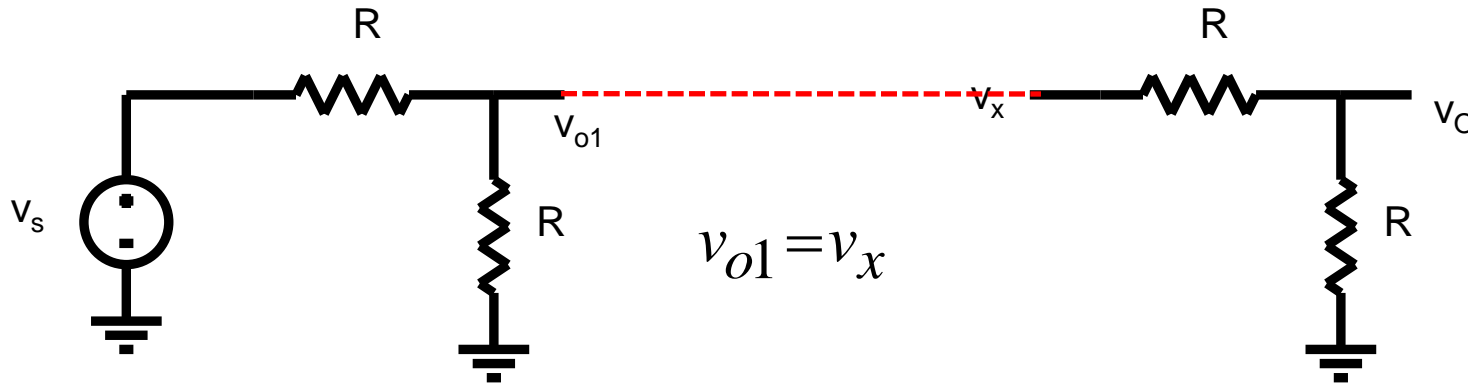

$$\frac{v_{o1}}{v_s} = 0.5$$


$$\frac{v_{o1}}{v_s} \neq 0.5$$

$$\frac{v_o}{v_x} = 0.5$$

Left-side circuit gets 'loaded' by the right-side circuit.

Left-side circuit's output vs. input characteristics get modified due to the loading.


Loading Effect

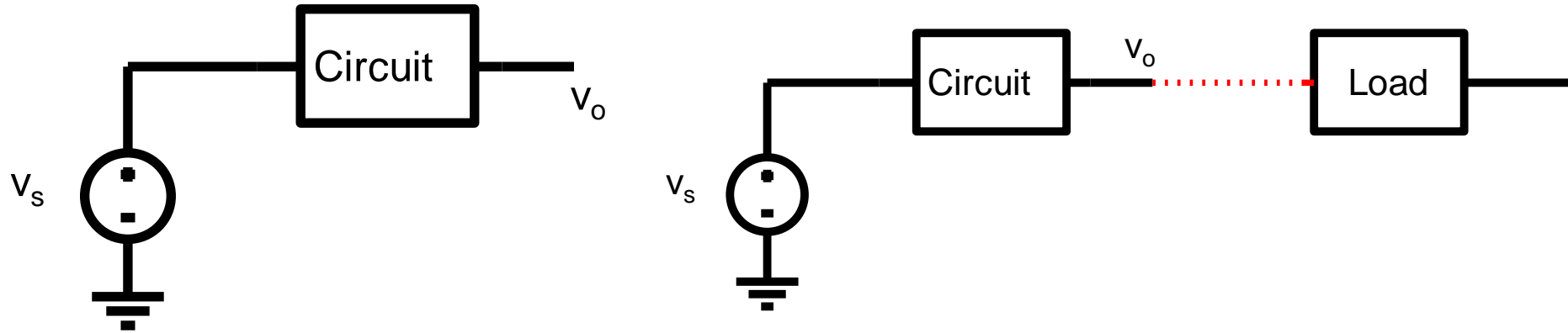

V_o in general gets altered when we connect a load to it

Under what conditions is change in V_o small upon connection of a load ?


Example 2

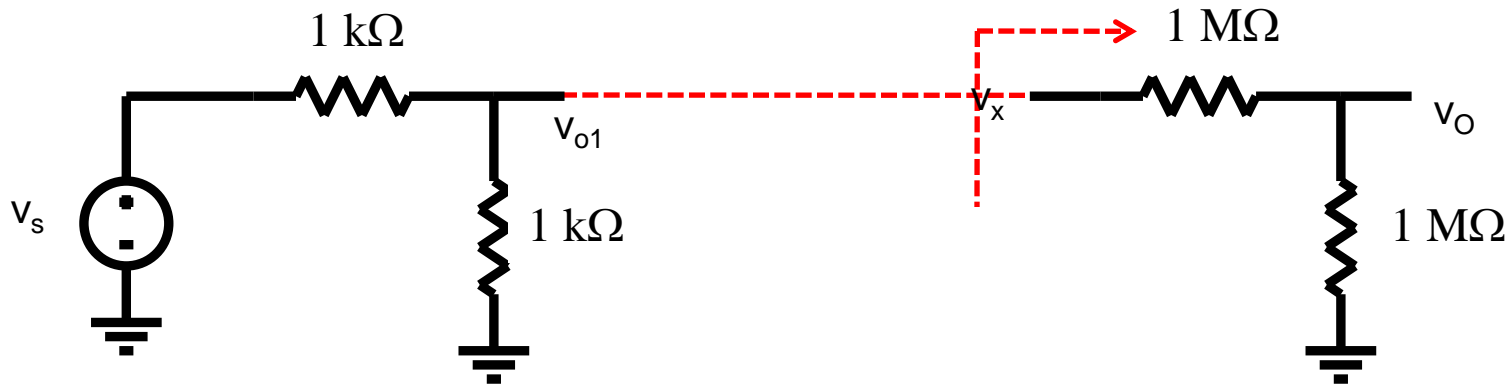

$$\frac{v_{o1}}{v_s} = 0.5$$

$$\frac{v_{o1}}{v_s} \cong 0.5$$

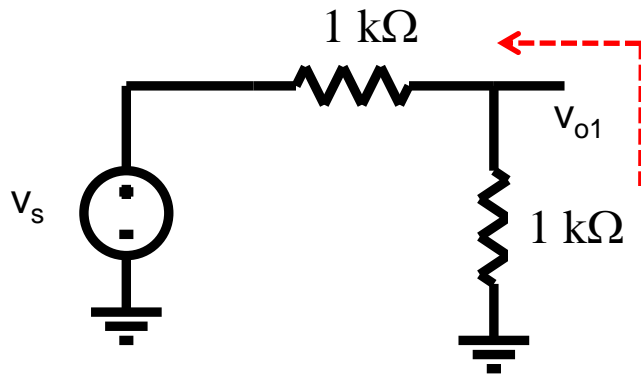We can describe this effect in terms of output resistance



$$R_o = 0.5\text{ k}\Omega$$


$$R_L = 2\text{ M}\Omega$$

Loading Effect

Whenever output resistance of a circuit is much smaller than the load resistance, the loading effect is minimal.

$$R_o \ll R_L$$

Cascading Circuits (contd.)

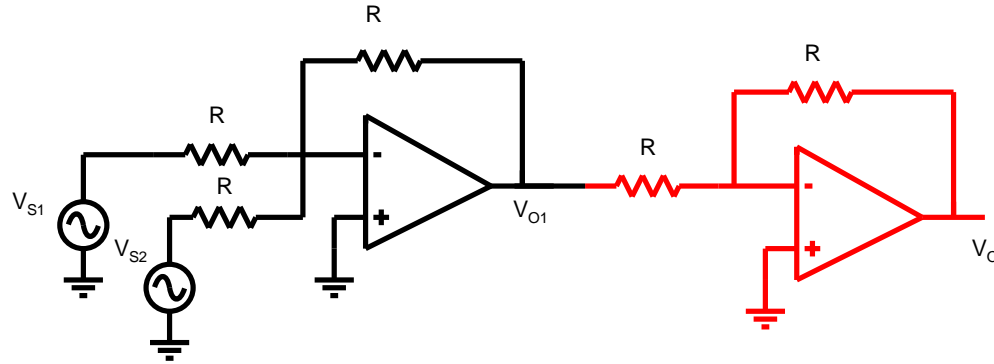

$$v_{O1} = -(v_{S1} + v_{S2})$$


$$v_O = -v_{O1}$$

$$v_O = (v_{S1} + v_{S2})$$


The assumption made here is that there is no loading

A reasonable because op-amps output has very low resistance

Subtractor

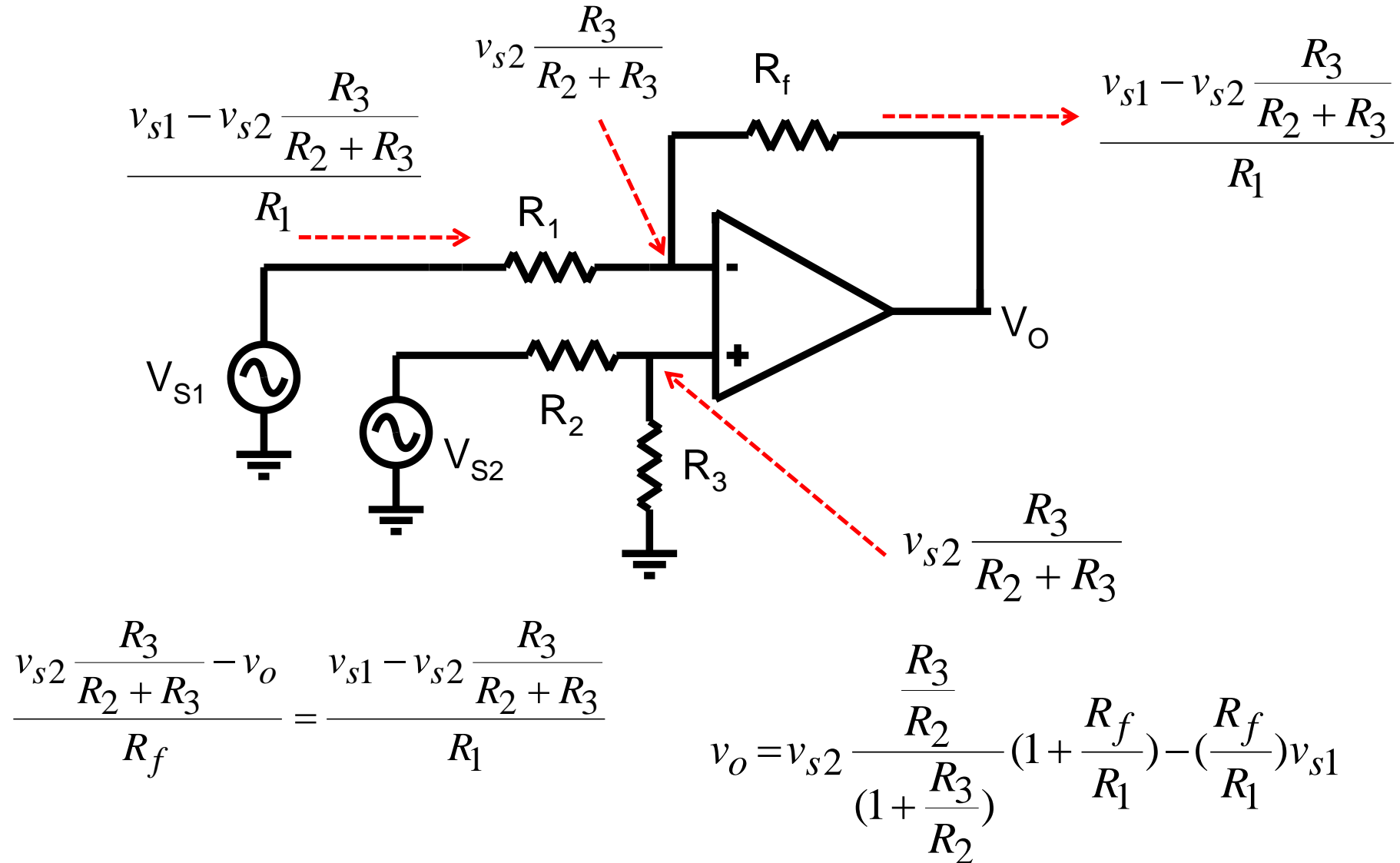


Subtractor Output

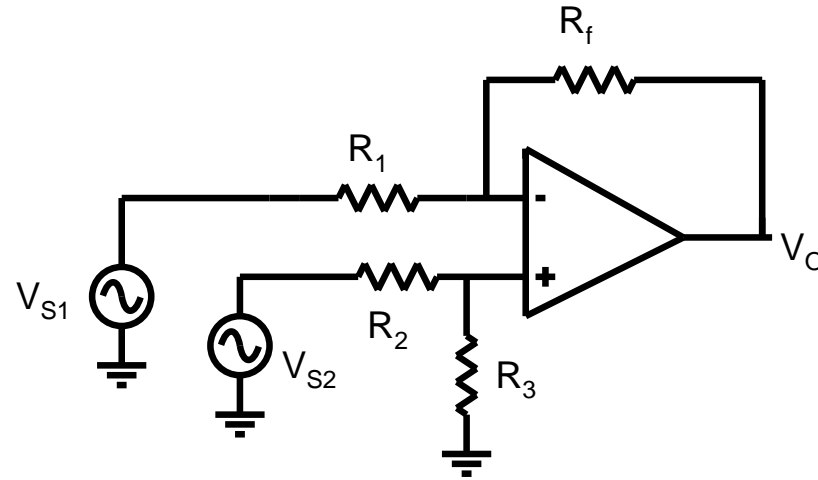


$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{\left(1 + \frac{R_3}{R_2}\right)} \left(1 + \frac{R_f}{R_1}\right) - \left(\frac{R_f}{R_1}\right) v_{s1} \quad \text{Choose } \frac{R_3}{R_2} = \frac{R_f}{R_1}$$

$$v_o = \frac{R_f}{R_1} (v_{s2} - v_{s1})$$


Subtractor: Alternative Analysis

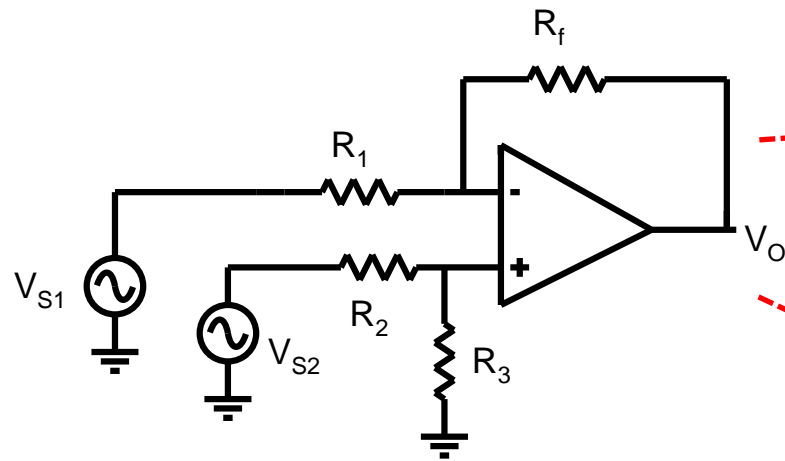

Inverting amplifier

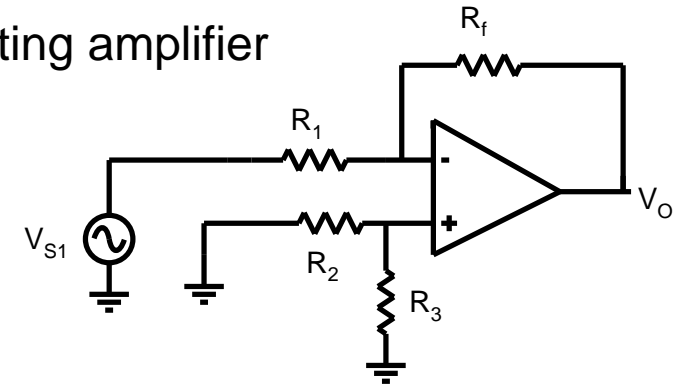

Non-inverting amplifier

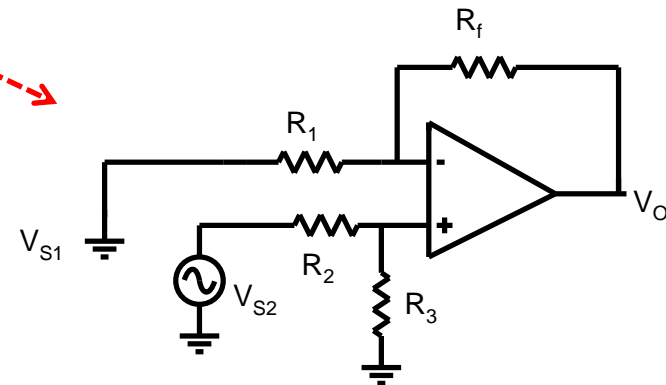


Use superposition theorem

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + \left\{ v_{s2} \frac{R_3}{(R_3 + R_2)} \times \left(1 + \frac{R_f}{R_1}\right) \right\}$$


Analysis is made simpler by **Re-Using** results derived earlier

Adder/Subtractor

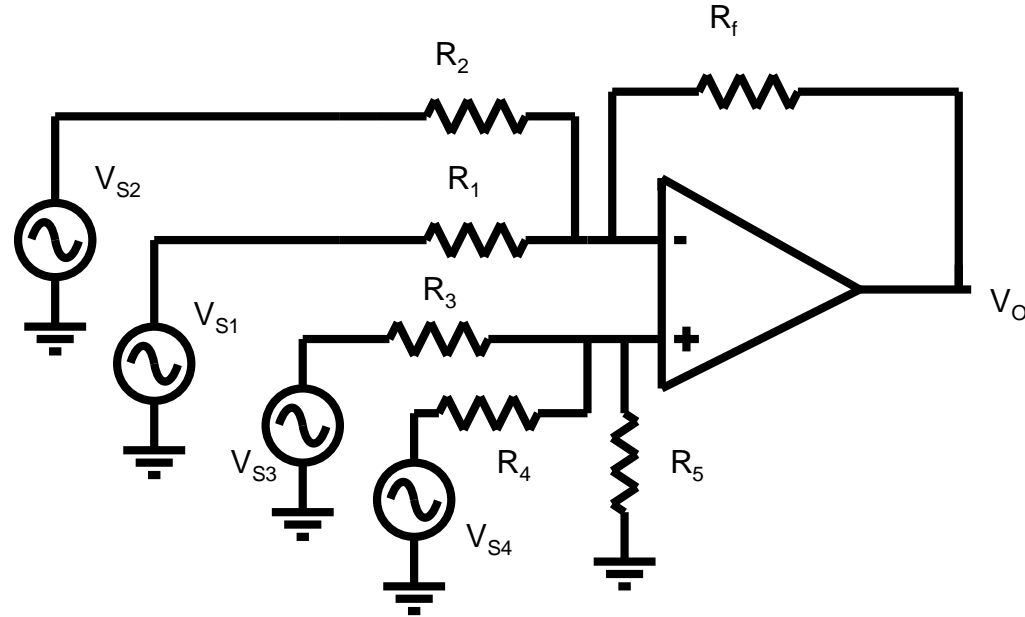

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + \left\{-\left(\frac{R_f}{R_2}\right)v_{s2}\right\} + \left\{v_{s3} \frac{R_5 \parallel R_4}{R_5 \parallel R_4 + R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)\right\} \\ + \left\{v_{s4} \frac{R_5 \parallel R_3}{R_5 \parallel R_3 + R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)\right\}$$


Adder/Subtractor – contd.

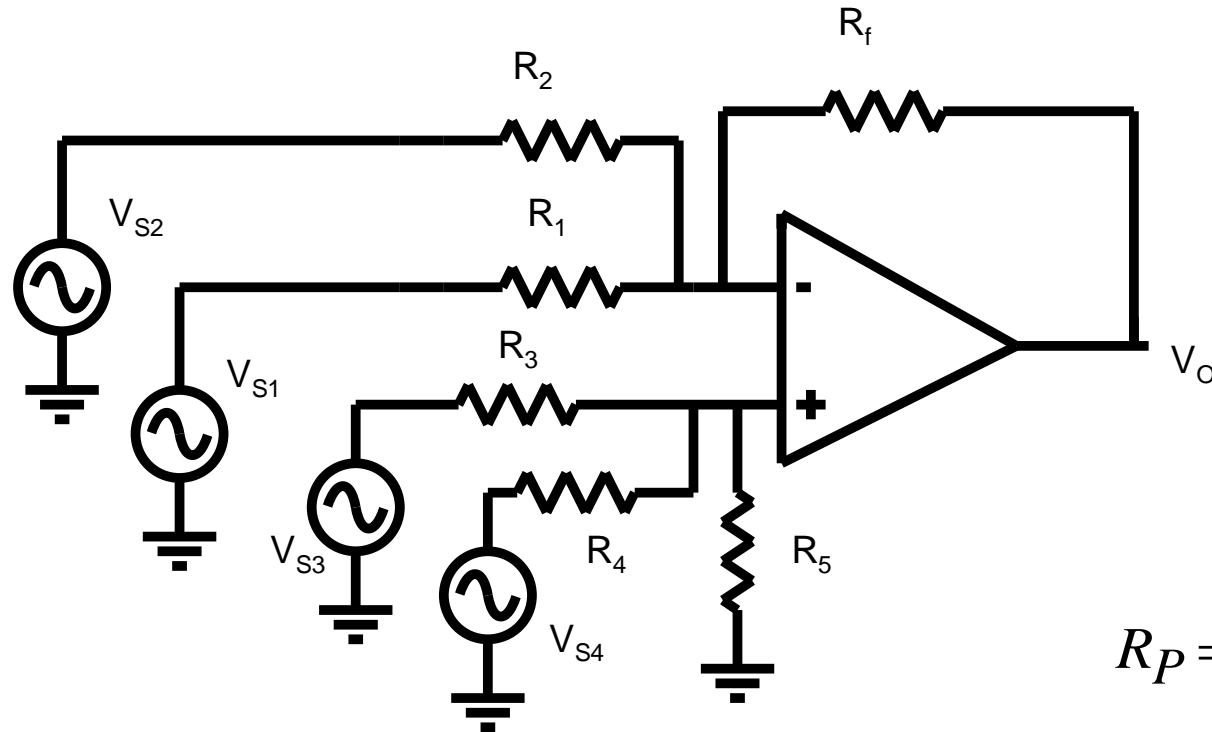

$$R_P = R_3 \parallel R_4 \parallel R_5$$

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_P}{R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) + v_{s4} \frac{R_P}{R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)$$

Example

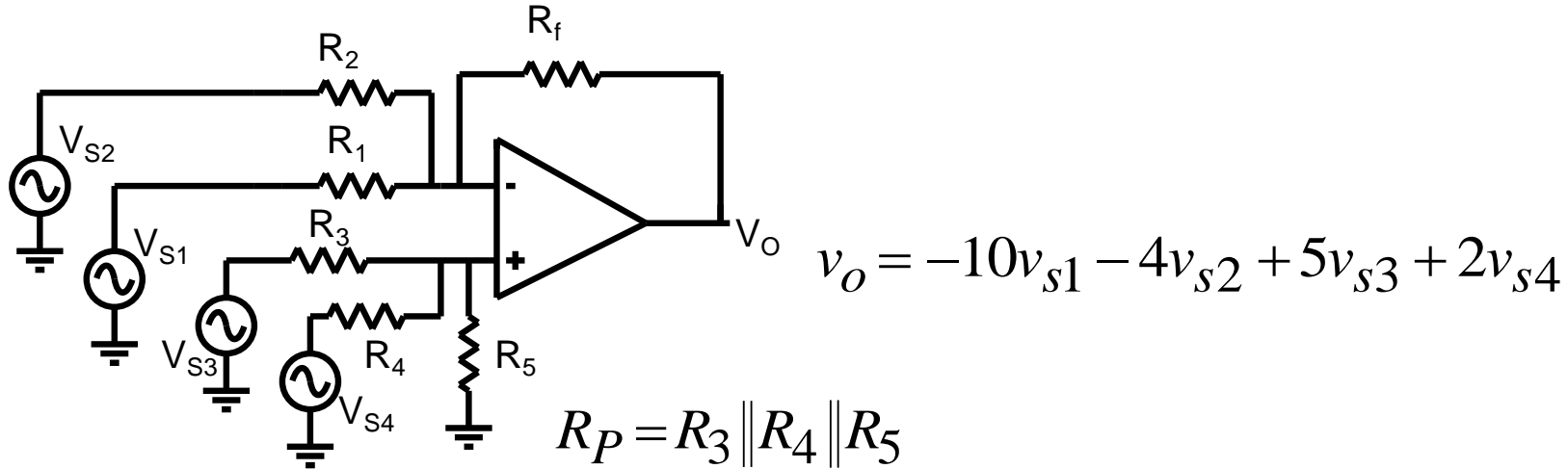


$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} - \left(\frac{R_f}{R_2}\right)v_{s2} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_3}v_{s3} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_4}v_{s4}$$

Choose : $R_f = 10 \text{ k}\Omega \Rightarrow R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 2.5 \text{ k}\Omega$

$$\Rightarrow \frac{R_P}{R_3} = 0.33 \quad \Rightarrow \frac{R_P}{R_4} = 0.133 \quad \Rightarrow \frac{R_4}{R_3} = 2.5$$

Choose : $R_3 = 1 \text{ k}\Omega \Rightarrow R_4 = 2.5 \text{ k}\Omega \Rightarrow R_P = 0.33 \text{ k}\Omega \Rightarrow R_5 = 0.625 \text{ k}\Omega$


Integrator

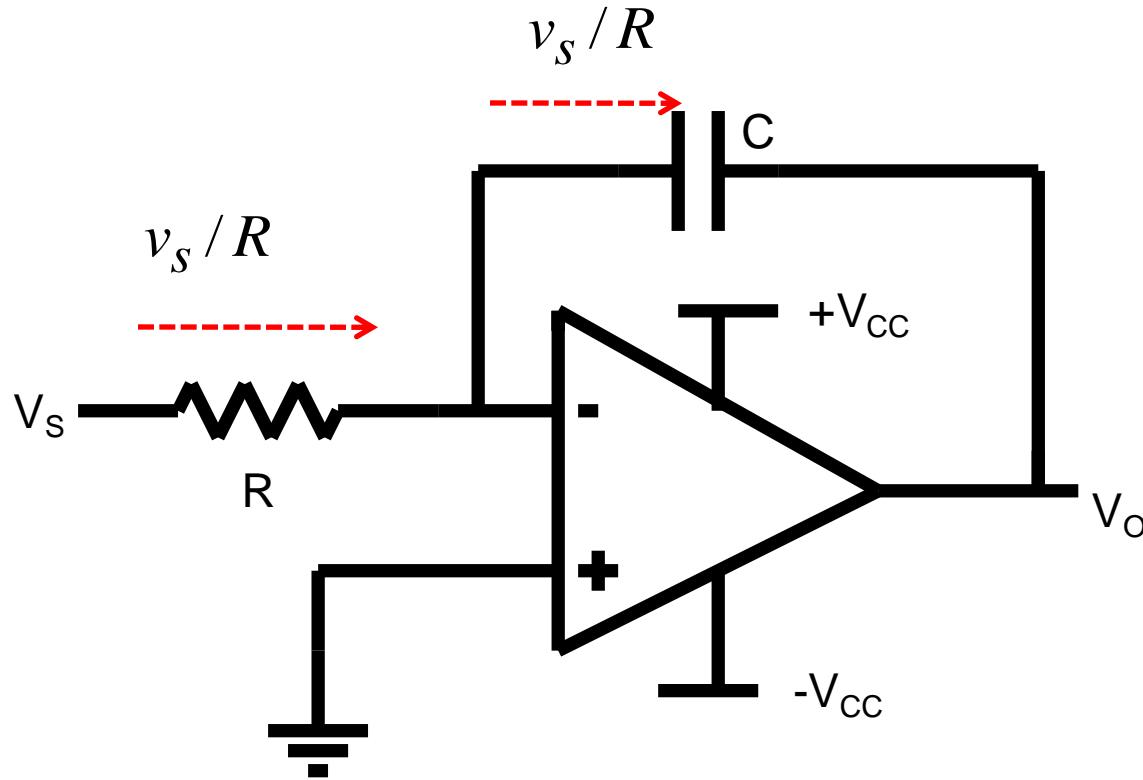

$$\frac{v_S}{R} = -C \frac{dv_O}{dt} \Rightarrow v_O(t) = -\frac{1}{RC} \int v_S dt$$


Caution: To ensure negative feedback for dc component in V_S , a large resistor is often connected in parallel to C . Else, the dc component of input might saturate the output voltage

Differentiator

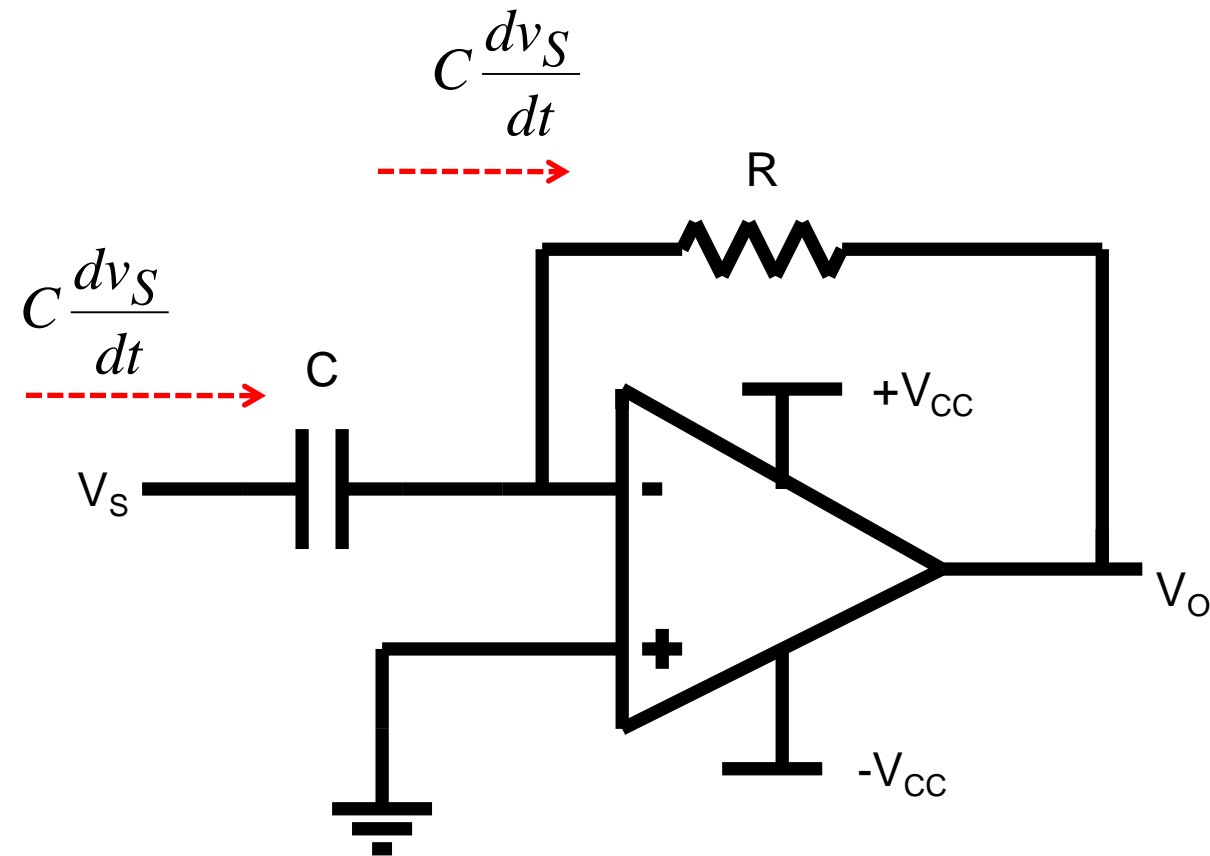


$$-\frac{v_O}{R} = C \frac{dv_S}{dt} \Rightarrow v_O(t) = -RC \frac{dv_S}{dt}$$

Log Amplifier

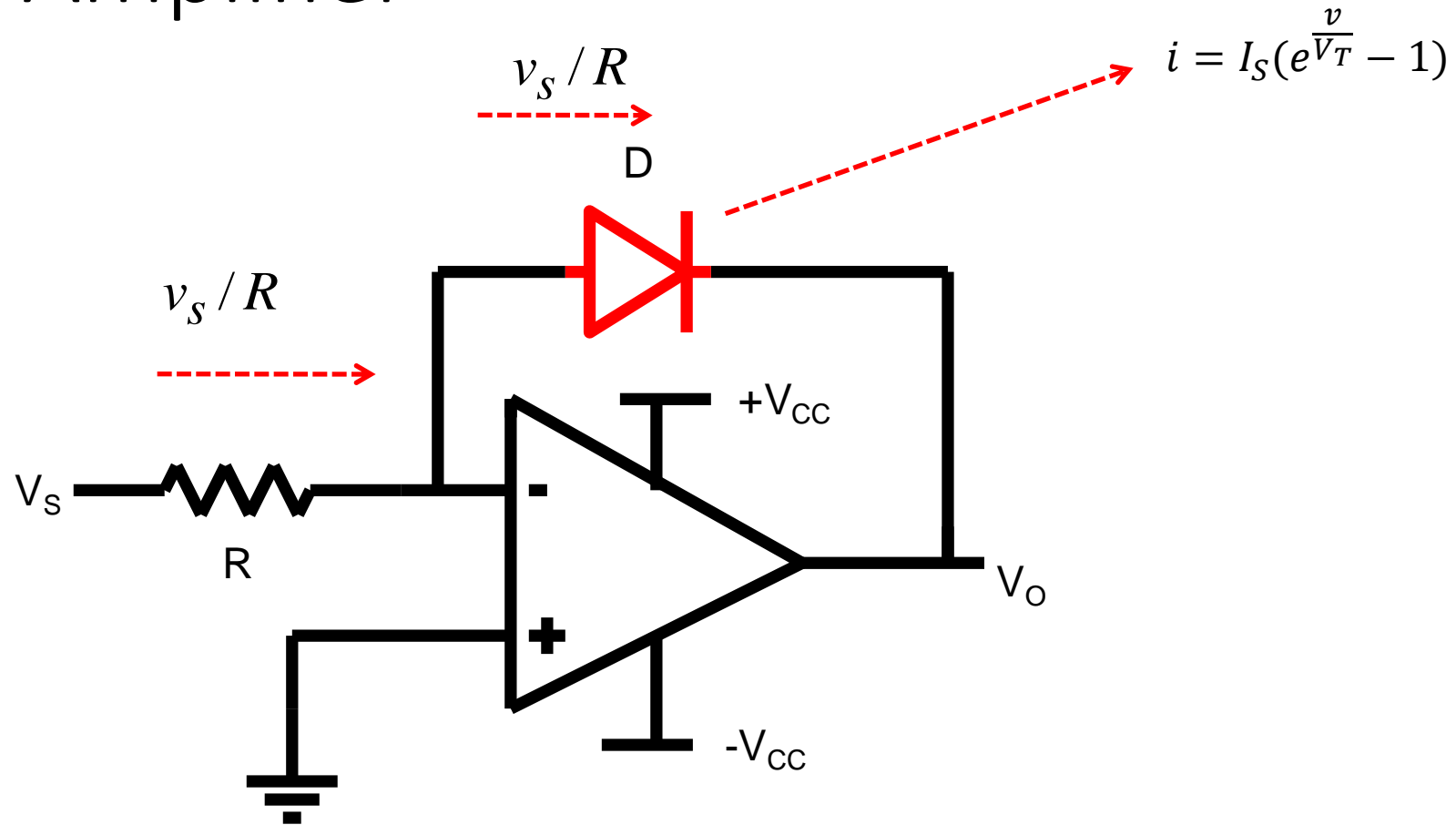

$$\frac{v_S}{R} = I_S \left(e^{-\frac{V_O}{V_T}} - 1 \right) \Rightarrow -v_O = V_T \times \ln \left(1 + \frac{v_S}{R I_S} \right) \cong V_T \times \ln \left(\frac{v_S}{R I_S} \right)$$


Antilog Amplifier

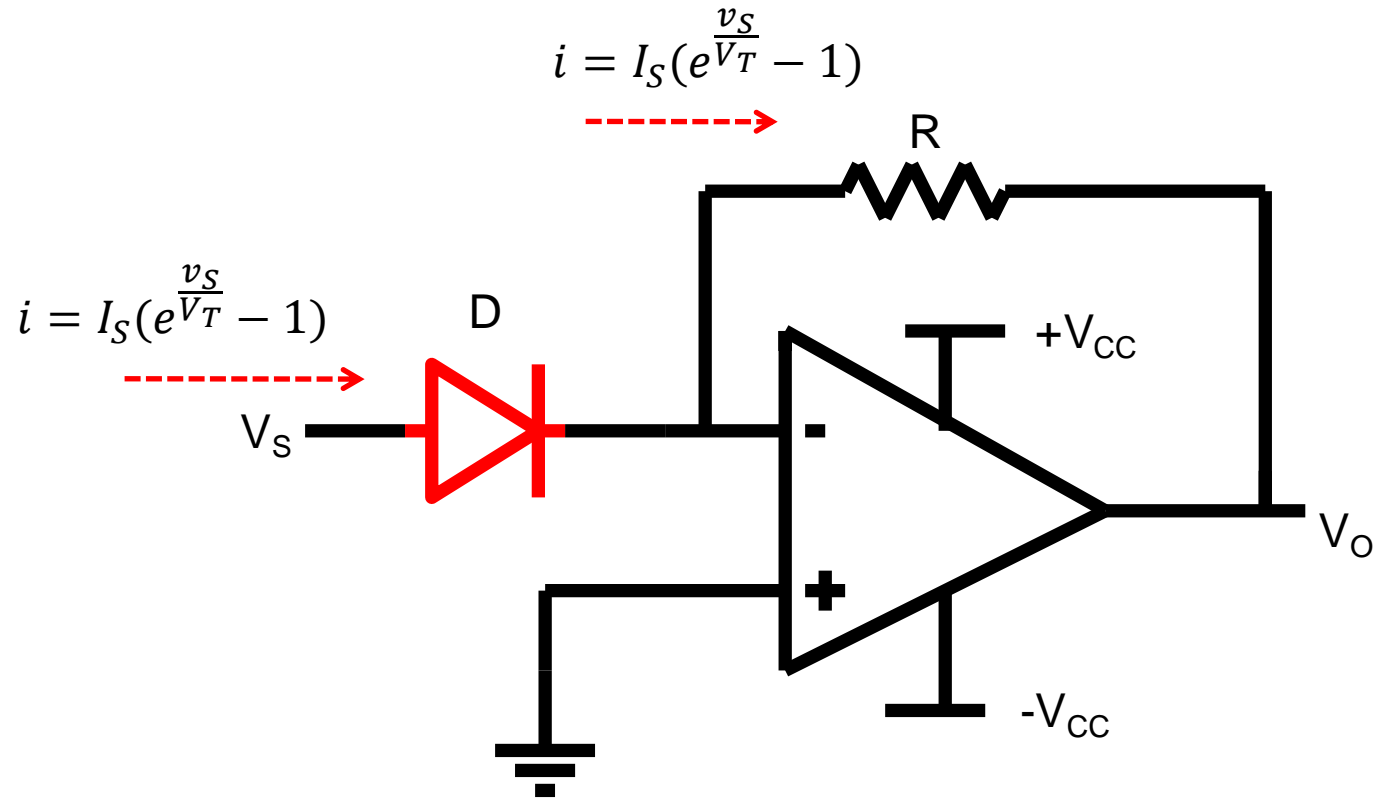

$$-\frac{v_O}{R} = I_S \left(e^{\frac{v_S}{V_T}} - 1 \right) \Rightarrow v_O = -R I_S \left(e^{\frac{v_S}{V_T}} - 1 \right) \cong -R I_S \times e^{\frac{v_S}{V_T}}$$




Multiplier

Use log and anti-log functions


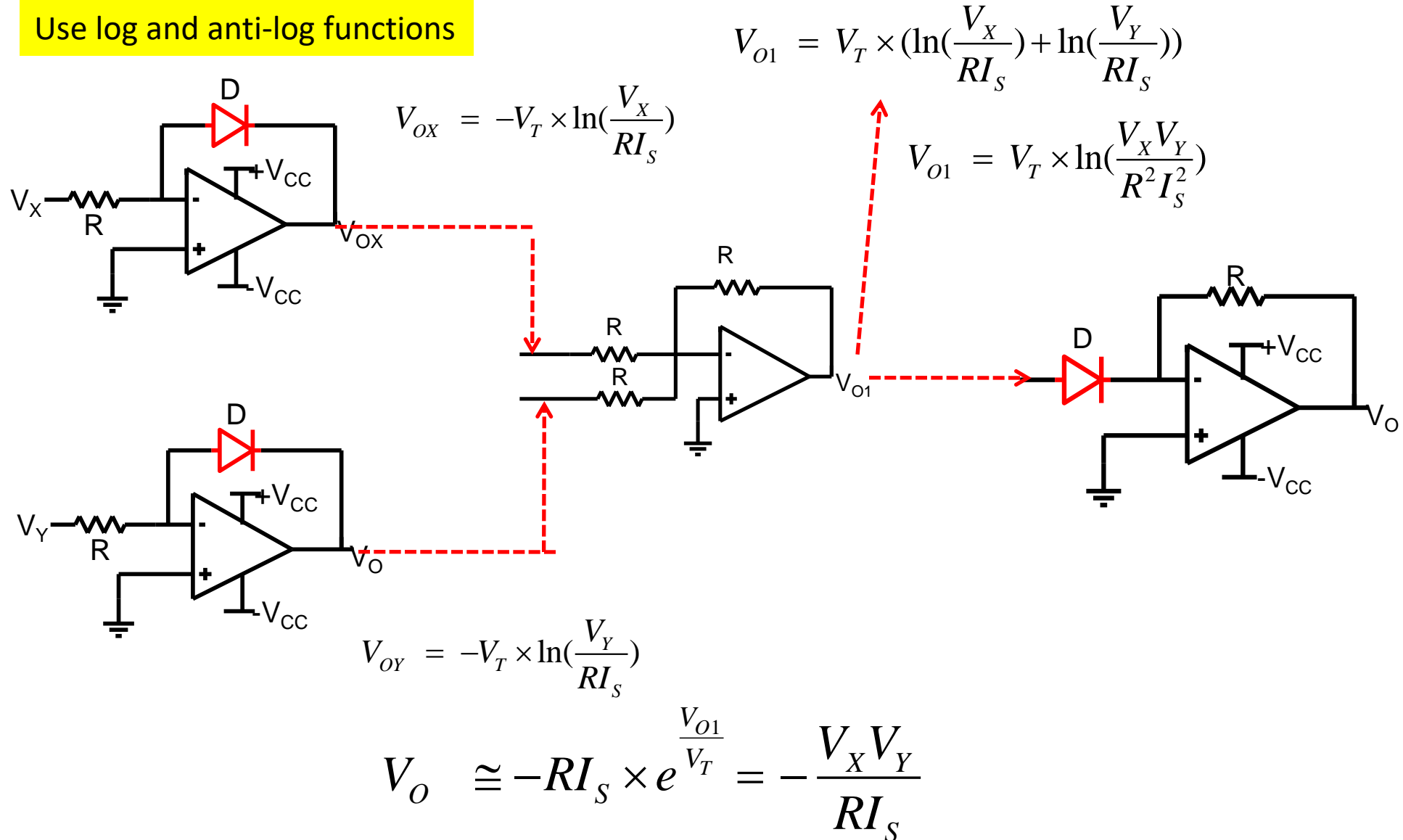


Comparator

Open Loop condition

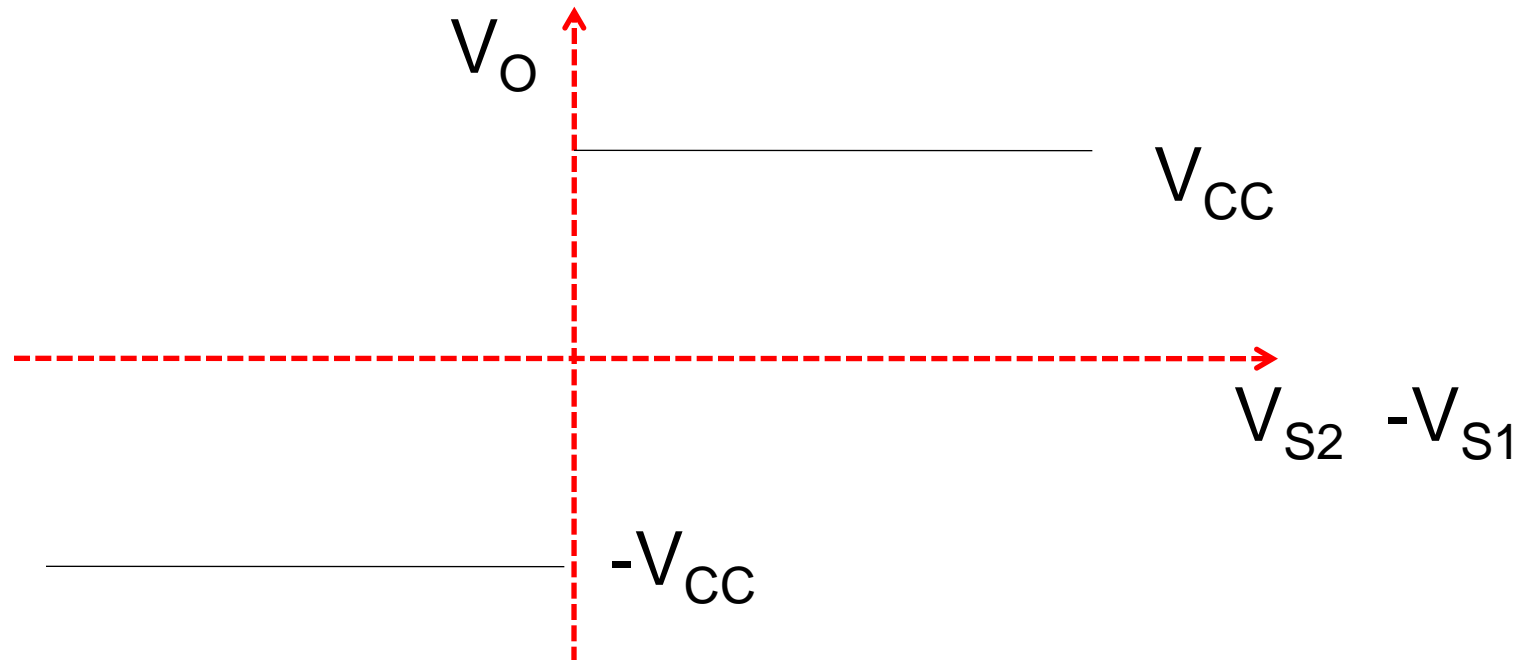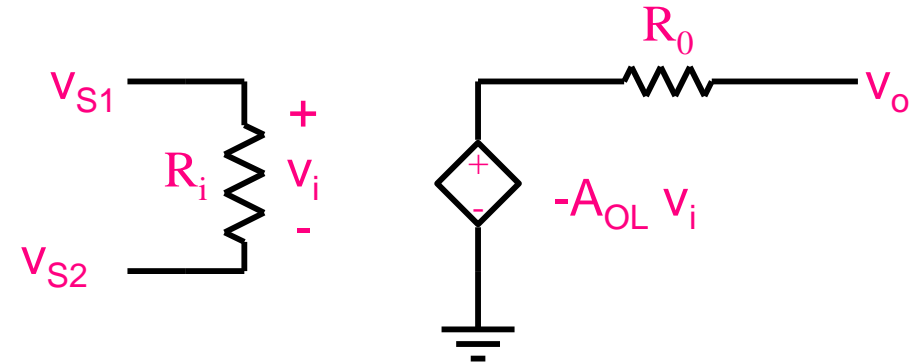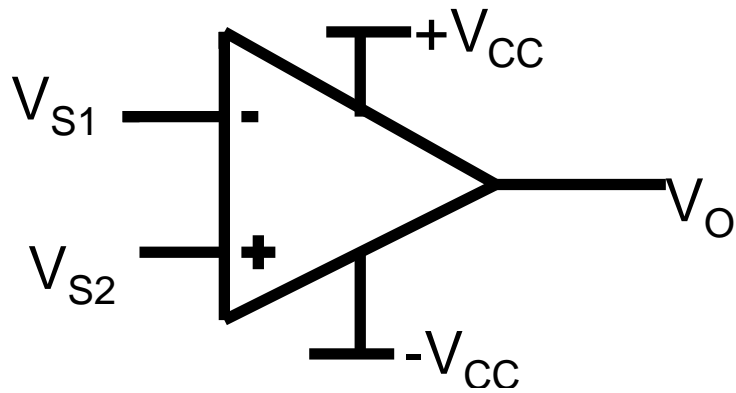


Example 1

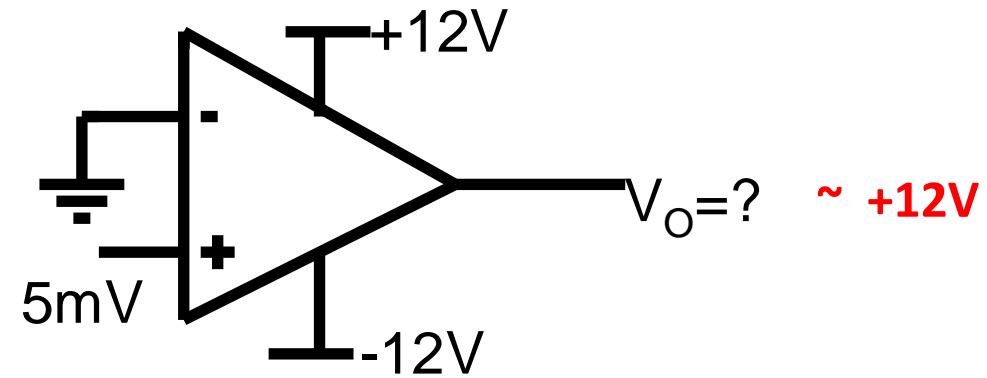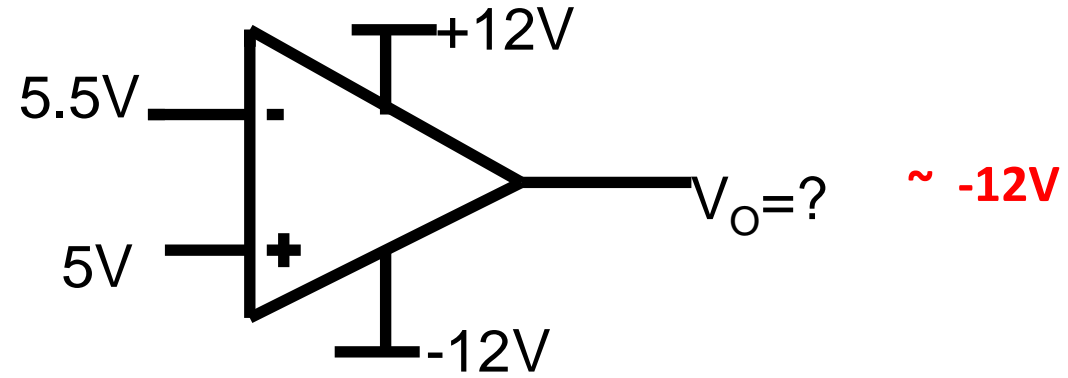

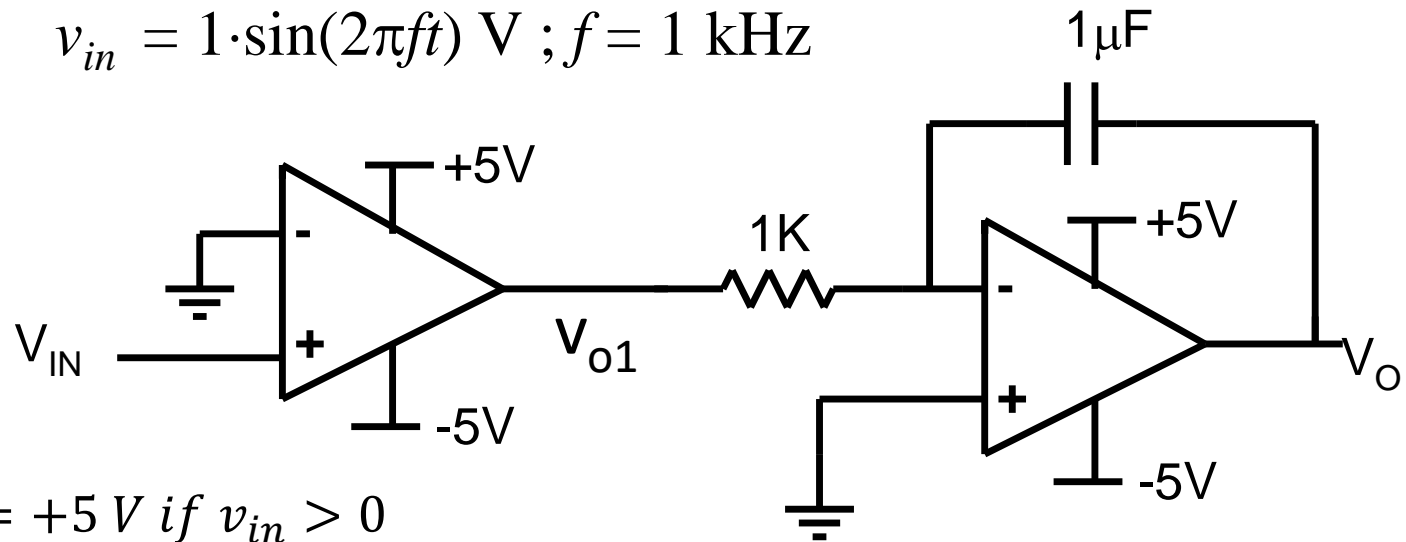Example 2

$$v_{in} = 1 \cdot \sin(2\pi ft) \text{ V} ; f = 1 \text{ kHz}$$



$$V_{O1} = +5 \text{ V if } v_{in} > 0$$

$$= -5 \text{ V if } v_{in} < 0$$

