
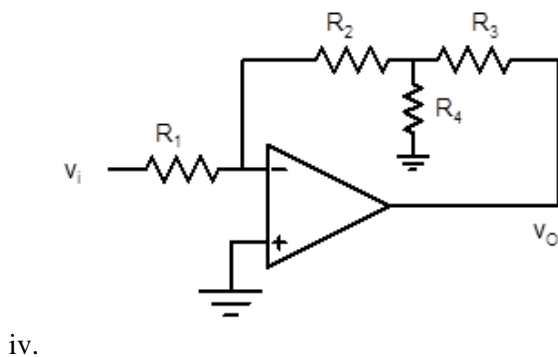
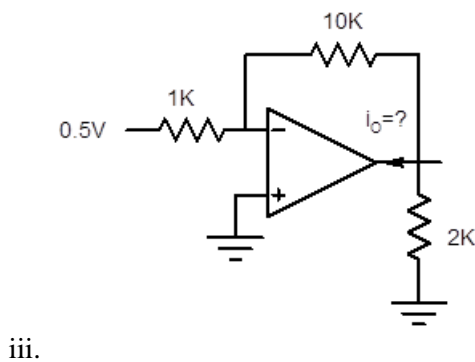
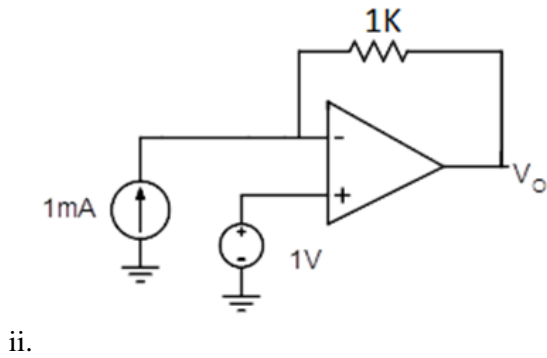


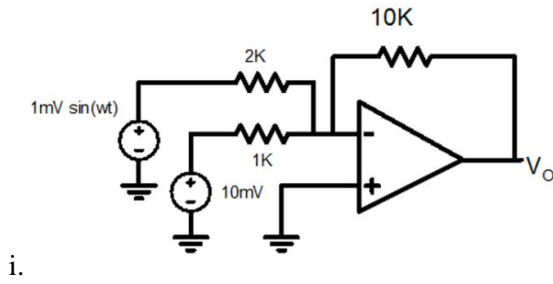
1. Determine the output of the ideal op-amp circuits shown below.




2. Design an op-amp circuit that would generate the following output voltage  $V_O = 2v_{s1} + 4v_{s2} - 8v_{s3} - 10v_{s4}$  where  $v_{s1}$ ,  $v_{s2}$ ,  $v_{s3}$  and  $v_{s4}$  are input voltages.

3. Design an op-amp circuit that can produce  $V_O = K \times V_{IN}^2$  where  $V_{in}$  is the input voltage.

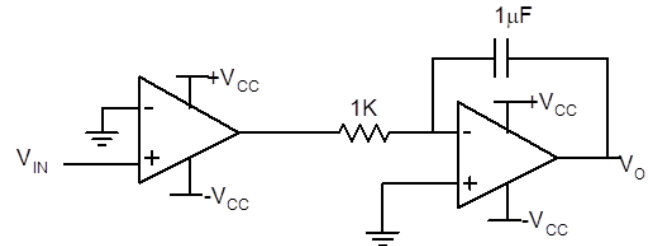4. Sketch the output voltage of the circuit shown below for  $V_{in} = 1V \sin(2\pi ft)$ ;  $f = 1KHz$  and supply voltages of  $\pm 5V$



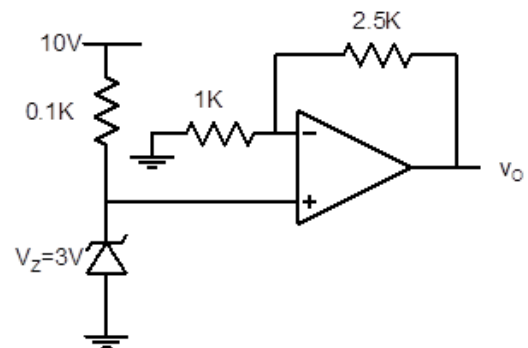5. Determine the output for the ideal op-amp circuit shown below.



6. Design a temperature sensor using a couple of OP-Amps and resistors.