


# ESC201: INTRODUCTION TO ELECTRONICS

## MODULE 6: DIGITAL CIRCUITS



**Dr. Shubham Sahay,**  
**Associate Professor,**  
**Department of Electrical Engineering,**  
**IIT Kanpur**


# Design Flow

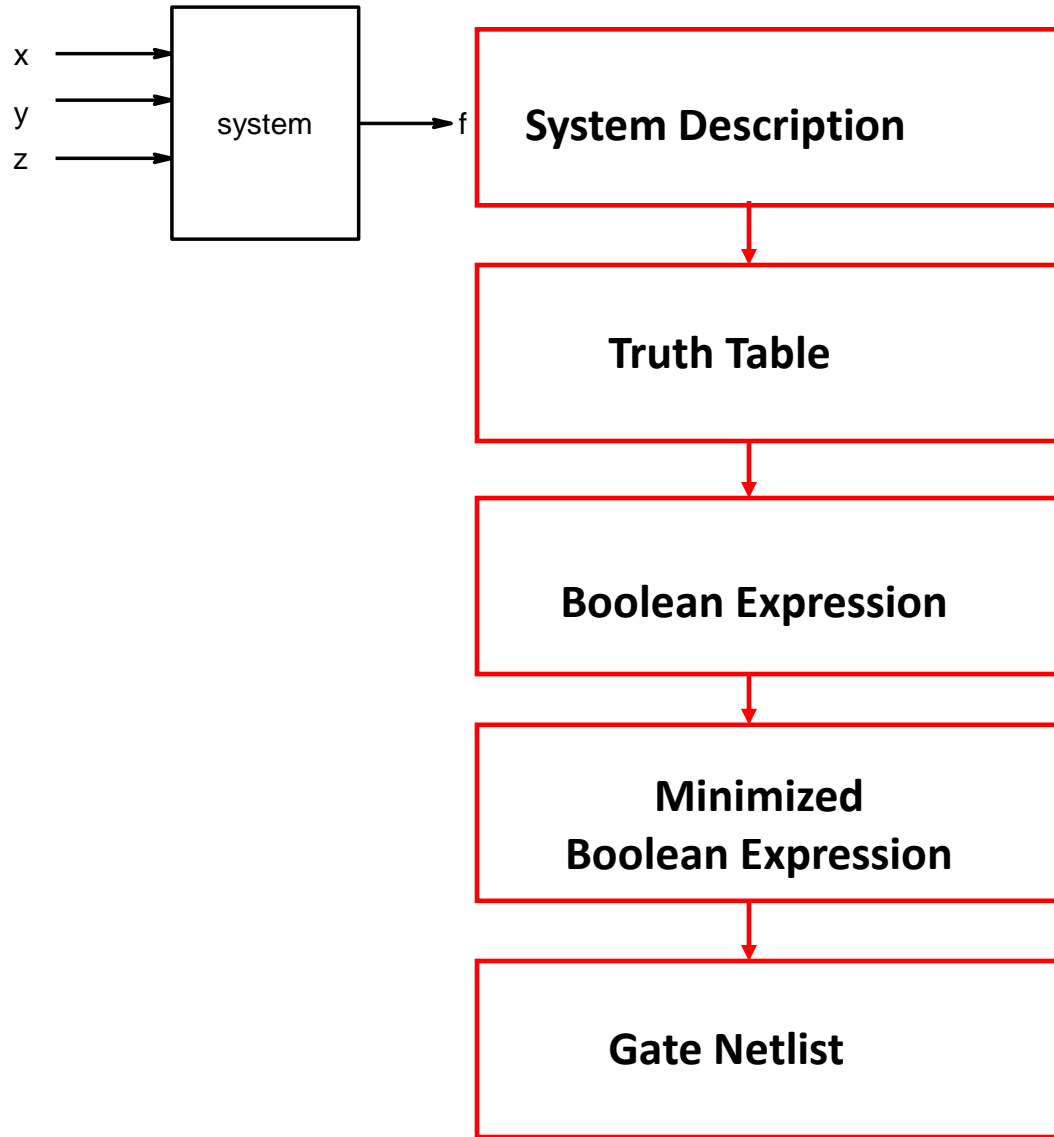

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.\bar{y}.z + x.y.z$$
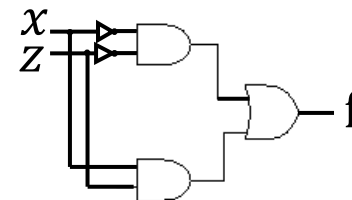
$$\Rightarrow f = \bar{x}.\bar{z} + x.z$$



# K-map Representation of Truth Table

x	y	min term
0	0	$\overline{x} \cdot \overline{y}$ m0
0	1	$\overline{x} \cdot y$ m1
1	0	$x \cdot \overline{y}$ m2
1	1	$x \cdot y$ m3

	y	0	1
x	0	m <sub>0</sub>	m <sub>1</sub>
1	1	m <sub>2</sub>	m <sub>3</sub>

Example

x	y	f <sub>1</sub>
0	0	0
0	1	1
1	0	1
1	1	0



	y	0	1
x	0	0	1
1	1	1	0

# Can We Group 3 Min Terms?

Can we do this ?

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	0

A green oval encircles the three 1s in the row where x=1 (columns yz=00, 01, 11). An 'X' is placed below the oval, indicating that this grouping is invalid.

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	0

Three red ovals are drawn, each encircling one of the 1s in the row where x=1 (columns yz=00, 01, 11). This illustrates that each 1 must be treated as a separate product term.

Note that each encirclement should represent a single product term.

**In this case it does not** represent a single product term.

$$\begin{aligned}
 f &= x.\bar{y}.\bar{z} + x.\bar{y}.z + x.y.z \\
 &= x.\bar{y} + x.z
 \end{aligned}$$

We do not get a single product term.

Grouping in 3 terms will not help in minimization of terms in function.

## Reordering of Numbering not Beneficial for Simplification

Can we use K-map with the following ordering of variables?

x \ yz	00	01	10	11
0	0	0	0	0
1	0	1	1	0

NOT A GOOD IDEA!

Can we combine these two terms into a single term ?

$$\begin{aligned}f &= x \cdot \bar{y} \cdot z + x \cdot y \cdot \bar{z} \\ &= x \cdot (\bar{y} \cdot z + y \cdot \bar{z})\end{aligned}$$

Note that no simplification is possible here.

K-map requires variable to change one bit between adjacent cells

- Continued -

$\begin{array}{c} yz \\ x \end{array}$		00	01	10	11
		0	1	0	1
0	0	0	1	0	1
1	0	0	0	0	0


NOT A GOOD IDEA!

These two terms can be combined into a single term but it is not easy to show that on the diagram.


$$\begin{aligned} f &= \bar{x}.\bar{y}.z + \bar{x}.y.z \\ &= \bar{x}.(\bar{y} + y).z = \bar{x}.z \end{aligned}$$

Kmap requires information to be represented in such a way that it is easy to apply the principle  $x + \bar{x} = 1$


Example

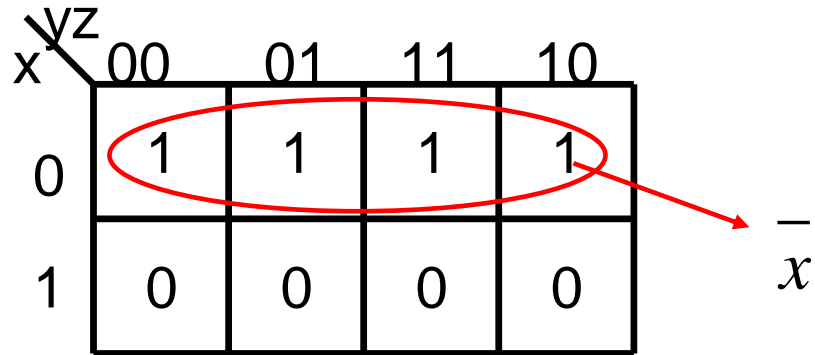


Example

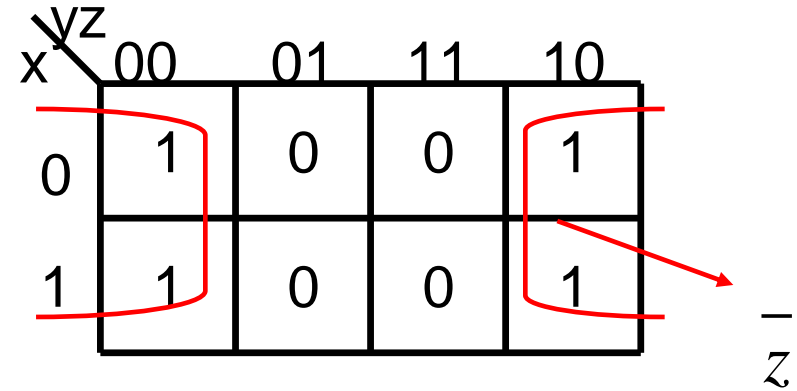

Example

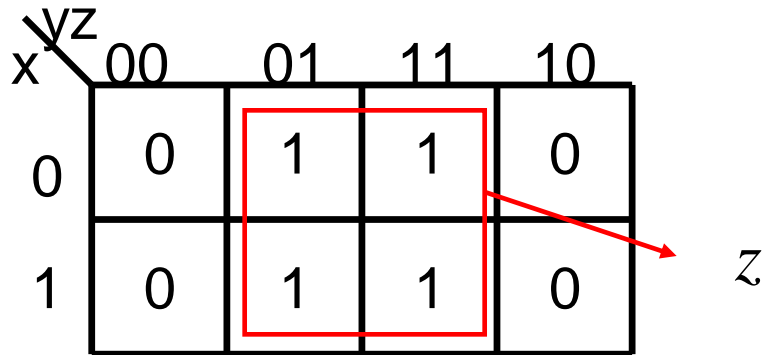


Example

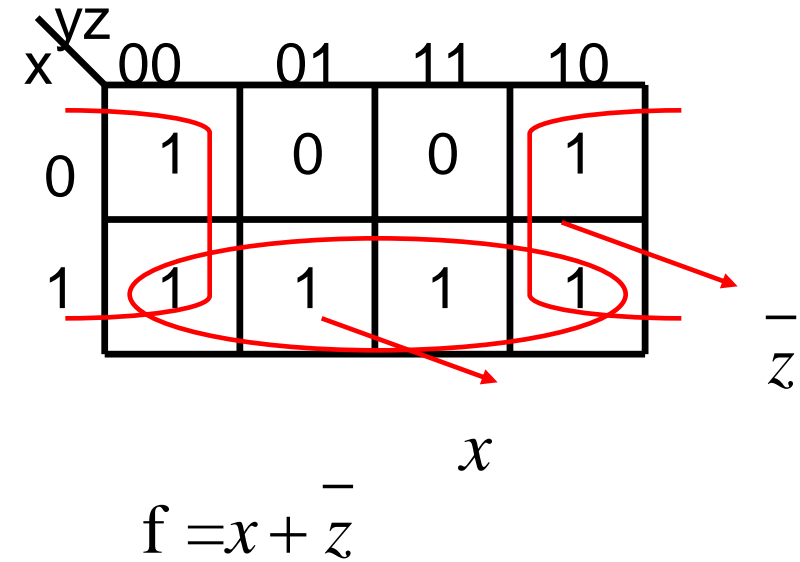

# 4-variable Minimisation

## Example

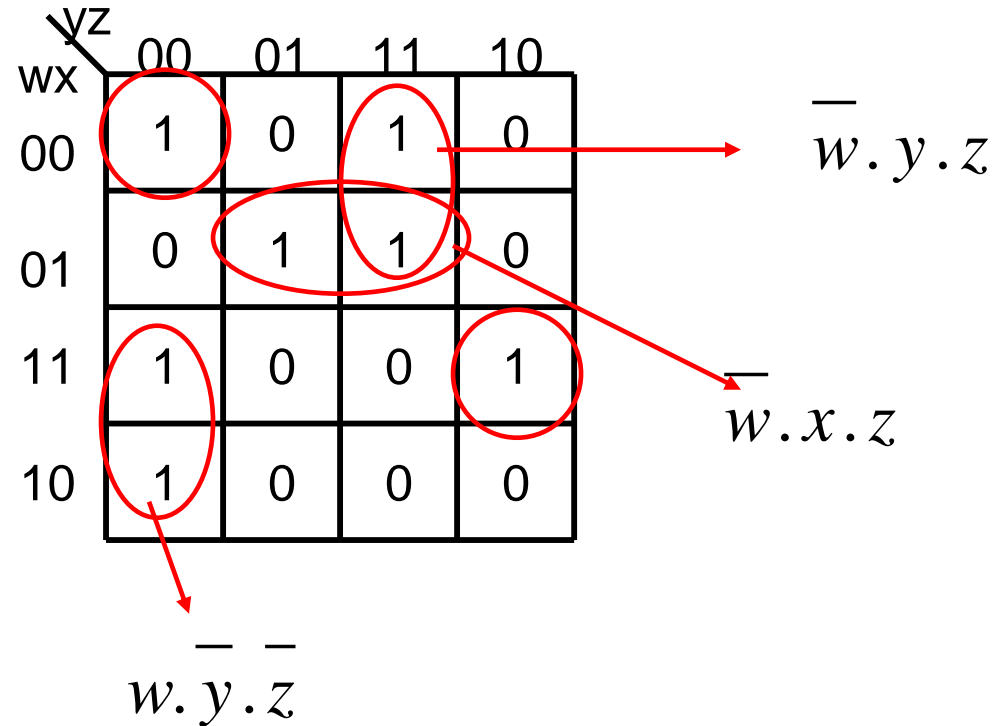

$$f = \overline{w}.y.z + \overline{w}.x.z + w.\overline{y}.\overline{z} + \overline{w}.\overline{x}.\overline{y}.\overline{z} + w.x.y.\overline{z}$$


But is this the simplest expression ?



# The K-Map Folds on Itself

K-map drawn on a torus, and in a plane. The dot-marked cells are adjacent.

- source: Wikipedia

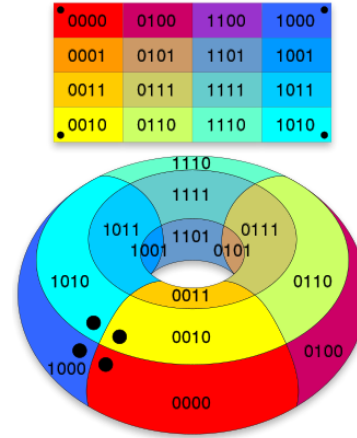

Example (continued)

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0


$$w \cdot x \cdot \bar{y} \cdot \bar{z} + w \cdot x \cdot y \cdot \bar{z} = w \cdot x \cdot \bar{z}$$

Example (continued)

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$w \cdot x \cdot \bar{y} \cdot \bar{z} + w \cdot x \cdot y \cdot \bar{z} = x \cdot \bar{y} \cdot \bar{z}$$

### Example (continued)

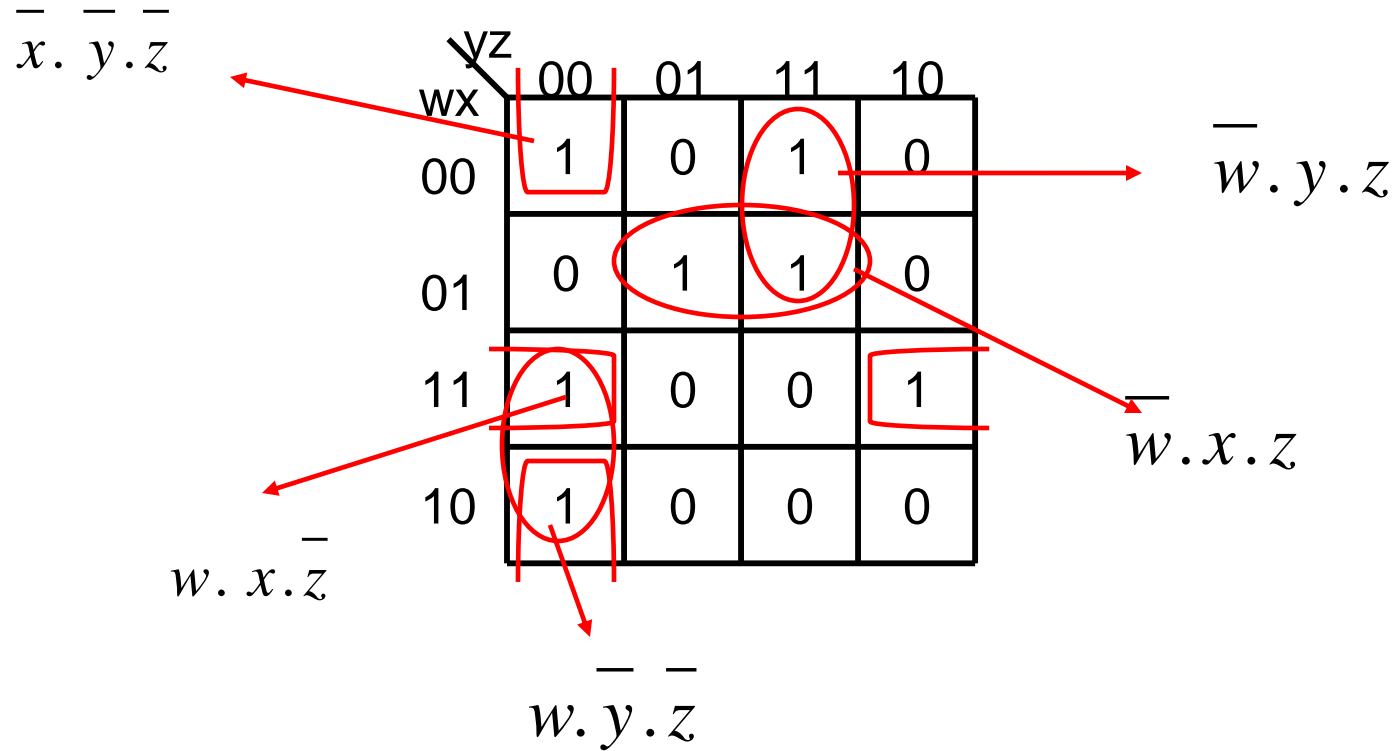

$$f = \overline{w}.y.z + \overline{w}.x.z + w.\overline{y}.\overline{z} + w.x.\overline{z} + \overline{x}.\overline{y}.\overline{z}$$

Is this the best that we can do ?

# Cover the 1's with Minimum Number of Groupings

Example (continued)

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}.y.z + \overline{w}.x.z + \overline{w}.\overline{y}.\overline{z} + \overline{w}.x.\overline{z} + x.\overline{y}.\overline{z}$$

Redundant

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}.y.z + \overline{w}.x.z + \overline{w}.x.\overline{z} + x.\overline{y}.\overline{z}$$

# Equivalent Solutions

## Example

wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

$$f = \overline{w}.x.\overline{y} + w.\overline{x}.z + \overline{w}.\overline{y}.z$$


wx \ yz	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	0	0	0	0
10	1	0	0	1

$$f = \overline{w}.x.\overline{y} + w.\overline{x}.z + x.\overline{y}.z$$


Both solutions are equivalent.

# Groupings of Four

## Example

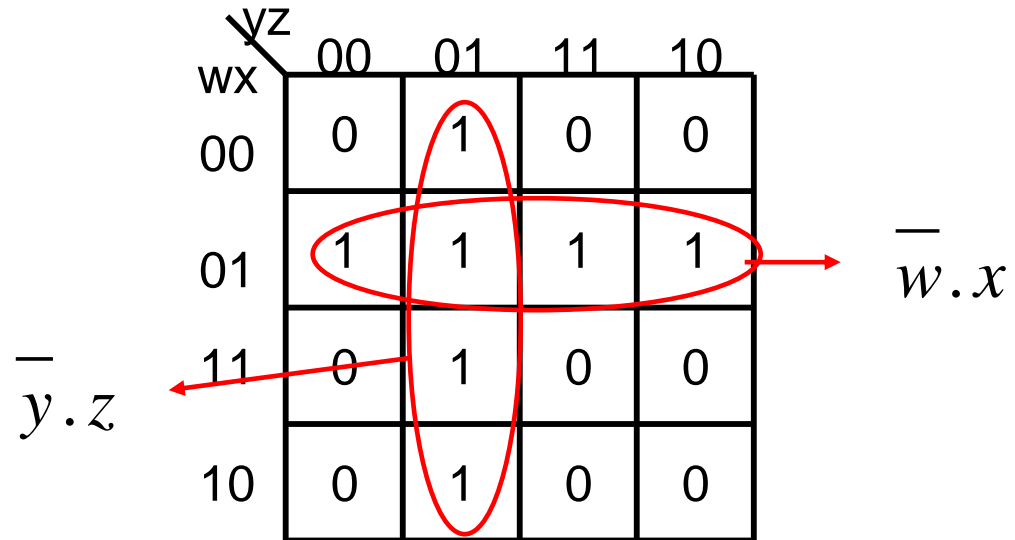

## Example

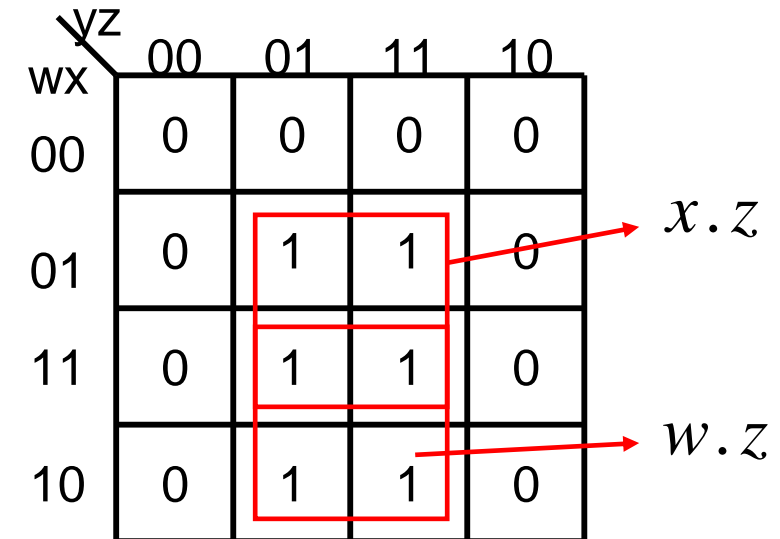

### Example

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

$$x \cdot \bar{z}$$

### Example

wx \ yz	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	0	0	0	0
10	0	1	1	0

$$\bar{x} \cdot z$$

### Example

wx \ yz	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

$$\bar{x} \cdot \bar{z}$$

### Example

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	0	0	0	0
10	1	0	1	0

??

# Groupings of Eight

Example

$\backslash yz$	00	01	11	10
$wx$				
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

Example

$\backslash yz$	00	01	11	10
$wx$				
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

Example

$\backslash yz$	00	01	11	10
$wx$				
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

Example

$\backslash yz$	00	01	11	10
$wx$				
00	1	1	1	1
01	0	0	0	0
11	0	0	0	0
10	1	1	1	1

$z$

$x$

$\bar{z}$

$\bar{x}$

### Example

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	1	1
11	1	1	1	1
10	0	0	0	1


### Example

wx \ yz	00	01	11	10
00	0	1	0	1
01	1	1	0	1
11	1	1	1	1
10	0	0	0	1



# Don't Care Terms

Example

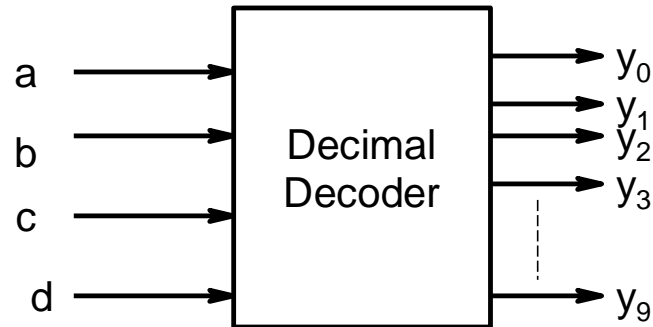

$y_3$

ab \ cd	cd			
	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x


$$y_3 = \bar{a}.\bar{b}.c.d$$

a	b	c	d	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1
1	0	1	0	0	x	x	x	x	x	x	x	x	x
1	0	1	1	0	x	x	x	x	x	x	x	x	x
1	1	0	0	0	x	x	x	x	x	x	x	x	x
1	1	0	1	0	x	x	x	x	x	x	x	x	x
1	1	1	0	0	x	x	x	x	x	x	x	x	x
1	1	1	1	0	x	x	x	x	x	x	x	x	x
1	1	1	1	1	x	x	x	x	x	x	x	x	x

# Choice of Don't Care Terms

Don't care terms can be chosen as 0 or 1. Depending on the problem, we can choose the don't care term as 1 and use it to obtain a simpler Boolean expression

**Example**

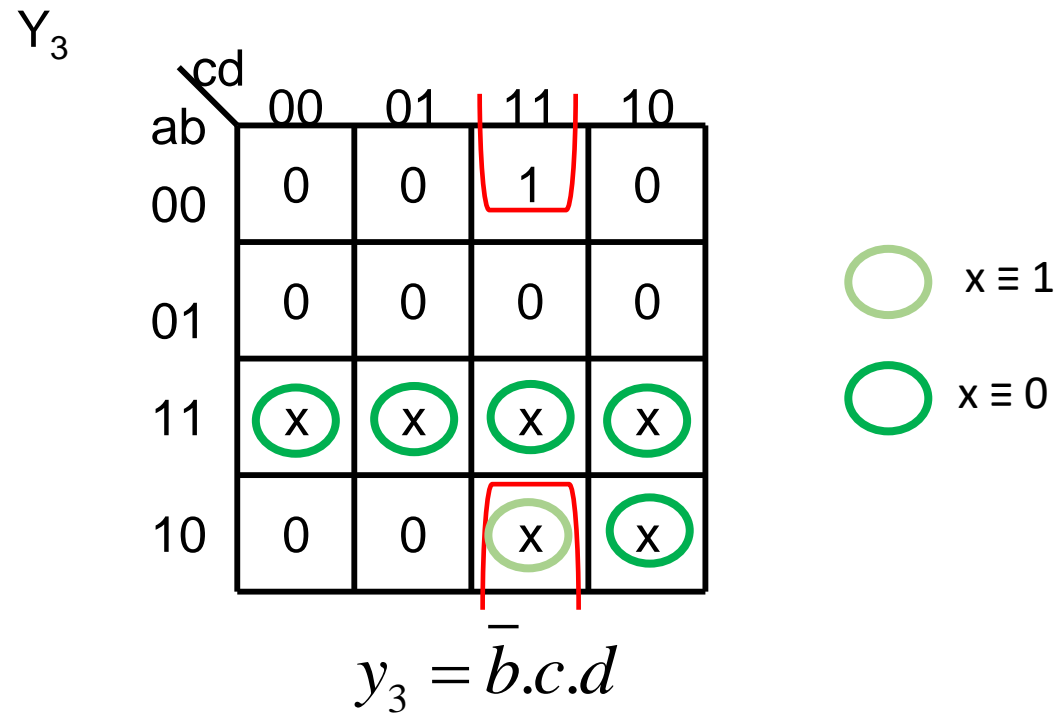

Don't care terms should only be included in encirclements if it helps in obtaining a larger grouping or smaller number of groups.

# Minimisation of PoS Terms using K-map

Example

x \ y	0	1
0	0	1
1	1	1

$$\begin{aligned}f &= x + \bar{x}.y + x.y \\&= x + (\bar{x} + x).y \\&= x + y\end{aligned}$$

Example

x \ y	0	1
0	0	1
1	1	1

$f = x + y$

Example

x \ y	0	1
0	0	1
1	0	1

$f = y$

Example

		y	
		0	1
x	0	1	0
	1	1	0

$\Rightarrow f = \bar{y}$

Example

		y	
		0	1
x	0	1	1
	1	0	0

$\Rightarrow f = \bar{x}$


Example

		yz			
		00	01	11	10
x	0	1	0	0	1
	1	0	1	1	0

$\bar{x} + z$  (pointing to the 0 in row 1, column 00)  
 $x + \bar{z}$  (pointing to the 0 in row 0, column 11)

$$f = (\bar{x} + z) \cdot (x + \bar{z}) \Rightarrow f = \bar{x} \cdot \bar{z} + x \cdot z$$

### Example

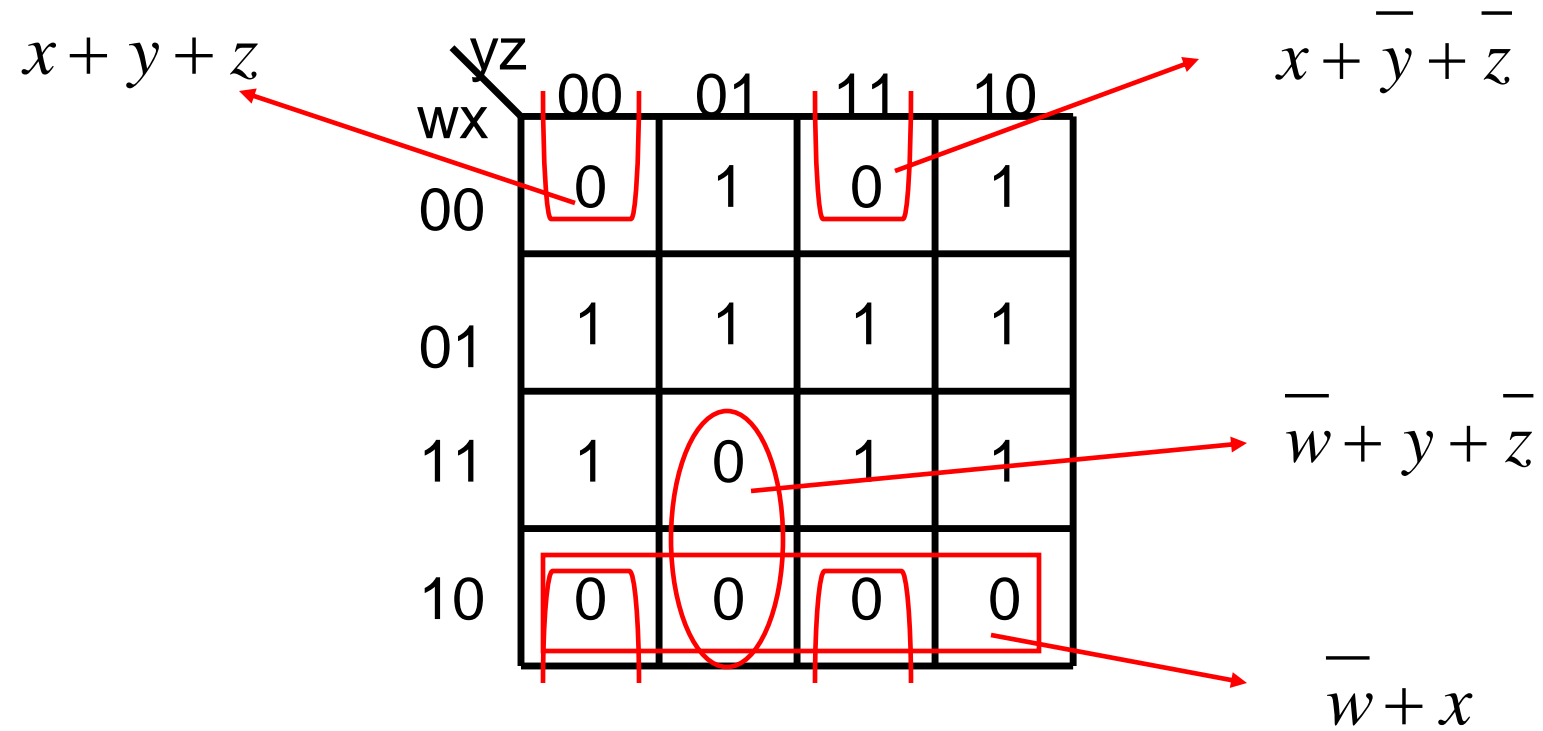

$$f = (x + y + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{w} + y + \bar{z}) \cdot (\bar{w} + x)$$

# Choosing x to be 0 to optimise PoS

Obtain the minimized PoS by suitably making don't care terms to be zero.

Rest of don't care(s) are to be chosen as one.

## Example



wx \ yz	00	01	11	10
00	1	x	0	1
01	1	0	1	1
11	0	x	1	1
10	1	x	1	x

For grouping you assume:

- all selected  $x^s$  are '0'
- not selected x is '1'

$$f = (x + w + \bar{z}).(\bar{x} + \bar{w} + y).(y + \bar{z})$$


# Design Flow

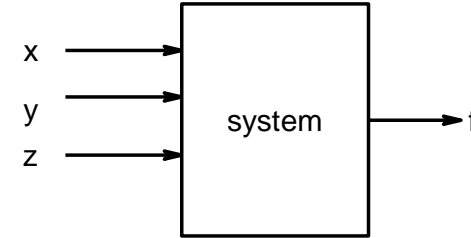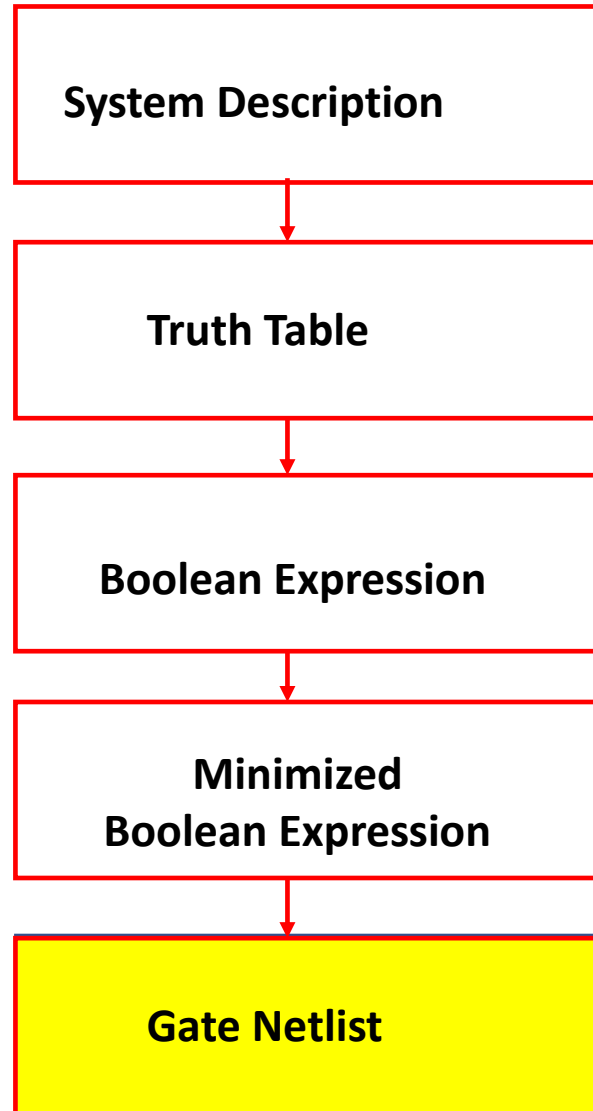

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.\bar{y}.z + x.y.z$$
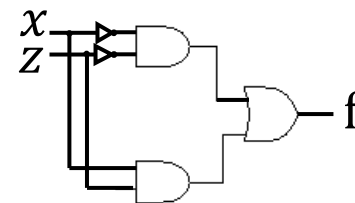
$$\Rightarrow f = \bar{x}.\bar{z} + x.z$$



# Boolean Functions

So far we have been looking at SoP or PoS forms

For example:

$$f = \bar{x} \cdot \bar{z} + x \cdot z \quad \text{or} \quad f = (\bar{x} + z)(x + \bar{z})$$

This requires AND, OR and NOT operations.

First choice use “Gates” to implement AND, OR and NOT operations.

(The Boolean function and interactions are gating the transmission of 1)




There may be other ways to implement the functions as well!



# The Basic Gates

Popular introductory gates to represent Boolean operations: {AND, OR and NOT}

Gate

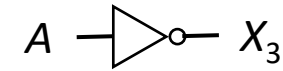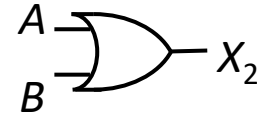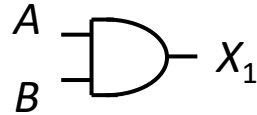

Operation

AND

OR

NOT

Algebraic  
Representation

$$X_1 = A \cdot B = A \wedge B$$

$$X_2 = A + B = A \vee B$$

$$X_3 = \overline{A} = A' = \neg A$$

Truth Table

A	B	X <sub>1</sub>
0	0	0
0	1	0
1	0	0
1	1	1

A	B	X <sub>1</sub>
0	0	0
0	1	1
1	0	1
1	1	1


A	X <sub>3</sub>
0	1
1	0

The three gates together form a basis set for representing Boolean relationship.

AND and OR gates with more than two inputs is a possibility and often used.



# Implementing Boolean expressions using gates

## Example

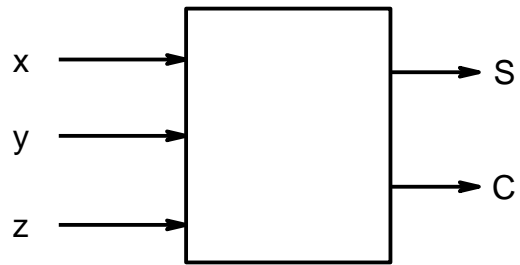

$$S = \bar{x}.\bar{y}.z + \bar{x}.y.\bar{z} + x.\bar{y}.\bar{z} + x.y.z$$


$$C = x.y + x.z + y.z$$

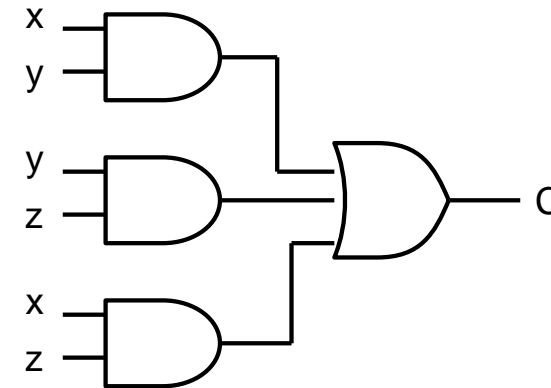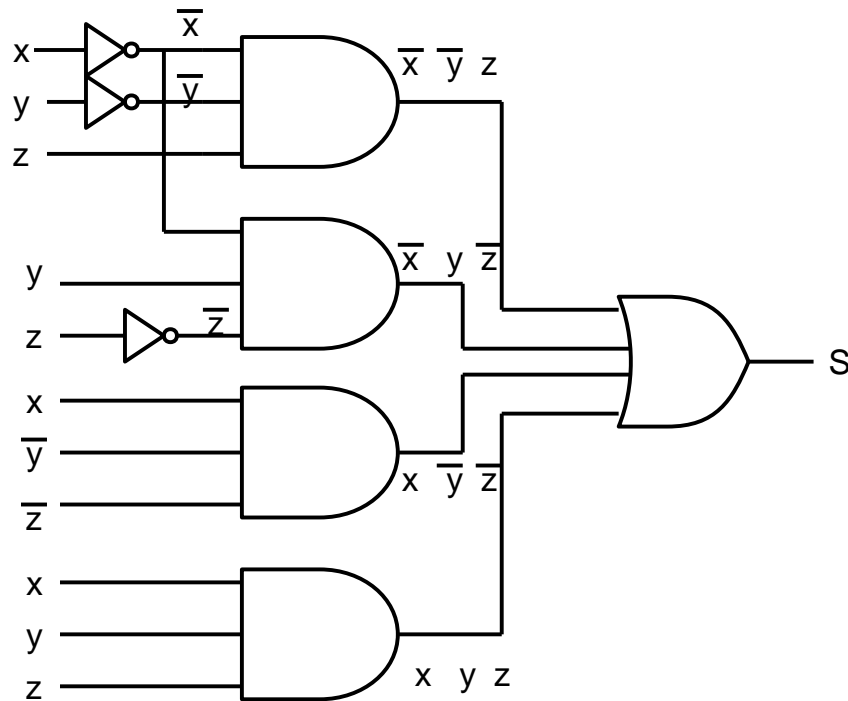

# Popular Universal Gates

Two gates are popular for implementing Boolean Logic in hardware

Gate

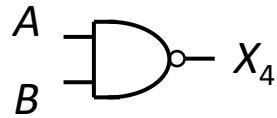

Operation


NAND

Algebraic  
Representation

$$X_4 = \overline{A \cdot B} = \overline{A} + \overline{B}$$

Truth Table

A	B	X <sub>1</sub>
0	0	1
0	1	1
1	0	1
1	1	0

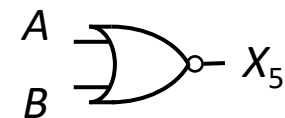

NOR


$$X_5 = \overline{A + B} = \overline{A} \cdot \overline{B}$$

A	B	X <sub>1</sub>
0	0	1
0	1	0
1	0	0
1	1	0



Each of these two gates form a basis set for representing Boolean relationship. They are examples of **Universal Gates** to implement Boolean functions. More than two inputs NAND and NOR gates is a possibility and are often used.

# Parsing the NAND and NOR Gates


NAND:  $y = \overline{x_1 \cdot x_2}$

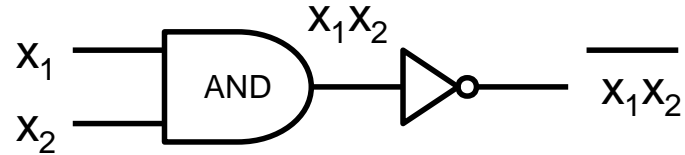

NOR:  $y = \overline{x_1 + x_2}$

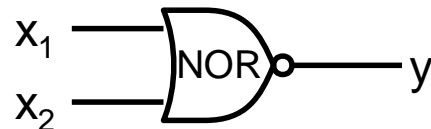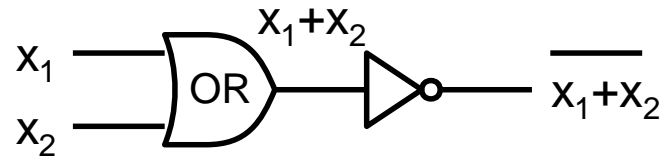

# Basic Boolean Operations with NAND

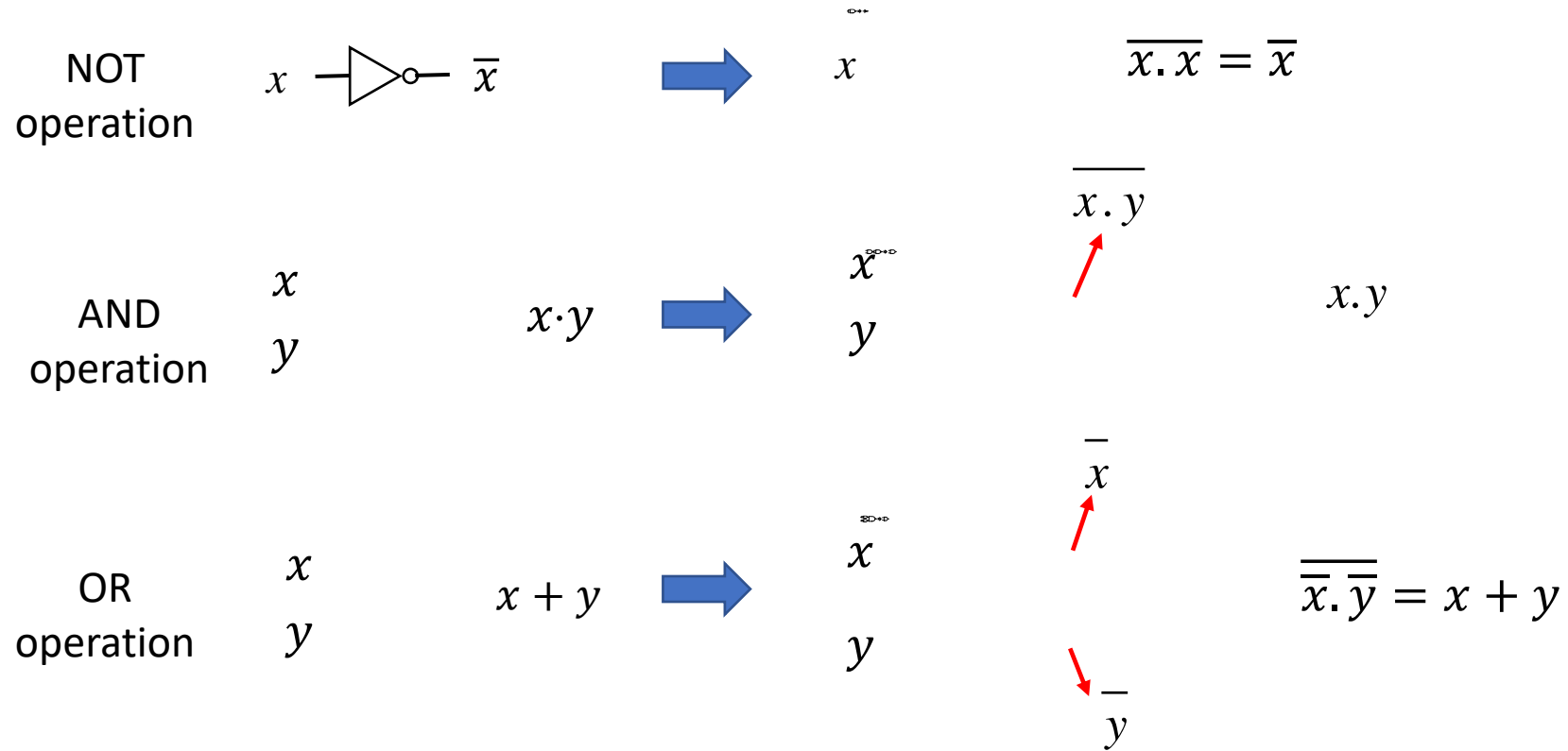


## Exercise

Implement NOT, AND and OR with NOR gates

## Implementing Boolean Function with Universal Gates

To implement using NOR gates, it is easiest to start with minimized Boolean expression in POS form

$$f = (a + b).(c + d).(g + h)$$

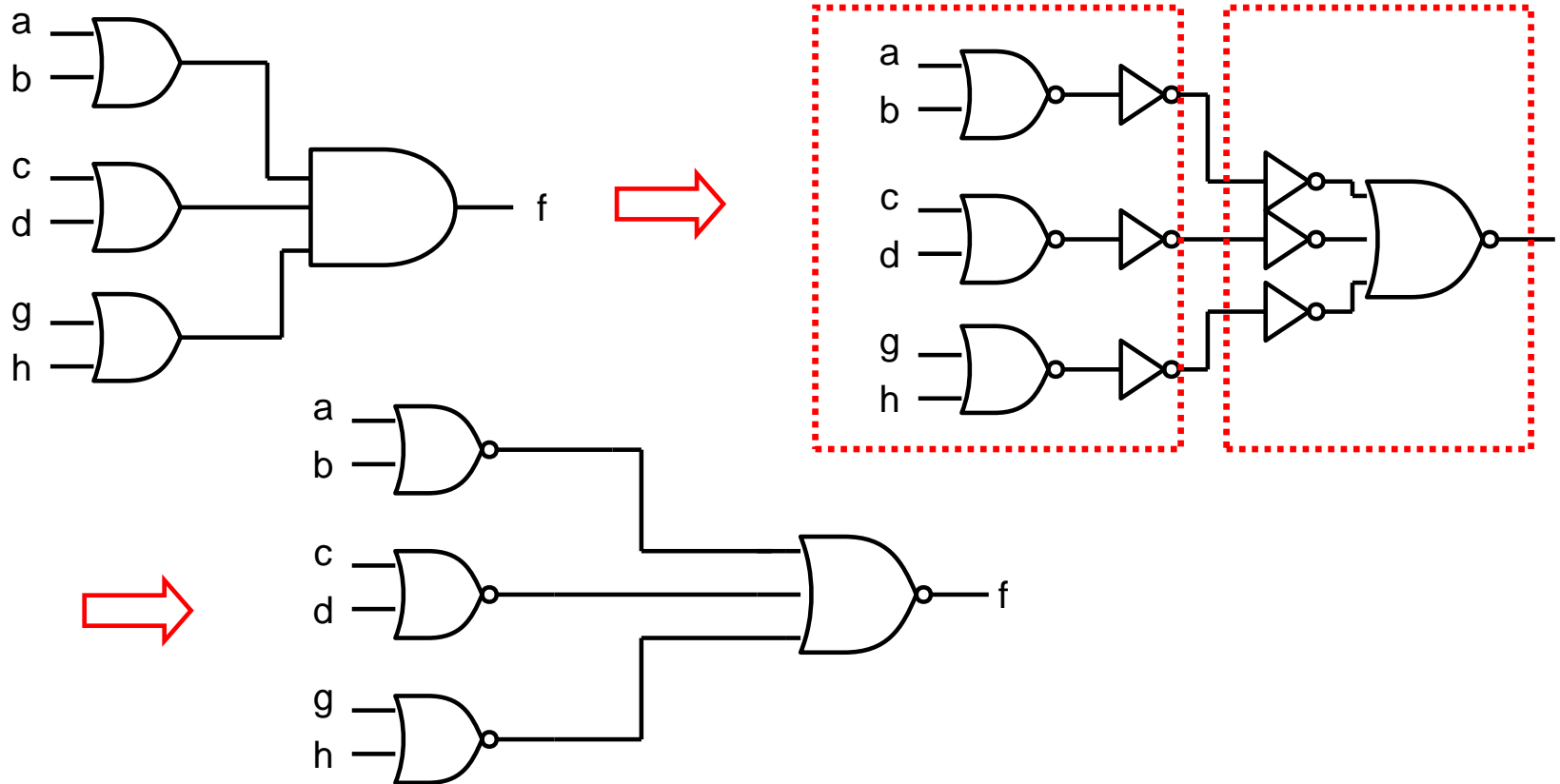


There is one-to-one mapping between OR-AND network and NOR network.

Similarly, there is a one-to-one mapping between AND-OR network and NAND network.

### Example

Implement  $f(x,z) = \bar{x}.\bar{z} + x.z$  using NOR gates



This is XNOR function!



x \ z	00	01	11	10
0	1	0	0	1
1	0	1	1	0

Find out PoS
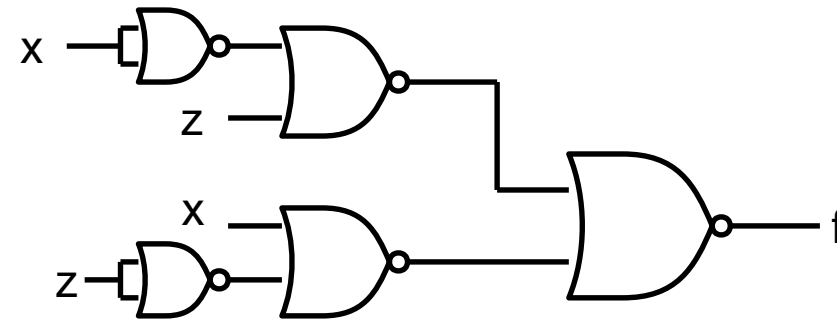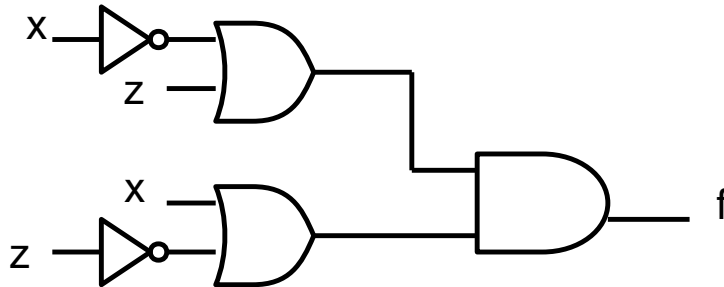
$$\Rightarrow f = (\bar{x} + z). (x + \bar{z})$$



Similarly SoP expression can be implemented as NAND network.

→ first convert to SoP expression      → then follow procedure outlined earlier