

## ESC201 Introduction to Electronics Lab 7 Handout for Lab Experiments

### Applications of Op-Amp in Negative Feedback

**Aim:** The aim of this lab is to study the application of operational amplifier (op-amp) in negative feedback.

**Introduction:** The op-amp as shown in Fig. A (a schematic), Fig. B (the actual chip denoted by the number 741), and Fig. C (a schematic of the chip with pin numbers), is among the most basic linear integrated circuits frequently employed in diverse low frequency applications.

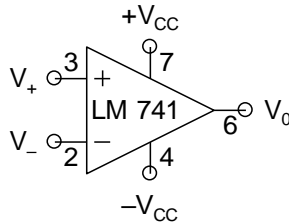


Figure A



Figure B

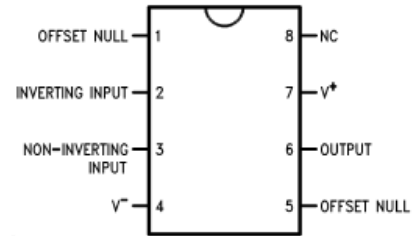


Figure C

The actual chip has four pins on each side, (fully shown in Fig. C only, and partly shown in Fig. B). Referring to Figs. A and C, the op-amp has two inputs, viz., inverting ( $V^-$ : pin no. 2) and non-inverting ( $V^+$ : pin no. 3), and one output ( $V_0$ : pin no. 6). Pin numbers 7 and 4 are used for the power supplies,  $+V_{CC}$  and  $-V_{CC}$  respectively. Pin numbers 1 and 5 will not be used in this experiment (*keep them open*).

**Note:** Use the FG from the DSO. The ground of the DC power supply, the FG and the DSO must be the same.

#### Experiment 1: Voltage Amplification using Op-Amp ( $5 \times 2 = 10$ marks)

##### A. Inverting Amplifier

Wire the circuit of Fig. E1a. Choose  $R_2 = 51 \text{ k}\Omega$ . Adjust the FG output to produce  $V_i = 0.1 \sin(\omega t) \text{ V}$  of 1 kHz frequency. Observe, measure and plot the  $V_i$  and  $V_0$  waveforms. Measure the voltage gain  $A_v \equiv V_0/V_i$ . What is its sign? Compare the experimental value with the theoretically calculated one.

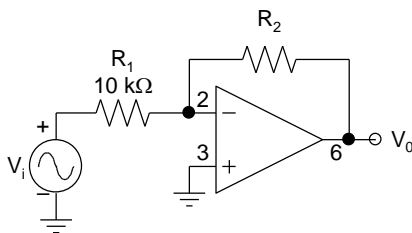


Figure E1a: Inverting Amplifier

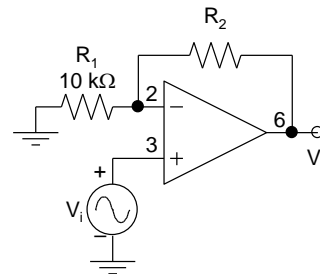


Figure E1b: Non-inverting Amplifier

##### B. Non-Inverting Amplifier

Wire the circuit of Fig. E1b. Choose  $R_2 = 51 \text{ k}\Omega$ . Adjust the FG output to produce  $V_i = 0.1 \sin(\omega t) \text{ V}$  of 1 kHz frequency. Observe, measure and plot the  $V_i$  and  $V_0$  waveforms. Measure the voltage gain.  $A_v \equiv V_0/V_i$ . What is its sign? Compare the experimental value with the theoretically calculated one.

#### Experiment 2: Difference Amplifier (DA) using Op-Amp ( $7 \times 2 = 14$ marks)

The aim of this part of the experiment is to study the performance of a DA by measuring its common-mode (CM) and differential-mode (DM) gains. In an ideal DA, the differential-mode gain  $A_d$  is infinite and the common-mode gain  $A_c$  is zero, thus giving an infinite common-mode rejection ratio ( $\text{CMRR} \equiv |A_d/A_c|$ ). However, in a practical op-amp circuit, since  $A_d$  is finite and  $A_c$  is not exactly zero (but quite small), the CMRR might be of the order of  $10^4$ . The circuit of Fig. E2a and E2b will work as a DA when  $R_2/R_1 = R'_4/R_3$  (where  $R'_4 = R_4 + \text{part of the } 10 \text{ k}\Omega \text{ potentiometer } R$ ), giving a voltage gain of  $R_2/R_1$ .

**A. Measurement of the Common-Mode Gain  $A_c$** 

Wire the circuit of Fig. E2a, i.e., apply  $V_i$  to one end of  $R_1$  as well as  $R_3$ . Adjust the FG output to produce a  $V_i = 10 \sin(\omega t)$  V of 1 kHz frequency. Observe, measure and plot the output voltage  $V_o$  and minimize its amplitude by adjusting the 10 k $\Omega$  potentiometer. Calculate the common-mode gain  $A_c \equiv (V_o/V_i)_{cm}$ .

*Perform this step as best as you can. As  $V_o$  decreases with the potentiometer adjustment, increase the sensitivity of the DSO channel by changing the amplification ratio and obtain the very minimum possible  $V_o$ . Keep this setting of the potentiometer unchanged for the next part of the experiment.*

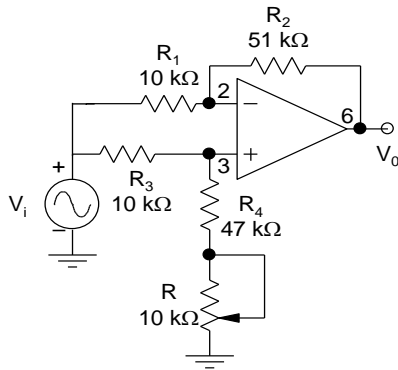


Figure E2a: Common Mode Circuit

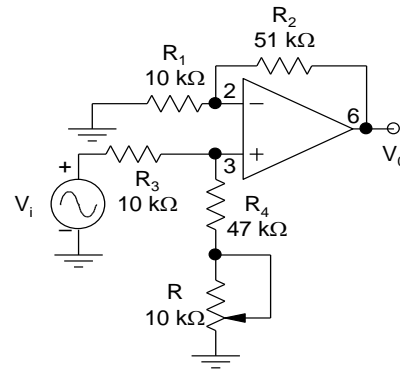


Figure E2b: Differential Mode Circuit

**B. Measurement of the Differential-Mode Gain  $A_d$** 

Wire the circuit of Fig. E2b, i.e., connect one end of  $R_1$  to ground and apply the input  $V_i$  to one end of  $R_3$ . Adjust the FG output to give  $V_i = 0.5 \sin(\omega t)$  V of 1 kHz frequency. Observe, measure and plot the output voltage  $V_o$ . Calculate the differential-mode gain  $A_d \equiv (V_o/V_i)_{dm}$  and compare it with the theoretical value.

**Experiment 3: Differentiator and Integrator OR High-Pass and Low-Pass Filters**

These circuits use op-amps (see Fig. E3a and Fig. E3b) to improve upon the less-than ideal behavior of the earlier attempted integrators and differentiators using only RC and RL circuits.

**A. Differentiator/High-Pass Filter ( $4 \times 2 = 8$  marks)**

- Wire the circuit of Fig. E3a with  $R = 1$  k $\Omega$ ,  $C = 0.1$   $\mu$ F. Apply input of 4 V p-p 1 kHz triangular wave. Observe, measure and plot both the input and output waveforms, and verify if the circuit is working as desired.
- Now, measure and plot the frequency response (both the magnitude and phase Bode plots) of the circuit for frequency range of 100 Hz to 500 kHz. Use input voltage of 4 V pp and take 100 data points for measurement.

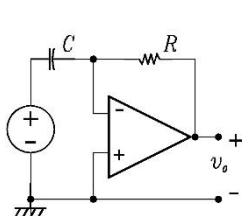


Figure E3a: Differentiator/High-Pass Filter

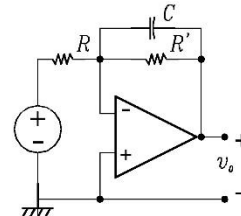


Figure E3b: Integrator/Low-Pass Filter

**B. Integrator/Low-Pass Filter ( $4 \times 2 = 8$  marks)**

- Wire the circuit of Fig. E3b with  $R = 10$  k $\Omega$ ,  $R' = 100$  k $\Omega$ ,  $C = 0.01$   $\mu$ F. Apply input of 4 V p-p 25 kHz square wave. Observe, measure and plot both the input and output waveforms, and verify if the circuit is working as desired. What is the role of the resistor  $R'$ ?
- Now, measure and plot the frequency response (both the magnitude and phase Bode plots) of the circuit for frequency range of 100 Hz to 500 kHz. Use input voltage of 4 V pp and take 100 data points for measurement.