
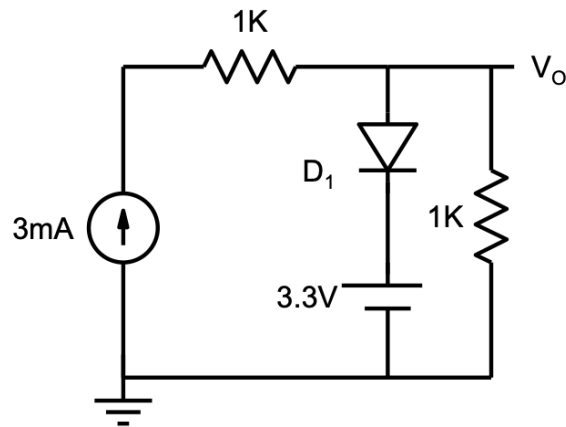


## Questions

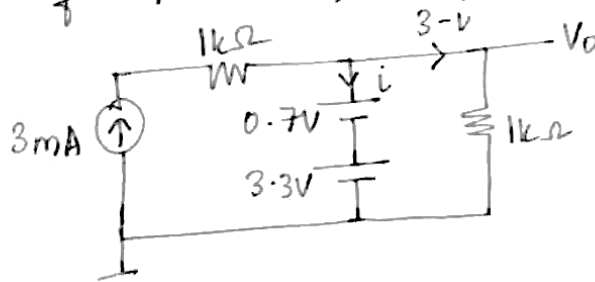1. Determine the output voltage with reference to ground for the circuits shown below assuming that cut-in voltage of the diode is  $0.7V$



Case i) If  $D_1$  is on, the circuit becomes:






apply KVL,  $4 - (3-i)1 = 0$   
 $\text{or } i = -1 \text{mA}$  which is not possible


$\therefore D_1$  is off.

Case ii)  $D_1$  is off,  $V_o = 3V$ .

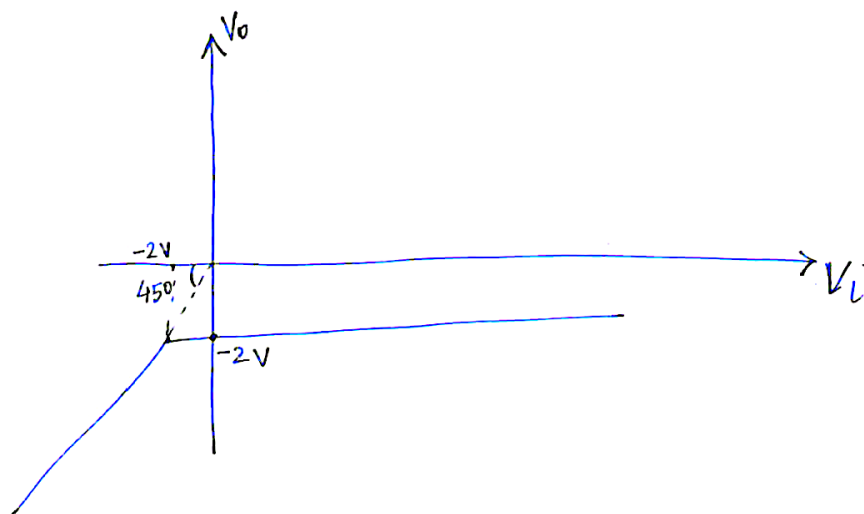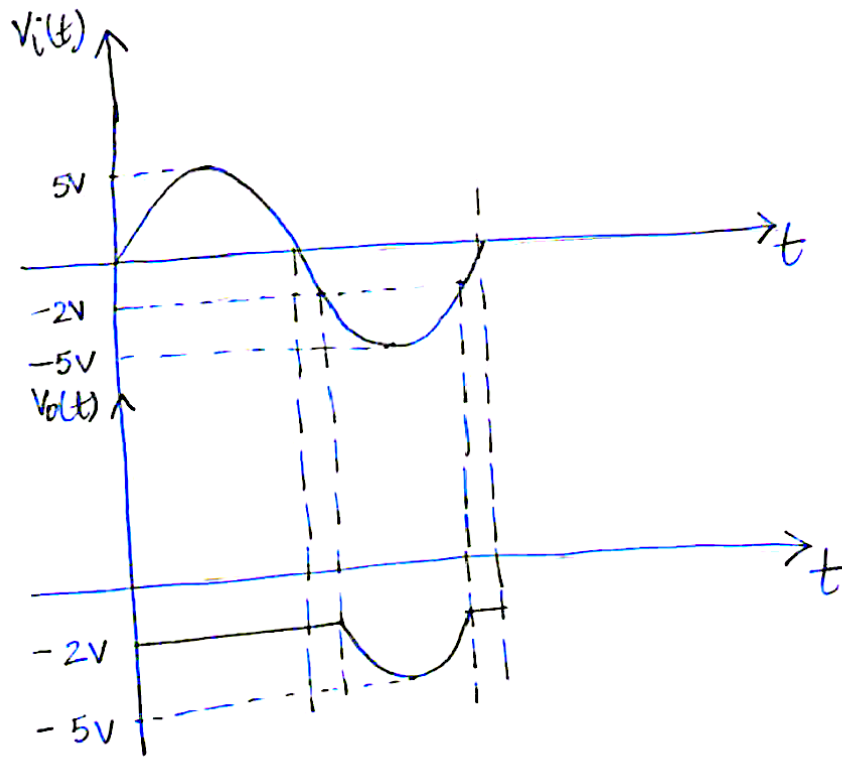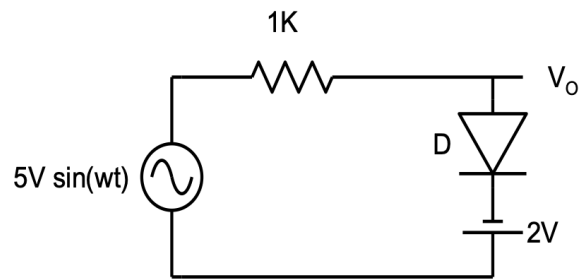2. Sketch the output voltage vs. input voltage characteristics for the circuit shown below assuming ideal diode.



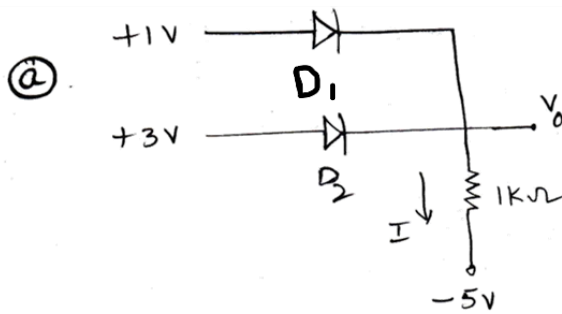
3. For circuits shown below, using ideal diodes, find the voltage ( $V_0$ ) and current ( $I$ ) indicated



case (i) :-

Assume both  $D_1$  and  $D_2$  are ON.

Then the circuit reduces to,

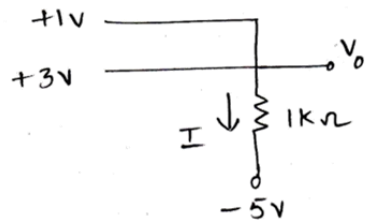


It can be seen that the case is contradicting. This implies  $D_1$  &  $D_2$  cannot be 'ON' simultaneously. Hence, the assumption is false.

case (ii) :-

Assume  $D_1$  is ON and  $D_2$  is OFF.

Then the circuit reduces to,

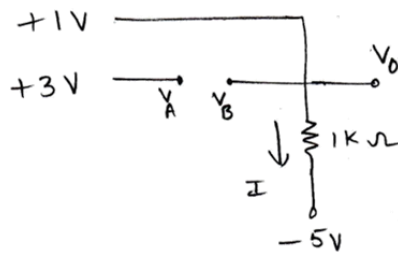


Here,  $V_0 = +1V = V_B$

But  $V_A = 3V \gg V_B \Rightarrow D_2$  must be ON.

Hence, our assumption is False.

case (iii) :-

Assume both  $D_1$  and  $D_2$  are OFF.

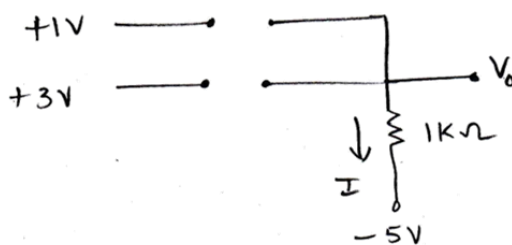


Here  $V_0 = -5V \Rightarrow$  this implies  $D_1$  and  $D_2$  must be ON [as in case (i)]. Again the assumption fails.

case (iv):-

Assume  $D_1$  is OFF and  $D_2$  is ON.

Then the circuit reduces to,

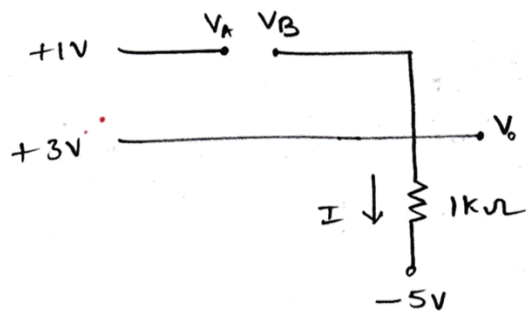

Here,  $V_O = +3V \Rightarrow$  which implies  $D_1$  is OFF  $[V_B > V_A]$


Hence the assumption is true.

$$\Rightarrow I = \frac{V_O - (-5V)}{1k\Omega} = \frac{3V - (-5V)}{1k\Omega} = 8mA$$

$\therefore$


$$\begin{array}{l} V_O = 3V \\ I = 8mA \end{array}$$

(b)

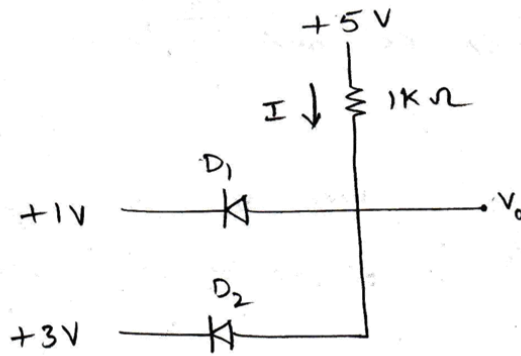

case (i):-

Assume both  $D_1$  &  $D_2$  are 'ON'

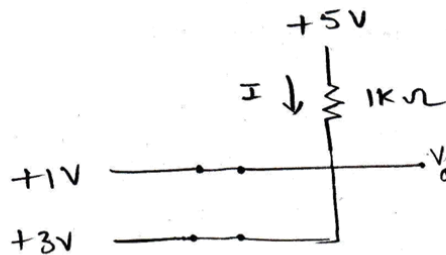


It can be seen that the case is contradicting and the two diodes cannot be 'ON' simultaneously.

Hence, the assumption is false.

case (ii):-


Assume both  $D_1$  &  $D_2$  are OFF.

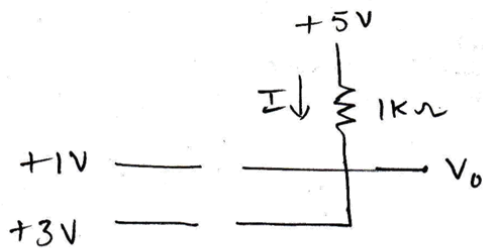

Then  $V_0 = 5V$ , which forces  $D_1$  and  $D_2$  to be forward biased; which again is a malcondition.

So, the assumption fails.

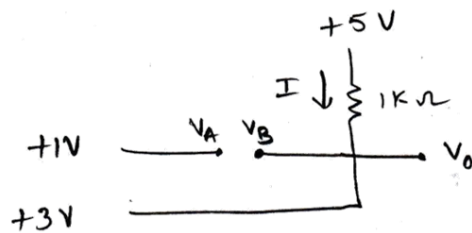
Case (iii):- Assume  $D_1$  is OFF and  $D_2$  is ON.



Here,  $V_0 = 3V$  which forces  $D_1$  to be ON.  $[V_0 > V_A]$

Hence, the assumption is incorrect.

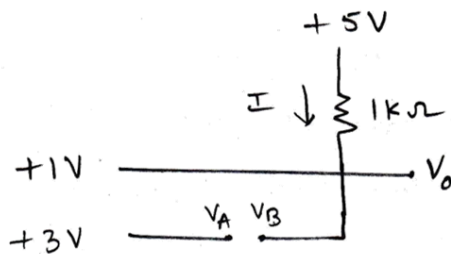Case (iv):- Assume  $D_1$  is ON and  $D_2$  is OFF



Here,  $V_0 = 1V$  which forces  $D_2$  to be OFF.  $[V_0 < V_A]$

So the assumption is correct.


Now,

$$I = \frac{5 - V_0}{1k} = \frac{5 - 1}{1k} = 4mA$$


$$\boxed{\begin{matrix} V_0 = 1V \\ I = 4mA \end{matrix}}$$

P-5

©

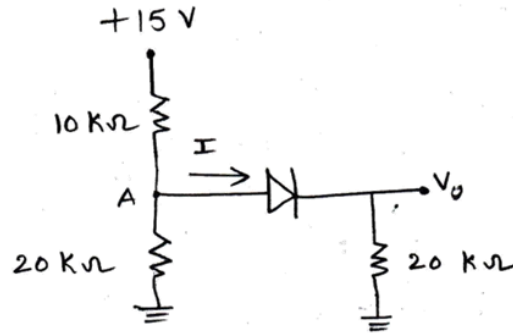

Assume the diode is OFF. Then,

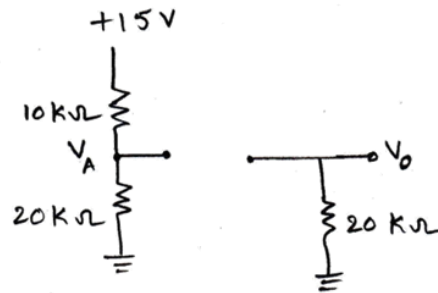


$$V_A = 15 \times \frac{20K}{20K + 10K}$$
$$= 15 \times \frac{20}{30} = 10V$$

and  $V_o = 0$

Since  $V_A > V_o \Rightarrow$  Diode is Forward Biased.

So the assumption is False.

When the diode is ON,

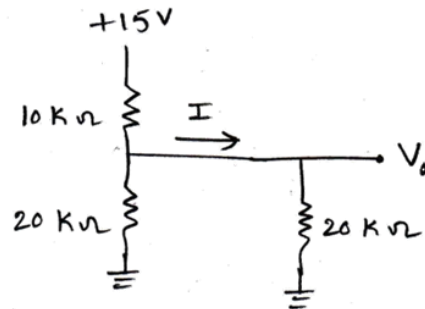


$$V_o = 15 \times \frac{(20K \parallel 20K)}{10K + (20K \parallel 20K)}$$
$$= 15 \times \frac{10K}{20K} = 7.5V$$

and,


$$I = \frac{V_o}{20K} = \frac{7.5}{20K} = 0.375mA$$

$$V_o = 7.5V$$
$$I = 0.375mA$$

(2)

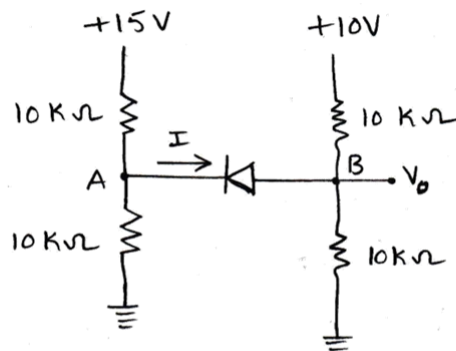

Assume that, the diode is OFF. Then,

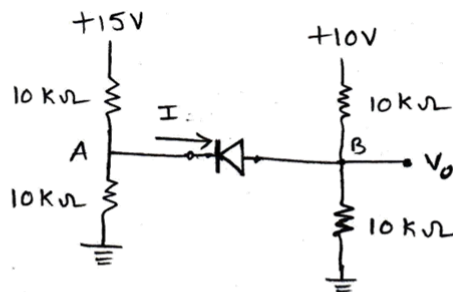

Now,

$$V_A = 15 \times \frac{10k}{10k+10k} = \frac{15}{2} = 7.5V$$

$$V_B = 10 \times \frac{10k}{10k+10k} = 10 \times \frac{1}{2} = 5V \Rightarrow V_B = 5V$$

Since  $V_A > V_B$  i.e., Diode is reverse biased i.e., OFF.

So, the assumption is correct and as the diode is reverse-biased, no current will flow through it i.e.,  $I=0$ .


$$\therefore V_o = V_B = 5V$$

$$V_o = 5V$$


$$I = 0A$$



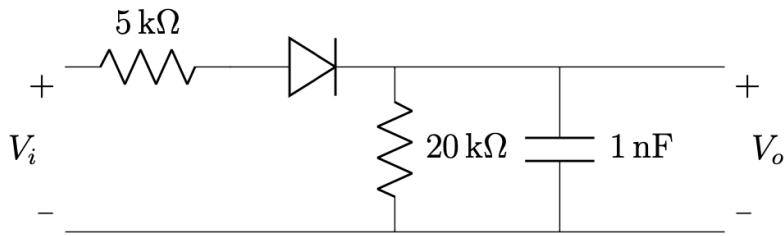
4. A rectangular pulse of 10 V amplitude and duration 4  $\mu\text{s}$  is applied as  $V_i$  at the input of circuit given. Determine and sketch  $V_o(t)$  for  $t > 0$  assuming that the diode is ideal and the initial voltage across the capacitor is zero.



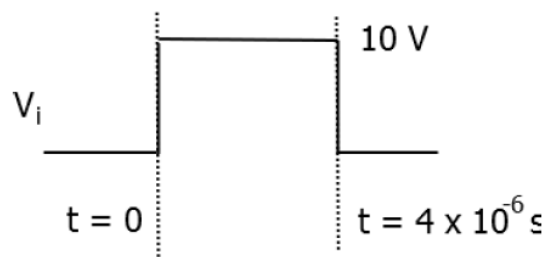
**Solution:** The pulse is shown as following.



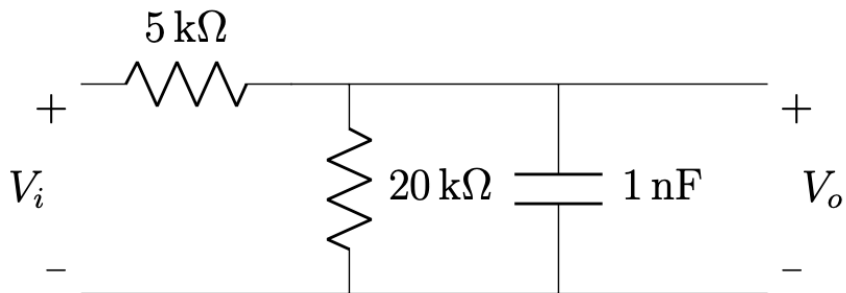For initial 4  $\mu\text{s}$ , the equivalent circuit is



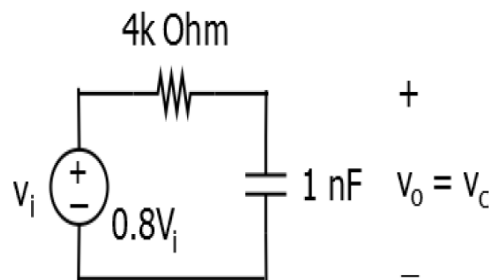Using thevenin equivalent, we can simplify it as



Hence,

$$v_o = (v_c(0) - v_c(\infty))e^{-t/\tau} + v_c(\infty)$$


Here  $v_c(0) = 0\text{ V}$ ;  $v_c(\infty) = 0.8\text{ V}_i = 8\text{ V}$  and  $\tau = RC = 4 \times 10^3 \times 10^{-9} = 4\text{ }\mu\text{s}$ .

$$v_o = 8 \left(1 - e^{-t/4 \times 10^{-6}}\right)$$

At  $t = 4\text{ }\mu\text{s}$ ,  $v_o = 8(1 - e^{-1}) = 5.05\text{ V}$

For  $t > 4\text{ }\mu\text{s}$ , the diode is reverse biased and hence off.

Hence, the equivalent circuit is

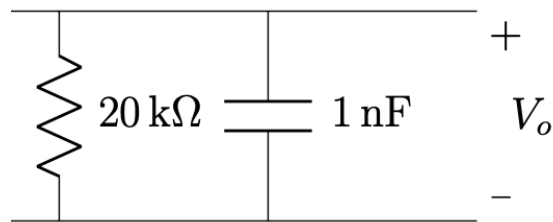


For this circuit,  $\tau' = 20 \times 10^3 \times 10^{-9} = 20\text{ }\mu\text{s}$  and  $t' = t - 4 \times 10^{-6}$


$$\begin{aligned} v_o &= 5.05 e^{-t'/\tau'} \\ &= 5.05 \exp \left[ - \left( \frac{t - 4 \times 10^{-6}}{20 \times 10^{-6}} \right) \right] \end{aligned}$$

Hence, we get
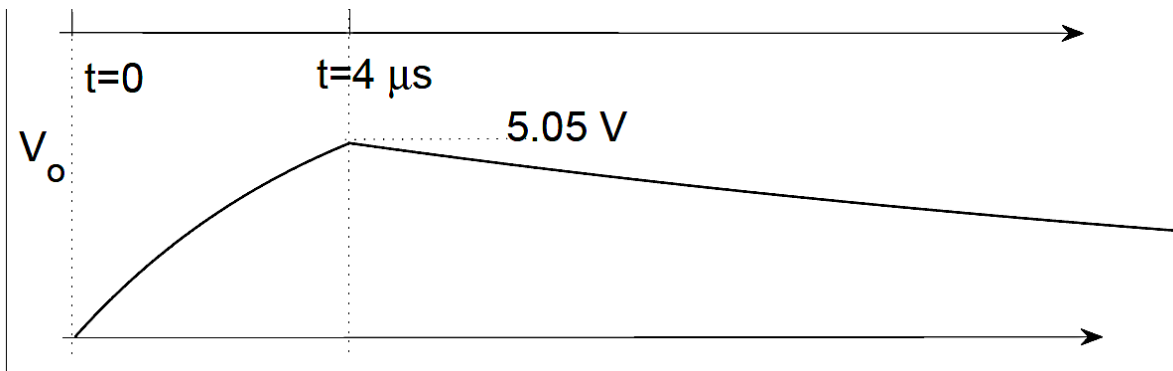
$$\begin{aligned} v_o(t) &= 8 \left(1 - e^{-t/4 \times 10^{-6}}\right) \quad \text{for } 0 \leq t \leq 4 \times 10^{-6}\text{ s} \\ &= 5.05 e^{-(t-4 \times 10^{-6})/20 \times 10^{-6}} \quad \text{for } t \geq 4 \times 10^{-6}\text{ s} \end{aligned}$$



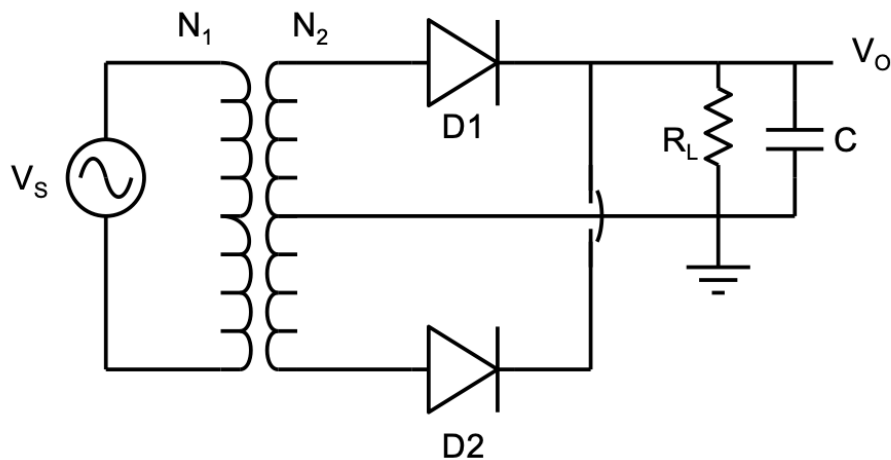5. Design the power supply circuit shown below that will supply 10V to a load of  $1000\Omega$  with ripple voltage less than 0.2V. As part of the design, determine transformer turns ratio, value of capacitance, diode peak current and peak inverse voltage. Assume that input is 220V rms with a frequency of 50Hz. Assume constant voltage-drop model (0.7 V) for diodes.



$$V_\gamma = 0.7V, V_o = 10V$$

$$\therefore V_i = V_o + V_\gamma = 10 + 0.7V = 10.7V$$

$$\frac{N_1}{N_2/2} = \frac{V_s}{V_i} = \frac{220 \times \sqrt{2}}{10.7}$$

$$\therefore \frac{N_1}{N_2} = \frac{110 \times \sqrt{2}}{10.7} = 14.53$$

$$\text{Ripple voltage, } V_r = \frac{V_M}{2fR_L C}$$

$$\text{Also, } V_r \leq 0.2V$$

$$\therefore \frac{V_M}{2fR_L C} \leq 0.2V$$

$$\Rightarrow \frac{10}{2 \times 50 \times 1000 \times C} \leq 0.2$$

$$\text{or } C \geq \frac{10}{100 \times 1000 \times 0.2} \text{ F}$$

$$\Rightarrow C \geq 0.5 \text{ mF}$$

$$R_L C = \frac{1000 \times 5}{10000} \text{ s} = 0.05 \text{ s}$$

$$\frac{T}{2} = \frac{1}{2 \times 50} \text{ s} = 0.01 \text{ s}$$

$\therefore R_L C \geq \frac{T}{2}$  is satisfied.

$$\begin{aligned} \text{Peak Inverse Voltage, PIV} &= 2V_M + V_r \\ &= 20 + 0.7 \text{ V} = 20.7 \text{ V} \end{aligned}$$

$$i_{D, \max} = \frac{V_M}{R_L} \left[ 1 + \pi \sqrt{\frac{2V_M}{V_r}} \right]$$

$$\Rightarrow i_{D, \max} = \frac{10}{1000} \left[ 1 + \pi \sqrt{\frac{2 \times 10}{0.2}} \right] \text{ A}$$

$$\Rightarrow i_{D, \max} = \frac{10}{1000} [1 + (\pi \times 10)] \text{ A}$$

$$\Rightarrow i_{D, \max} = \frac{10}{1000} (1 + 31.4) \text{ A}$$

$$\Rightarrow i_{D, \max} = 0.32 \text{ A}$$

$$i_{D, \text{avg}} = \frac{1}{2} \left( \frac{V_M}{R_L} \right)$$

$$\Rightarrow i_{D, \text{avg}} = \frac{1}{2} \times \frac{10}{1000} \text{ A}$$

$$\Rightarrow i_{D, \text{avg}} = 5 \text{ mA}$$