

Name: Shubham Sahay Roll. No.

Department of Electrical Engineering,

Indian Institute of Technology, Kanpur

ESC201

Mini-Quiz IV

18/02/2025

Total Marks: 5

Time: 10 minutes

Instructions

- Please write your name and roll number first.
- Read the question carefully and answer it in the question paper itself.



- 1) For the back-to-back connected diodes shown below, the doping concentration of the p-type Si and n-type Si are $N_A = 10^{18} \text{ cm}^{-3}$ and $N_D = 10^{16} \text{ cm}^{-3}$, respectively.

- (a) Show the direction of electric field at the two depletion regions in the figure itself.

(1 mark)

- (b) Assume the **current source model** for the diodes and find out the voltage across the diodes D1 (V_{D1}) and D2 (V_{D2}) when a square wave with an amplitude of 5 V is applied to this system. [Take $\eta = 1$, $V_F = V_\gamma = 0.7$ V and $V_T = 26$ mV] **(4 marks)**

(4 marks)

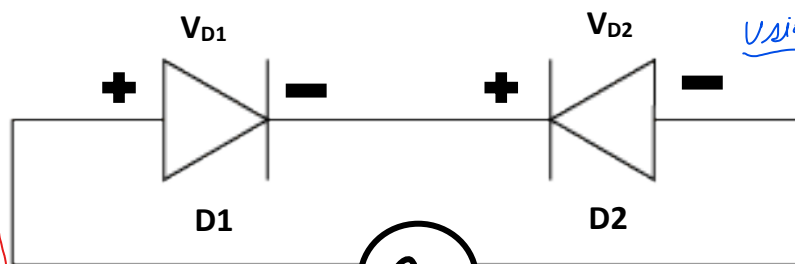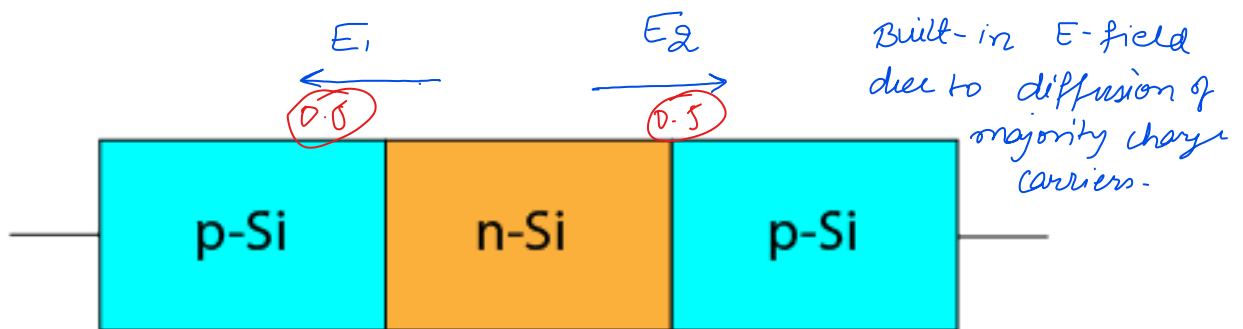

Using simplest model for diode:

$$V_{D1} = 0 \text{ (SC)}$$
$$V_{O2} = 5V(OC)$$

when $V_{\text{applied}} = 5V$

$V_{D1} = 5V, V_{D2} = 0$
when $V_{\text{applied}} = -5V$

Reference! However,

→ $I = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$

$\rightarrow I = I_S (e^{\frac{V_D}{nV_T}} - 1)$
 $\approx I_S e^{\frac{V_D}{nV_T}} \quad \forall \quad V_D \gg nV_T$
 $\approx -I_S \quad \forall \quad V_D \ll -nV_T$

this simply tells us that current **5V**
 I_S flows from n to p & not from p to n

→ Case - 2 $V_{\text{applied}} = 5V$

Case = V_{app} = -5 V
clearly; D1 will be in forward bias & D2 will be in reverse bias (as in series)

→ Since D_1 & D_2 are in series \Rightarrow
 $\Rightarrow I_{D1} = I_{D2} = I_{D2} = I_A$ why?

$$\Rightarrow e^{\frac{V_{D1}}{V_T}} - 1 = 1 \Rightarrow \ln 2 = \frac{V_{D1}}{V_T} \Rightarrow V_{D1} = V_T \ln 2$$

$V_{P2} = 5 - V_{D1} = 4.50V$
 \rightarrow why; when $V_D = -5V$; $V_D \neq V_{D2}$
 $\Rightarrow I_{D1} = I_{D2} = I_S \left[e^{\frac{V_{D2}}{V_T}} \right]$

Note the difference! However,

if someone used this model or similar, only deduct 1.5 marks

$V_{\text{drop across } R_2} = -V_{O2}$ if they have identified everything else correctly

$$V_d \text{ drops across diode} = -4.3 \times 10^3 \text{ V}$$

$= -I_3 = I_8$
asly F.R. voltage is not large!
2 D_1 in R.B & D_2 in F.B.
1.99V 0.5

$v_{01} = -4.55$
0.5'