

ESC201: INTRODUCTION TO ELECTRONICS


MODULE 3: FREQUENCY DOMAIN ANALYSIS



Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur

Recap

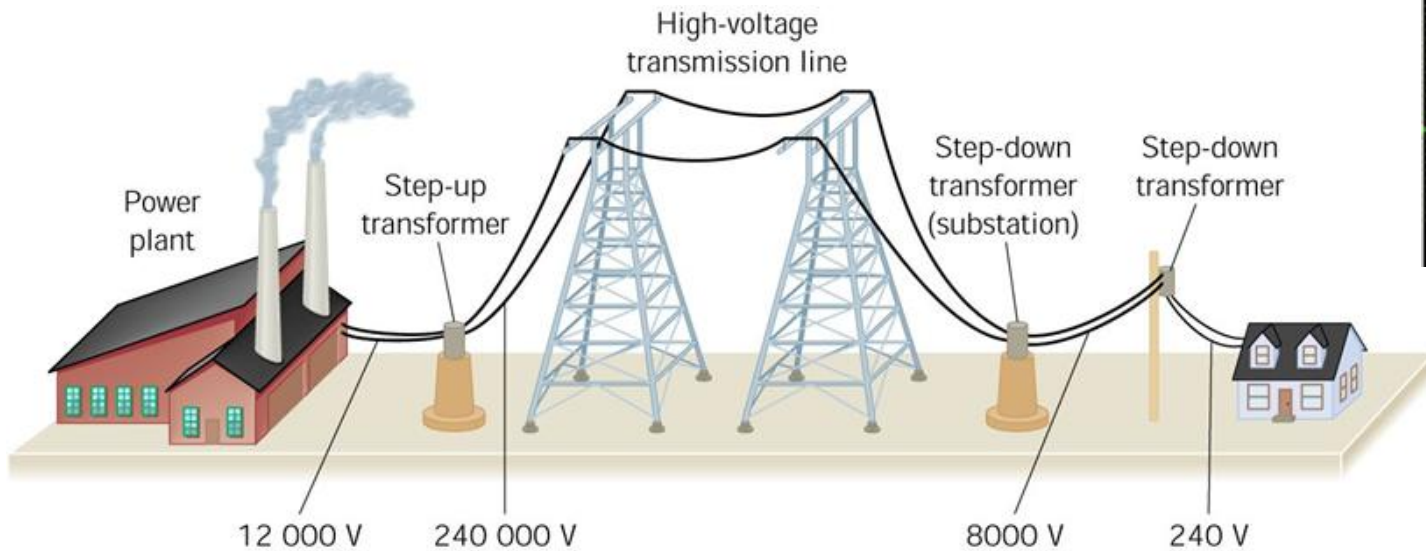- Negative Capacitance: converting MSE problem to electronics domain
- Series and Parallel RLC circuits: Nightmare to solve them.




War of currents: AC vs DC



Tell Westinghouse to stick to air brakes. He knows all about them.

-Thomas Edison

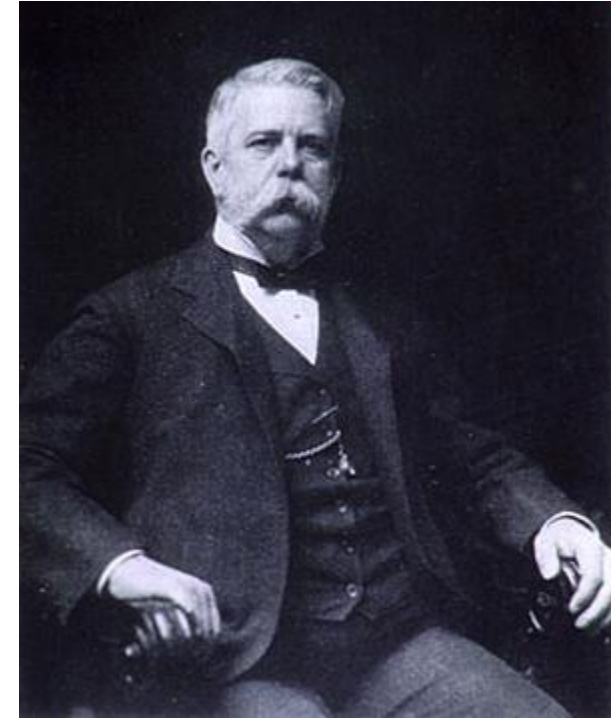

George Westinghouse
formed an alliance with
Nikola Tesla


Fourier Analysis

$$A \sin\left(\frac{N\pi t}{T}\right) \rightarrow \frac{1}{N} \sin\left(\frac{N\pi t}{T}\right)$$

Sinusoids have following interesting property



- Derivative is a sinusoid
- Integral is a sinusoid

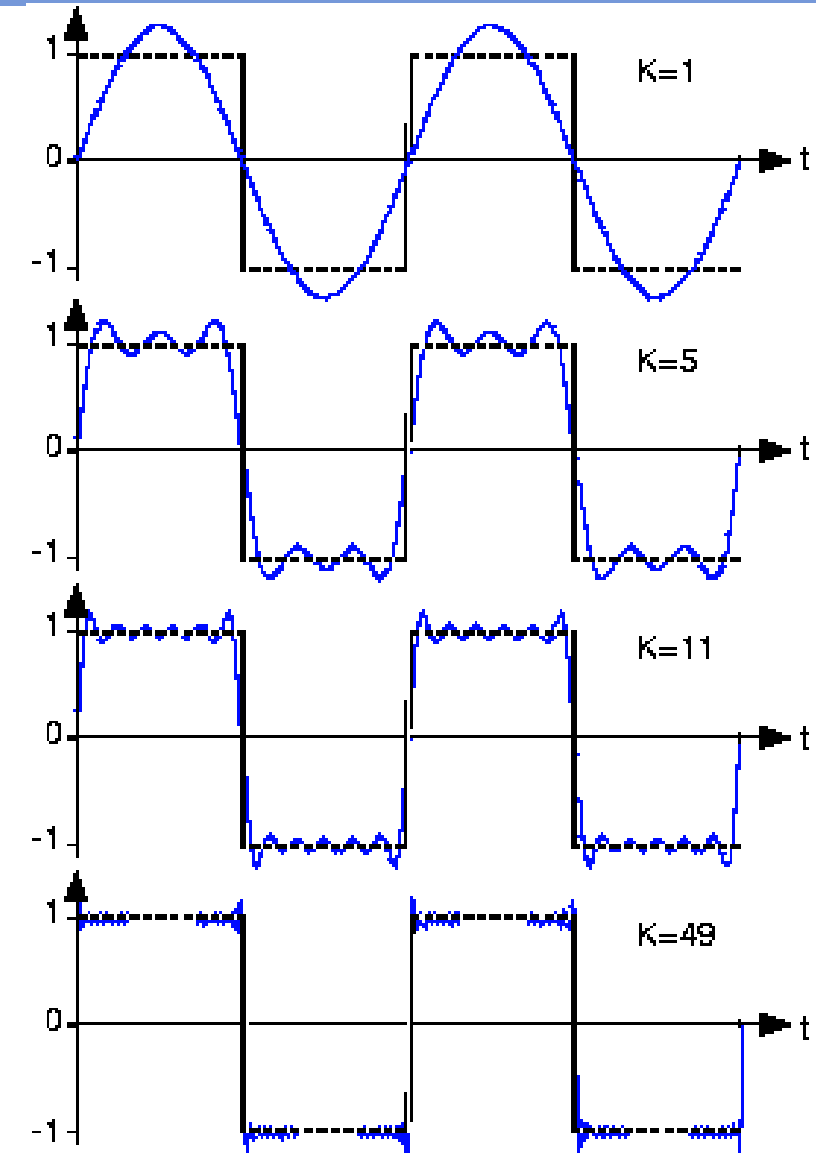Output is sinusoidal signal with same frequency!



Transient & forced response

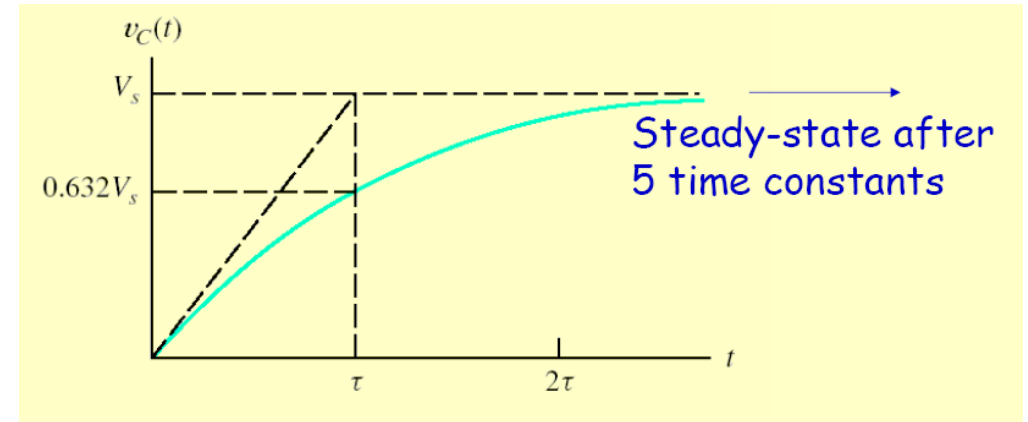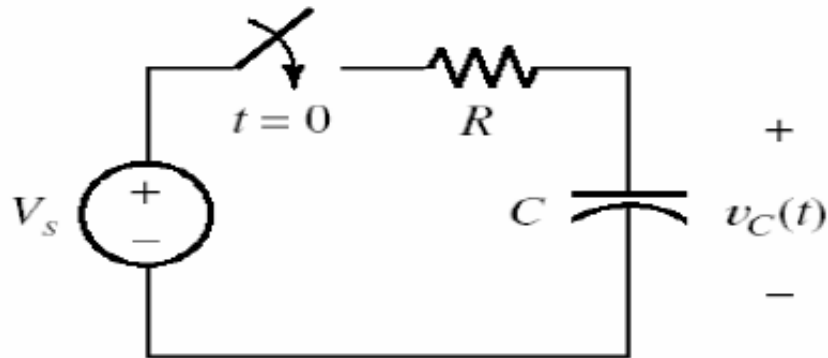- Split solution into two components:
 - Transient (time-dependent component)
 - Forced (steady-state)



$$v_C(t) = V_s - V_s e^{-t/\tau}$$



Steady-state or forced response

Transient response

Sinusoidal steady state

Sinusoidal Steady-State

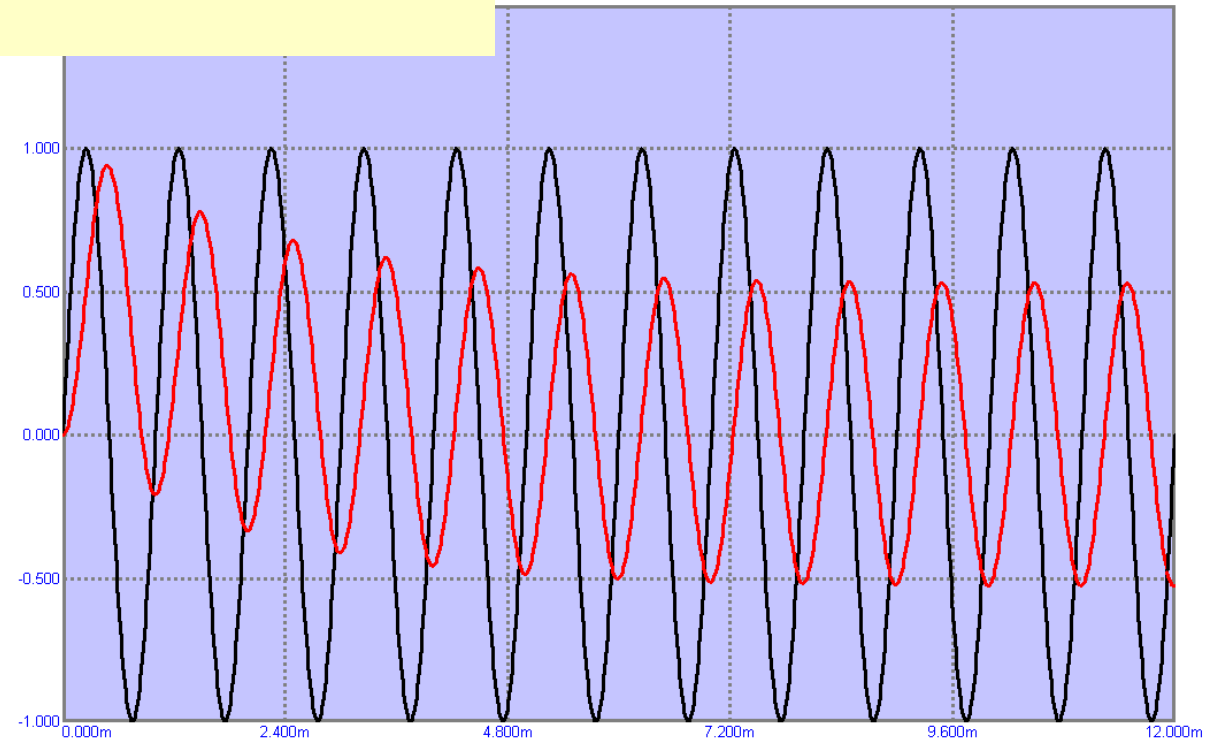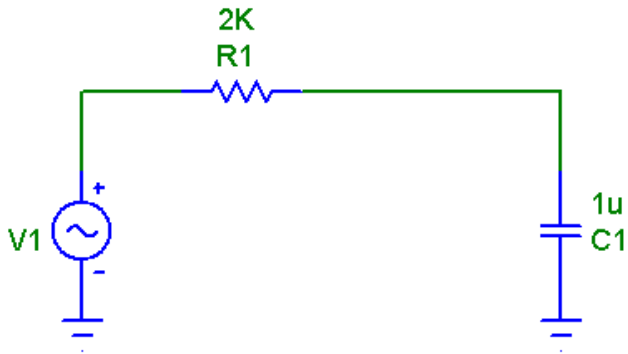- Whenever the forced input to the circuit is sinusoidal the response will be sinusoidal
- If the input persists, the response will persist and we call it steady-state response




Preliminaries: Representation of Sinusoidal Signals

Canonical Form


$$v(t) = V_m \cos(\omega t + \theta)$$

peak
value


phase

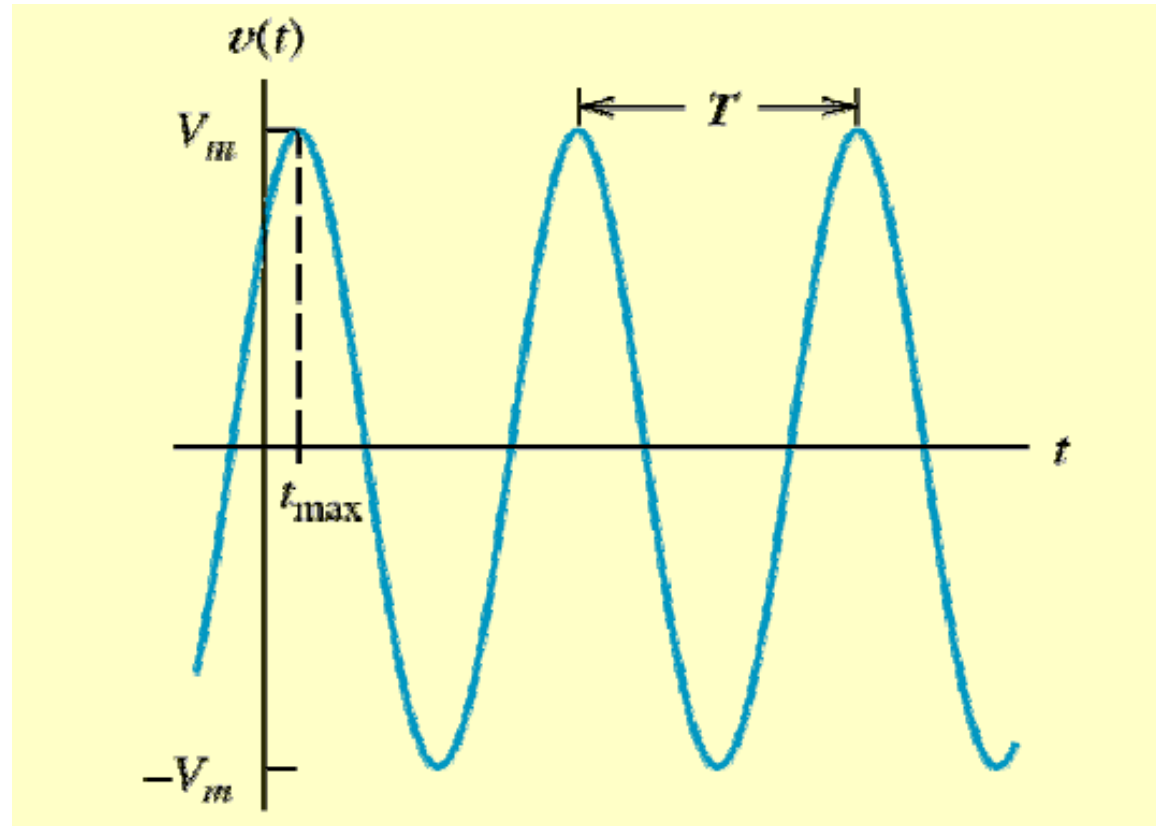

Representation of Sinusoidal Signals

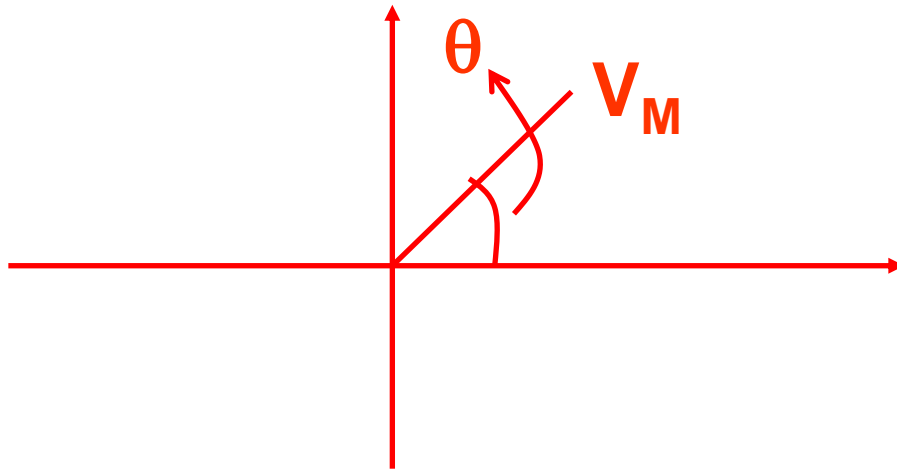

$$v(t) = V_m \cos(\omega t + \theta)$$

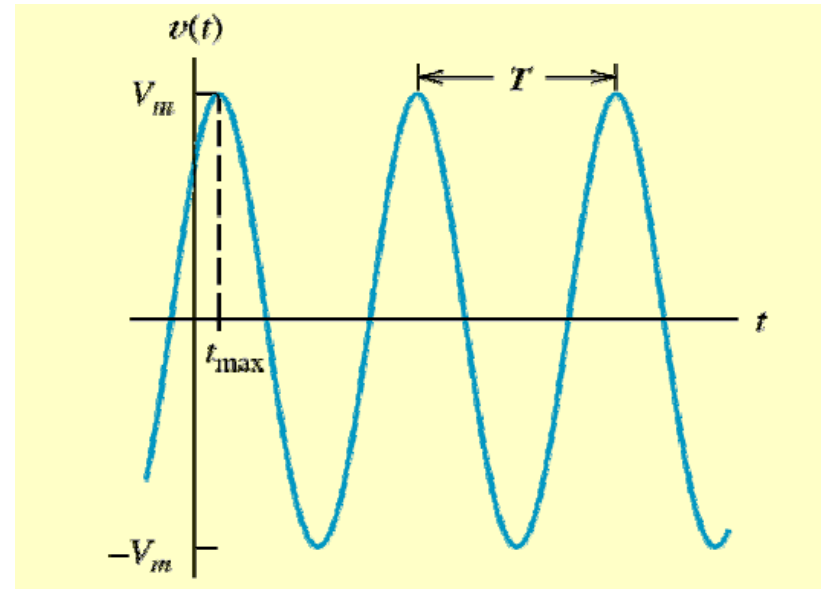

ω is the **angular frequency** in radians per second

T is the **period**, where $f = \frac{1}{T}$ is the **frequency**

$$\omega = \frac{2\pi}{T}$$

$$\omega = 2\pi f$$

θ is the **phase angle**

Representation of Sinusoidal Signals...

$$5 \sin(4\pi t - 60^\circ)$$

$$= 5 \cos(4\pi t - 60^\circ - 90^\circ)$$

Amplitude = 5 ;
Phase = -150°

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\sin(z) = \cos(z - 90^\circ)$$

Phase in radians: $360^\circ = 2\pi$ $\theta = \frac{-150}{360} \times 2\pi = -2.618$ radians

$$\omega = 4\pi \text{ rad/s}$$

$$\omega = \frac{2\pi}{T} = 4\pi \Rightarrow T = 0.5s$$

$$f = \frac{1}{T} = 2\text{Hz}$$

Preliminaries:

Find the phase difference between the two currents

$$i_1 = 4 \sin(377t + 25^\circ)$$

Canonical Form $x(t) = x_m \cos(\omega t + \theta)$

$$i_2 = -5 \cos(377t - 40^\circ)$$

$$i_1 = 4 \cos(377t + 25^\circ - 90^\circ)$$

$$\theta_1 = -65^\circ$$

$$\theta_1 - \theta_2 = -205^\circ$$

$$i_2 = 5 \cos(377t - 40^\circ + 180^\circ)$$

$$\theta_2 = 140^\circ$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$


$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Phase relationship

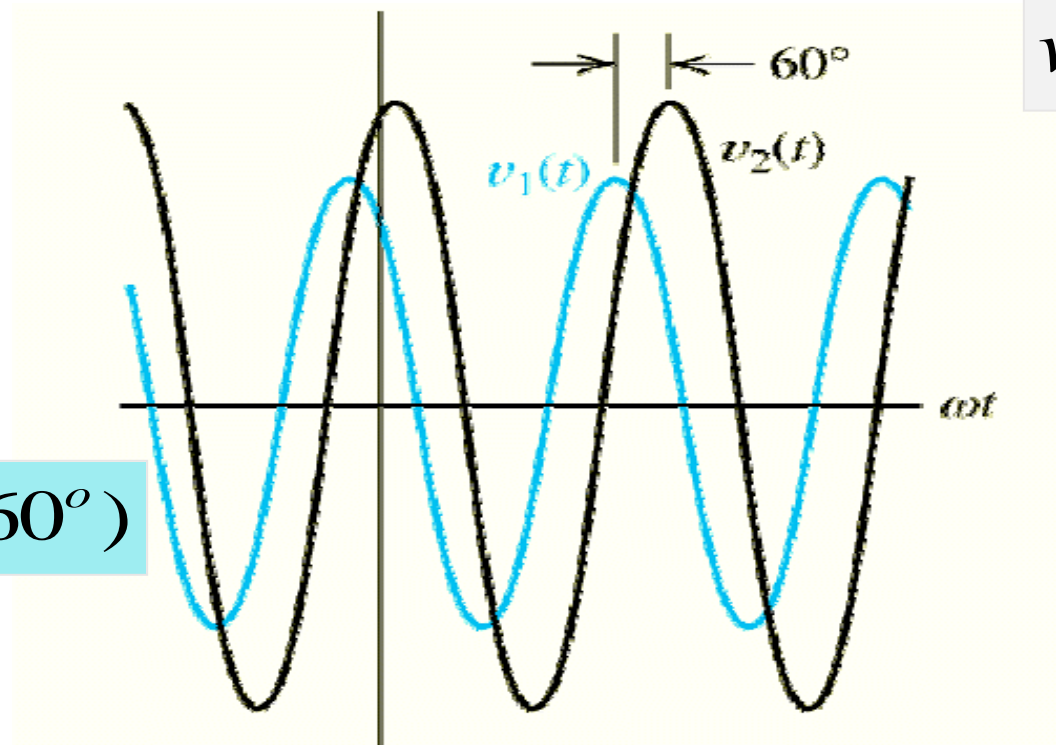
$$v_1(t) = v_{1m} \cos(\omega t + 60^\circ)$$



$$v_2(t) = v_{2m} \cos(\omega t)$$

The peaks of $v_1(t)$ occur 60° before the peaks of $v_2(t)$.

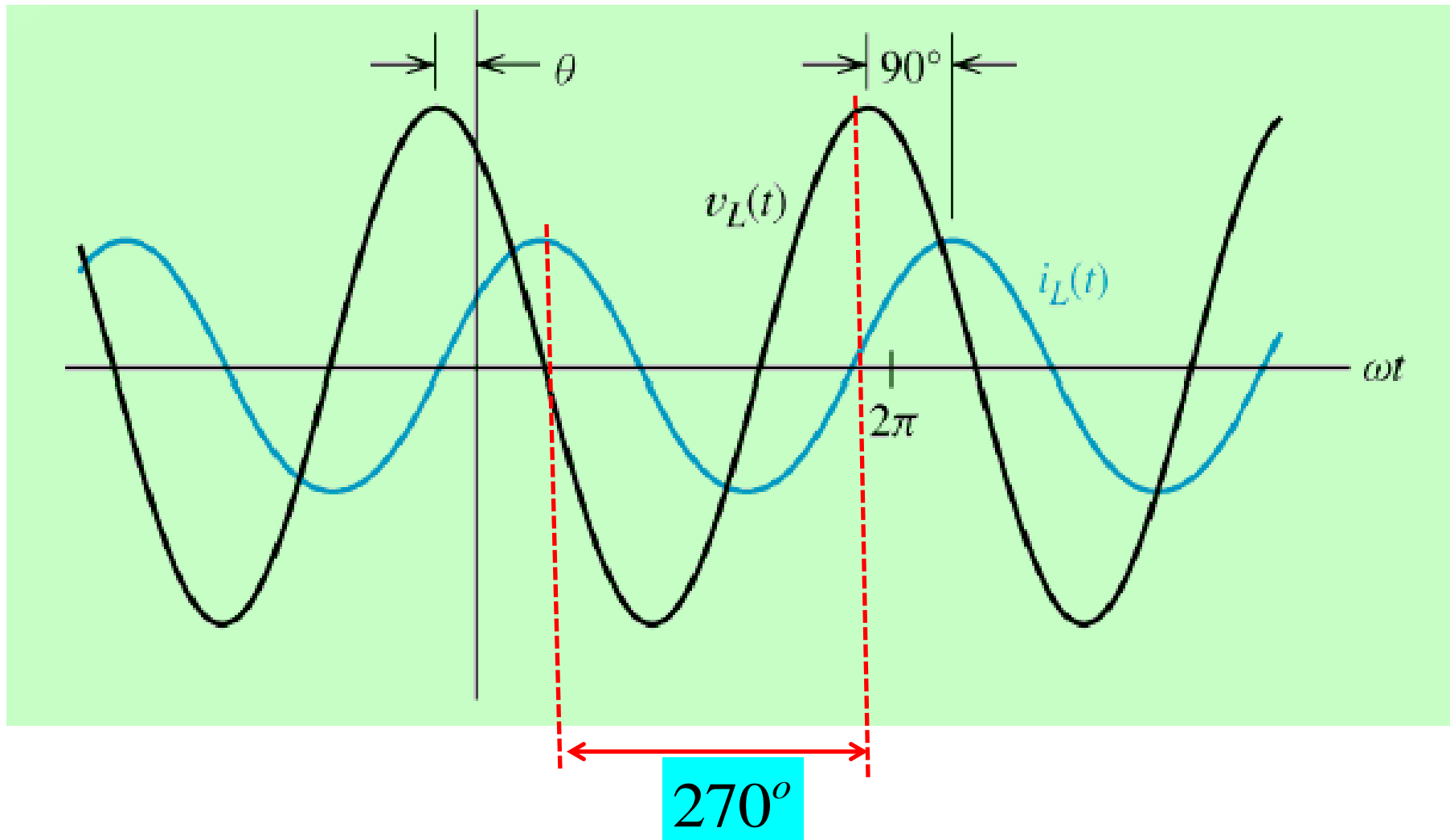In other words, $v_1(t)$ leads $v_2(t)$ by 60° .



Voltage leads current by 90° or lags current by 270° ?

Phase difference is usually considered between -180 to 180°

Add or subtract 360° to bring the phase between -180 to 180°

$$i_1 = 4 \cos(377t - 65^\circ)$$

$$i_2 = 5 \cos(377t + 140^\circ)$$

Does i_2 lead i_1 ?

$$\theta_1 - \theta_2 = -205^\circ$$



$$\theta_1 - \theta_2 = -205^\circ + 360^\circ = 155^\circ$$

i_1 leads i_2 by 155°

Circuit Analysis under Sinusoidal Signals

Given


$$v(t) = V_0 \cos(200t + 45^\circ)$$

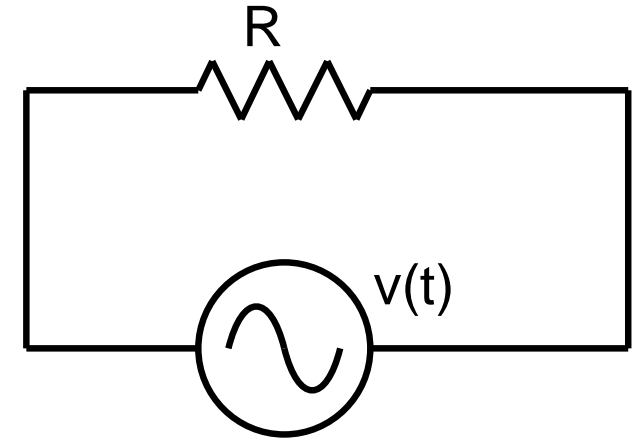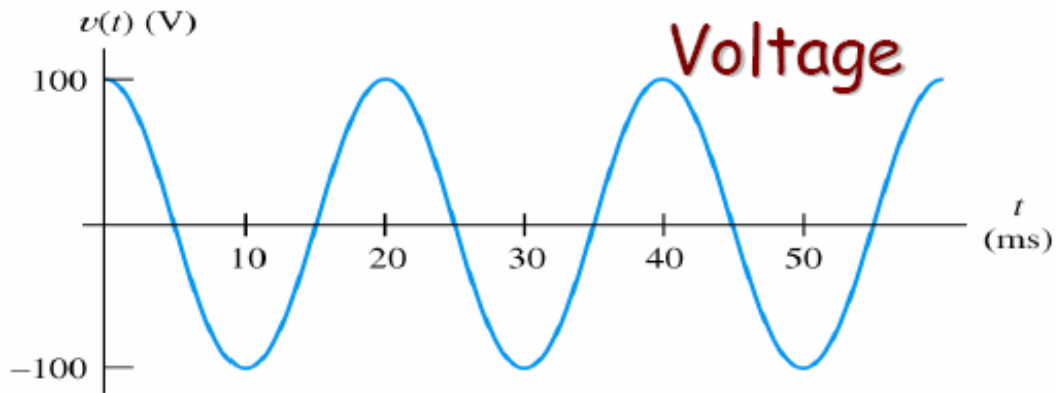

Compute current in R



$$i(t) = \frac{v(t)}{R} = \frac{V_0}{R} \cos(200t + 45^\circ)$$

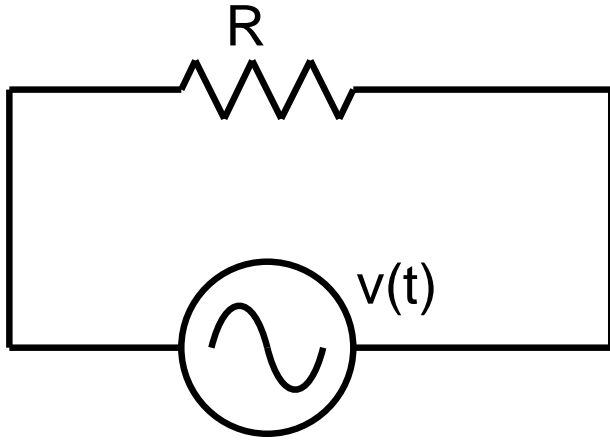Power dissipation with sinusoidal Voltage



$$p = v(t)i(t) = \frac{v(t)^2}{R}$$

$$p(t) = 200 \cos^2 100\pi t \text{ W}$$

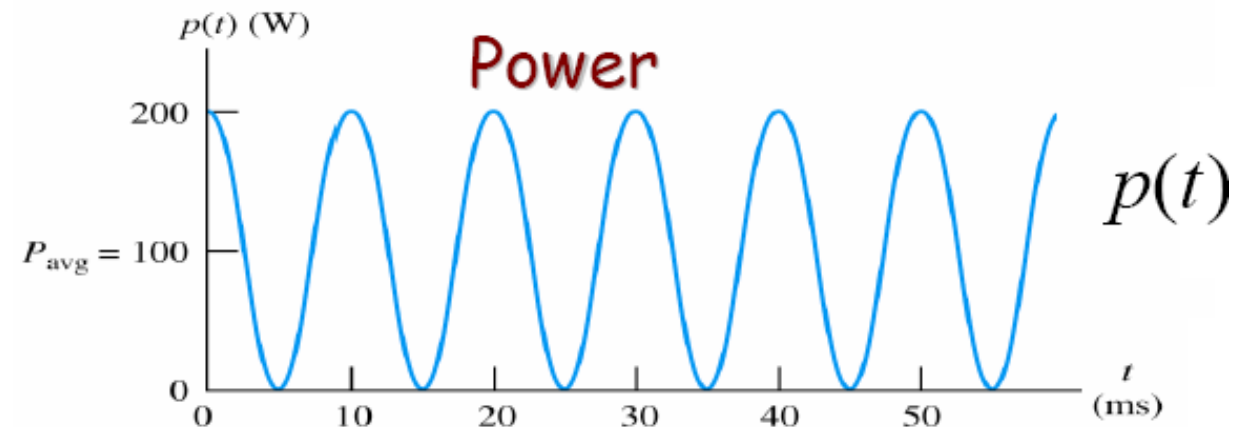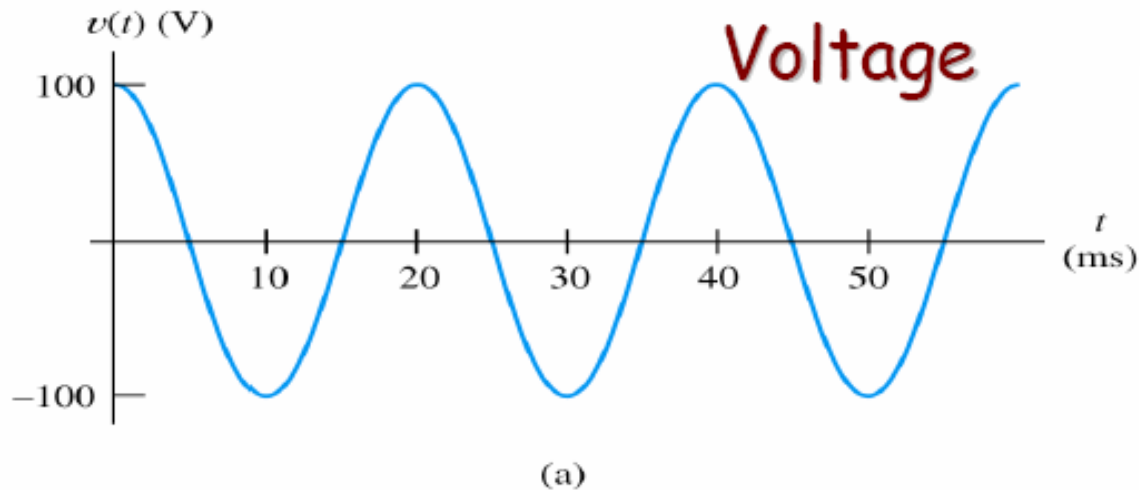

Average Power


X: $x_1, x_2, x_3, \dots \dots \dots x_N$

$$x_{avg} = \frac{1}{N} \sum x_i$$

If X is continuous, its average over a time t_1

$$x_{avg} = \frac{1}{t_1} \int_0^{t_1} x(t) dt$$

For periodic signals

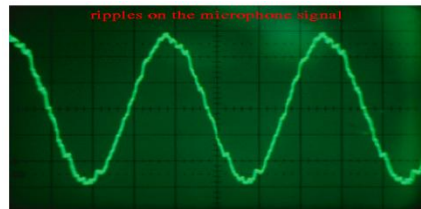

$$x_{avg} = \frac{1}{T} \int_0^T x(t) dt$$

Average Power

$$x_{avg} = \frac{1}{T} \int_0^T x(t) dt$$

$$p(t) = \frac{v(t)^2}{R}$$

$$p_{avg} = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt$$

$$p_{avg} = \frac{\frac{1}{T} \int_0^T v(t)^2 dt}{R}$$

$$p_{avg} = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} \right]^2}{R}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$p_{avg} = \frac{V_{rms}^2}{R}$$

This is true for any periodic waveform

RMS voltage and current

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$v(t) = V_m \cos(\omega t + \theta)$$


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\int_0^T \cos^2(\omega t + \theta) dt = \int_0^T \frac{1 + \cos(2\omega t + 2\theta)}{2} dt$$

$$= \frac{T}{2} + \frac{1}{4\omega} \sin(2\omega t + 2\theta) \Big|_0^T = \frac{T}{2}$$

The **RMS** value for a sinusoid is the peak value divided by the square root of 2

Power dissipation simplified

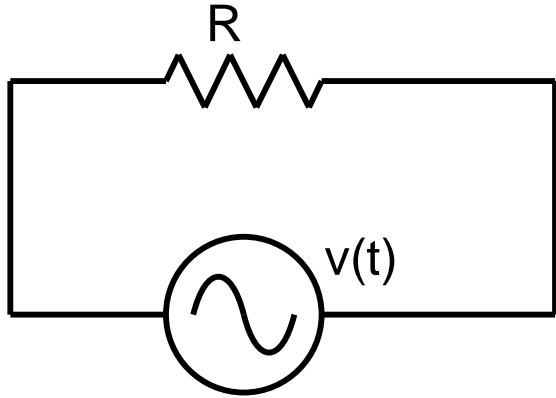

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \theta)$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P_{avg} = \frac{V_m^2}{2R}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = \frac{1}{2} I_m^2 R$$


Circuit Analysis under Sinusoidal Signals

Given

$$v(t) = 2 \cos(200t + 45)$$

$$v_R(t) = 1.85 \cos(200t + 23.2)$$



Compute $v_L(t)$

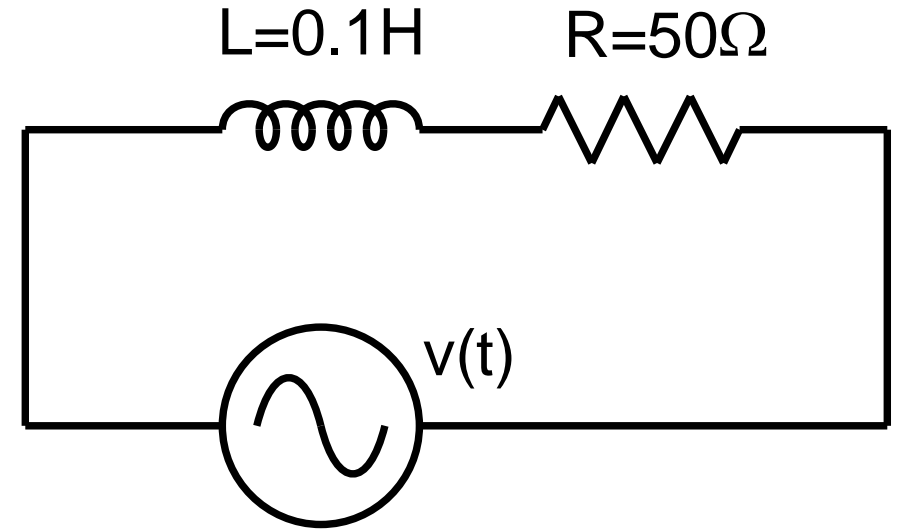


$$\begin{aligned} v_L(t) &= v(t) - v_R(t) \\ &= 2 \cos(200t + 45) - 1.85 \cos(200t + 23.2) \end{aligned}$$

Solving such circuits requires us to add/subtract sinusoids !

Representation of Sinusoidal Signals

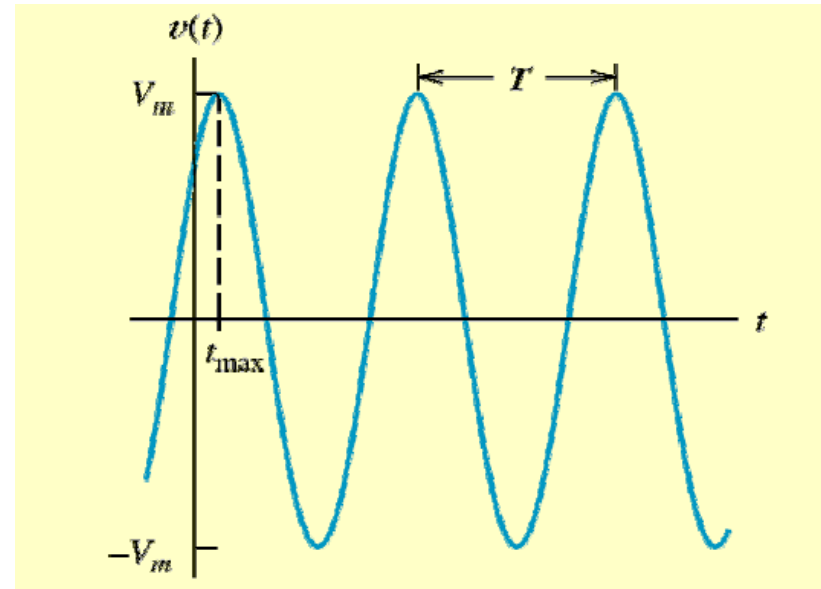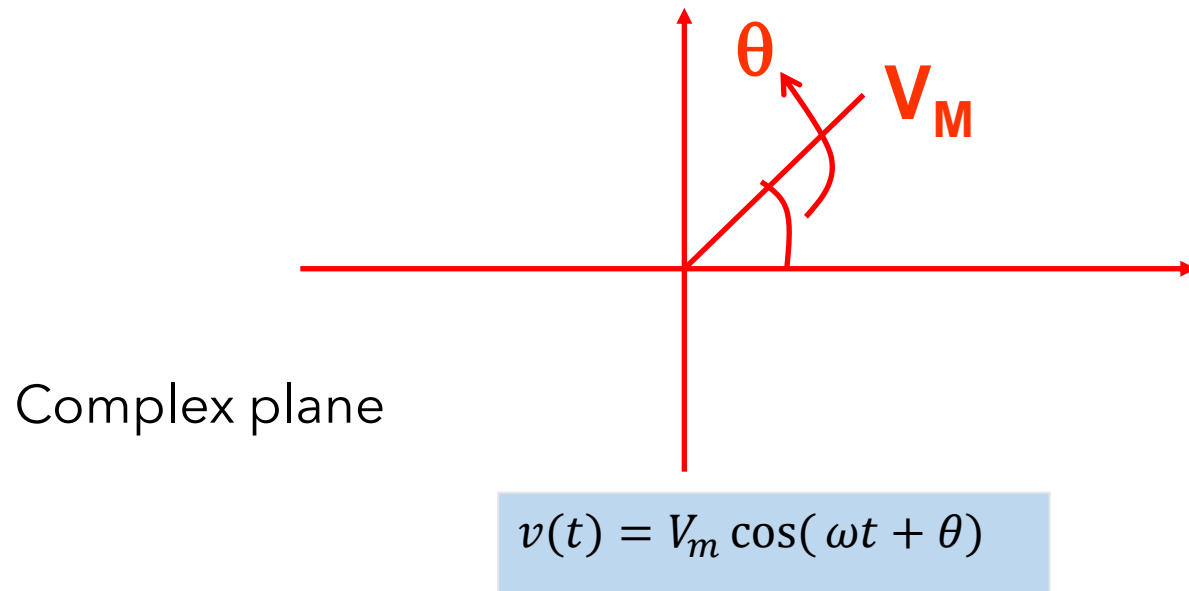

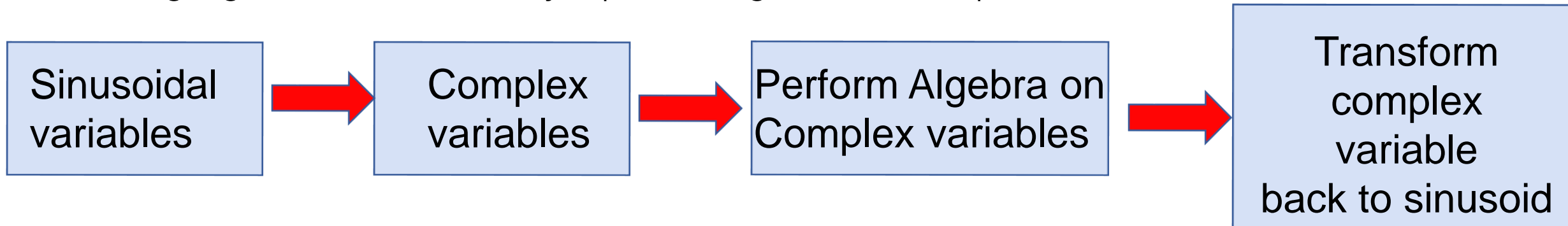Performing algebra on sinusoids by representing them as complex numbers




Complex Numbers

$$z = x + jy$$

Real part \nearrow \nwarrow Imaginary part


$\sqrt{-1}$

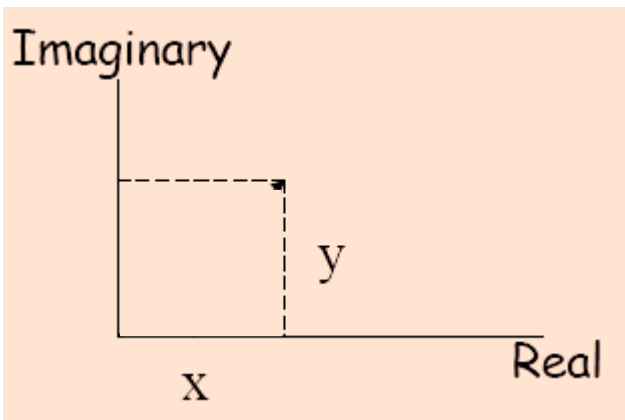- Complex number can be represented as a point in the complex plane (2D)




$$z = a\angle\theta$$

- Polar representation

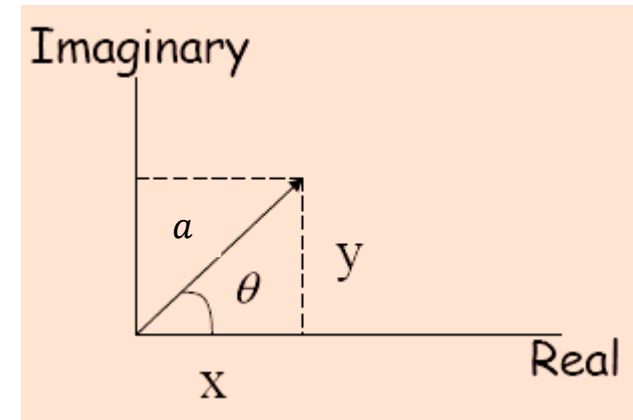


Complex Numbers

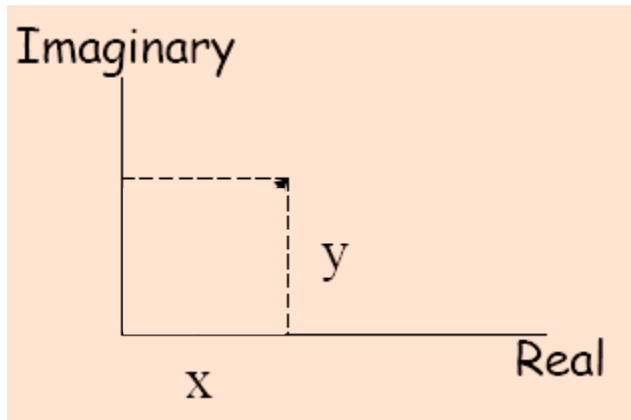

$$z = x + jy$$

$$x = a \cos \theta$$

$$y = a \sin \theta$$

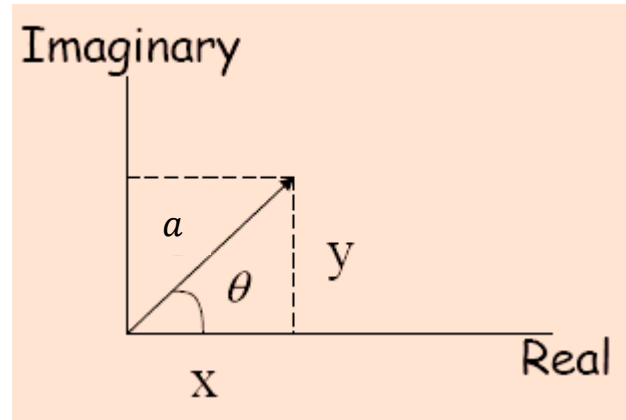

$$z = a \angle \theta$$

$$z = x + jy$$

$$z = a \cos \theta + ja \sin \theta$$

$$z = a(\cos \theta + j \sin \theta) = ae^{j\theta}$$

absolute value

$$|z| = a$$

$$|z| = \sqrt{x^2 + y^2}$$

phase/angle

$$\text{Angle}(z) = \theta$$

$$\tan \theta = \frac{y}{x}$$

Euler Identity

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{j\theta} = 1 \angle \theta$$

$$z = a \angle \theta = ae^{j\theta} = a(\cos \theta + j \sin \theta)$$

Examples

$$z_1 = 5 \angle 30^\circ$$

$$\begin{aligned} z_1 &= 5 \cos(30^\circ) + j5 \sin(30^\circ) \\ &= 4.33 + j2.5 = x + jy \end{aligned}$$

$$z_2 = 10 + j5$$

$$\begin{aligned} z_2 &= \sqrt{(10)^2 + (5)^2} \angle \tan^{-1}\left(\frac{5}{10}\right) \\ &= 11.18 \angle 26.57^\circ \end{aligned}$$

$$1 \angle 90^\circ = \cos 90 + j \sin 90 = j$$

$$z_3 = -10 + j5$$

$$z_3 = \sqrt{(10)^2 + (5)^2} \angle 153.43^\circ$$

Complex Numbers

$$z_1 = 5 + j5 \quad z_2 = 3 - j4$$

$$z_1 + z_2 = (5 + j5) + (3 - j4) = 8 + j1$$

$$z_1 - z_2 = (5 + j5) - (3 - j4) = 2 + j9$$

To **add** or **subtract** two complex numbers, convert them first into rectangular form and then perform the operations

Complex Numbers Multiplication/Division

$$z_1 = 5 + j5 \quad z_2 = 3 - j4$$

$$\begin{aligned} z_1 z_2 &= (5 + j5)(3 - j4) \\ &= 15 - j20 + j15 - j^2 20 \\ &= 15 - j20 + j15 + 20 \\ &= 35 - j5 \end{aligned}$$

Complex conjugate of z is:

$$z^* = x - jy$$

$$\begin{aligned} \frac{z_1}{z_2} &= \frac{5 + j5}{3 - j4} \times \frac{z_2^*}{z_2^*} \\ &= \frac{5 + j5}{3 - j4} \times \frac{3 + j4}{3 + j4} \\ &= \frac{15 + j20 + j15 + j^2 20}{9 + j12 - j12 - j^2 16} \\ &= \frac{15 + j20 + j15 - 20}{9 + j12 - j12 + 16} \\ &= \frac{-5 + j35}{25} \\ &= -\frac{5}{25} + j\frac{35}{25} \\ &= 0.2 + j1.4 \end{aligned}$$

Complex Numbers Multiplication/Division

$$\begin{aligned} z_1 z_2 &= |z_1| e^{j\theta_1} \times |z_2| e^{j\theta_2} \\ &= |z_1| |z_2| e^{j(\theta_1 + \theta_2)} \end{aligned}$$


$$\begin{aligned} \frac{z_1}{z_2} &= \frac{|z_1| e^{j\theta_1}}{|z_2| e^{j\theta_2}} \\ &= \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)} \end{aligned}$$

$$\begin{aligned} z_1 z_2 &= |z_1| \angle \theta_1 \times |z_2| \angle \theta_2 \\ &= |z_1| |z_2| \angle (\theta_1 + \theta_2) \end{aligned}$$

$$\begin{aligned} \frac{z_1}{z_2} &= \frac{|z_1| \angle \theta_1}{|z_2| \angle \theta_2} \\ &= \frac{|z_1|}{|z_2|} \angle (\theta_1 - \theta_2) \end{aligned}$$

To multiply and divide complex numbers, it is easier to use polar coordinates

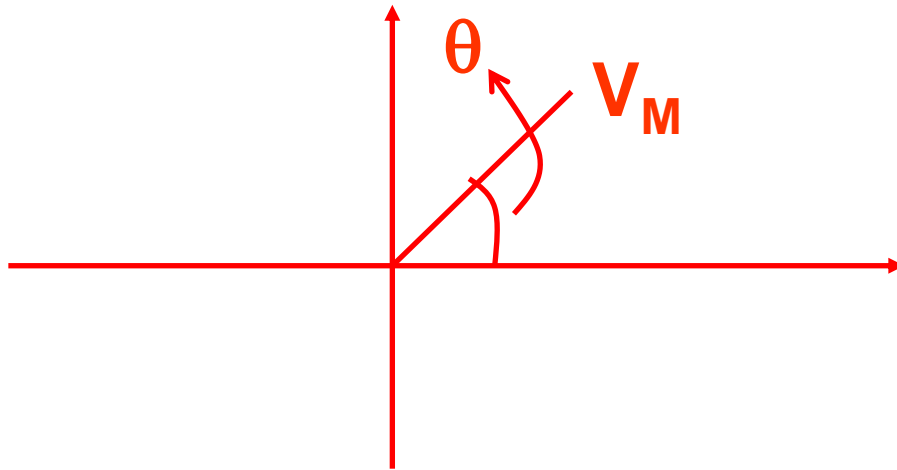Representation of Sinusoidal Signals: Phasors




Complex plane

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\rightarrow V_m \angle \theta = V_m e^{j\theta}$$




$$V_m \angle \omega t + \theta$$

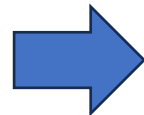

$$\text{Re}(V_m \angle \omega t + \theta)$$



$$V_m \cos(\omega t + \theta)$$

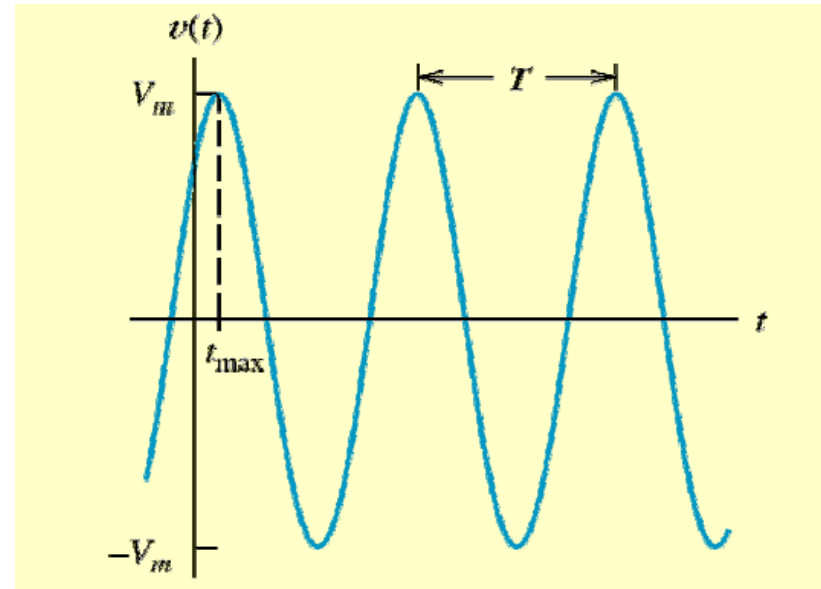

Example

$$v_1(t) = 20 \cos(200t - 45^\circ)$$

$$v_2(t) = 10 \cos(200t + 60^\circ)$$

$$20 \cos(\omega t - 45^\circ) \longrightarrow \mathbf{V}_1 = 20 \angle -45^\circ$$

$$14.14 - j14.14$$

$$10 \sin(\omega t + 60^\circ) \longrightarrow \mathbf{V}_2 = 10 \angle -30^\circ$$

$$8.660 - j5$$

$$\mathbf{V}_s = \mathbf{V}_1 + \mathbf{V}_2$$

$$= 20 \angle -45^\circ + 10 \angle -30^\circ$$

$$= 14.14 - j14.14 + 8.660 - j5$$

$$= 23.06 - j19.14$$

$$= 29.97 \angle -39.7^\circ$$

$$v_s(t) = 29.97 \cos(\omega t - 39.7^\circ)$$

Impedance Model

- Let us try to understand the “complex world” in time domain only

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\text{Re}(V_m \angle \omega t + \theta)$$


- Actual signal is the real part of the phasor.
- Complex signals will represent actual signal via their real part
- If ωt is not written then

$$v(t) = V_m \cos(\omega t + \theta)$$

$$V_m \angle \theta$$

- shows the frequency coefficient

Impedance Model (R)

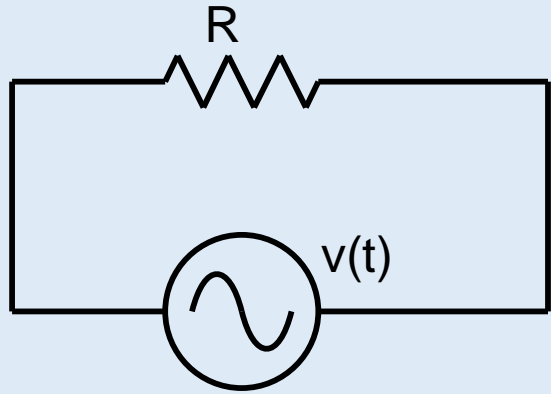

$$v(t) = V_M \cos(\omega t + \theta)$$

- Fix the input sinusoid frequency & consider steady state
- All currents & voltages are sinusoids at the same frequency


$$v_R(t) = V_M \cos(\omega t + \theta)$$

$$i_R(t) = \frac{V_M}{R} \cos(\omega t + \theta)$$


$$V_R = V_M \angle \theta$$

$$I_R = \frac{V_M}{R} \angle \theta$$

$$I_R = \frac{V_R}{R}$$

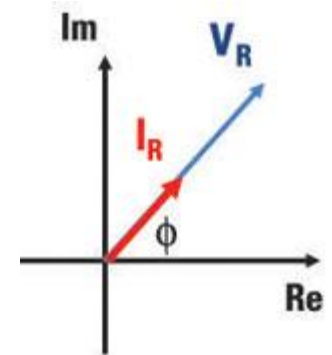

Impedance Model (C)

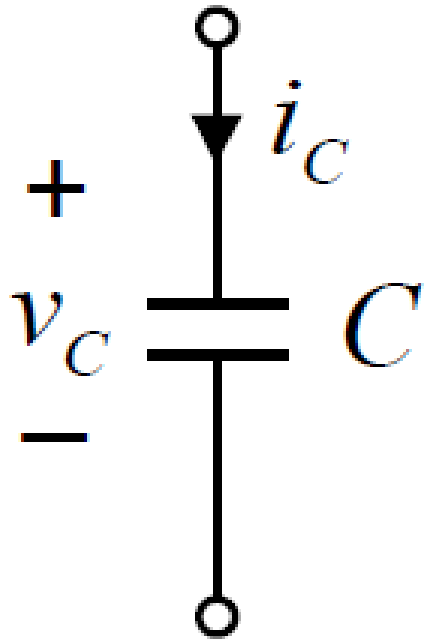

$$v_C(t) = V_M \cos(\omega t + \theta)$$

$$V_C = V_M \angle \theta$$

In a capacitor, current leads voltage by 90°

Generalized Ohm's Law for Capacitors in terms of Phasors

Dr. Shubham Sahay ESC201

$$i_C(t) = C \frac{dv_C}{dt}$$

$$i_C(t) = \omega C V_M \cos(\omega t + \theta + 90^\circ)$$


$$I_C = \omega C V_M \angle \theta + 90$$

$$I_C = \omega C \angle 90 \times V_M \angle \theta$$


$$I_C = j\omega C V_C$$

$$V_C = I_C Z_C$$
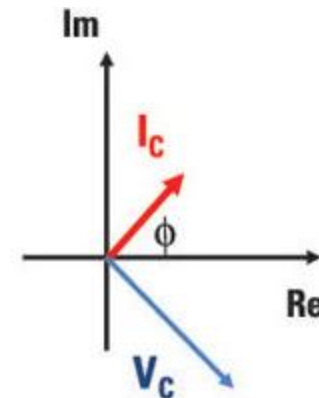
$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$



Impedance Model (L)

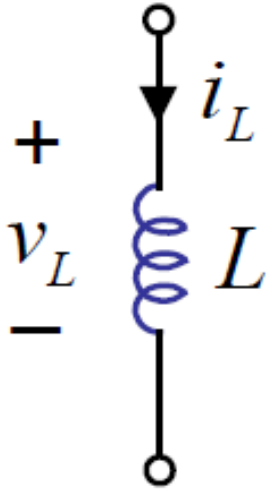

$$i_L(t) = I_M \cos(\omega t + \theta)$$

$$I_L = I_M \angle \theta$$

$$v_L(t) = L \frac{di_L}{dt}$$

$$v_L(t) = \omega L I_M \cos(\omega t + \theta + 90^\circ)$$

$$V_L = \omega L I_M \angle \theta + 90$$


$$V_L = \omega L \angle 90 \times I_M \angle \theta$$

$$V_L = j\omega L I_L$$

In a capacitor, current lags voltage by 90°


$$V_L = I_L Z_L$$

$$Z_L = j\omega L$$

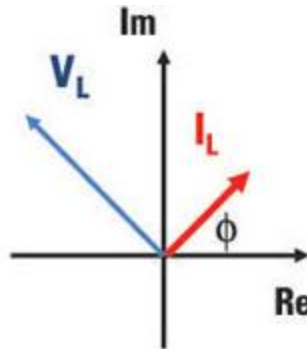

Impedance Model

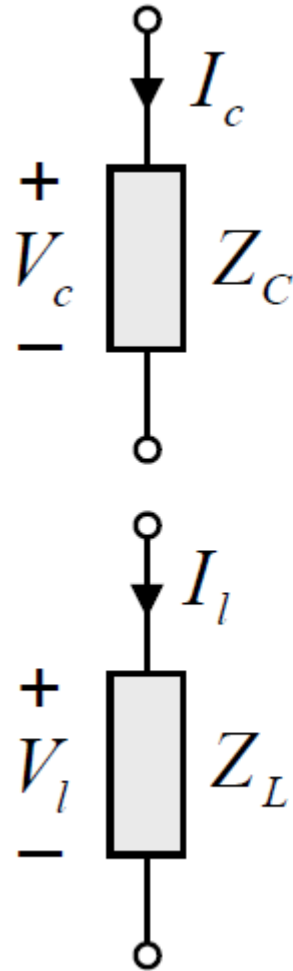Generalized Ohm's Law for in terms of Phasors




$$V_c = Z_c I_c$$
$$Z_c = \frac{1}{j\omega C}$$

impedance

$$V_l = Z_l I_l$$
$$Z_l = j\omega L$$

Example

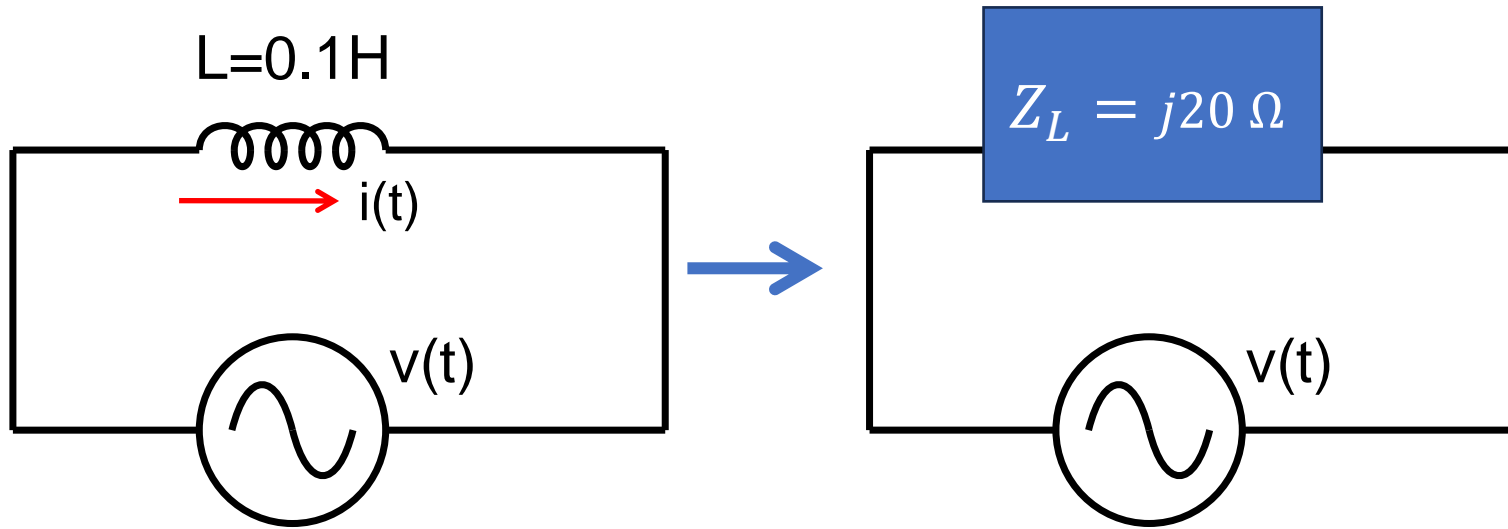

$$v(t) = 2 \cos(200t + 45) \text{ V}$$

$$\omega = 200 \text{ rad/s}$$

$$V_L = 2 \angle 45 \text{ V}$$

$$Z_L = j\omega L = j20\ \Omega$$

$$i(t) = ?$$

$$i(t) = 0.1 \cos(200t - 45) \text{ A}$$

$$V_L = I_L Z_L$$


$$\Rightarrow I_L = \frac{V_L}{Z_L}$$

$$I_L = \frac{2 \angle 45 \text{ V}}{j20\ \Omega}$$

$$= \frac{2 \angle 45}{20 \angle 90} \text{ A}$$


$$= 0.1 \angle -45 \text{ A}$$

Series-parallel operations

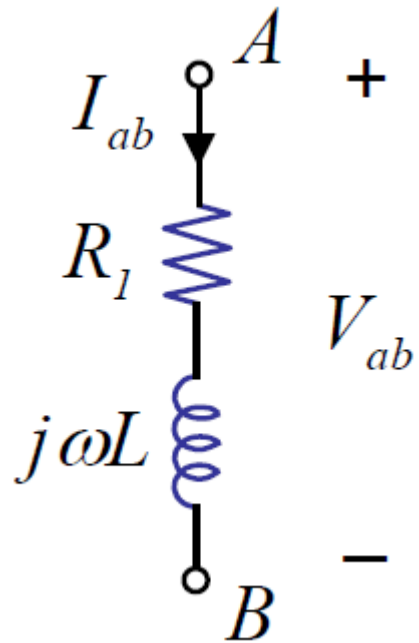

$$Z_{AB} = \frac{V_{ab}}{I_{ab}} = R_1 + j\omega L$$


Example: RL Circuit

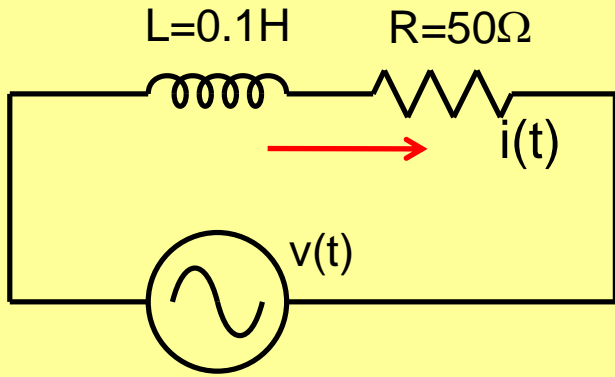

$$v(t) = 2 \cos(200t + 45) \text{ V}$$

$$i(t) = ?$$

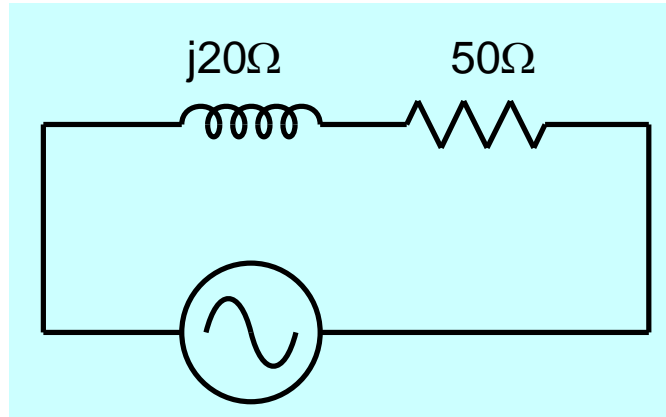
$$i(t) = 0.037 \cos(200t + 23.2) \text{ A}$$



$$\omega = 200 \text{ rad/s}$$

$$V = 2\angle 45 \text{ V}$$


$$Z_L = j\omega L = j20 \Omega$$

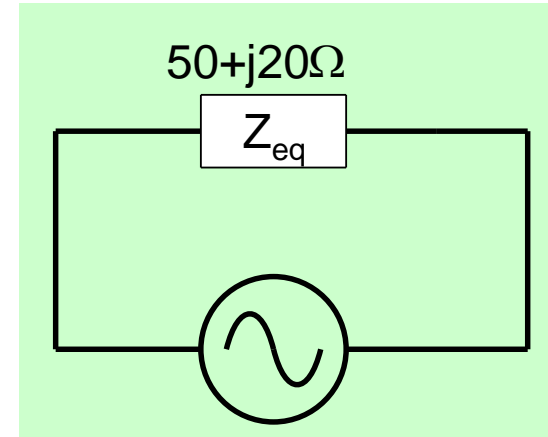

$$\begin{aligned} I &= \frac{2\angle 45}{50 + j20} \\ &= \frac{2\angle 45}{53.85\angle 21.8} \\ &= 0.037\angle 23.2 \text{ A} \end{aligned}$$

$$V_R = 2\angle 45 \times \frac{50}{50 + j20} \text{ V}$$

Example: RC

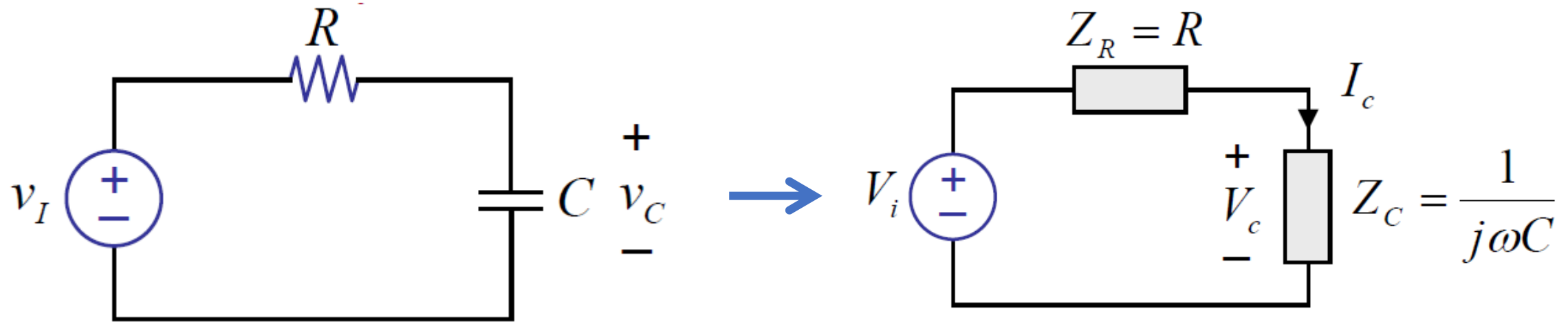

$$V_c = \frac{1}{1 + j\omega RC} V_i$$

Can apply KCL, KVL, Thevenin, Norton equivalents, superposition series/parallel, node method

Big Picture

