

ESC201: INTRODUCTION TO ELECTRONICS





MODULE 5: AMPLIFIERS





Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur



Factors Determining Current

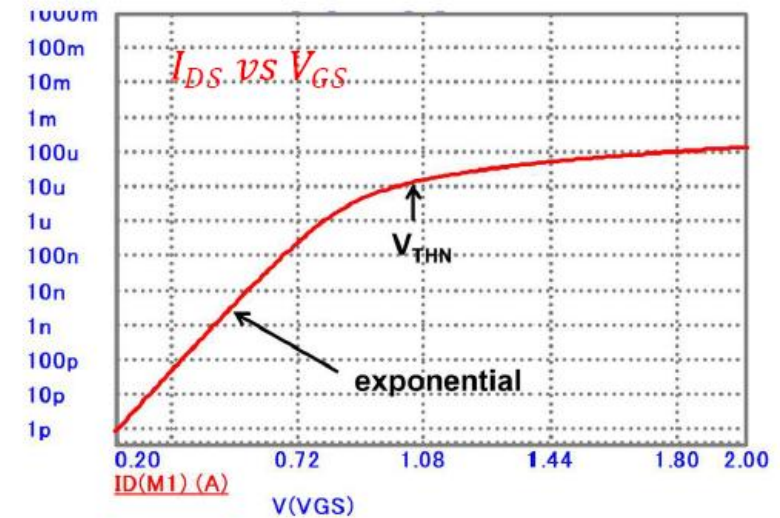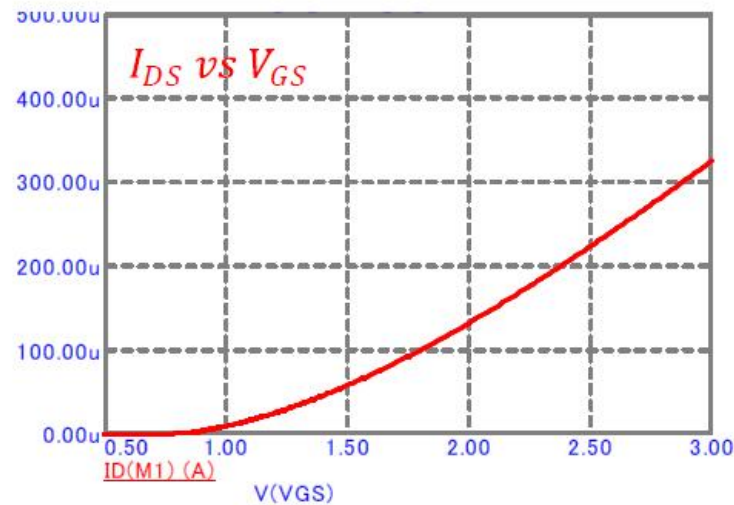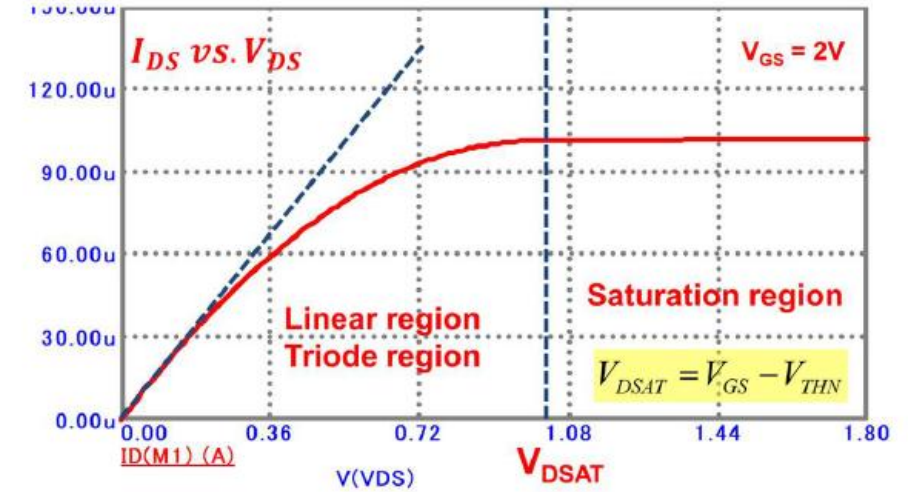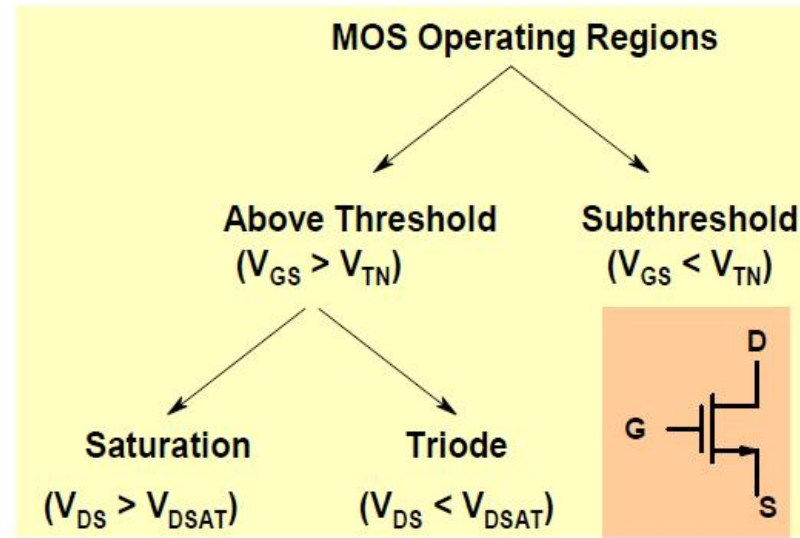


DC and AC model of a MOSFET

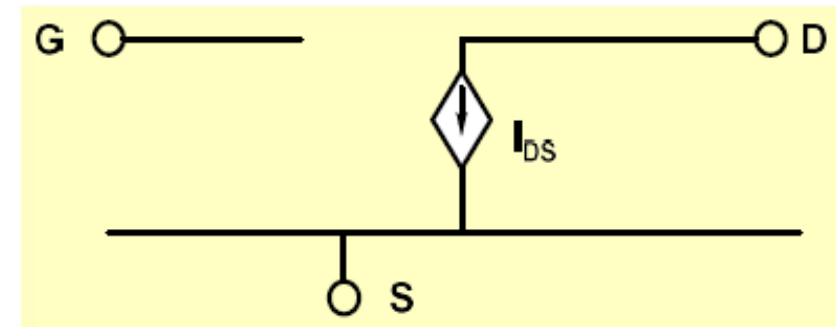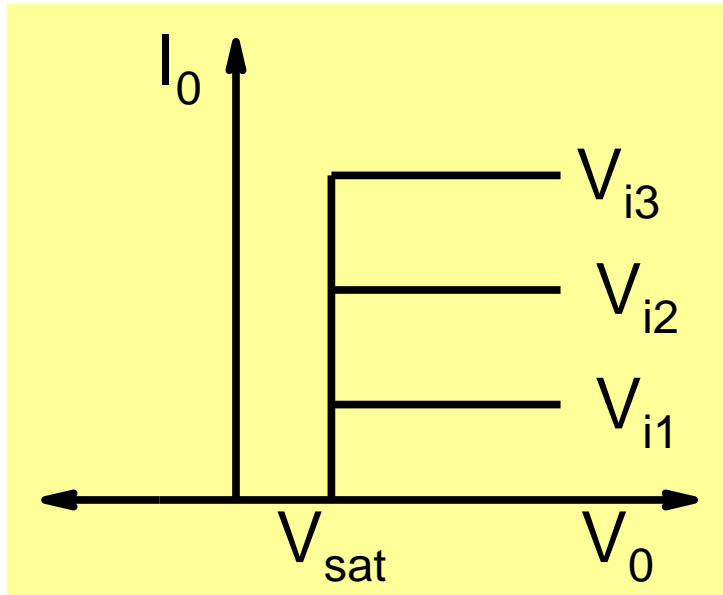

$$I_{DS} = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2 ; \beta_N = KP_N \times \frac{W}{L}$$

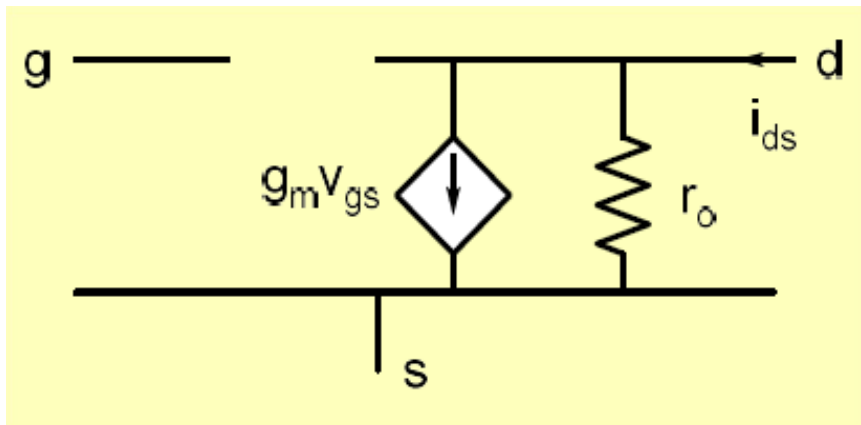KP_N : Transconductance parameter $\frac{\mu A}{V^2}$




$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$r_o = \frac{1}{\lambda_n I_{DSQ}}$$



λ_N is the channel length modulation parameter

Example 3

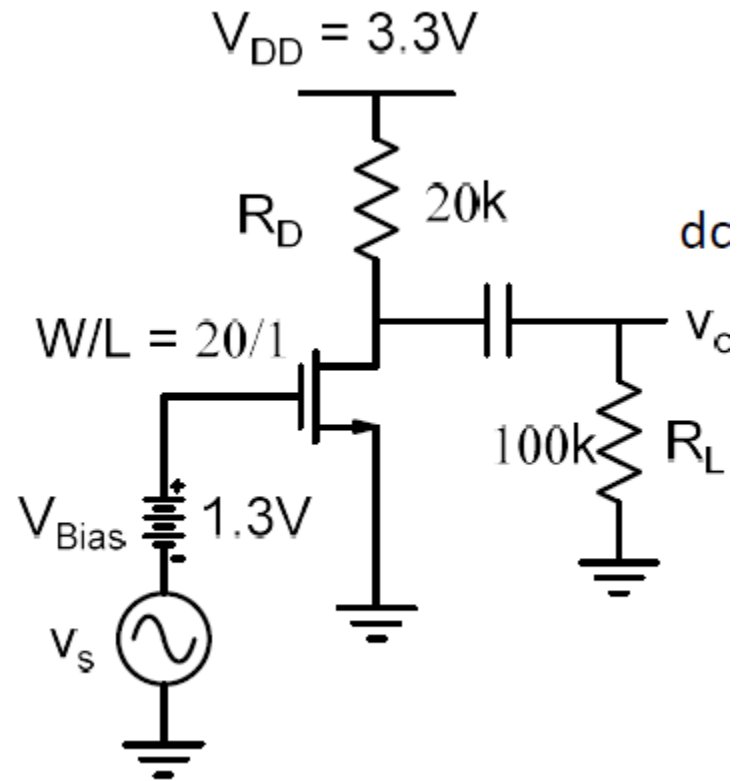

Amplifier Design

Requires specialized knowledge

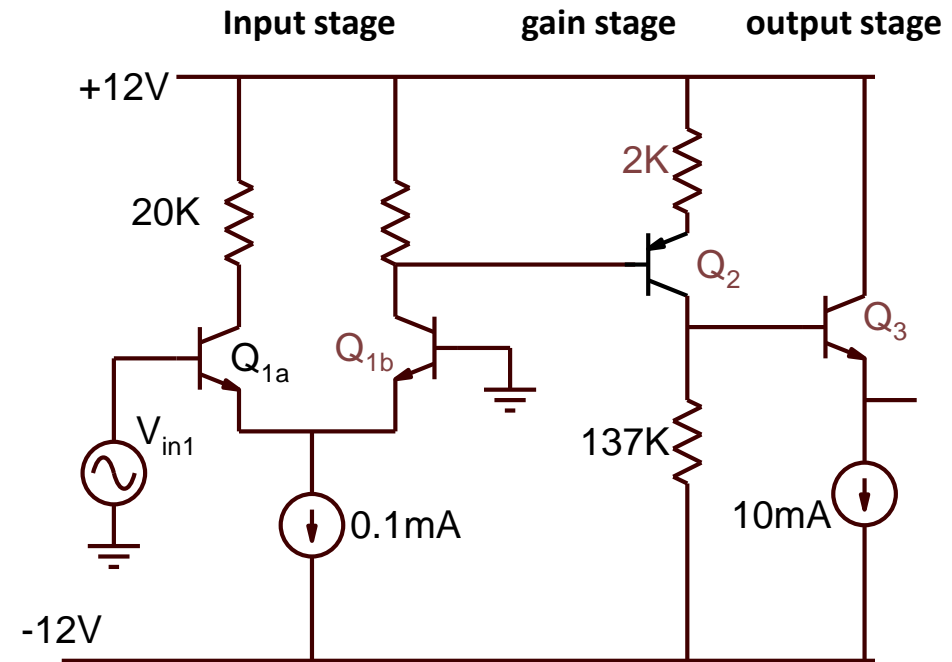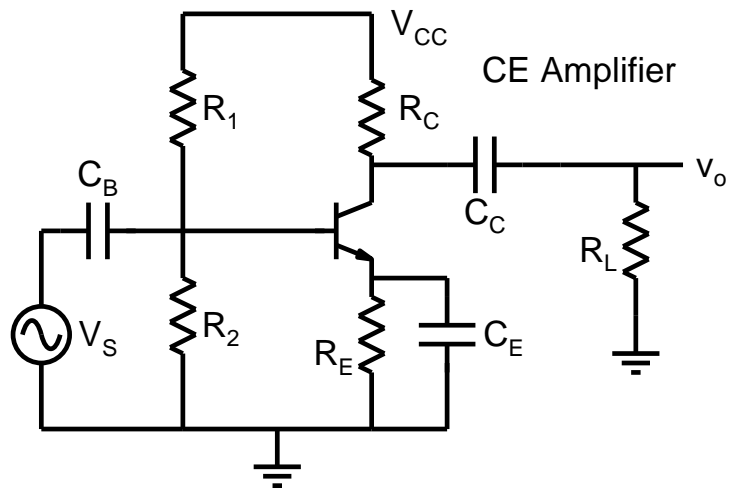


It is not possible for every user to design his/her own amplifier !

Handling Amplifier Design Complexity

Let experts have fun designing and implementing amplifiers!

They can make it available to everybody else as a commodity product

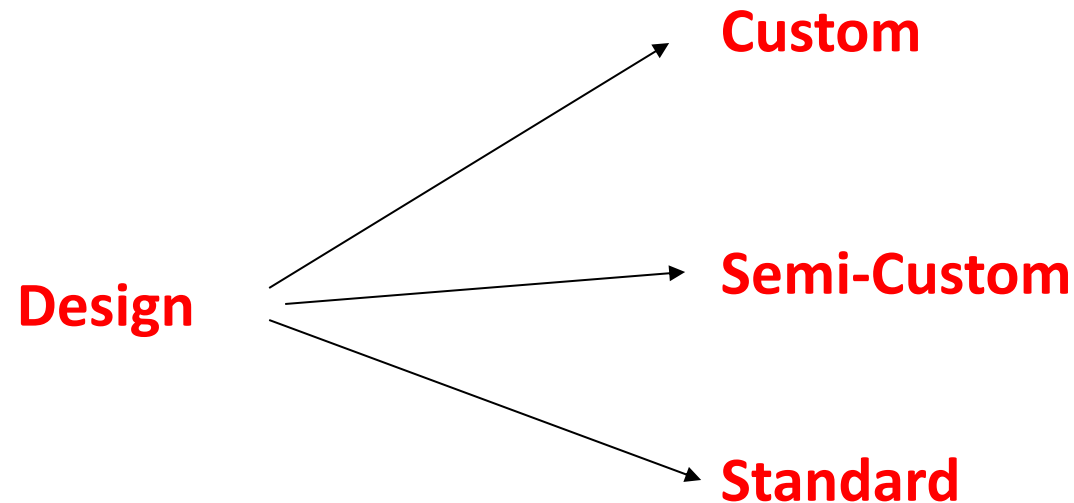Although this is done, it does not satisfy all the users due to diverse requirements




Semi-custom: partially completed design which is customized by the user

Op-amp is a good illustration of the advantages of semi-custom approach

Difference Amplifier

An amplifier that is:

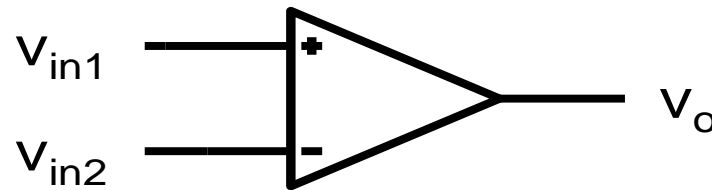- sensitive to difference in input voltages; and
- insensitive to what is common.



$$v_{id} = v_{in1} - v_{in2}$$

$$v_{ic} = \frac{v_{in1} + v_{in2}}{2}$$

$$v_o = A_d v_{id} + A_{cm} v_{ic}$$

A_d : Differential mode gain


A_{cm} : Common mode gain

$$A_d \gg A_{cm}$$

$$\text{Common Mode Rejection Ratio: } CMRR = \frac{A_d}{A_{cm}}$$

Popularly called **op-amp**


Operational Amplifier

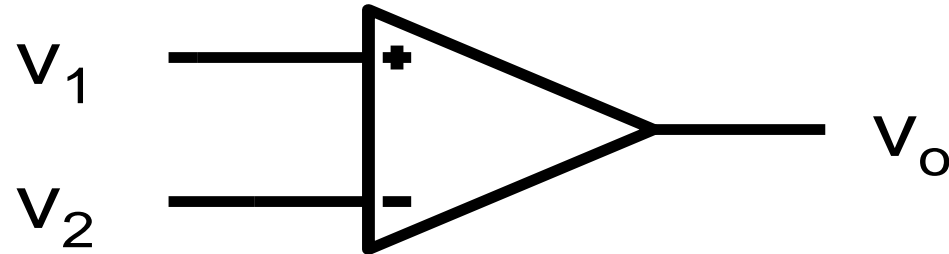

A **special** kind of difference amplifier

1. Very High Differential-mode voltage gain
2. Very High Common mode Rejection ratio
3. Very High Input Resistance
4. Very Low output Resistance
5.

Ideal Operational Amplifier

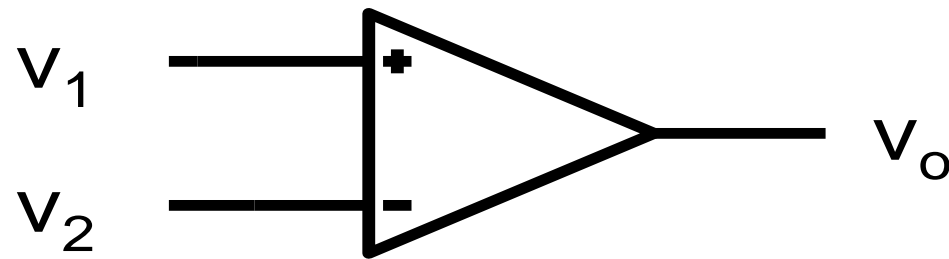

1. Infinite Differential-mode voltage gain
2. Infinite Common mode Rejection ratio
3. Infinite Input Resistance
4. Zero output Resistance
5.

A Commercially Available Op-amp

LM741

Operational Amplifier


The LM741C is identical to the LM741/LM741A except that the LM741C has their performance guaranteed over a 0°C to +70°C temperature range, instead of -55°C to +125°C.

General Description

The LM741 series are general purpose operational amplifiers which feature improved performance over industry standards like the LM709. They are direct, plug-in replacements for the 709C, LM201, MC1439 and 748 in most applications.

The amplifiers offer many features which make their application nearly foolproof: overload protection on the input and output, no latch-up when the common mode range is exceeded, as well as freedom from oscillations.

Dual-In-Line or S.O. Package

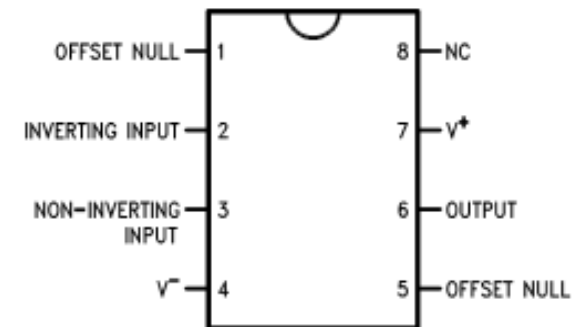

Electrical Characteristics

(V_{CC} = 15V, V_{EE} = -15V, T_A = 25°C, unless otherwise specified)

Parameter	Symbol	Conditions	Min.	Typ.	Max.	Unit
Input Resistance (Note1)	R _I	V _{CC} = ±20V	0.3	2.0	-	MΩ
Large Signal Voltage Gain	G _V	R _L ≥ 2kΩ, V _{CC} = ±20V, V _{O(P-P)} = ±15V	-	-	-	V/mV
		V _{CC} = ±15V, V _{O(P-P)} = ±10V	20	200	-	
Common Mode Rejection Ratio	CMRR	R _S ≤ 10kΩ, V _{CM} = ±12V	70	90	-	dB
		R _S ≤ 50Ω, V _{CM} = ±12V	-	-	-	


Note:

1. Guaranteed by design.

Op-amp Circuit


- The circuit appears to be complicated
- Circuit contains several transistors and resistors.

Schematic Diagram

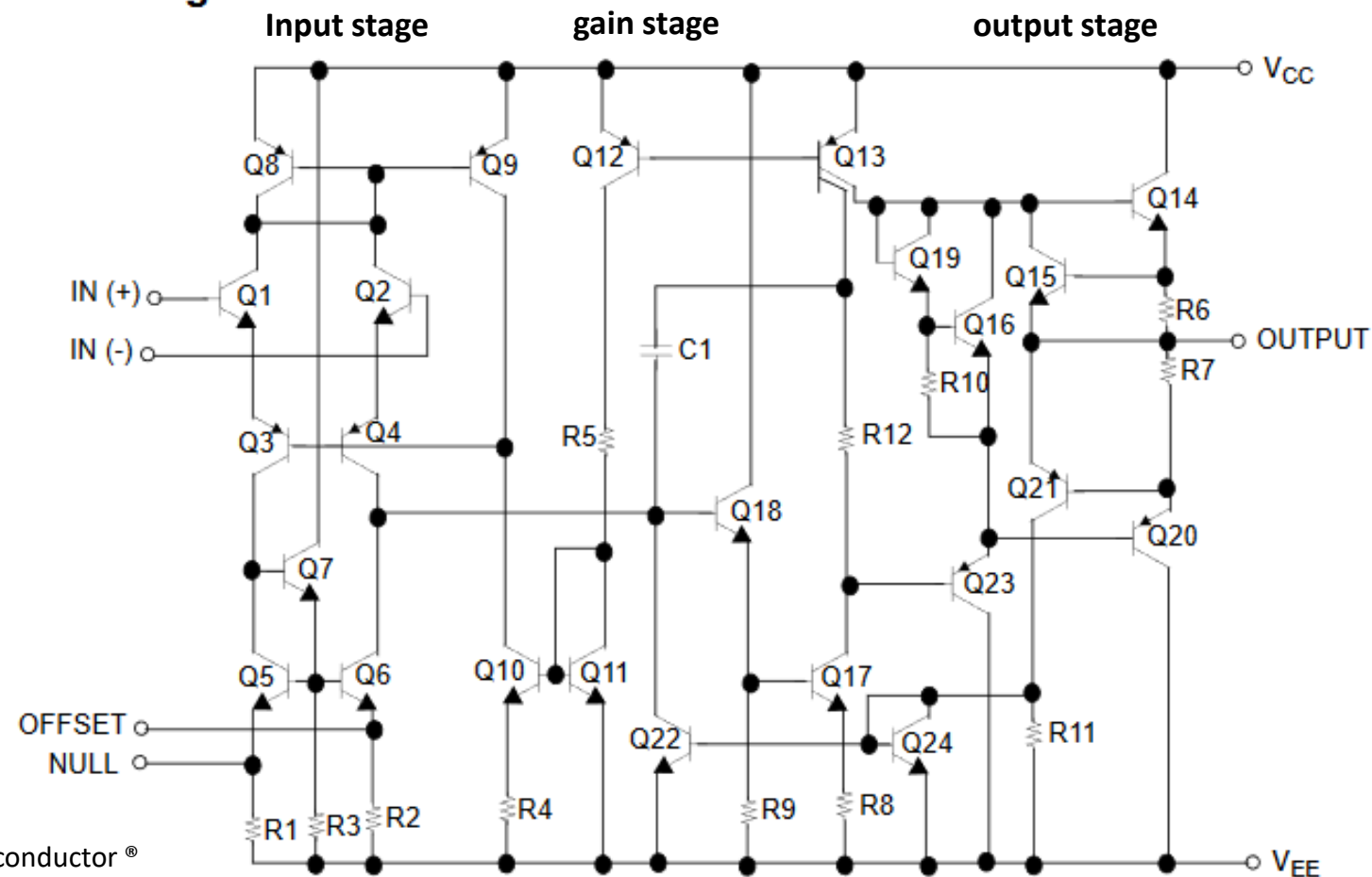


Equivalent Circuit Model

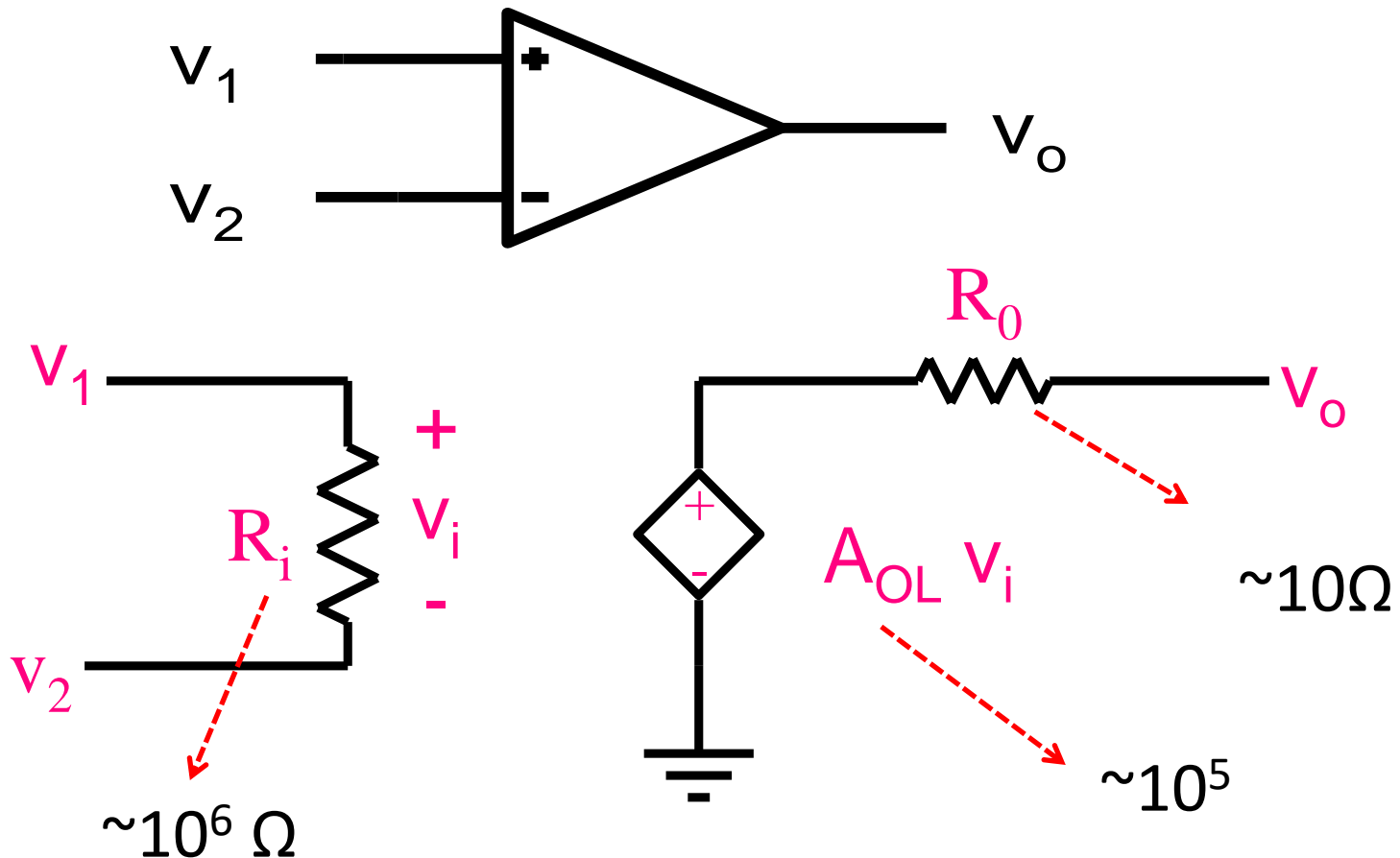A simple equivalent circuit model of an op-amp





This assumes very high CMRR

Regions of Operation of Op-amp

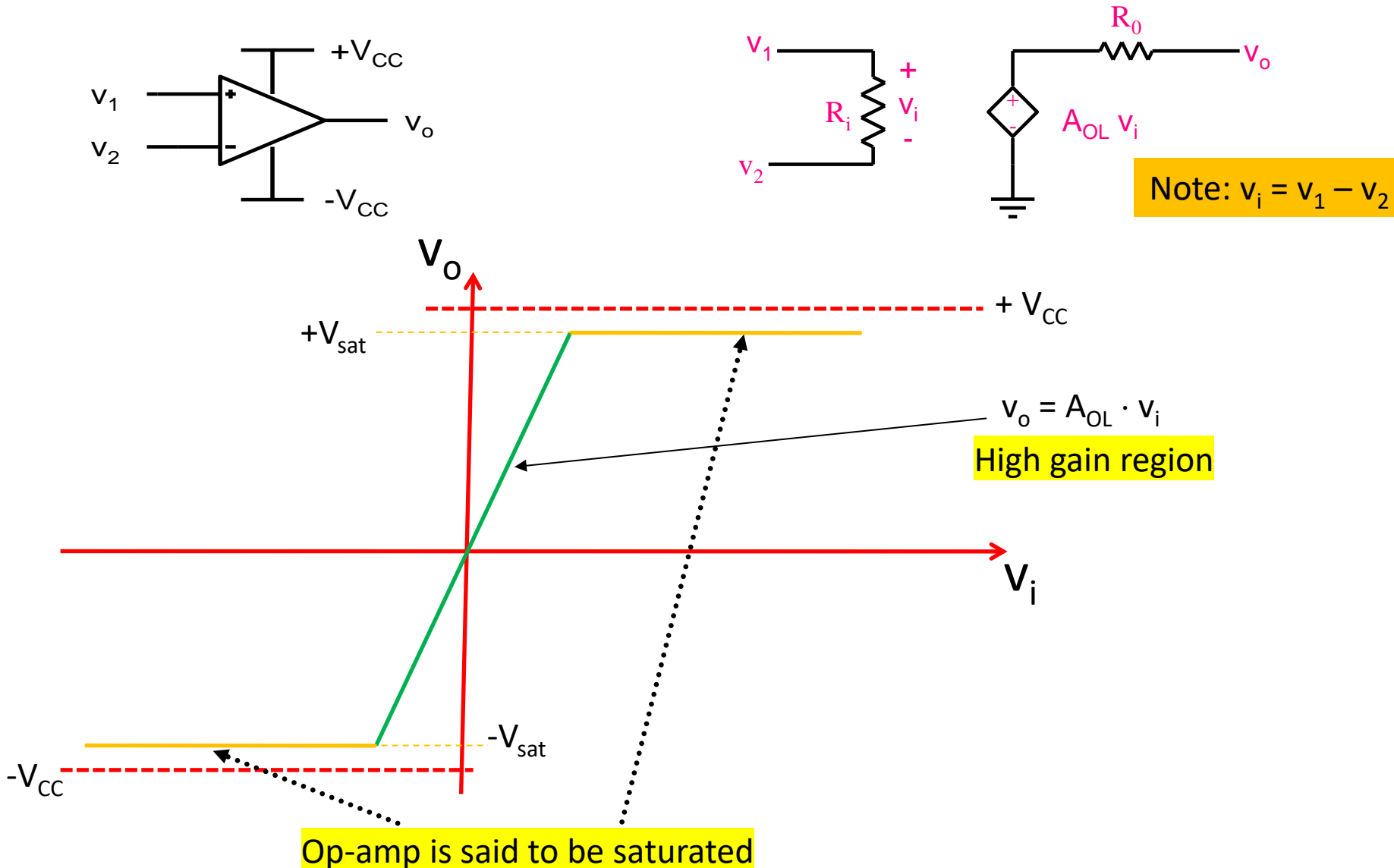


Choice of Input Terminals

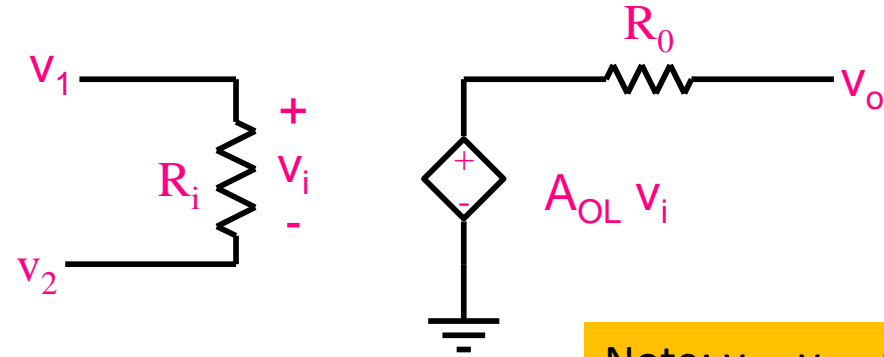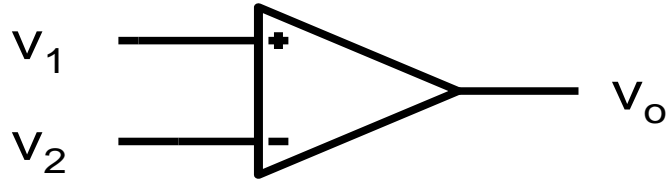


Note: $v_i = v_1 - v_2$


Input to positive terminal

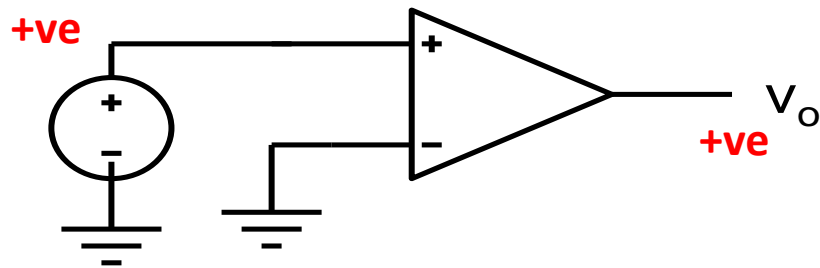



Input to negative terminal

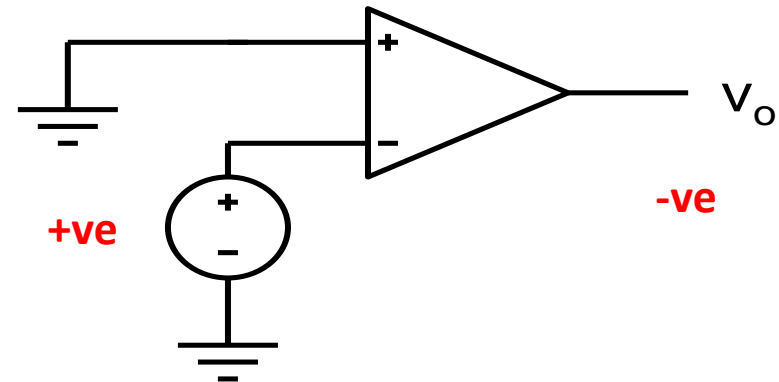




Amplifying an Input Signal

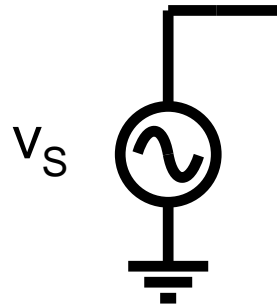
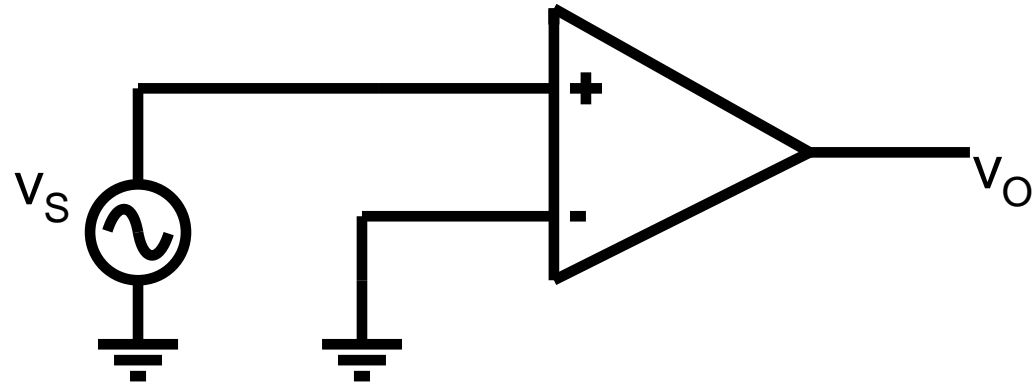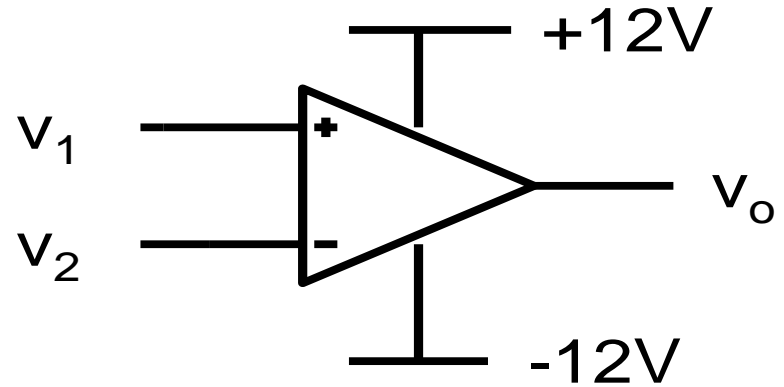
$$v_s = 1 \cdot \sin(\omega t) \text{ mV}$$



The Output value?

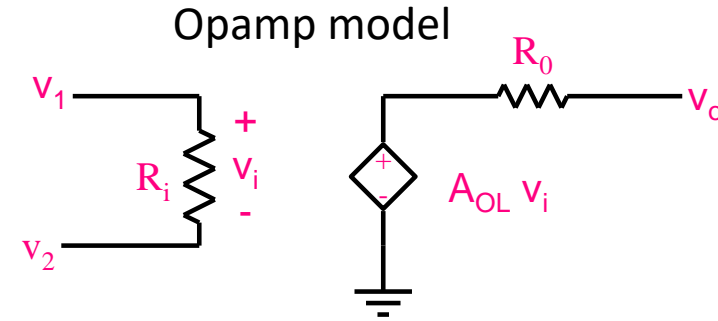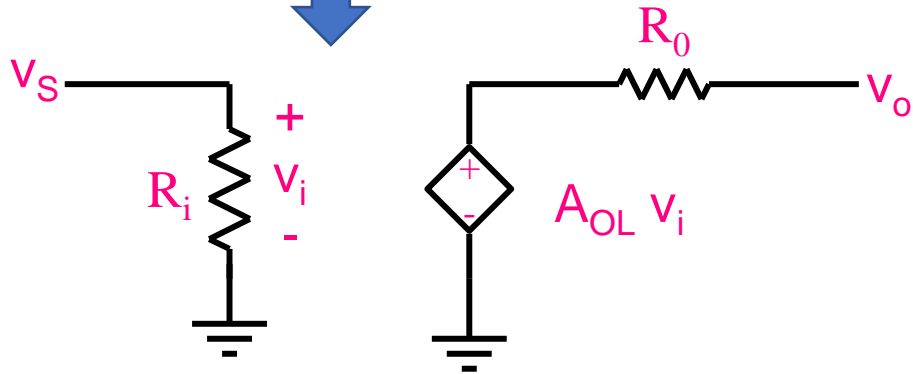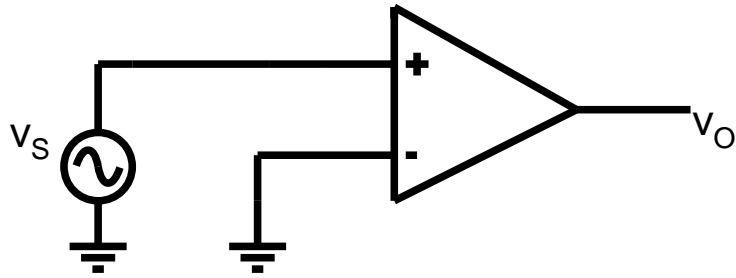

We know gain $A_{OL} \sim 10^5$

$$v_o = A_{OL} \cdot v_s = 10^2 \cdot \sin(\omega t) \text{ V}$$




But opamp voltage is limited to* $\pm 12V$

* Op-amp supply voltage may vary depending on the op-amp


So, op-amp will enter saturation region of operations for some input voltages!

Also to note that A_{OL} is not precisely defined and can vary with op-amps

Simulation Results

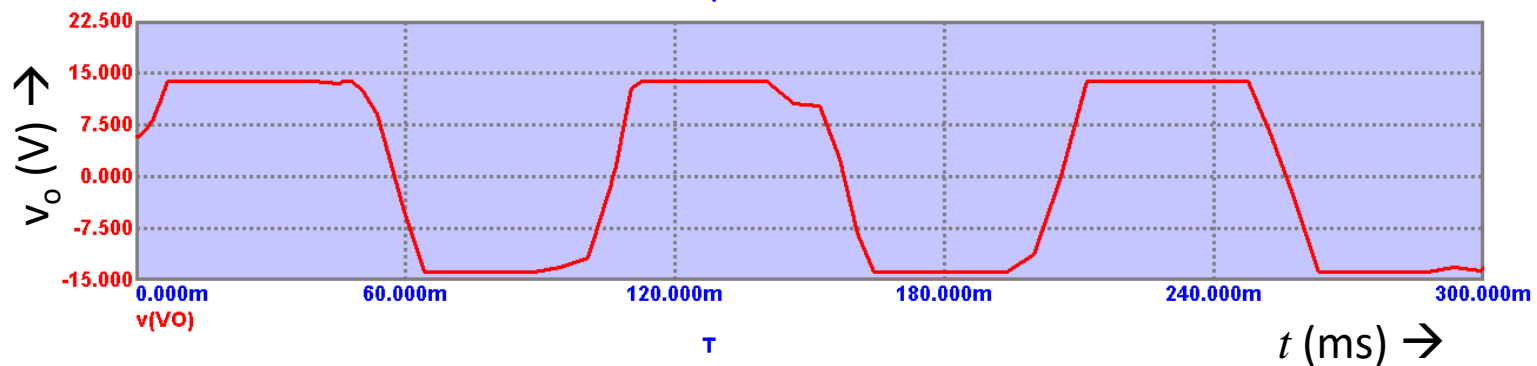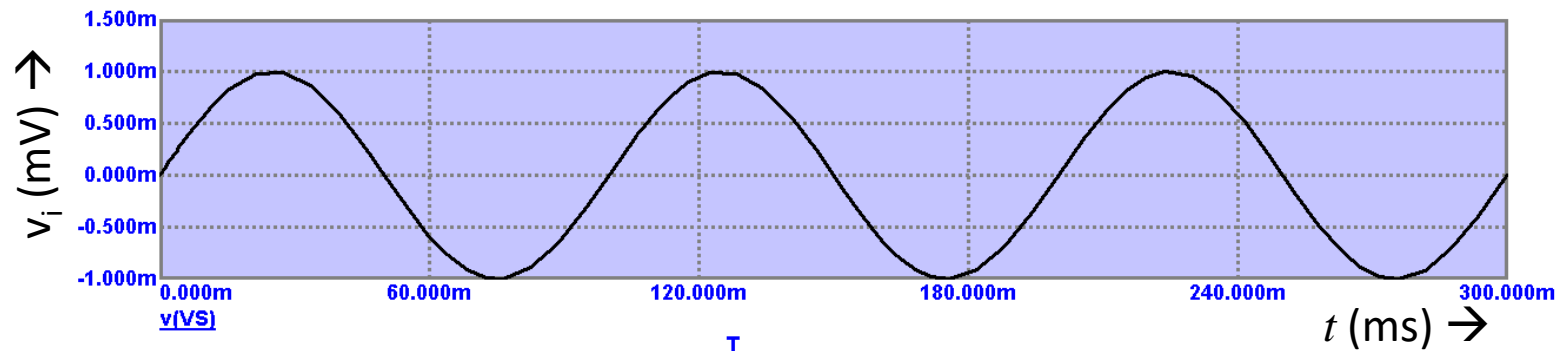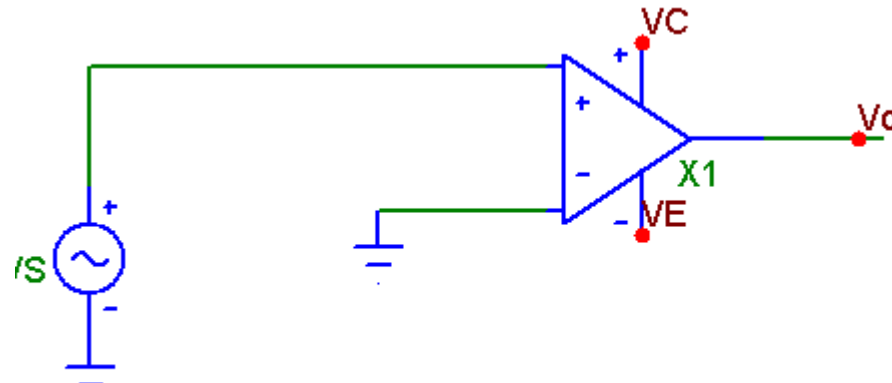


How to amplify not so small signals?

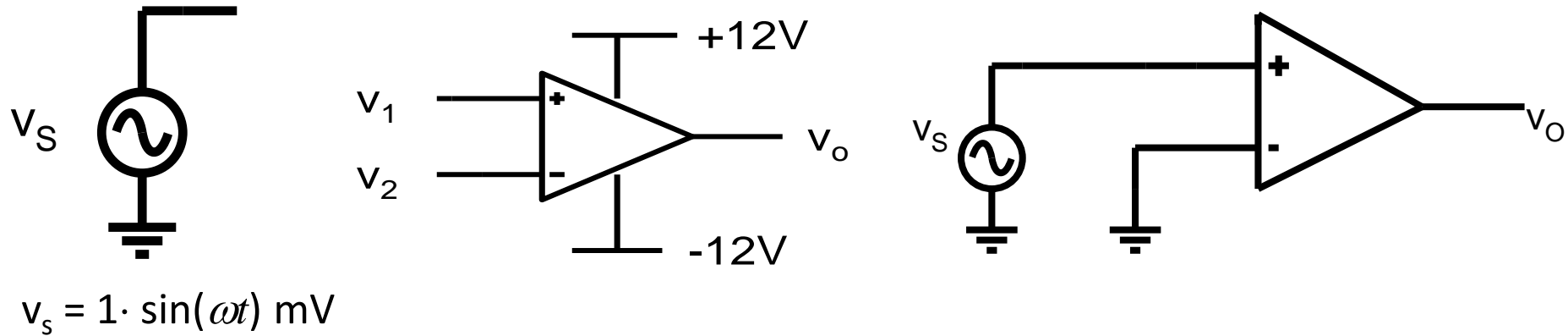

1. Attenuate the signal to 0.1mV and then amplify ? 😊
2. Or

And how do we tackle the variation in value of A_{OL} ?
Precise value of A_{OL} varies from device to device

How to amplify not so small signals?

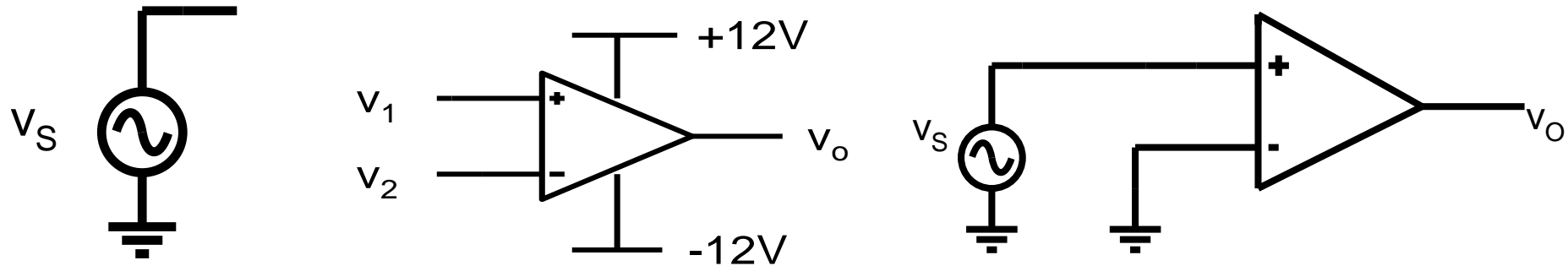

$$v_s = 1 \cdot \sin(\omega t) \text{ mV}$$


1. Attenuate the signal to 0.1mV and then amplify ? 😊
2. Or

And how do we tackle the variation in value of A_{OL} ?
Precise value of A_{OL} varies from device to device

The electronic circuit designers again come to the rescue!

A Better Solution

Use amplifier with negative **feedback**

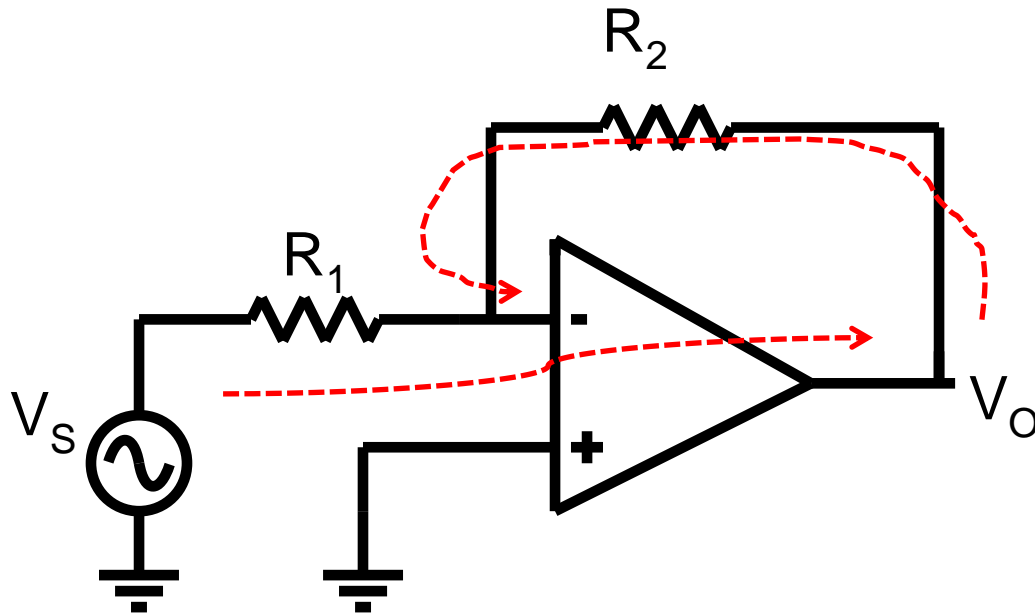

$$\frac{v_o}{v_S} = -\frac{R_2}{R_1}$$

Feedback signal helps input voltage: **positive feedback**

Feedback signal opposes input voltage: **negative feedback (as in the circuit above)**


Negative feedback helps overcome requirement of small signal restrictions!

The actual gain here will depend overwhelmingly on resistances attached.


The **amplification gain has to be high**, but **its precise value is not significant**.

Feedback

Open loop system

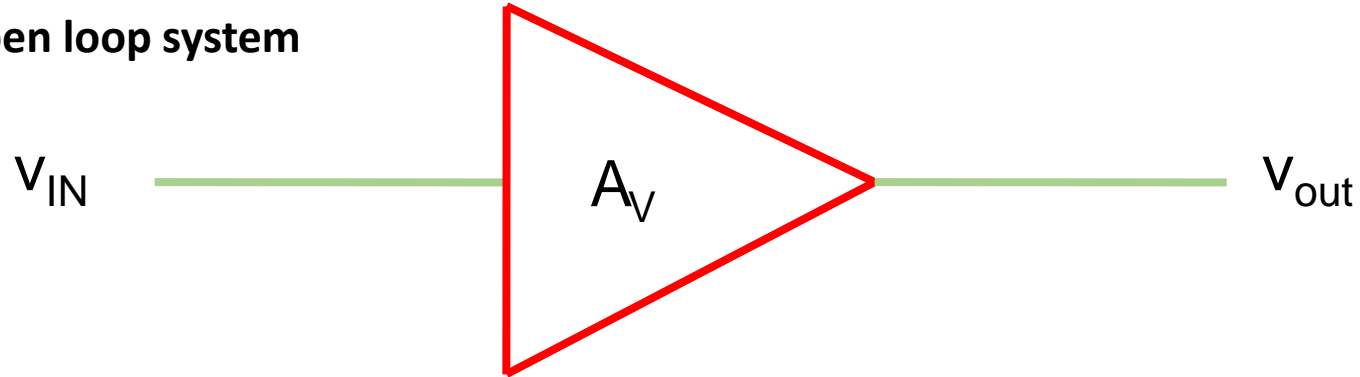


A closed loop system


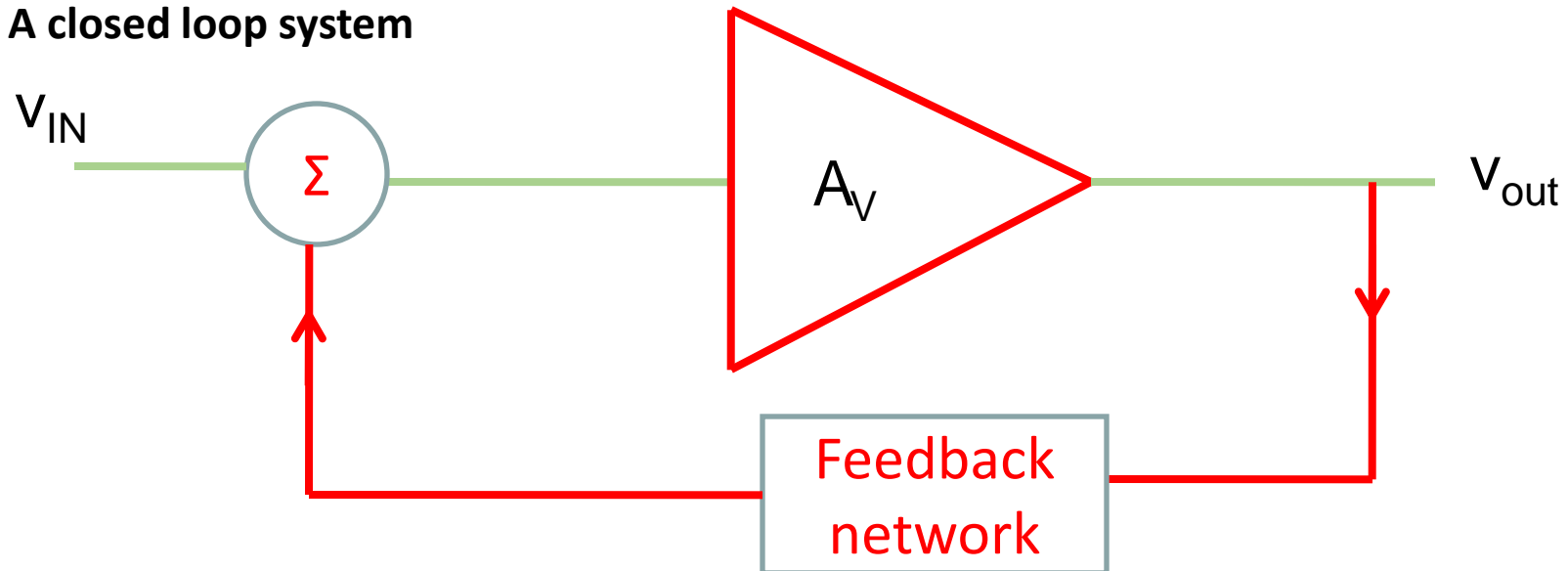


The summing circuit in closed loop system may add or subtract

Negative and Positive Feedback

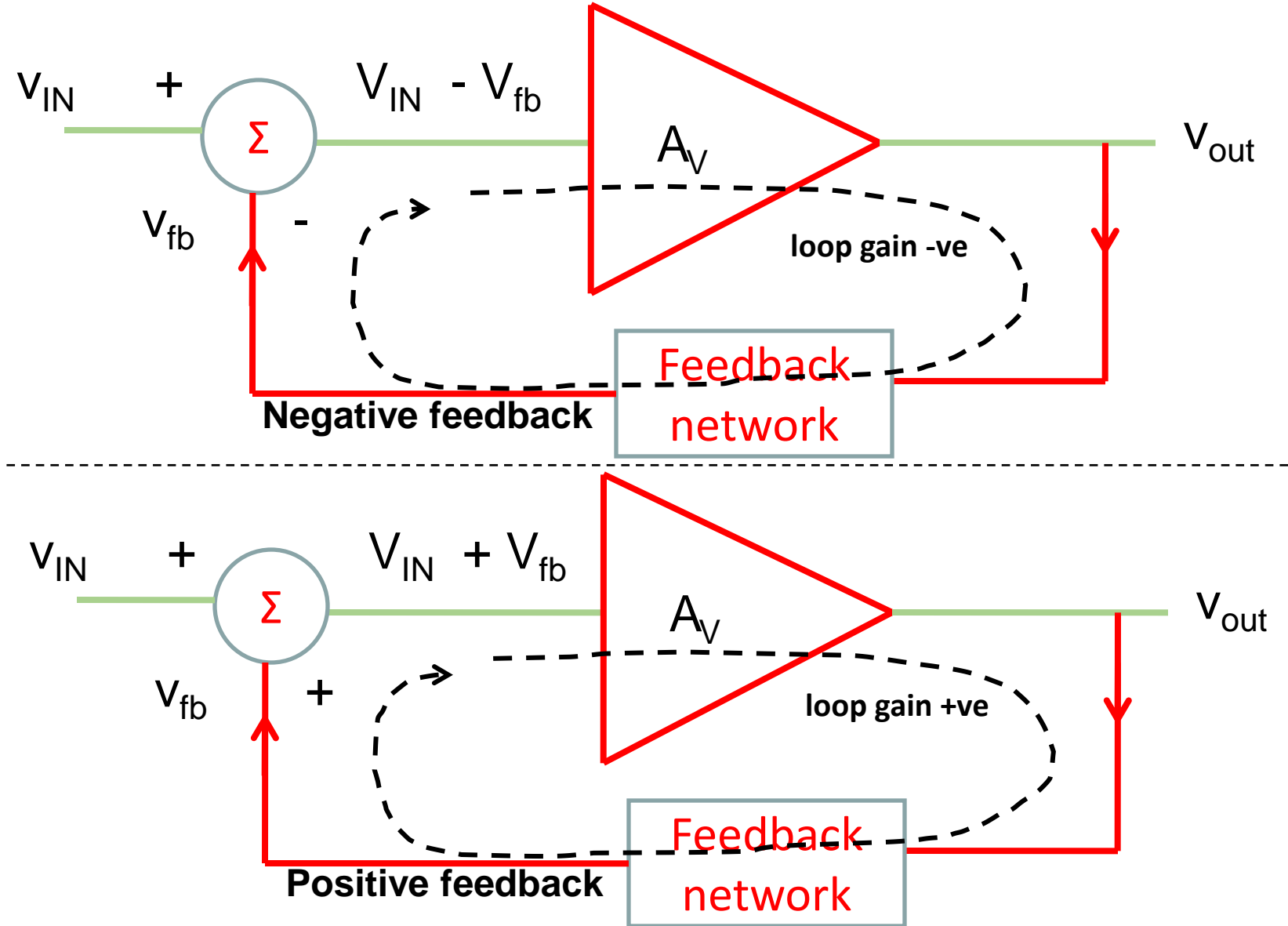

Negative and Positive Feedback

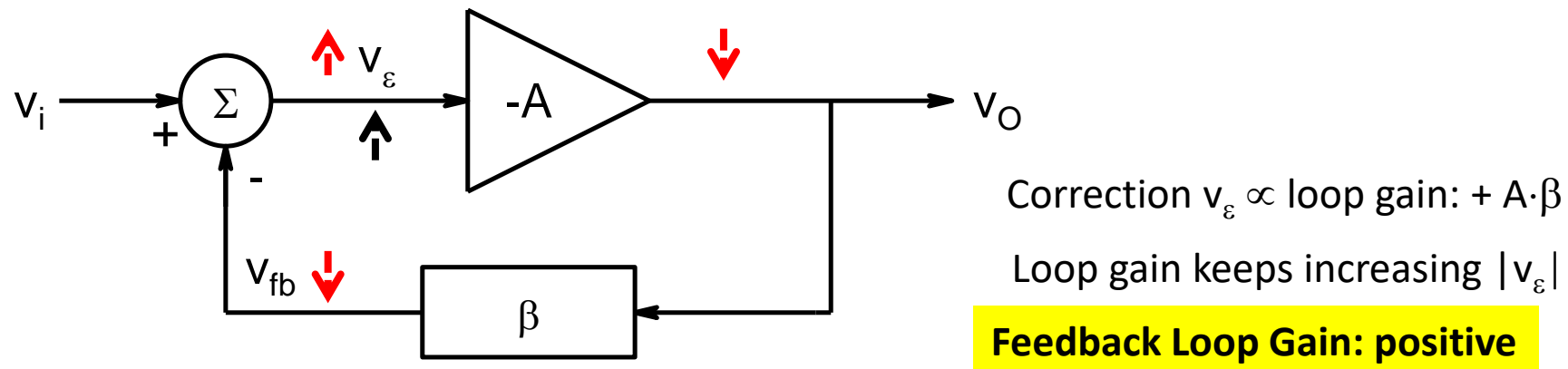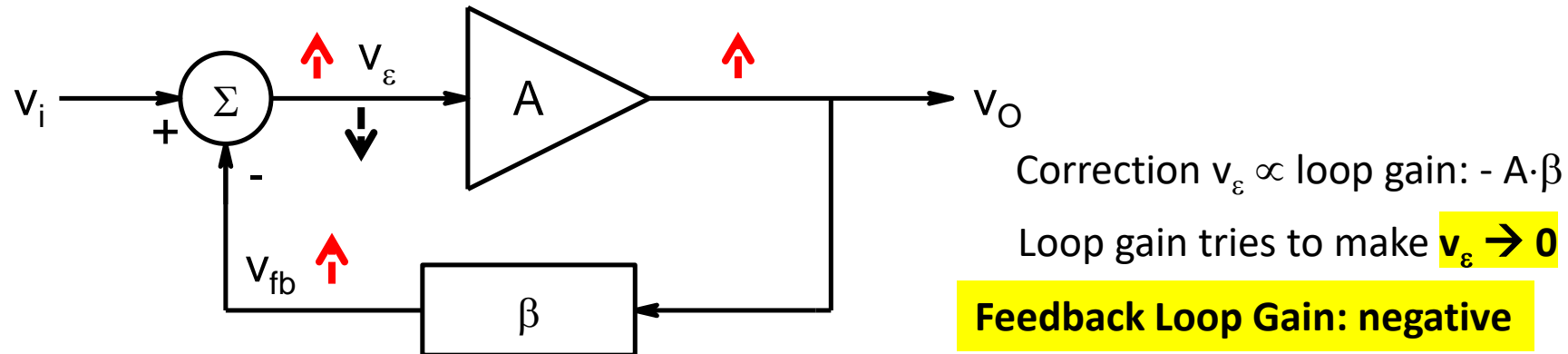

Note:

- The loop gain is evaluated by going around the feedback loop.
- Its sign will depend on signs of forward gain, feedback gain and add/substrate operation at the 'summation' point