


ESC201: INTRODUCTION TO ELECTRONICS

MODULE 6: DIGITAL CIRCUITS



Dr. Shubham Sahay,
Associate Professor,
Department of Electrical Engineering,
IIT Kanpur


Sequential Circuits

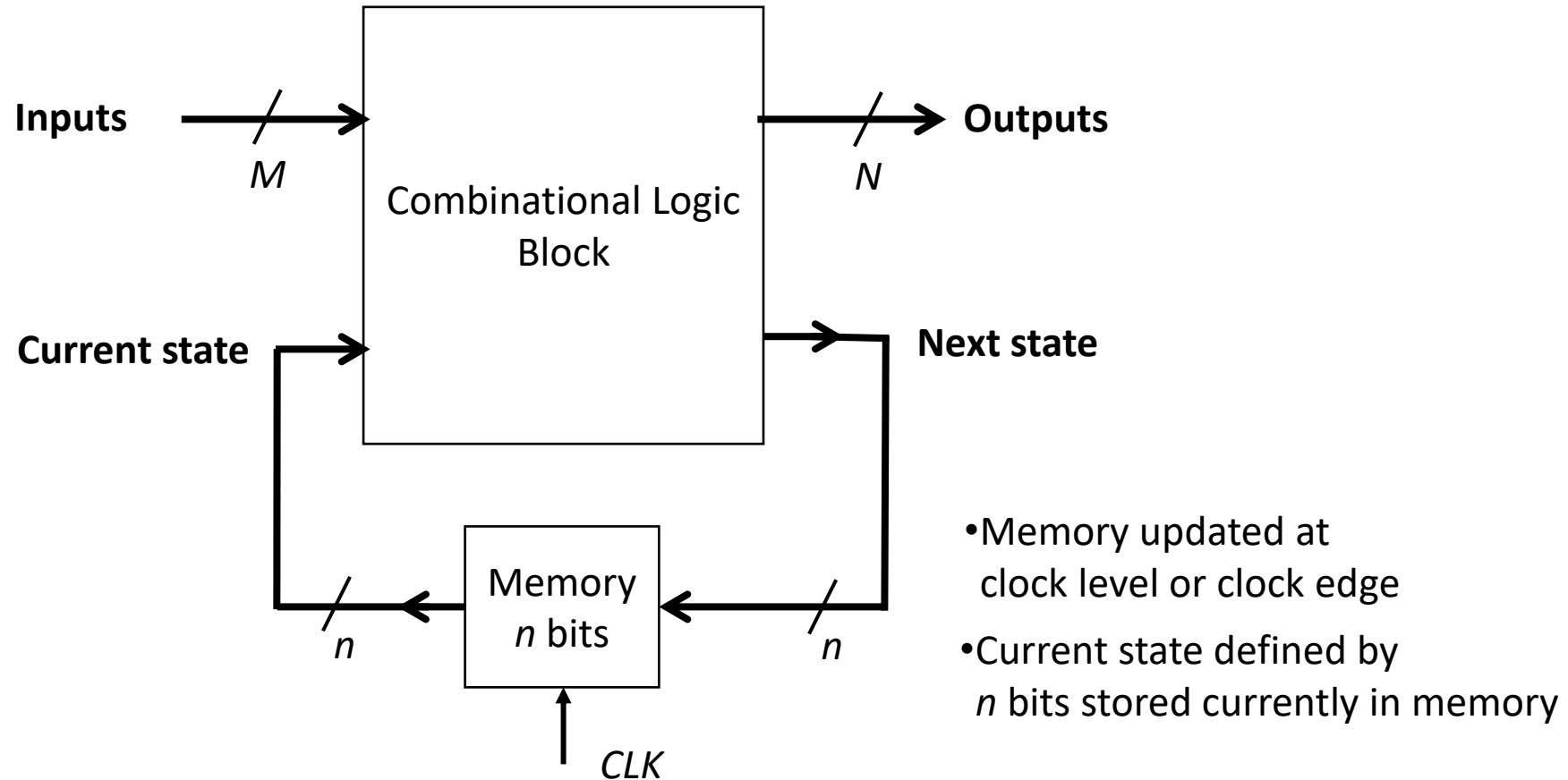

- Output will change as per current state and the input given!
- Can decide what will be the next state based on current state and inputs
→ Beginning of decision making and intelligence!

Static *SR* Flip-Flop* with NOR Gates

 $S \equiv$ 'set' latch output value Q ; and $R \equiv$ 'reset' latch output value Q



For NOR gate, Any input being "1" will make output "0".


Input $S = R = 1$ is prohibited because when it comes out of that state to $S = R = 0$, we do not know whether Q becomes 0 or 1, leading to unpredictability of future states.

If $S = R = 1$ state occurs, make the next state compulsorily
 $S = 1, R = 0$ or $S = 0, R = 1$ state.

* 'Flip-Flop' as defined in Rabaey et al.'s book is
any bi-stable component "formed by cross-coupling of gates"

Static *SR* Flip-Flop with NAND Gates

 NAND gate implementation is in the dual space as with NOR gate implementation



S	R	Q	\bar{Q}	Remark
0	0	Q	\bar{Q}	Hold
0	1	0	1	Re-set
1	0	1	0	Set
1	1	1	1	Prohibited

For NAND gate, Any input being “0” will make output “1”.

Input $S = R = 1$ is prohibited because when it comes out of that state to $S = R = 0$, we do not know whether Q becomes 0 or 1, leading to unpredictability of future states.

If $S = R = 1$ state occurs, make the next state compulsorily $S = 1, R = 0$ or $S = 0, R = 1$ state.

- *SR* Latch (set-reset latch)
- *JK* Latch
- *D* Latch (delay latch)
- *T* Latch (toggle latch)

Let us look at the

- Characteristics table for each latch
- Excitation table for each latch


* Note that registers can be built combining latches.

Defining* Latch and Register


Latch

Q “transparent” to $Input$ for clock level

Positive Latch

 


Negative Latch

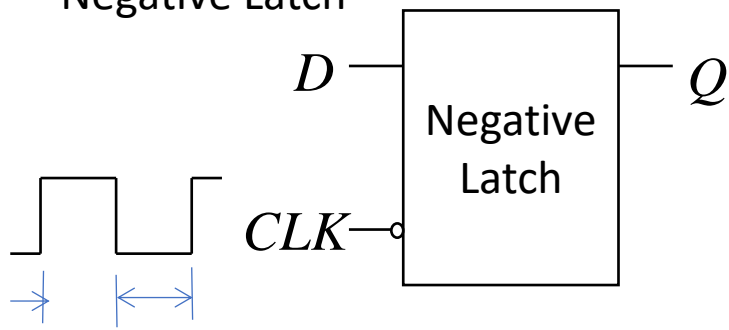


Registers

Q “transparent” to $Input$ for clock edge


Positive Register

 

Negative Register

 

 * Defined according to *Rabaey, Chandrakasan & Nikolic*
Definitions may vary in other text books



Characteristics Table


Inputs		Outputs		Remark
S	R	Q_{n+1}	$\overline{Q_{n+1}}$	
0	0	Q_n	$\overline{Q_n}$	Hold
0	1	0	1	Re-set
1	0	1	0	Set
1	1	0	0	Prohibited

Subscript n is current clock cycle
 Subscript $n+1$ is next clock cycle

Excitation Table

Desired transition		Required Inputs	
Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

Here x represents a don't care state

 

Characteristics Table

Inputs		Outputs		Remark
J	K	Q_{n+1}	\overline{Q}_{n+1}	
0	0	Q_n	\overline{Q}_n	Hold
0	1	0	1	Re-set
1	0	1	0	Set
1	1	\overline{Q}_n	Q_n	Toggle


Subscript n is current clock cycle
 Subscript $n+1$ is next clock cycle

Excitation Table

Desired transition | Required Inputs

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Here x represents a don't care state

 

Characteristics Table

Inputs		Outputs		Remark
D		Q_{n+1}	$\overline{Q_{n+1}}$	
0		0	1	Reset
1		1	0	Set

Excitation Table

Desired transition		Required Inputs
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1


Subscript n is current clock cycle

Subscript $n+1$ is next clock cycle

Positive and Negative Latches with MUX

with 2 to 1 Multiplexer (MUX)

Positive Latch

 


Write (Feedback is broken)

When $CLK = 1$, $Q = D$

Read (+ve Feedback is restored)

When $CLK = 0$, Q value does not change

Negative Latch

 


Write (Feedback is broken)

When $CLK = 0$, $Q = D$

Read (+ve Feedback is restored)

When $CLK = 1$, Q value does not change

 A positive and negative latch combination can help you build a register.



Characteristics Table

Inputs		Outputs		Remark
T		Q_{n+1}	$\overline{Q_{n+1}}$	
0		Q_n	$\overline{Q_n}$	Hold
1		$\overline{Q_n}$	Q_n	Toggle

Excitation Table

Desired transition		Required Inputs
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Subscript n is current clock cycle

Subscript $n+1$ is next clock cycle

Exercise

- Can you build a D latch from a JK latch?
- Given a latch, with logic gates one may build any other latch.
- Give it a try!