


1. Draw the Bode magnitude plot for the following transfer functions.

(a) $H(j\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$

(b) $H(j\omega) = \frac{(j\omega)^2(j\omega + 100)}{(j\omega + 1)(j\omega + 10)(j\omega + 1000)}$


Solutions:

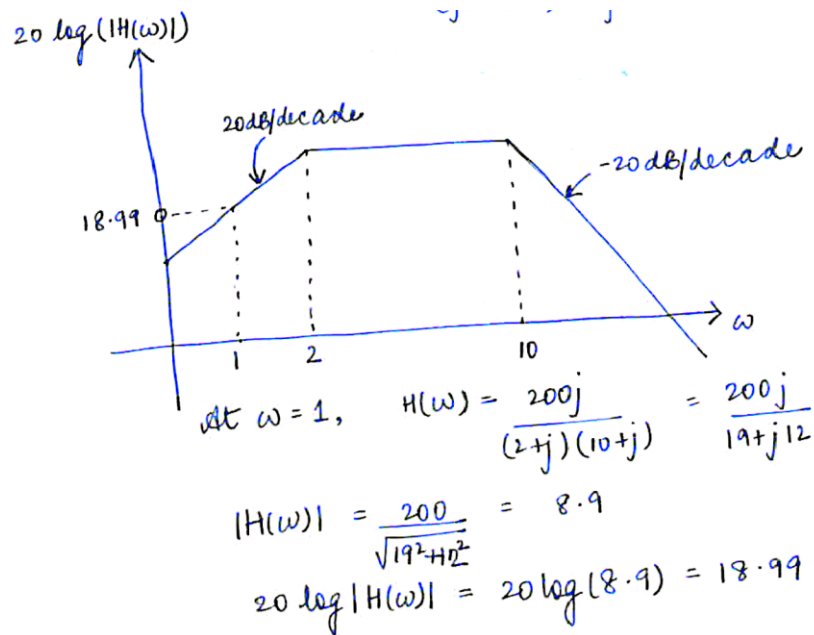(a) a) $H(j\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$



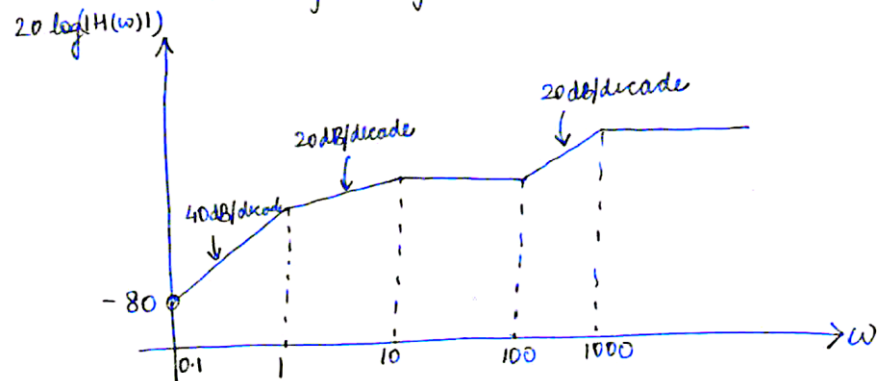(b) $H(j\omega) = \frac{(j\omega)^2(j\omega + 100)}{(j\omega + 1)(j\omega + 10)(j\omega + 1000)}$

$$(b) \quad H(j\omega) = \frac{(j\omega)^2 (j\omega + 100)}{(j\omega + 1)(j\omega + 10)(j\omega + 1000)}$$




At $\omega = 0.1$,

$$|H(\omega)| = \left| \frac{(j(0.1))^2 (j(0.1) + 100)}{(j(0.1) + 1)(j(0.1) + 10)(j(0.1) + 1000)} \right| = 10^{-4}$$

$$20 \log |H(\omega)| = -80 \log(10) = -80$$

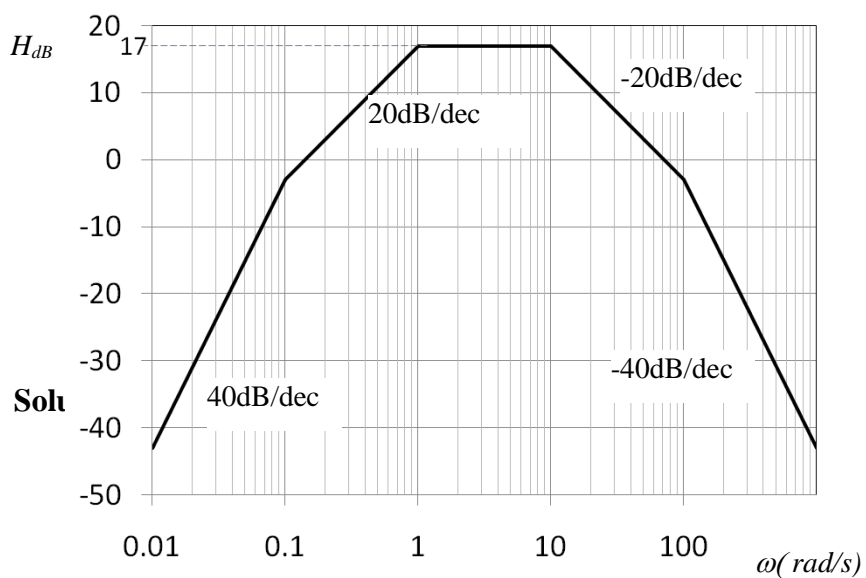2. Find the transfer function for the following Bode plot.



$$H(\omega) = \frac{A(j\omega)^2}{\left(\frac{1+j\omega}{0.1}\right)(1+j\omega)\left(\frac{1+j\omega}{10}\right)\left(\frac{1+j\omega}{100}\right)}$$

$$H(\omega=1) = 17 \text{ dB}$$

$$\Rightarrow 17 = 20 \log \left| \frac{A}{(1+j10)(1+j)(1+0.1j)(1+0.01j)} \right|$$


$$= 20 \log \left(\frac{A}{10 \times 1 \times 1 \times 1} \right)$$

$$\Rightarrow 20 \log A = 17 + 20 = 37$$

$$\therefore A = 10^{37/20} = 70.79$$

$$\therefore H(\omega) = \frac{70.79(j\omega)^2}{(j\omega+0.1)(j\omega+1)(j\omega+10)(j\omega+100)}$$

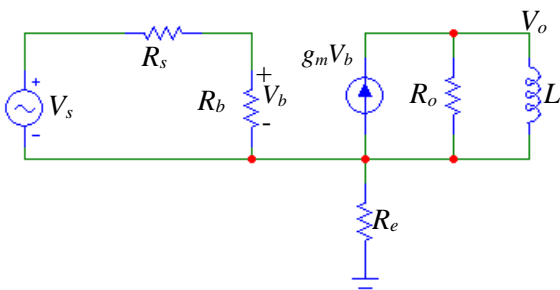3. Determine the transfer function (V_o/V_s) for the following circuit.



Solution:

$$V_b = \frac{R_b V_s}{R_b + R_s}$$

$$I_b = \frac{V_b}{R_b} = \frac{V_s}{R_s + R_b}$$

Applying nodal

$$-gmV_b + \frac{V_0}{R_0} + \frac{V_0}{j\omega L} = 0$$

$$V_0 \left(\frac{1}{R_0} + \frac{1}{j\omega L} \right) = gmV_b$$


$$\Rightarrow V_0 \left(\frac{j\omega L + R_0}{j\omega L R_0} \right) = gmV_b$$

$$\Rightarrow V_0 = \frac{j\omega gm R_0 L}{j\omega L + R_0} \cdot V_b$$

$$\Rightarrow V_0 = \frac{j\omega L R_0 gm}{j\omega L + R_0} \cdot \frac{R_b V_s}{R_b + R_s}$$

$$\therefore \frac{V_0}{V_s} = \frac{j\omega gm R_0 R_b L}{(j\omega L + R_0)(R_b + R_s)}$$

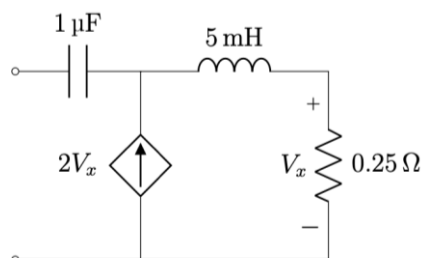
4. Determine the resonant frequency for circuit shown below.



Solution:

Calculate the Z_{eq} of the circuit and make imaginary part to be zero to calculate the resonant frequency.

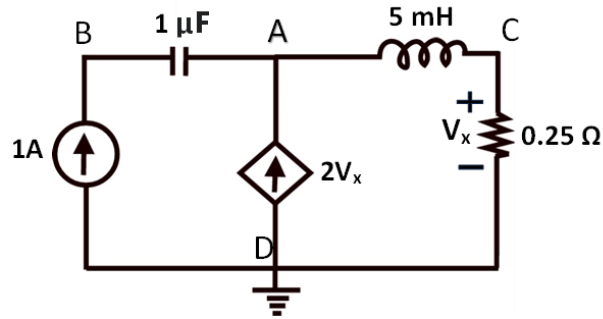To calculate the impedance, we connect a current source.



Applying KCL at node A:

$$\begin{aligned}
 -1 - 2V_x + \frac{V_x}{0.25} &= 0 \\
 \Rightarrow -1 - 2V_x + 4V_x &= 0 \\
 \Rightarrow 2V_x &= 1 \\
 \Rightarrow V_x &= 0.5V
 \end{aligned}$$

Let say the voltage drop across the current source is V_1 .

Then applying KVL in BACDB,

$$\begin{aligned}
 -V_1 + \frac{1}{j\omega C} \cdot 1 + j\omega L(1 + 2V_x) + V_x &= 0 \\
 \Rightarrow V_1 &= \frac{1}{j\omega C} + j\omega L(1 + 2 \times 0.5) + 0.5 \\
 \Rightarrow V_1 &= \frac{1}{j\omega C} + j\omega L \times 2 + 0.5
 \end{aligned}$$

Hence, the impedance is

$$Z_{eq} = \frac{V_1}{1} = \frac{1}{j\omega C} + j\omega L \times 2 + 0.5.$$

At resonance $\text{Im}(Z_{eq}) = 0$


$$\begin{aligned}
 -\frac{1}{\omega_0 C} + 2\omega_0 L &= 0 \\
 \Rightarrow \frac{1}{\omega_0 C} &= 2\omega_0 L
 \end{aligned}$$

$$\omega_0 = \frac{1}{\sqrt{2}LC} = \frac{1}{\sqrt{2} \cdot 5 \cdot 10^{-3} \cdot 10^{-6}}$$

$$\omega_0 = 10^4 \text{ rad/sec}$$



$$f_0 = \frac{\omega_0}{2\pi} = \frac{10^4}{2\pi} = 1591.5 \text{ Hz}$$

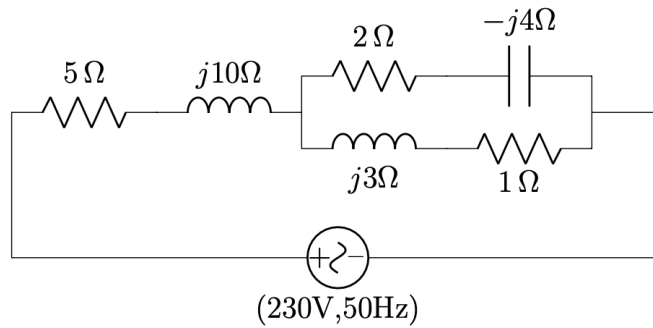8. Find the average power and reactive power, in the network shown in figure below



Solution

The resultant circuit is

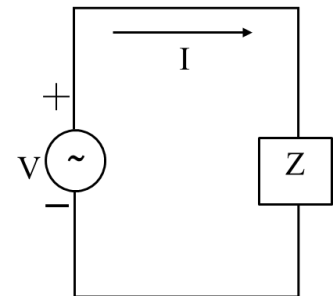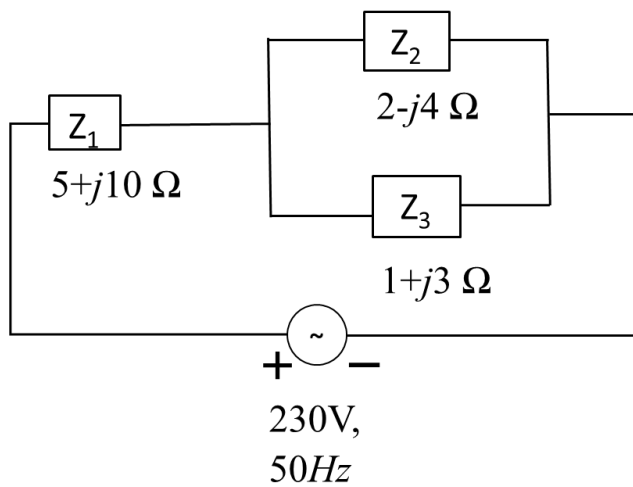

Here,

$$\begin{aligned}
 Z &= Z_1 + (Z_2 \parallel Z_3) = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} \\
 &= 5 + j10 + \frac{(2 - j4)(1 + j3)}{2 - j4 + 1 + j3} \\
 &= 5 + j10 + \frac{14 + j2}{3 - j} = 5 + 10j + \frac{(14 + 2j)(3 + j)}{10} \\
 &= 5 + 10j + \frac{1}{10}(42 + 6j + 14j - 2) \\
 &= 5 + 10j + 4 + 2j = 9 + j12 \Omega
 \end{aligned}$$

& $V_{rms} = 230 \text{ Volts.}$

Then

$$\begin{aligned}
 I_{rms} &= \frac{V_{rms}}{Z} = \frac{230}{9 + j12} = \frac{230(9 - j12)}{225} = 9.2 - j12.27 = 15.33 \angle -53.13^\circ \text{ A} \\
 \Rightarrow \theta &= 53.13^\circ
 \end{aligned}$$

\therefore Average Power,

$$P_{avg} = V_{rms} I_{rms} \cos \theta = 230 * 15.33 * \cos(53.13^\circ) = 2115.54 \text{ W}$$


∴ Reactive Power,

$$P_{react} = V_{rms} I_{rms} \sin \theta = 230 * 15.33 * \sin(53.13^\circ) = 2820.72 \text{ W}$$

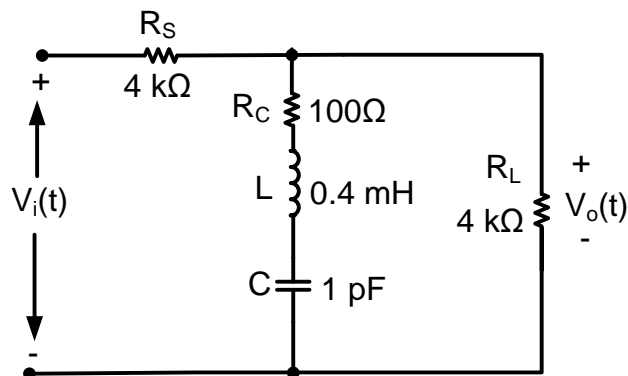
9. A band-reject (notch) filter is shown below. Derive the expression of its transfer function H in the form

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = K \left[\frac{(1 + ja)}{(1 + jb)} \right].$$

Find out the expressions for the coefficients K, a and b. Determine the magnitudes of this transfer function at very low and very high frequencies from physical arguments. What is the resonance frequency of this circuit? What is the magnitude of the transfer function at this resonance frequency? Also calculate the level of rejection (in dB) at resonance frequency.



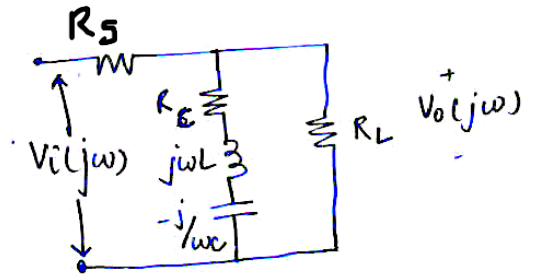Converting to phasor domain,
let the equivalent impedance
of the two parallel branches
be Z_1 .



$$\therefore Z_1 = R_L \parallel \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]$$

$$\Rightarrow Z_1 = \frac{R_L \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L + R_C + j \left(\omega L - \frac{1}{\omega C} \right)}$$

Applying voltage division,

$$V_o(j\omega) = \frac{Z_1 \times V_i(j\omega)}{Z_1 + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_1}{Z_1 + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L + R_C + j \left(\omega L - \frac{1}{\omega C} \right) + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C + j R_L \left(\omega L - \frac{1}{\omega C} \right)}{R_L R_C + j R_L \left(\omega L - \frac{1}{\omega C} \right) + R_s R_L + R_s R_C + j R_s \left(\omega L - \frac{1}{\omega C} \right)}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C + j R_L \left(\omega L - \frac{1}{\omega C} \right)}{R_L R_C + R_S R_L + R_S R_C + j \left(\omega L - \frac{1}{\omega C} \right) (R_S + R_L)}$$

converting to the desired form,

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C \left[1 + \frac{j}{R_C} \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L R_C + R_S R_L + R_S R_C \left[1 + \frac{j (R_S + R_L)}{(R_L R_C + R_S R_L + R_S R_C)} \left(\omega L - \frac{1}{\omega C} \right) \right]}$$

$$\therefore K = \frac{R_L R_C}{R_L R_C + R_S R_L + R_S R_C}$$

Substituting the values of R_L, R_S, R_C , $K = \frac{1}{42}$

$$a = \frac{1}{R_C} \left(\omega L - \frac{1}{\omega C} \right), \quad b = \frac{(R_S + R_L) \left(\omega L - \frac{1}{\omega C} \right)}{(R_L R_C + R_S R_L + R_S R_C)}$$

For very low frequencies, $\omega \rightarrow 0$, $X_L \rightarrow 0$ and $X_C \rightarrow \infty$.
Therefore, the R-L-C branch is open circuited.

$$|H(j\omega)|_{\omega \rightarrow 0} = \frac{R_L}{R_L + R_S} = \frac{4k}{4k + 4k} = 0.5$$

for very high frequencies, $\omega \rightarrow \infty$, $X_L \rightarrow \infty$, $X_C \rightarrow 0$.
again, the R-L-C branch is open circuited.

$$\therefore |H(j\omega)|_{\omega \rightarrow \infty} = \frac{R_L}{R_S + R_L} = 0.5$$

For resonance, $\text{Im}[H(j\omega)] = 0$

$$\therefore K \left[\frac{1 + ja}{1 + jb} \times \frac{1 - jb}{1 - jb} \right] = K \left[\frac{1 - jb + ja + ab}{1 + b^2} \right] = K \left[\frac{1 + j(a-b) + ab}{1 + b^2} \right]$$

$$\Rightarrow a - b = 0$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{0.4 \times 10^{-3} \times 10^{-12}}} \text{ Hz}$$

$$f_r = 7.96 \text{ MHz}$$

$$|H(j\omega)|_{\omega=2\pi f_r} = k \left| \frac{1+ab}{1+b^2} \right|$$


Substituting values,
 $(a)_{f_r} = -0.08961$
 $(b)_{f_r} = -0.00189$

$$= \frac{1}{42} \left[\frac{1 + (-0.08961)(-0.00189)}{1 + (-0.00189)^2} \right]$$


$$= 23.809 \times 10^{-3}$$

$$\text{Rejection} = 20 \log_{10}(23.809 \times 10^{-3}) \text{ dB} = -32.465 \text{ dB}.$$

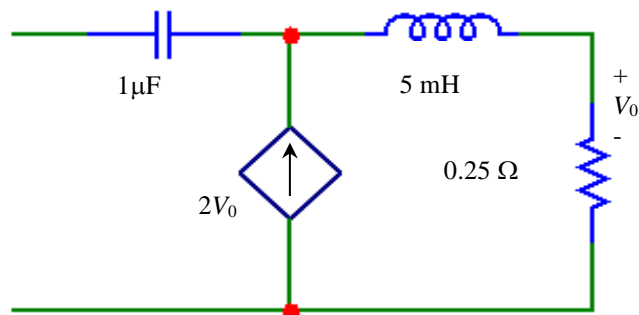10. Determine the resonant frequency of the following circuit



Solution:

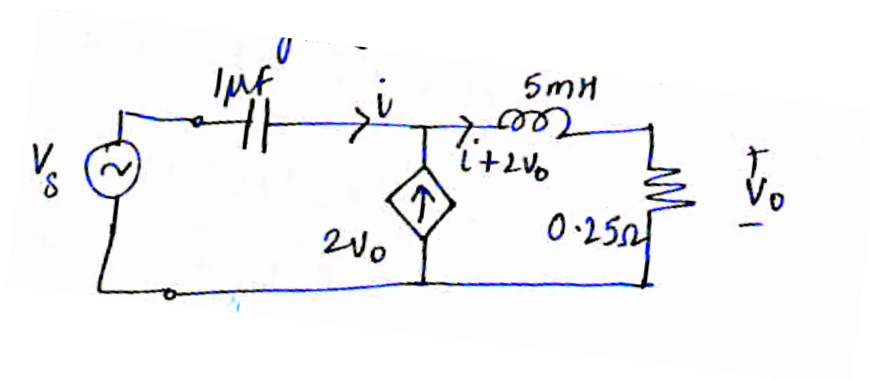


$$V_o = (i + 2V_o)0.25$$

$$\therefore V_o = 0.25i + 0.5V_o$$

$$\Rightarrow 0.5V_o = 0.25i$$

$$\text{or } \frac{V_o}{i} = \frac{0.25}{0.5} = \frac{1}{2}$$

Converting to phasor domain,

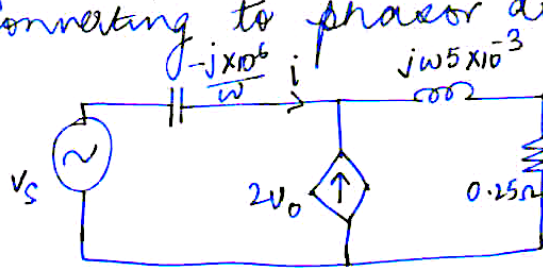

$$V_s + j \frac{10^6}{\omega} i - j\omega 5 \times 10^{-3} (i + 2V_o) - V_o = 0$$

$$\Rightarrow V_s + j \frac{10^6}{\omega} i - j\omega 5 \times 10^{-3} i - j\omega 10^{-2} V_o - V_o = 0$$

$$\Rightarrow V_s = (j\omega 5 \times 10^{-3} - j \frac{10^6}{\omega}) (2V_o) + j\omega 10^{-2} V_o + V_o$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{1}{1 + j(\omega \times 2 \times 10^{-2} - \frac{2 \times 10^6}{\omega})}$$

At resonance, $X_L = X_C$

$$\therefore \omega_r = 10^4 \text{ rad/sec}$$