

## ESC201 Introduction to Electronics Lab 6 Handout for Lab Experiments

### Characteristics of MOSFET and MOSFET-based Circuits

**Aim:** In this lab, you will observe the DC characteristics of MOSFET and MOSFET-based inverters. You will also extract the MOSFET parameters, e.g., threshold voltage ( $V_T$ ) and transconductance parameter ( $K_n$ ).

The simplest model for the current  $I_D$  of the NMOS will be  $I_D = 0$  for  $V_{GS} < V_T$ , and for  $V_{GS} > V_T$ , current in saturation is  $I_D = 0.5K_n(V_{GS} - V_T)^2$ , and current in linear region is  $I_D = K_n[V_{GS} - V_T - V_{DS}/2]V_{DS}$ .

You will be using the IC CD4007 (shown in Fig. P1a) which contains multiple n- and p-channel MOSFETs. The way an IC is mounted on a breadboard is shown in Fig. P1b so that no two pins of the IC are connected.

**Precautions:** MOSFETs are highly susceptible to damage through electrostatic discharge. Touch the ground wire of power supply to discharge static electricity from your body before handling MOSFET.

For most of the applications with CD4007, it is extremely important to connect pin 14 to the most positive supply of the circuit and pin 7 to the most negative supply of the circuit (or the ground) as shown in Fig. P1b.

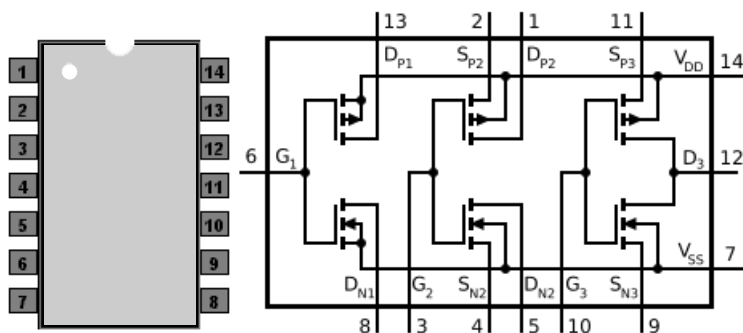


Figure P1a: CD4007 Pin Diagram

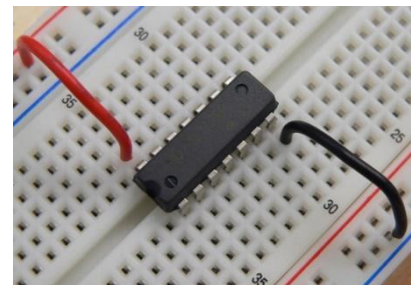


Figure P1b: CD4007 on Breadboard

#### Experiment 1: Observing the Output Characteristic of NMOS ( $3 \times 4 = 12$ marks)

- Wire the circuit shown in Fig. E1a with  $R_D = 1\text{ k}\Omega$ . The pin numbers for CD4007 are given in the figure.
- Using the FG, apply an ac triangular pulse of 1 kHz frequency with peak-to-peak voltage from 0 V to 5 V. Use the offset and amplitude knob of the FG to obtain the signal (you may need to check it using the DSO).
- Observe and trigger the waveforms properly in Normal mode before changing the display to XY mode.
- Rotate the potentiometer knob to vary  $V_{GS}$  and observe different  $I_D$  vs.  $V_{DS}$  characteristics for different  $V_{GS}$ .
- You can measure the corresponding value of  $V_{GS}$  using the DMM.
- The maximum range of  $V_{DS}$  for the circuit shown in Fig. E1a will lie on the load line as shown in Fig. E1b.

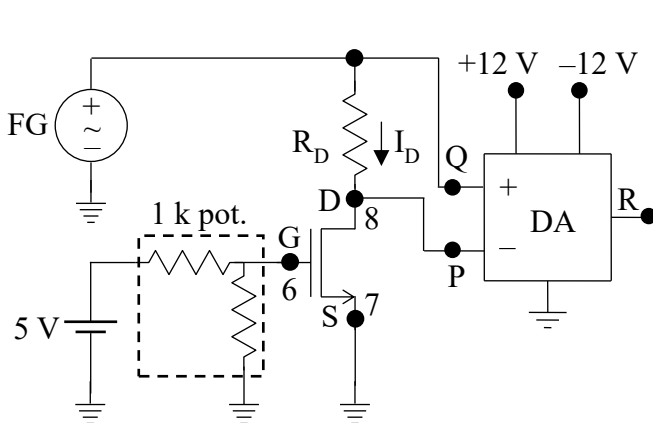


Figure E1a

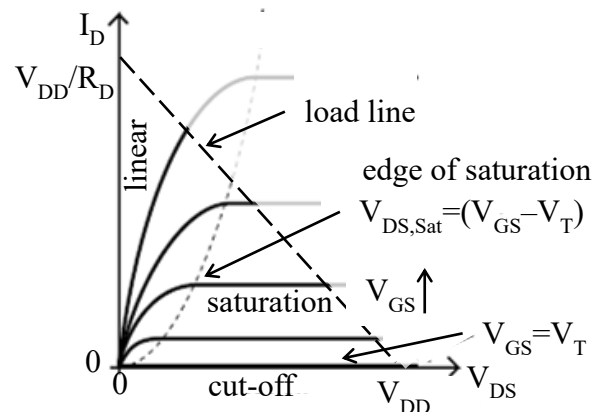


Figure E1b: Output Characteristic of NMOS

1. For  $R_D = 1\text{ k}\Omega$ , observe, measure and plot the  $I_D$  vs  $V_{DS}$  characteristics for  $V_{GS} = 0\text{ V}$ ,  $2.5\text{ V}$ ,  $5\text{ V}$ . Find approximately the threshold voltage ( $V_T$ ) by observing when  $I_D$  becomes almost negligible while changing  $V_{GS}$  using the 1k pot, and then, measuring the corresponding value of  $V_{GS}$  using the DMM.
2. Set  $V_{GS} = 2.5\text{ V}$  by rotating the potentiometer knob and find the value of  $V_{DS,\text{sat}}$  at the edge of saturation and the corresponding value of  $I_{D,\text{sat}}$  in the saturation region (but close to the edge of saturation). From the results obtained, find the threshold voltage ( $V_T$ ) and transconductance parameter ( $K_n$ ) of the NMOS.
3. Find the maximum value of  $V_{DS}$  for  $V_{GS} = 2.5\text{ V}$  and  $5\text{ V}$ . Also, find  $I_D$  in each case when  $V_{DS}$  has its maximum value. Plot the line from the obtained ( $I_D$ ,  $V_{DS}$ ) data and find the intercept to both I and V axes.
4. Put  $R_D = 100\text{ }\Omega$  and repeat step 3 above. Observe, measure and write down the changes along with a plot. Note that the current-to-voltage conversion will be different because of a different resistance value used.

### Experiment 2: Observing the Load-line for NMOS Inverter ( $3 \times 2 = 6$ marks)

- Set up the circuit shown in Fig. E2a with  $R_D = 1\text{ k}\Omega$ . The pin numbers for CD4007 are given in the figure.
- Using the FG, apply an ac triangular pulse of  $1\text{ kHz}$  frequency with peak-to-peak voltage from  $0\text{ V}$  to  $5\text{ V}$ . Use the offset and amplitude knob of the FG to obtain the signal (you may need to check it using the DSO).
- Connect CH-1 to the drain terminal of the NMOS and CH-2 to the output of the DA.
- Observe and trigger the waveforms properly in Normal mode before changing the display to XY mode.

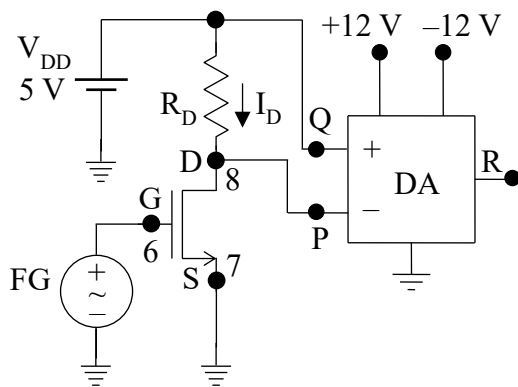


Figure E2a

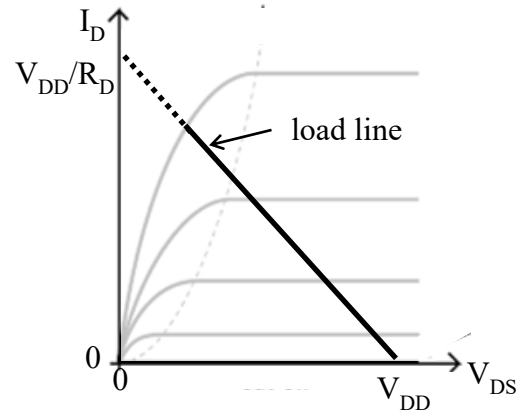


Figure E2b: Load-line for NMOS Inverter

1. For  $R_D = 1\text{ k}\Omega$ , observe the load-line on the DSO. Find two points on the load line, measure the current and voltage values at those two points. Plot the entire load line and find the intercept to both I and V axes. Compare your result with that obtained in part 3 of experiment 1 above and comment.
2. Put  $R_D = 100\text{ }\Omega$  and repeat the step above. Observe, measure and write down the changes in the load line along with the plot of it. Compare your result with that in part 4 of experiment 1 above and comment.

### Experiment 3: Observing the Transfer Characteristic of NMOS ( $3 \times 2 = 6$ marks)

- Set up the circuit of Fig. E2a with  $R_D = 100\text{ }\Omega$ . The pin numbers for CD4007 are given in the figure.
  - Using the FG, apply an ac triangular pulse of  $1\text{ kHz}$  frequency with peak-to-peak voltage from  $0\text{ V}$  to  $5\text{ V}$ . Use the offset and amplitude knob of the FG to obtain the signal (you may need to check it using the DSO).
  - Observe and trigger the waveforms properly in Normal mode before changing the display to XY mode.
1. Observe, measure and plot the  $I_D$  vs  $V_{GS}$  characteristics. Using the cursor, measure the value of the current  $I_D$  for  $V_{GS} = 0$ . Also, measure the value of threshold voltage ( $V_T$ ) from the  $I_D$  vs  $V_{GS}$  characteristics.
  2. Check if the NMOS is in the saturation region (i.e., the quadratic part of  $I_D$  vs  $V_{GS}$  characteristic) or not for  $V_{GS} = 2.5\text{ V}$ . Measure the current  $I_D$  for  $V_{GS} = 2.5\text{ V}$ , and calculate the value of the transconductance parameter  $K_n$ . Compare these results with those obtained in part 2 of experiment 1, and comment.

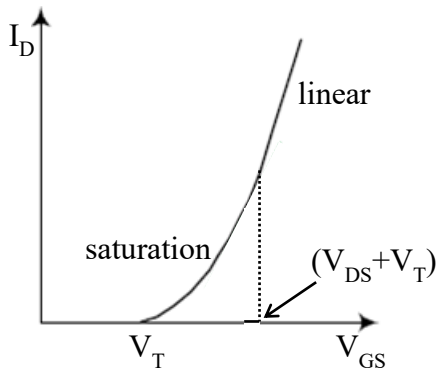


Figure E3: Transfer Characteristic of NMOS

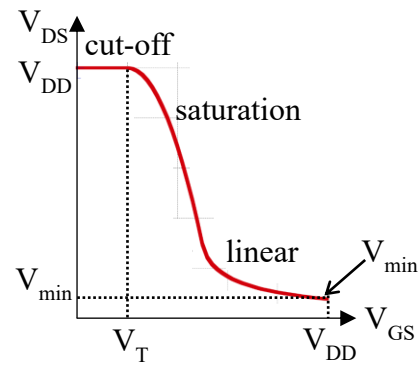


Figure E4: VTC of NMOS Inverter

**Experiment 4: Observing the VTC of an NMOS based Circuit ( $3 \times 2 = 6$  marks)**

- Set up the circuit of Fig. E2a with  $R_D = 1 \text{ k}\Omega$ . The pin numbers for CD4007 are given in the figure.
  - Connect CH-1 to the FG output (connected to the gate of the NMOS) to observe  $V_{GS}$  and CH-2 to the drain of the NMOS to observe  $V_{DS}$ .
  - Using the FG, apply an ac triangular pulse of 100 Hz frequency and peak-to-peak voltage from 0 V to 5 V. Use the offset and amplitude knob of the FG to obtain the signal (you may check it using the DSO CH-1).
  - Observe and trigger the waveforms properly in Normal mode before changing the display to XY mode.
- For  $R_D = 1 \text{ k}\Omega$ , observe, measure and plot the VTC (similar to that shown in Fig. E4). Also, measure the output voltage ( $V_{min}$ ) for  $V_{GS} = 5 \text{ V}$ , and write it down. From the data, calculate the value of the threshold voltage  $V_T$  and the transconductance parameter  $K_n$ . Compare these results with those obtained before.
  - Now, change the frequency of the input signal from 100 Hz to 100 kHz in multiples of 10, and observe how the VTC is changing and plot them. Note down if there is any hysteresis in the VTC, and comment.

**Experiment 5: Functionality of the NMOS based Circuit ( $2 \times 5 = 10$  marks)**

Now, set up the circuit of Fig. E2a with  $R_D = 10 \text{ k}\Omega$ . Using the FG, apply an ac triangular pulse of 100 Hz frequency and peak-to-peak voltage from 0 V to 5 V.

- Observe, measure and plot the VTC. Note down the changes you observe in the VTC from that obtained in previous part. Measure the value of the output voltage ( $V_{min}$ ) for  $V_{GS} = 5 \text{ V}$  and note it down.
- Calculate the value of  $V_{GS}$  at the edge of saturation for the NMOS (use the  $K_n$  and  $V_T$  values which you found earlier for this calculation). Find the gain of the circuit from the VTC near the edge of saturation (i.e., near the value of  $V_{GS}$  that you calculated). Choose two points on the VTC near the edge of saturation and measure accurately the voltages at these two points on the VTC using cursor. You may need to zoom in and adjust the scale. From these two points, calculate the slope which will give the gain at that point.

Now, using the FG, apply an ac square pulse of 1 kHz frequency with peak-to-peak voltage from 0 V to 5 V and duty cycle of 50%. Use the offset and amplitude knob of the FG to obtain the signal.

- Check the functionality of the NMOS circuit by observing both the input and the output waveforms on the DSO in the Normal mode. Measure and plot both the input and the output waveforms.
- Now connect CH-1 to the output of the DA and observe  $I_D$ . Measure and plot the waveforms for both  $V_{DS}$  and  $I_D$  (after proper conversion from voltage to current).
- Using the Multiply option from the Math function, find the instantaneous power as well as the average power dissipated across the NMOS, and write it down.