

ESC201: INTRODUCTION TO ELECTRONICS


MODULE 1: CIRCUIT ANALYSIS





Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur

Re-cap

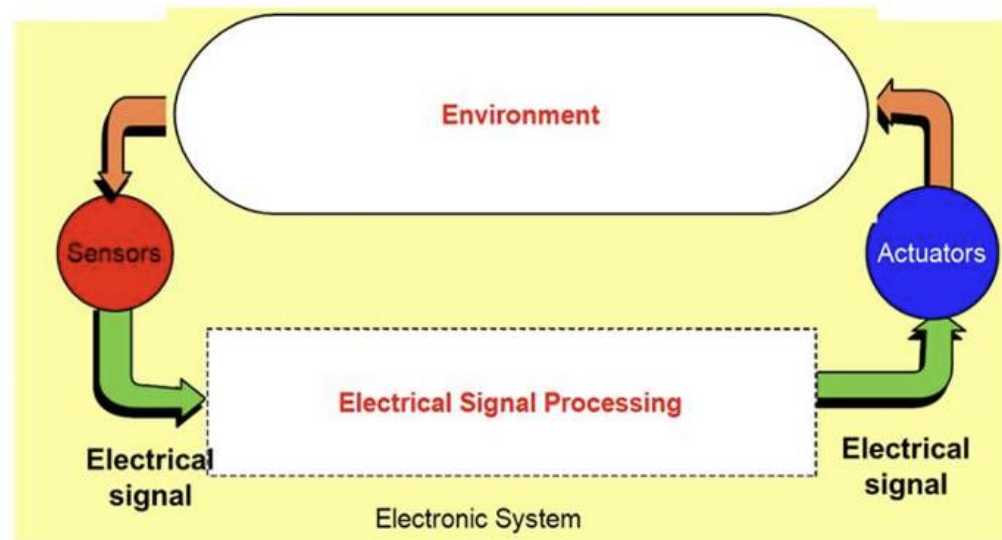
- Why electronics?
- Easily available electrical energy can be controlled precisely with electronics.
- 'Imagination' is the limit!
- Can solve problems in other domains: make them smart!!.



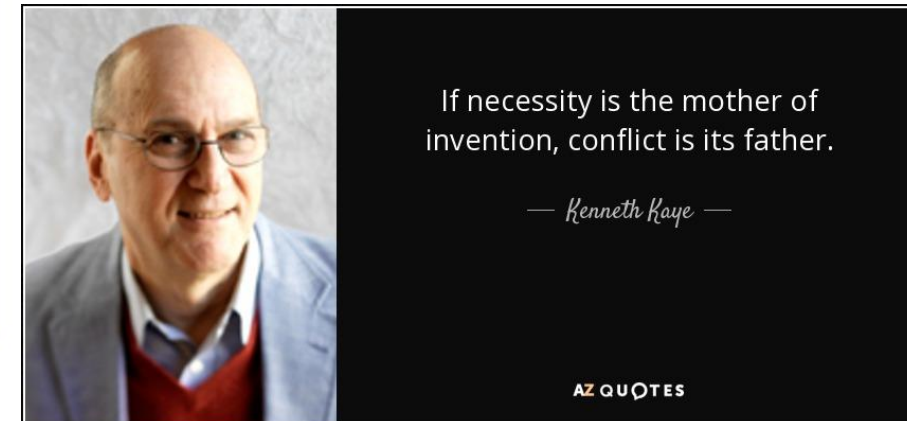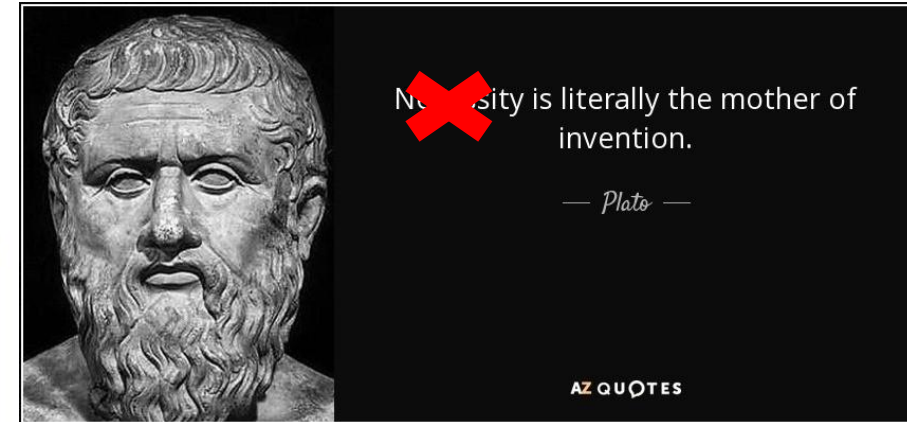Solve Problem by transforming them
to an electronics problem



Why ESC201?

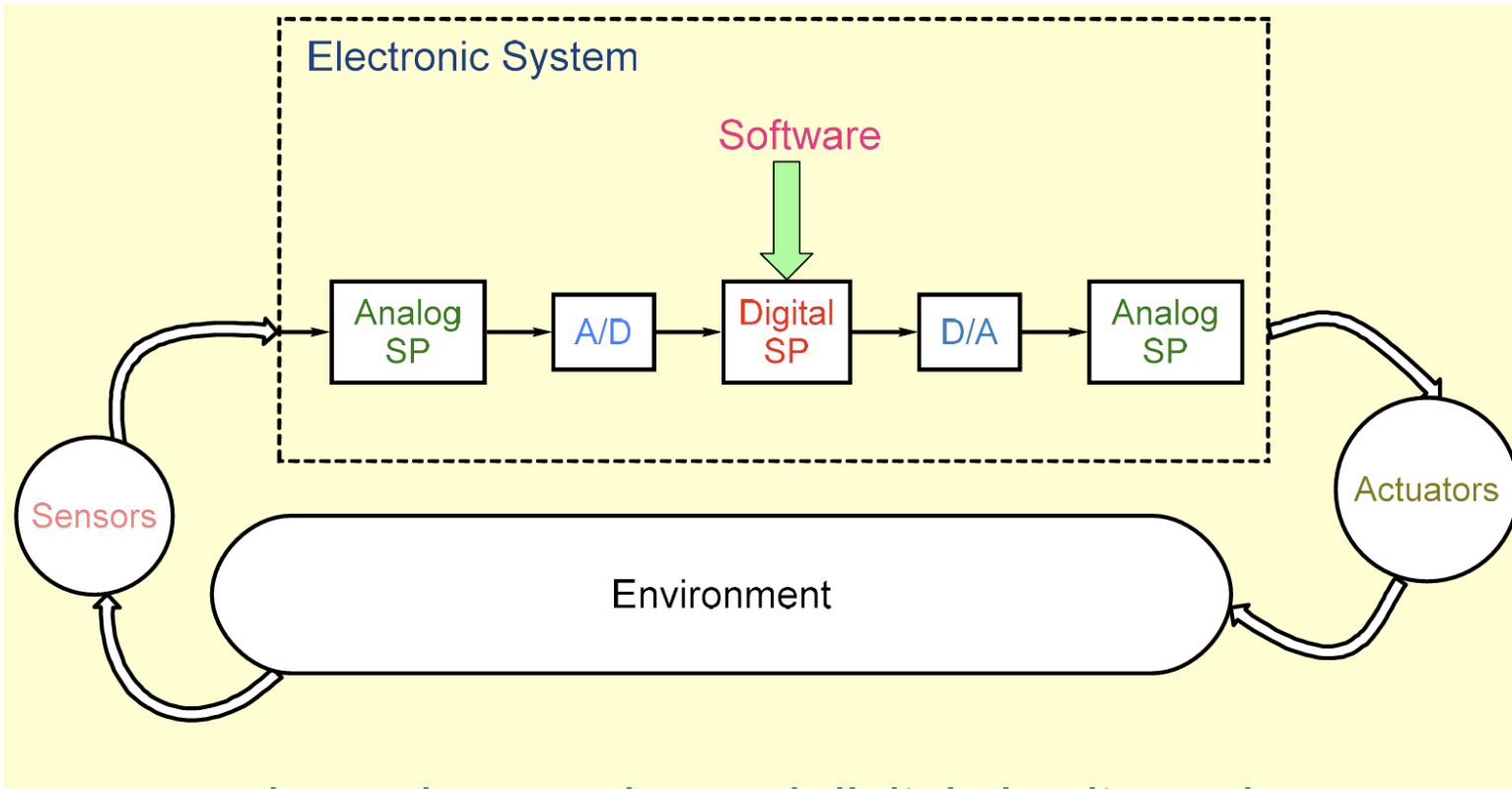

Learn how analog and digital circuits work

Tools for circuit Analysis

- ☐ Fundamentals of electrical circuits--3
- ☐ Transient Analysis of RLC Circuits--2
- ☐ Sinusoidal Steady State Analysis--4

Analog Circuits

- ☐ Semiconductors, Diodes, Circuits-----3
- ☐ Transistors and Amplifiers---4
- ☐ Operational Amplifier based Analog circuits -4

Digital Circuits

- ☐ Logic gates, Combinational circuits ---4
- ☐ Flip-flops, Sequential Circuit---4
- ☐ Data Converters----3

Charge

Unit of electric charge: Coulomb

$$1 \text{ C} = 1 \text{ A} \times 1 \text{ s}$$

Common symbols: q or Q

An electronic charge: $-1.6 \times 10^{-19} \text{ C}$

Electron carries negative charge

Proton carries positive charge

Negative charge carriers:

- electrons, negative ions, ...

Positive charge carriers:

- positive ions, holes (absence of electrons), ...

Charles-Augustin de Coulomb
(14 June 1736 – 23 August 1806)




Wikipedia

Current

- The time rate of flow of electrical charge
- Unit: **ampere** (A) → which is coulomb per second (C/s)
- Ampere is one of the seven basic SI units
- Popular symbol is i or I

$$i(t) = \frac{dq(t)}{dt}$$

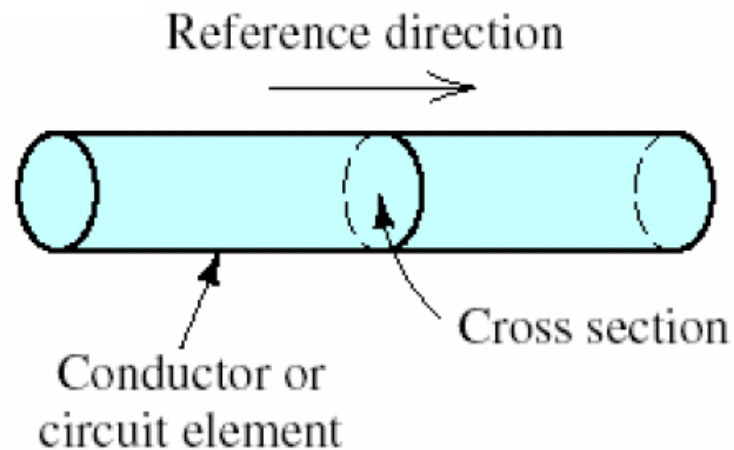

André-Marie Ampère
1775-1836




commons.wikimedia.org

Electrical Current

Flow of electrons through a wire or other electrical conductor gives rise to current

- Electrons are negatively charged particles

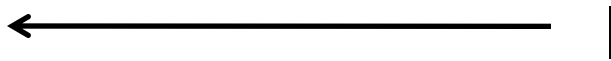The charge per electron is **$-1.602 \times 10^{-19} \text{ C}$**




10^{16} electrons flow per second

How much current flows? $i(t) = \frac{dq(t)}{dt}$

$$I = \frac{Q}{t} = \frac{-1.6 \times 10^{-19} \times 10^{16}}{1} = -1.6 \times 10^{-3} \text{ A}$$

Electrical Current

Current has a magnitude and a direction

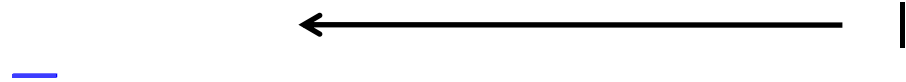


10^{16} electrons flow per second

Direction of current flow is opposite to direction of electron flow

Large number of electrons has to flow for appreciable current.



Exercise 1: For $q(t) = 2 - 2e^{-100t}$, for $t > 0$ and $q(t) = 0$ for $t < 0$, find $i(t)$.

Sign of current

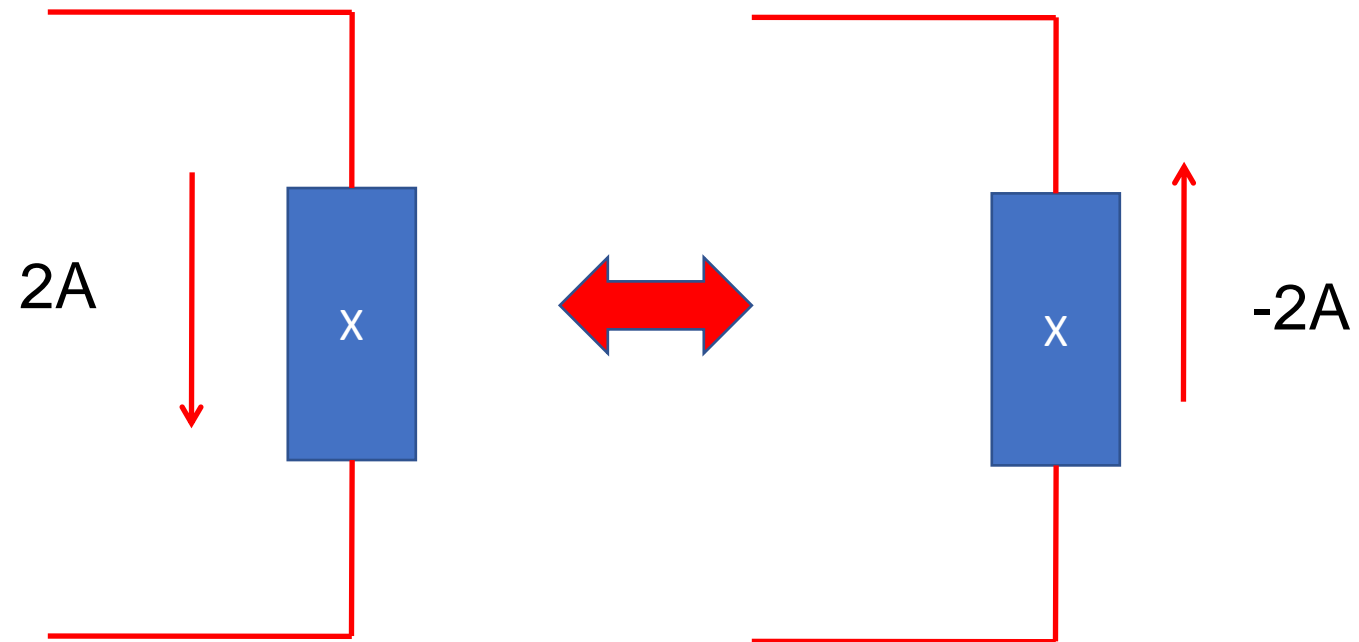

Direct Current (DC) & Alternating Current (AC)

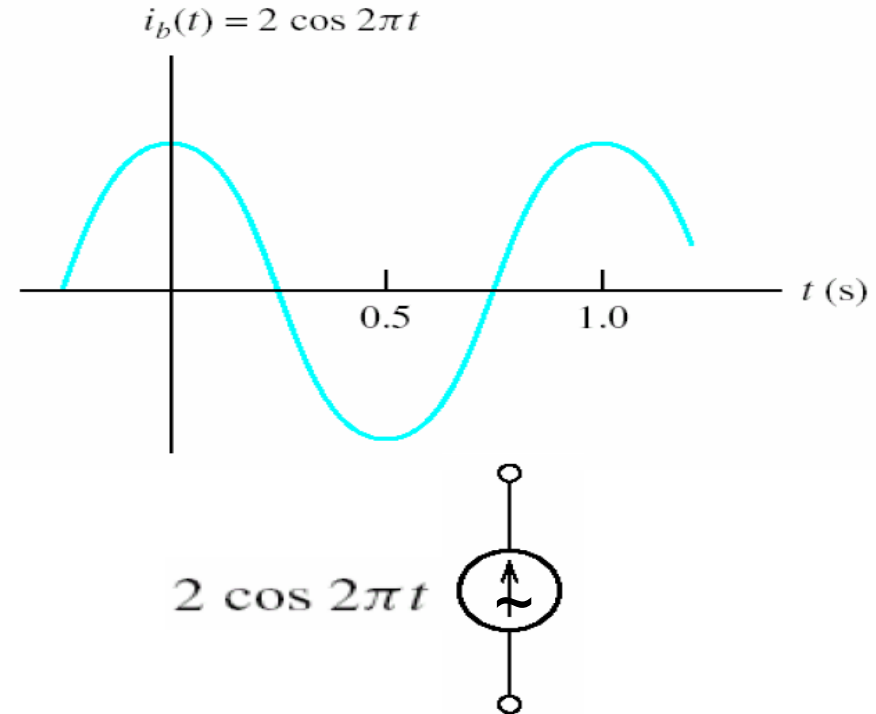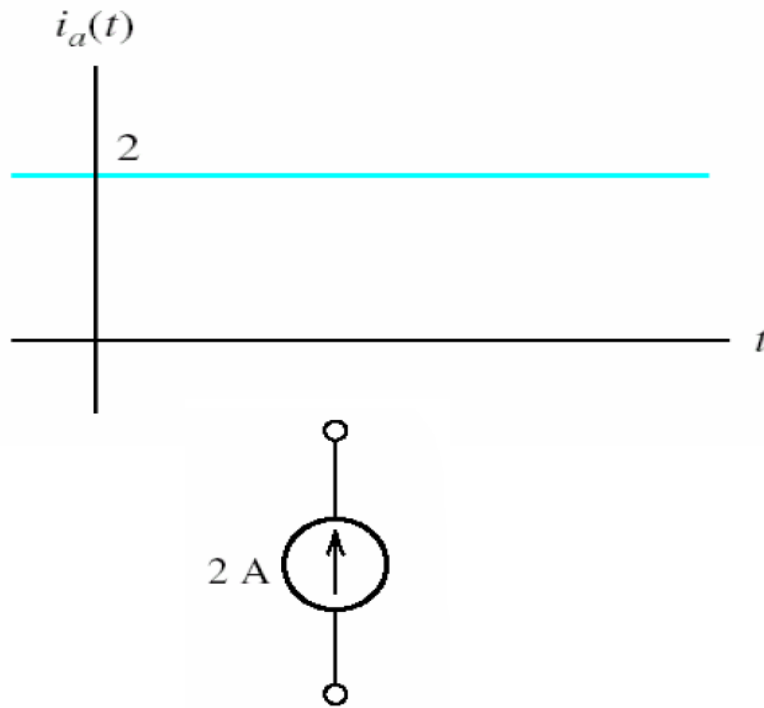
When current is constant with time, we say that we have direct current, abbreviated as DC.



On the other hand, a current that varies with time, reversing direction periodically, is called alternating current, abbreviated as **AC**


Voltage

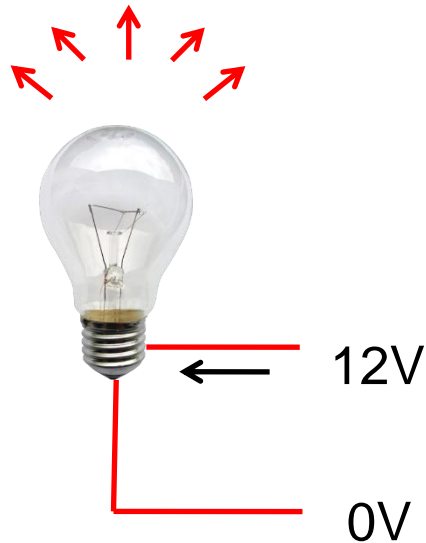- Voltage difference causes current to flow
- Potential difference for a unit positive charge between two points
 - Work done to move unit positive charge between two points
- Units of Voltage: volt (V)
- Popular symbol: v or V



Dr. Shubham Sahay ESC201

Light comes on

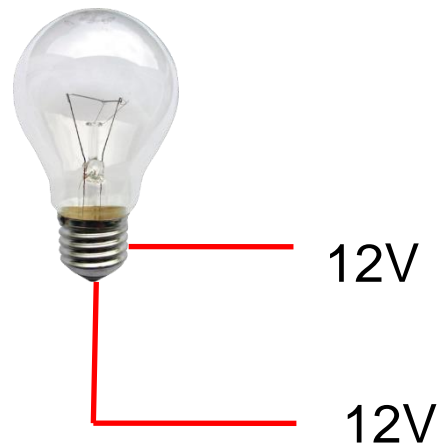


Light does not come on




Alessandro Giuseppe Antonio
Anastasio Volta 1745-1827

Voltage Is Relative

- In practice, it is ΔV that matters

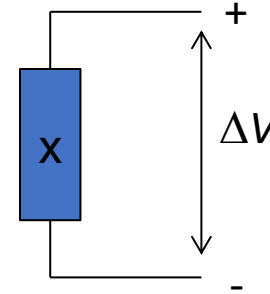


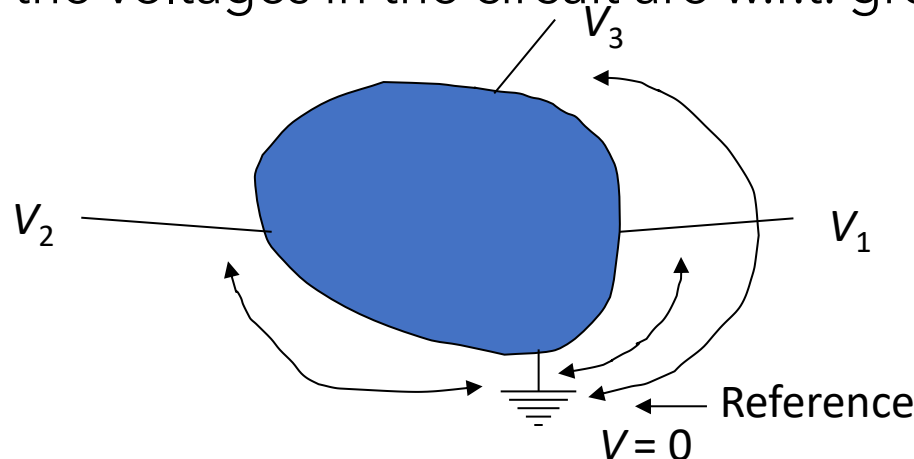- In a circuit (system), we choose a reference
 - Reference is called "ground"
 - Rest of the voltages in the circuit are w.r.t. ground




Water Analogy

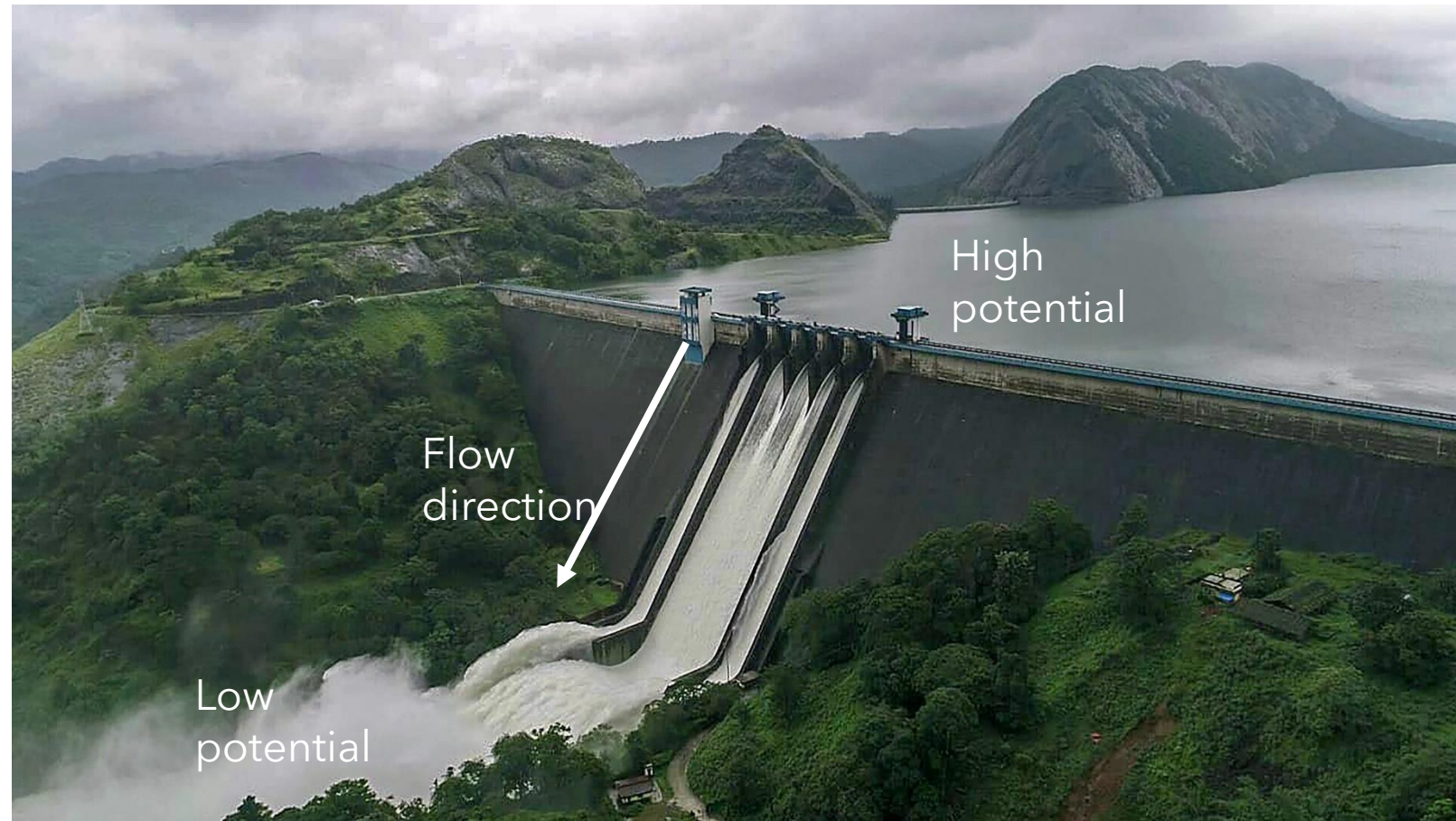
- Current flow from high voltage to low voltage
- (Potential) energy is consumed in the path
- Higher resistance: smaller flow



Voltage Sign

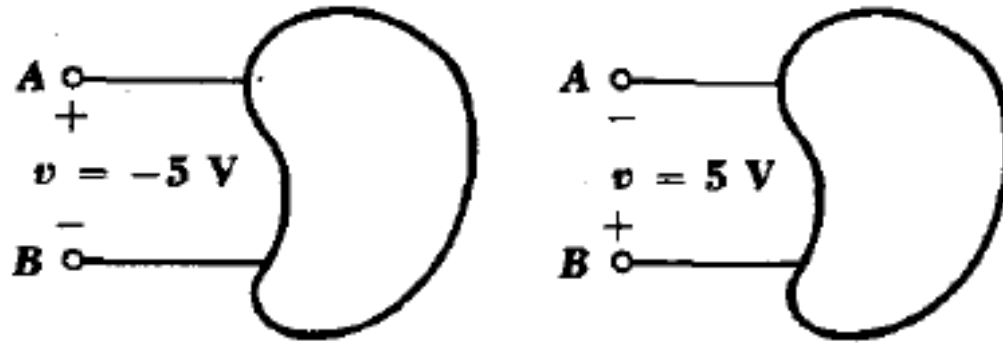

Terminal B is 5 V higher
than terminal A

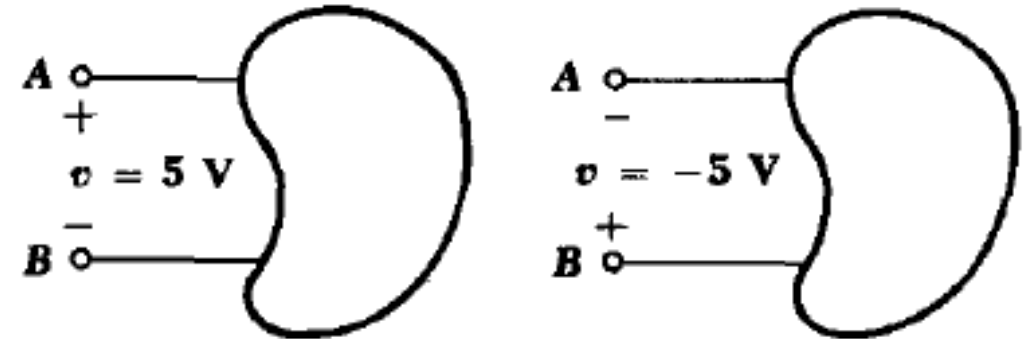


Terminal A is 5 V higher
than terminal B

DC and AC voltages





$$V_+ - V_- = 12V$$

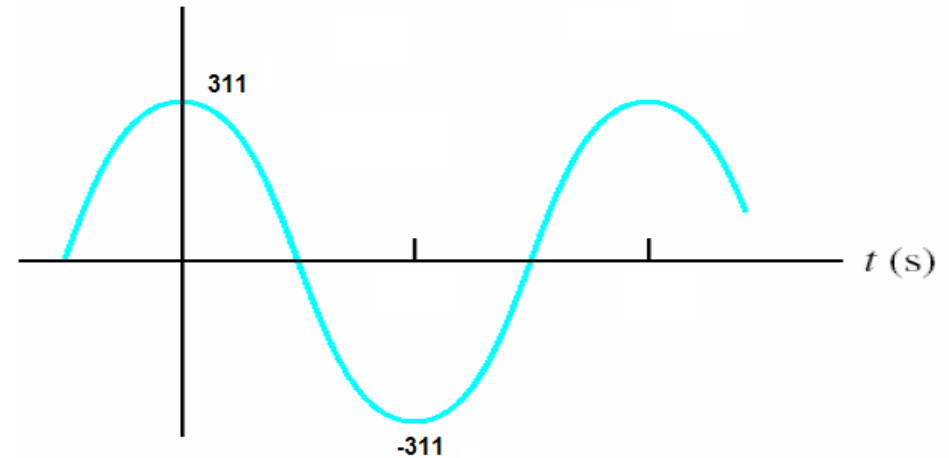

Electrical elements

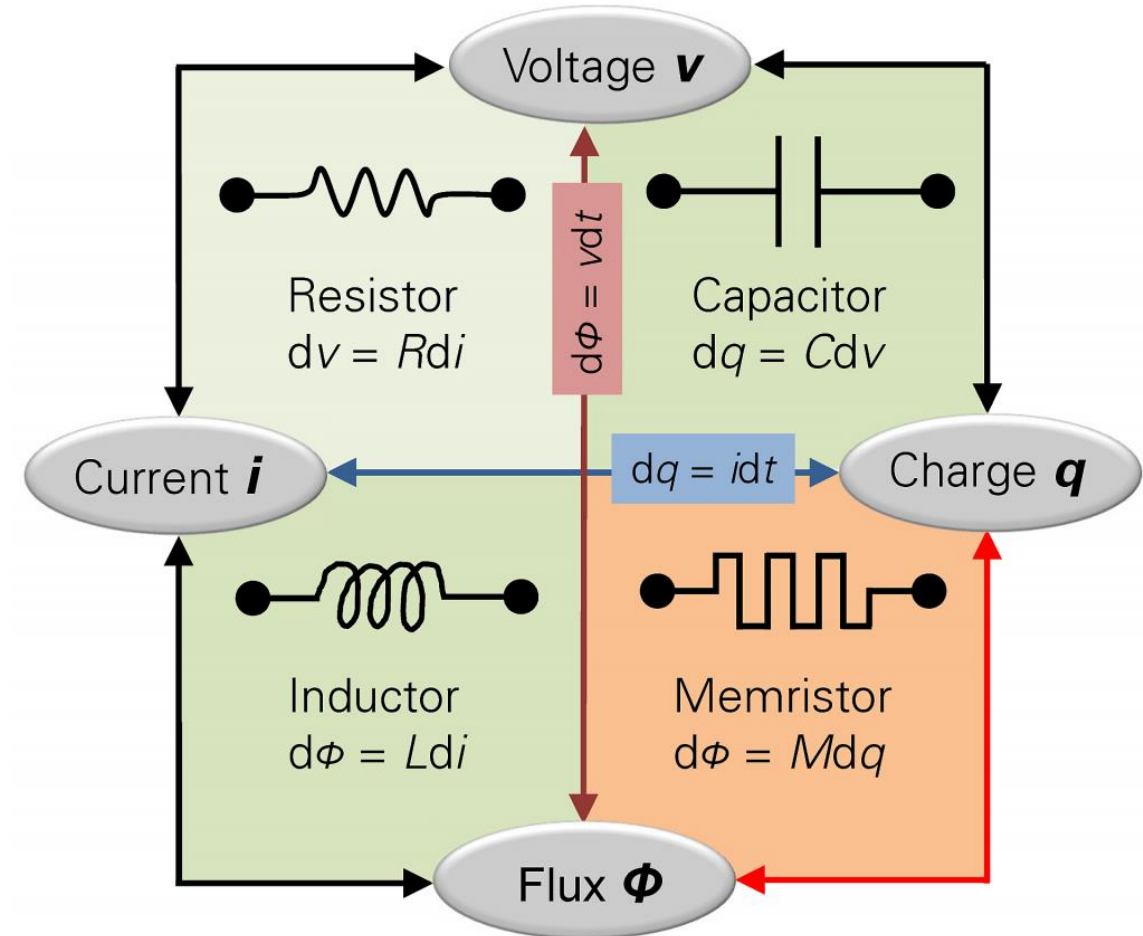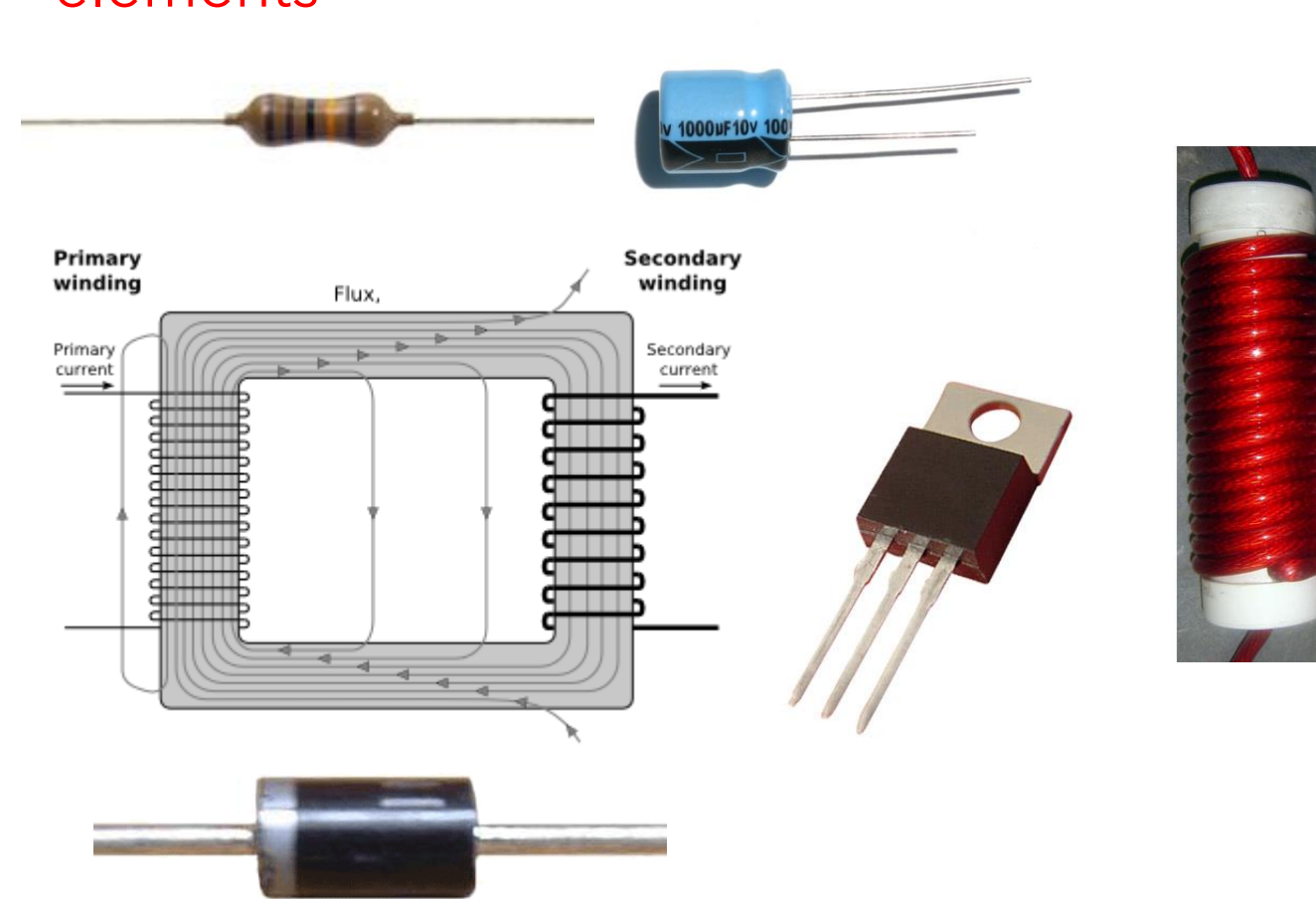Electrical Systems are made of Voltage sources, wires and a variety of **electrical elements**



A Circuit

A path for current to flow




<https://www.britannica.com/technology/electric-circuit>

Electrical systems with closed current paths are often called electrical circuits


Electric Shocks

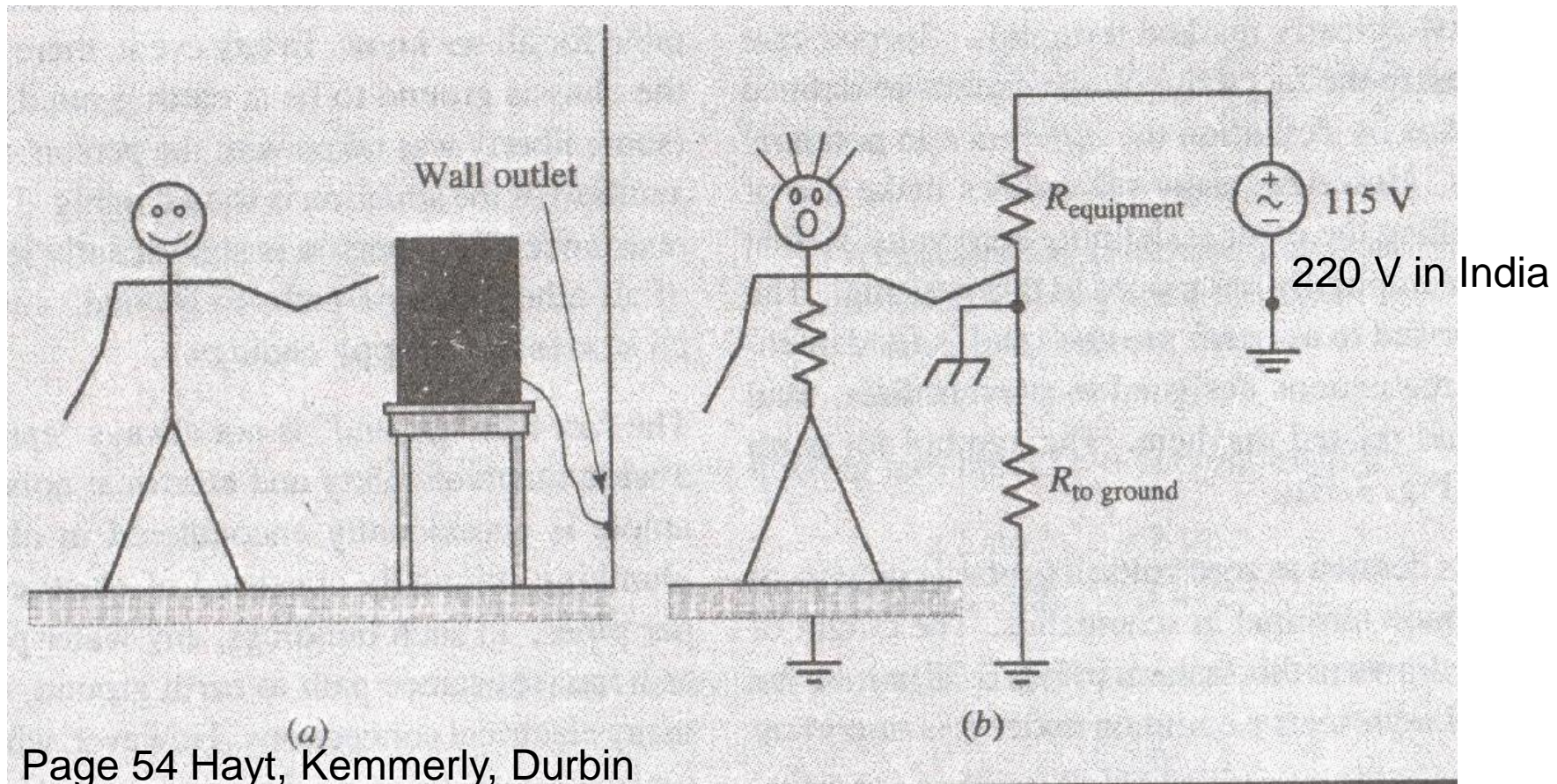Small currents (70–700 mA) can trigger fibrillation in the heart.
Larger currents will permanently damage the heart



Electrical Circuit

Analyze circuit

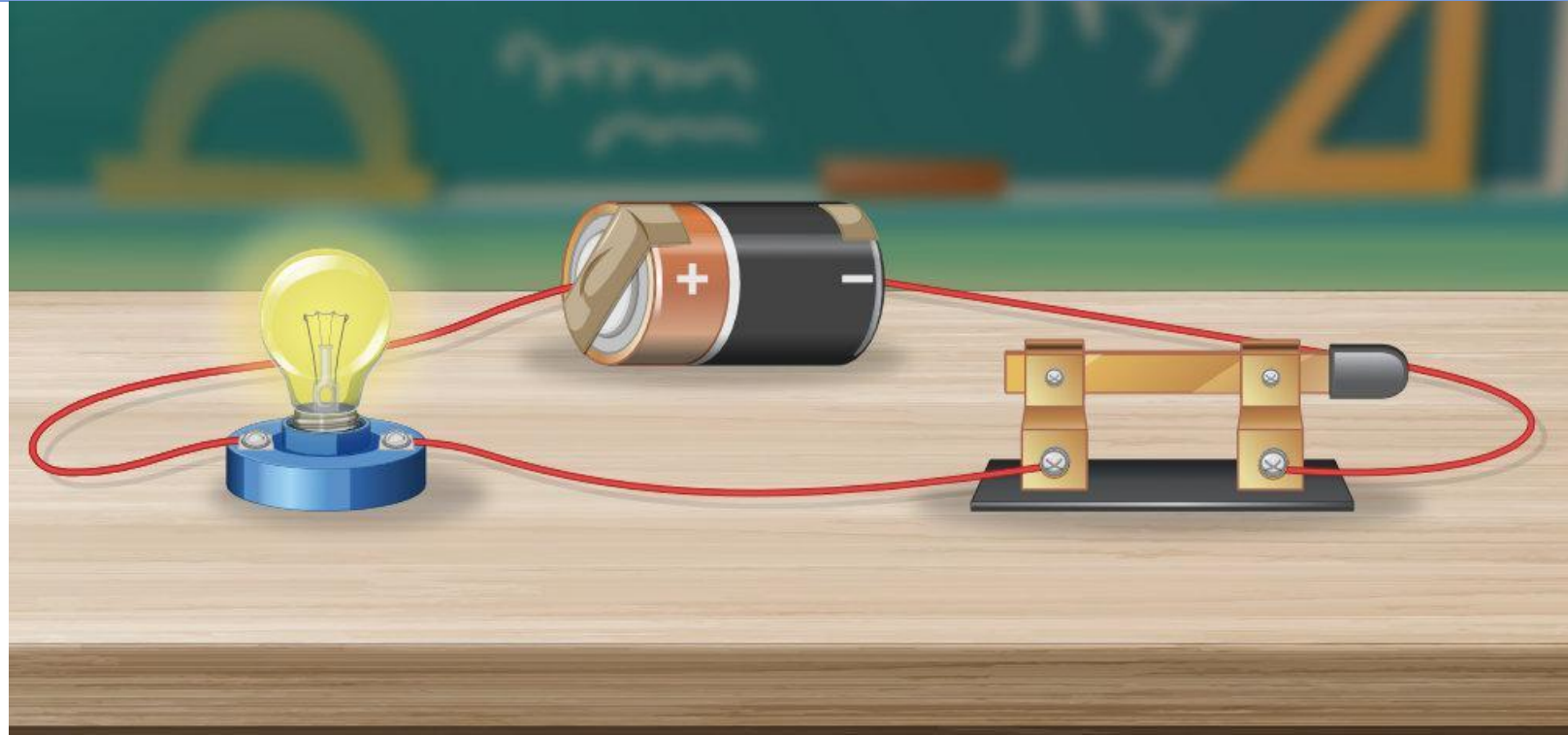

Questions


Compute current given voltage

Compute light intensity generated from bulb

How to solve these questions?


Back to Maxwell's Equations

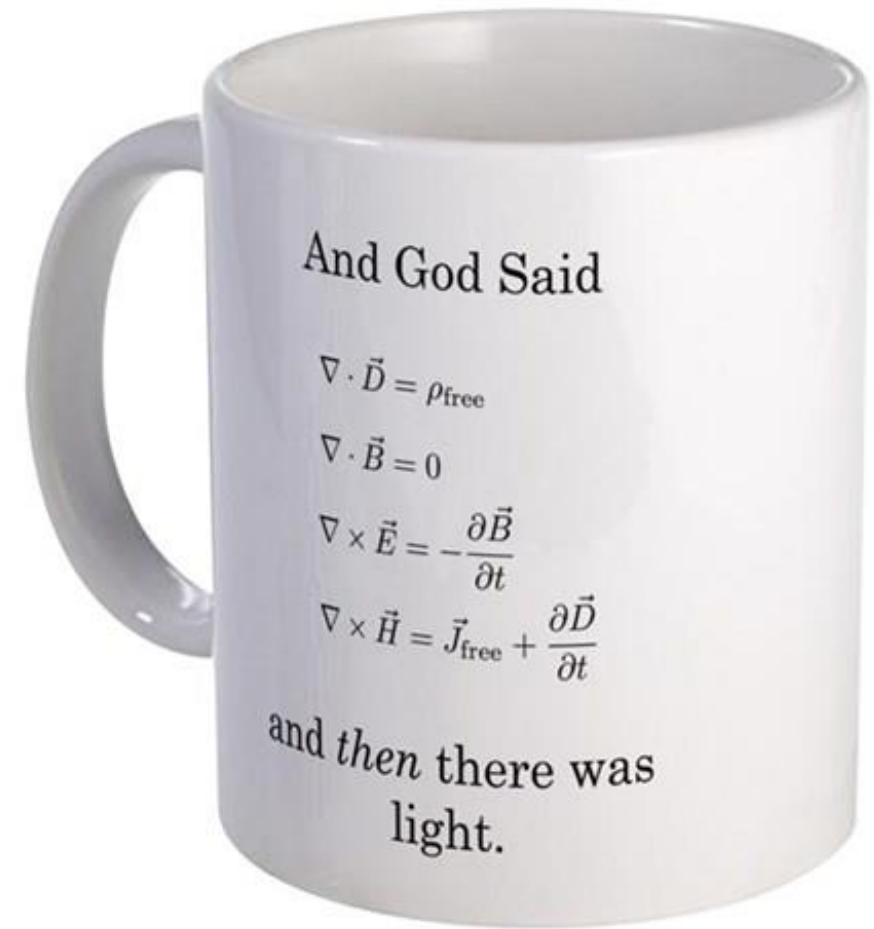- Should we write Maxwell's equations everytime
- Gainful employment of Maxwell's equations to build interesting systems
- Create an abstraction layer
 - Avoid dealing with Maxwell's eq



Abstraction

- Example: point mass abstraction

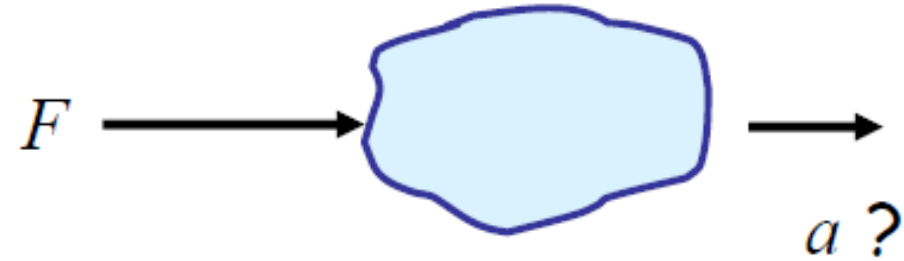

- What is the acceleration? $a = F/m$
- Ignoring the object's shape, rigidity, temperature
- Point-mass discretization or *lumping*
- Useful at all levels

Lumped Circuit Abstraction

1. $\nabla \cdot \mathbf{D} = \rho_v$
2. $\nabla \cdot \mathbf{B} = 0$
3. $\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t}$
4. $\nabla \times \mathbf{H} = \frac{\partial \mathbf{D}}{\partial t} + \mathbf{J}$



V	I
3	1
6	2
9	3
12	4


Ohm's Law

$$V = I * R$$

voltage in volts current in amps resistance in ohms


Bulb's behavior

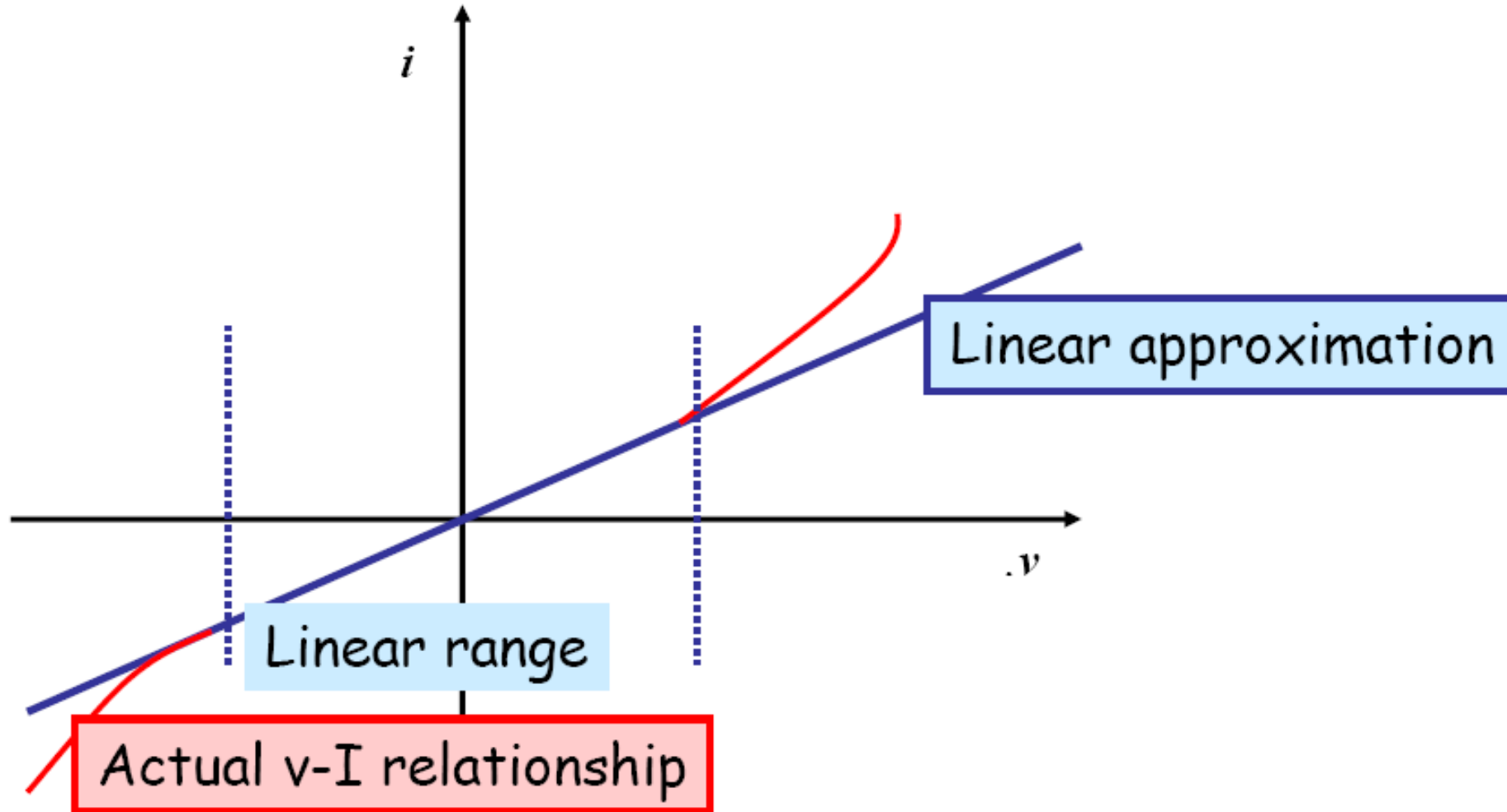Any electrical element which obeys ohms law can be modeled as a resistor




Can we model an electric bulb as a resistor?

Bulb's behavior

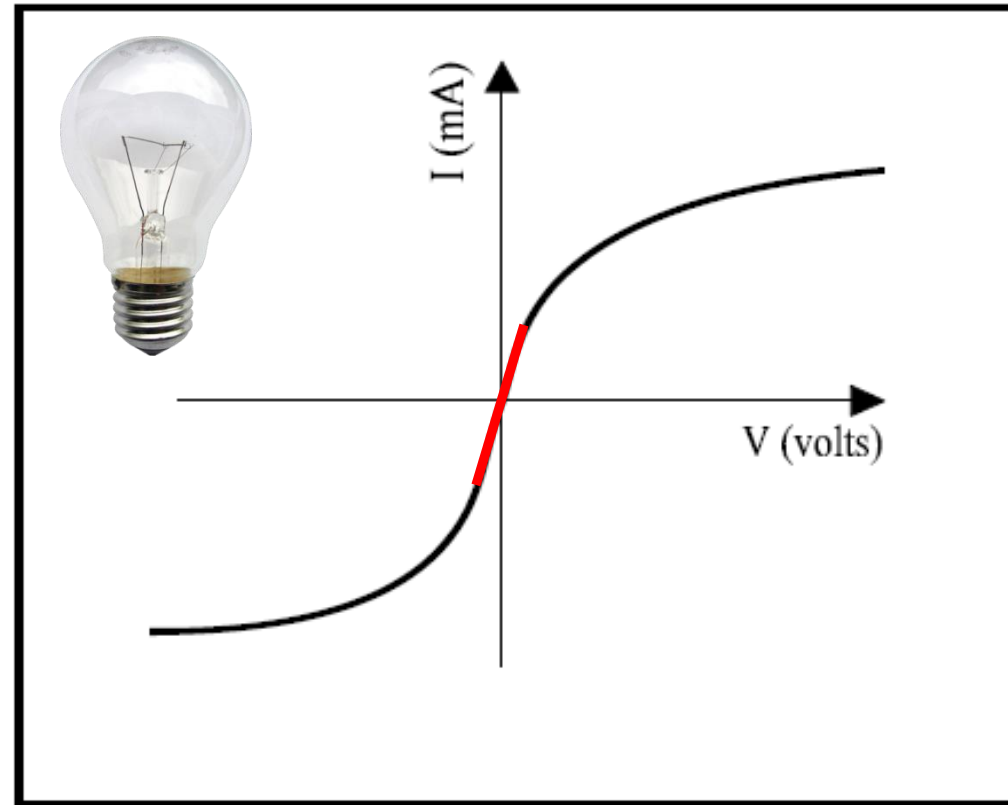

Even though characteristics are non-linear, over a certain range, the bulb can be thought of as a **resistor**

Resistor

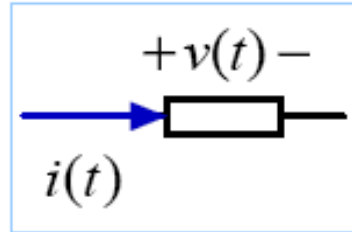

$$v(t) = R \times i(t)$$

Ohm's law

The constant, R , is called the resistance of the component and is measured in units of Ohm (Ω)

Standard Multiples of Ohm

$M\Omega$ Mega Ohm ($10^6 \Omega$)

$k\Omega$ Kilo Ohm ($10^3 \Omega$)




Georg Simon Ohm
1789-1854

Resistor Symbol:



Conductance

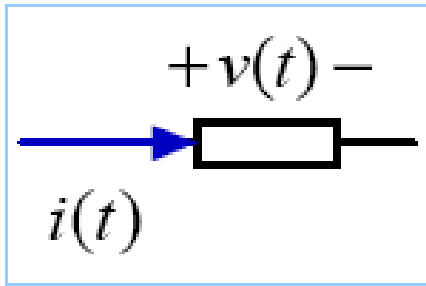

$$v(t) = R \times i(t)$$


$$i(t) = \frac{v(t)}{R} = G \times v(t)$$

$G = 1/R$ is called conductance and its unit is Siemens (S)



Ernst Werner von Siemens
1816-1892

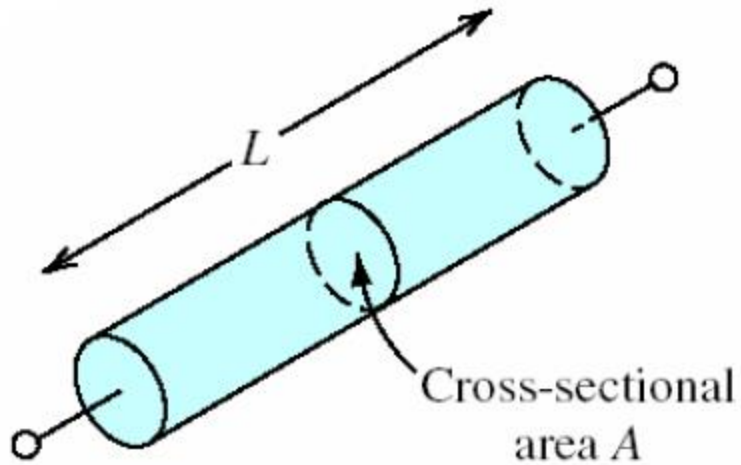Resistance Related to Physical Parameters



$$R = \rho \times \frac{L}{A}$$


Resistance is affected by the **dimensions** and **geometry** of the resistor as well as the **particular material** used

ρ is the resistivity of the material in ohm meters [$\Omega\cdot\text{m}$]

- Conductors (Aluminum, Carbon, Copper, Gold)
- Insulators (Glass, Teflon)
- Semiconductors (Silicon)

Short vs Open Circuit


Two special resistor values

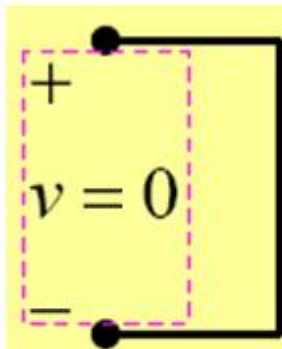

Short
Circuit

$$R = 0$$

$$G = \infty$$

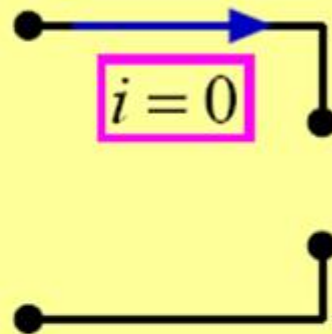





Open
Circuit

$$R = \infty$$



$$G = 0$$

$$R = \frac{v}{i}$$
$$G = \frac{i}{v}$$



Short & open circuit

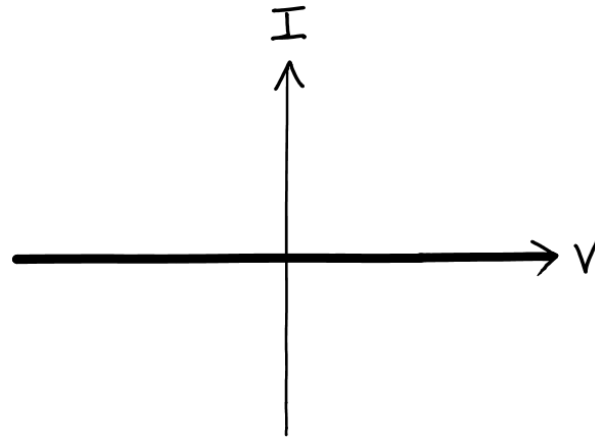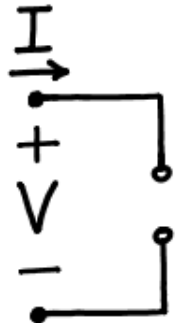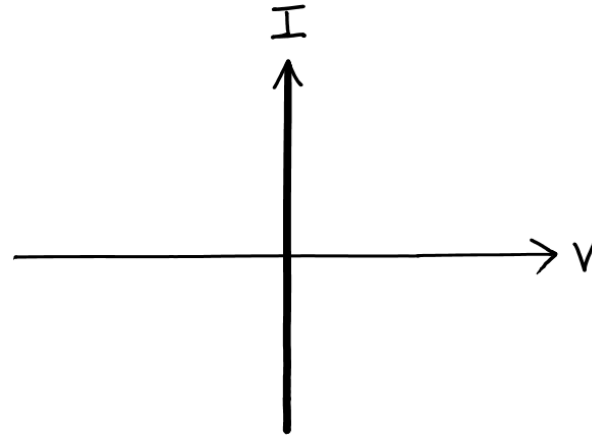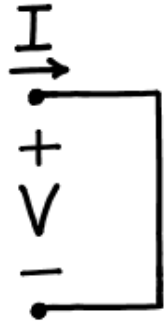

Voltage Source

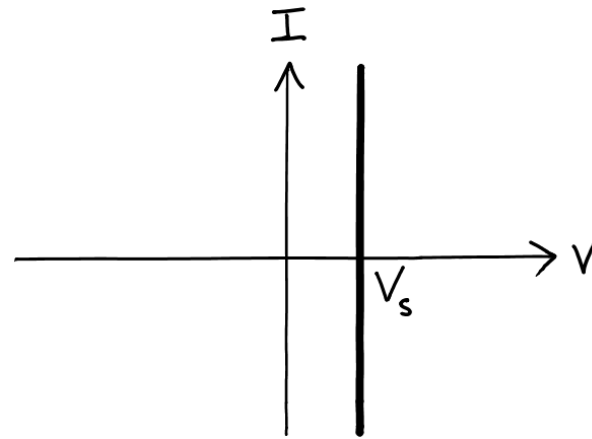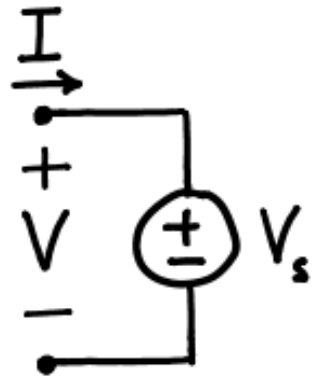


Current Source

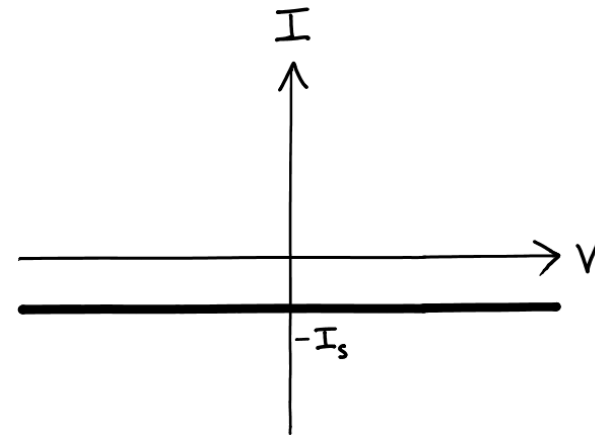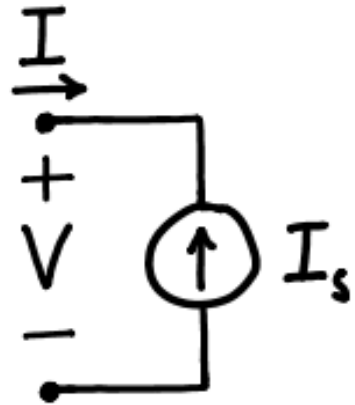

Power

- A battery stores energy (measured in Joules)
- Power delivered by the battery = $V \times I$
- Power **delivered** by battery when current flows out of the positive terminal (discharging)
- Otherwise, battery **consumes** energy (charging)

Variable Convention

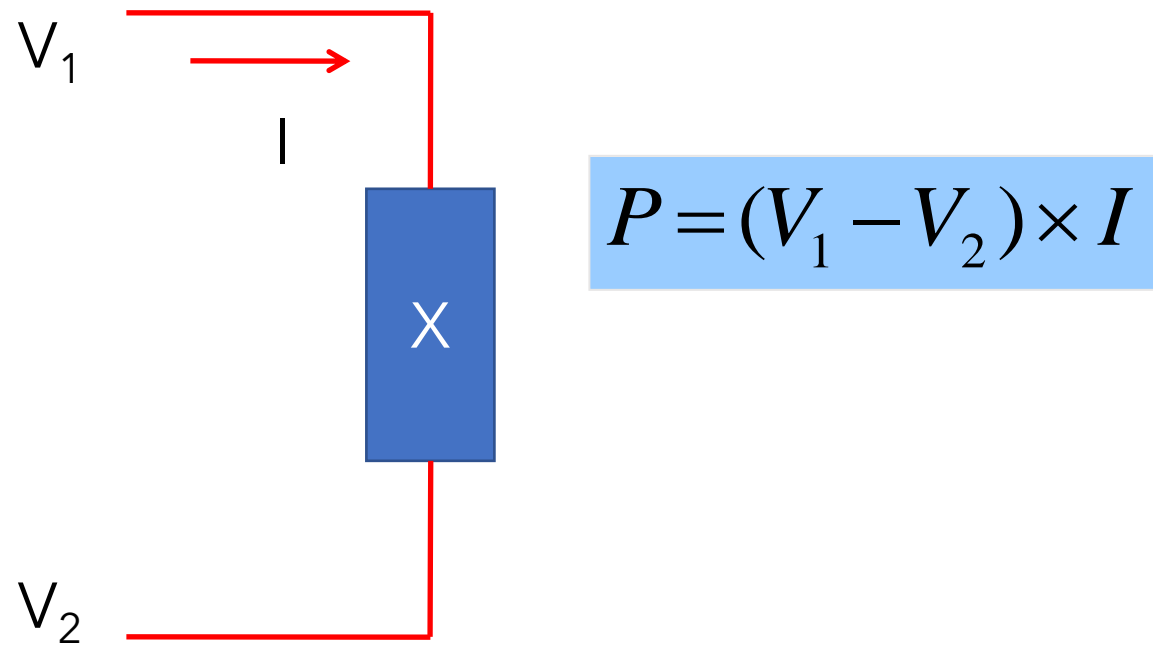


If $V_1 > V_2$ then P is positive and it means that power is being delivered to the electrical element X

If $V_1 < V_2$ then P is negative and it means that power is being extracted from the electrical element X .

X is a source of power !


Associated variables convention

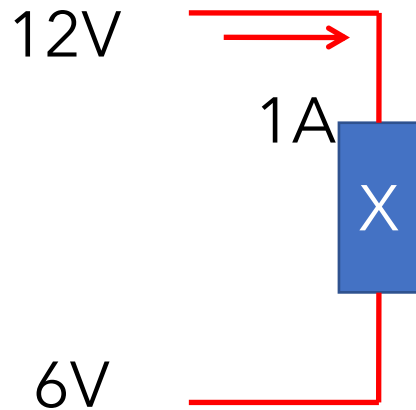

$P = ?$

$$P = (V_1 - V_2) \times I$$
$$= (12 - 6) \times 1 = 6W$$

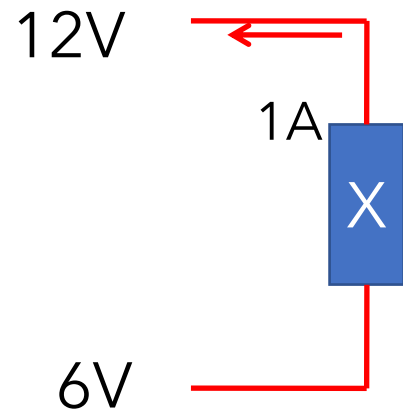Power is being delivered to the electrical element X




$P = ?$

$$P = (V_1 - V_2) \times I$$
$$= (12 - 6) \times -1 = -6W$$

Power is supplied by element x instead of dissipation


Spot the battery!

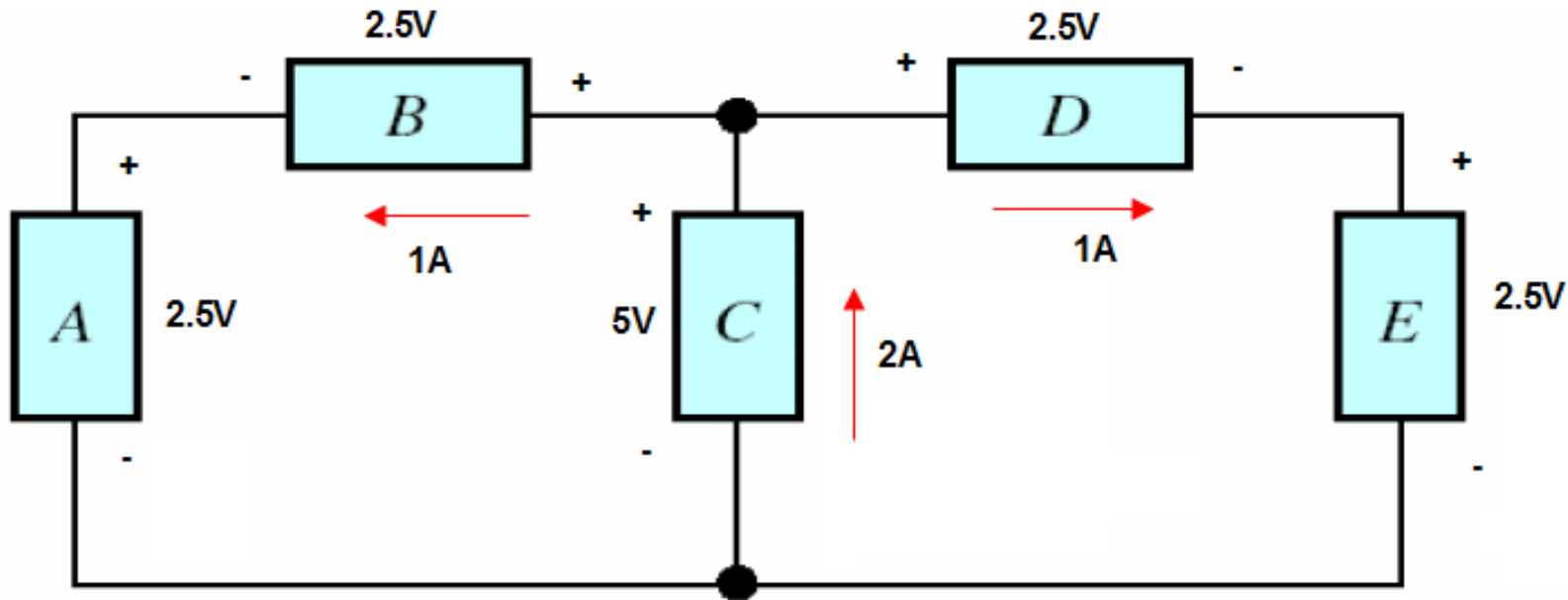- Given that there is only one battery, which one is it?



A battery is a source of power, so power dissipated is negative

Power dissipated in a resistor

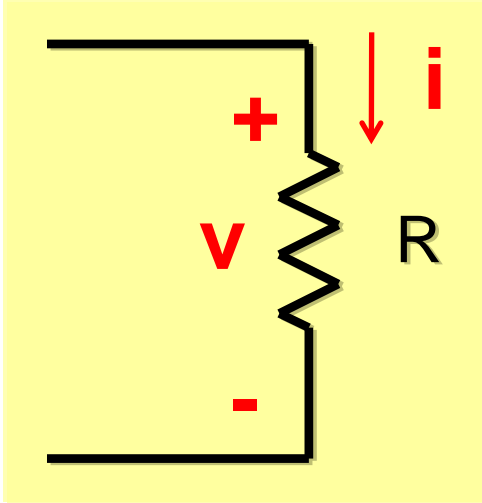

$$v = i \times R$$

$$i = \frac{v}{R}$$


$$P = v \times i$$

$$P = i^2 \times R$$

$$P = \frac{v^2}{R}$$


Nodes

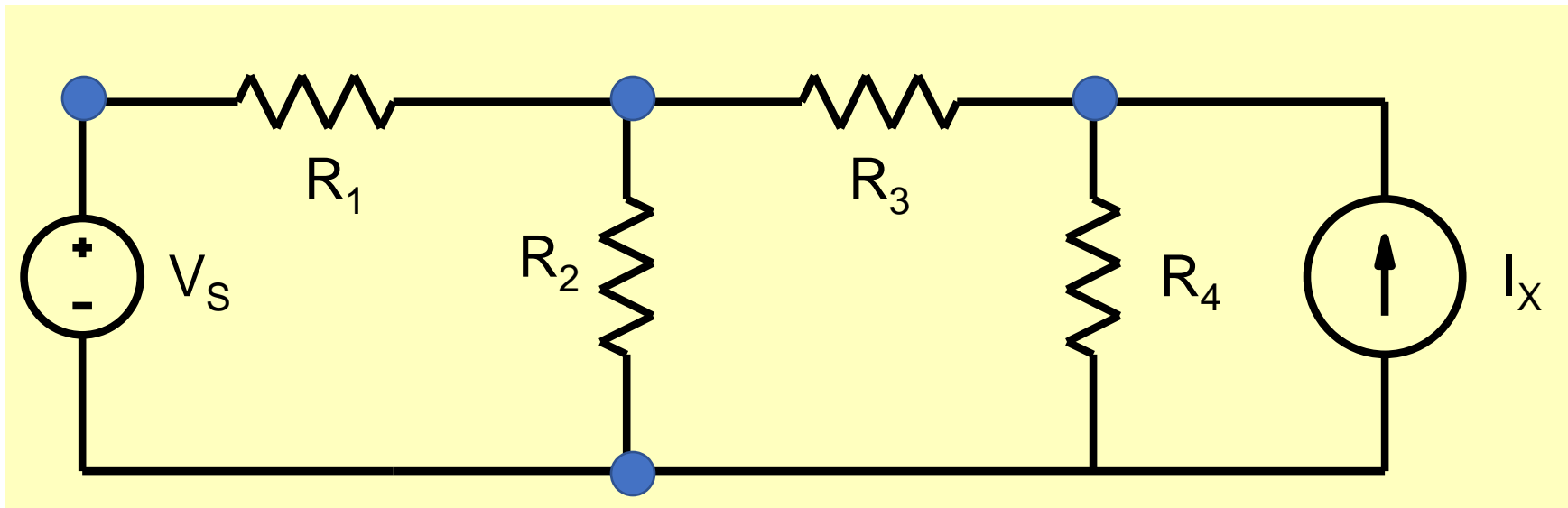Node: A point where 2 or more circuit elements are connected.



What is a Loop?

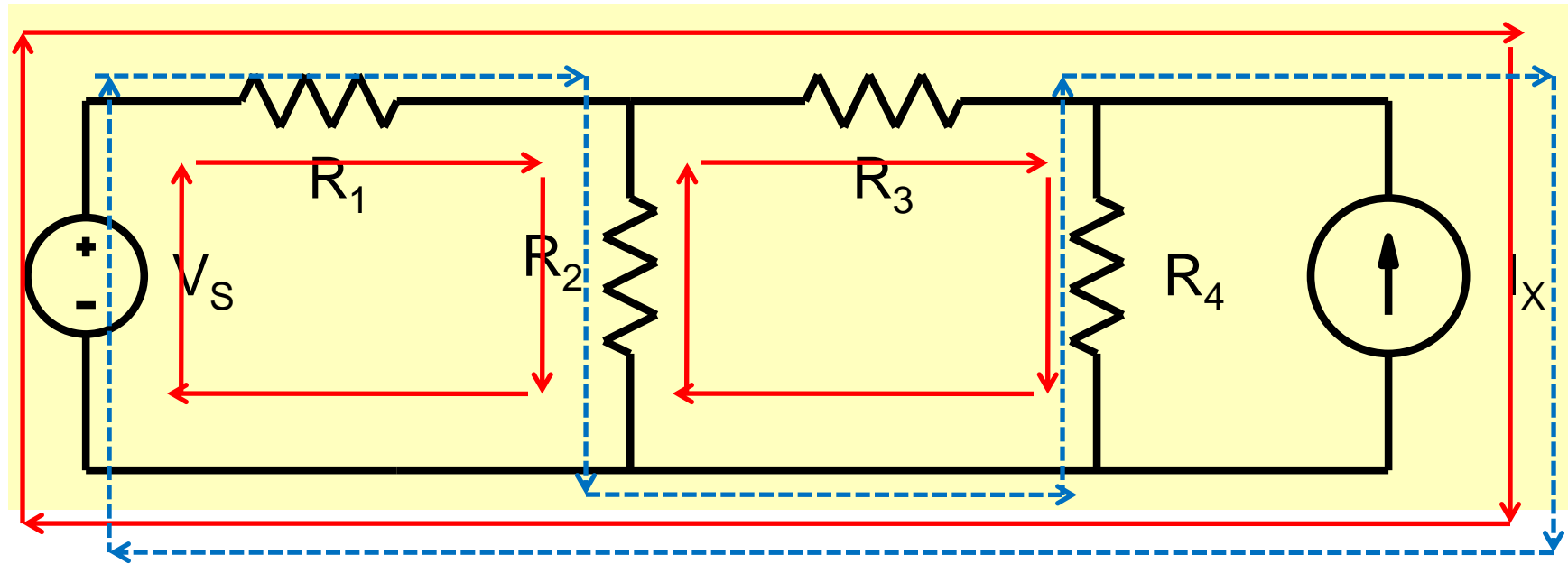
A **loop is formed by tracing a closed path** through circuit elements without passing through any intermediate node more than once



This is not a valid loop !

Circuit Analysis

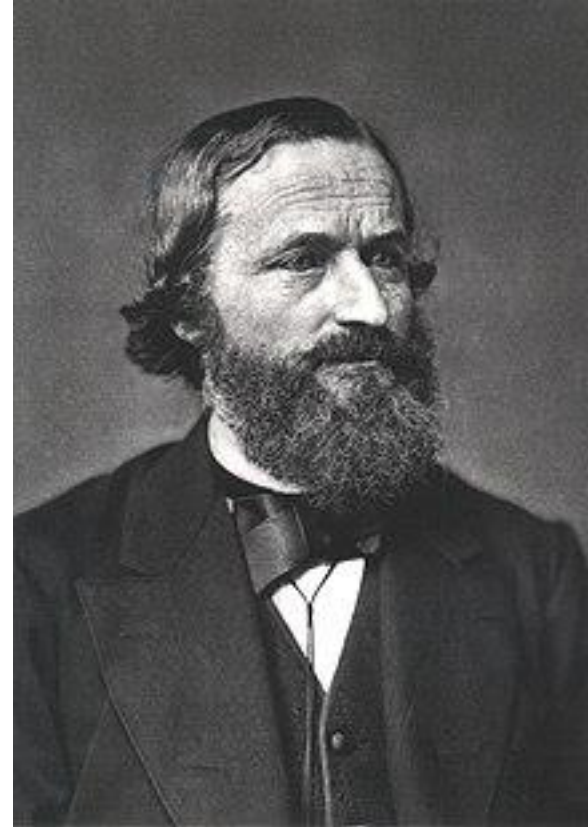
- Kirchhoff's Laws
- KCL and KVL
- Conservation of Charge and Energy



Gustav Kirchhoff

Kirchoff's Current Law (KCL)

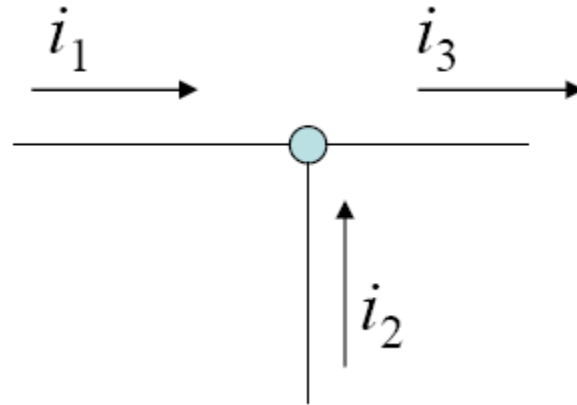
Sum of currents entering a node is equal to sum of currents leaving a node



$$i_1 + i_2 = i_3$$

A direct result of conservation of charge

Kirchhoff's Current Law (KCL)

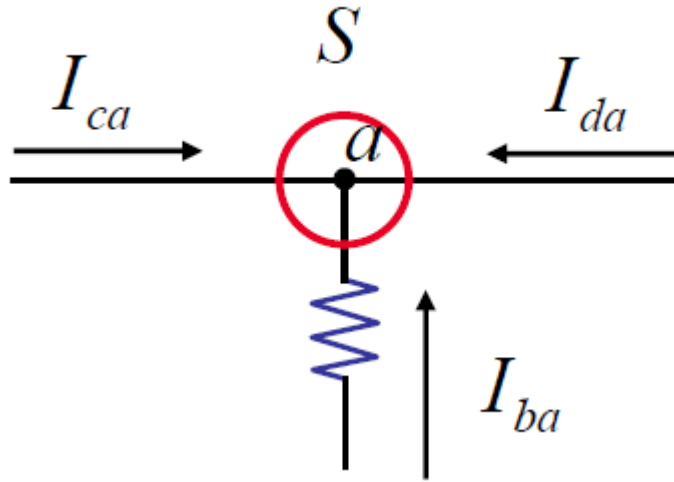


$$I_{ca} + I_{da} + I_{ba} = 0$$


At any node in a circuit, the sum of all current arriving is 0

$$\sum_{j=1}^N i_j = 0$$

KCL: examples

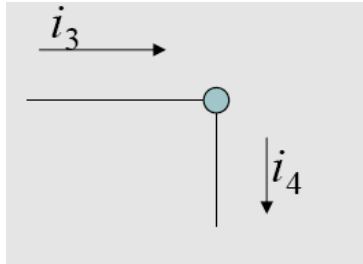

$$i_3 = i_4$$

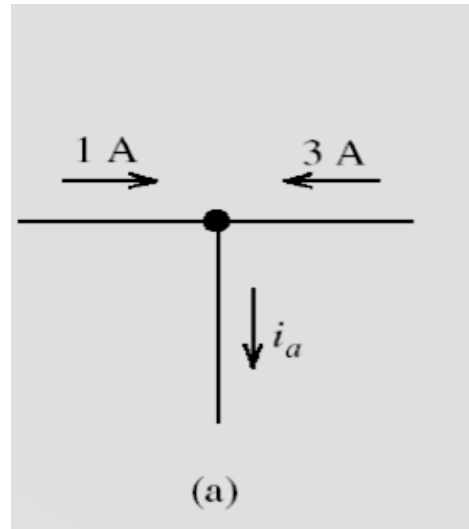


$$1 + 3 - i_a = 0$$

$$i_a = 4A$$

KCL: examples


$$1 + 3 - i_1 = 0$$

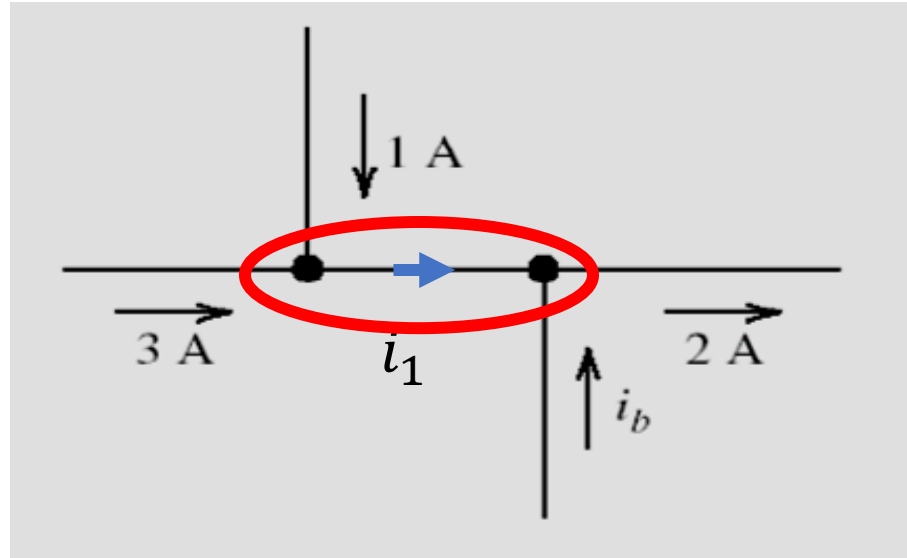


$$i_b - 2 + i_1 = 0$$

$$1 + 3 + i_b - 2 = 0$$

$$i_b = -2A$$

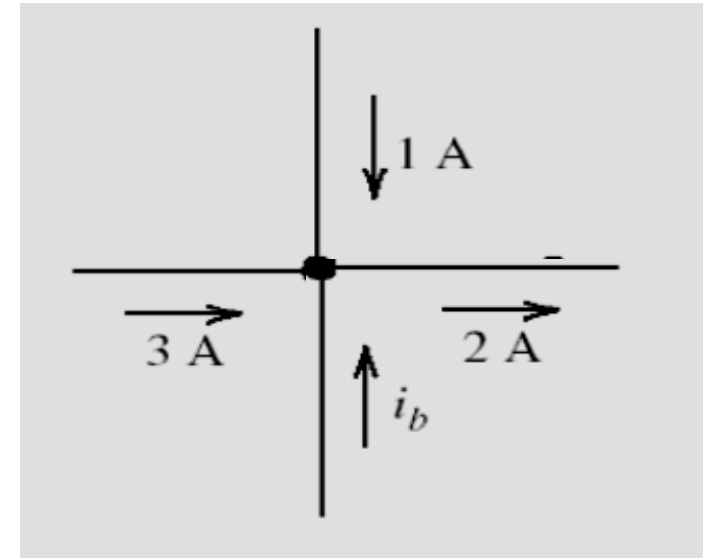


KCL: combining nodes

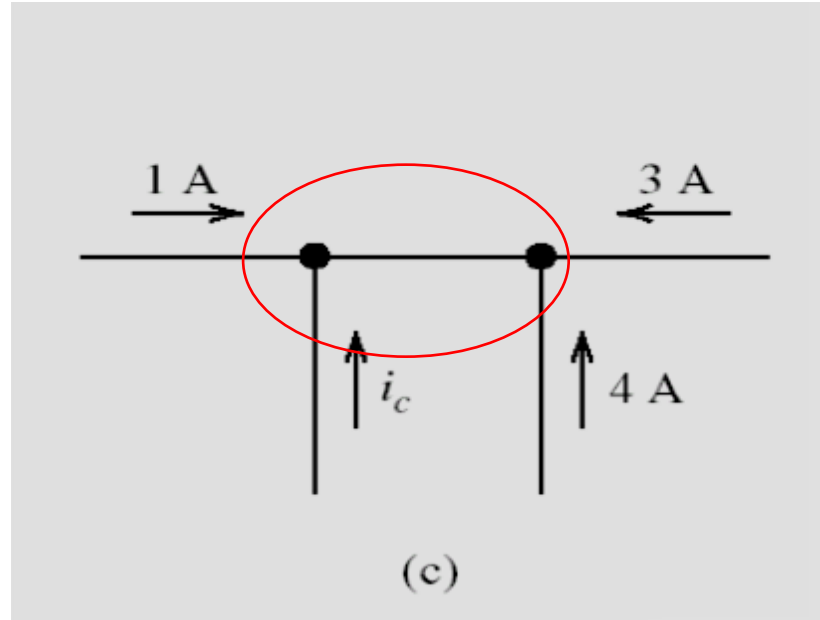


$$1 + 3 + i_c + 4 = 0$$

$$i_c = -8A$$

KCL: generalization

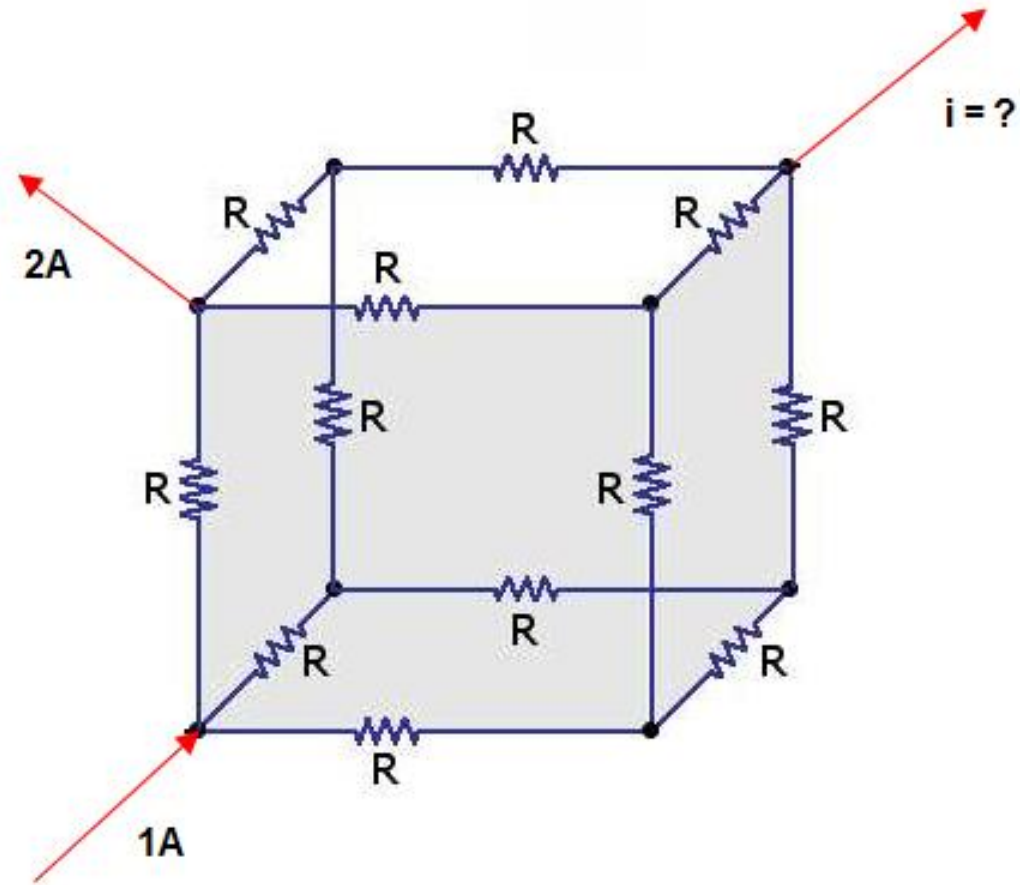


KCL: general form

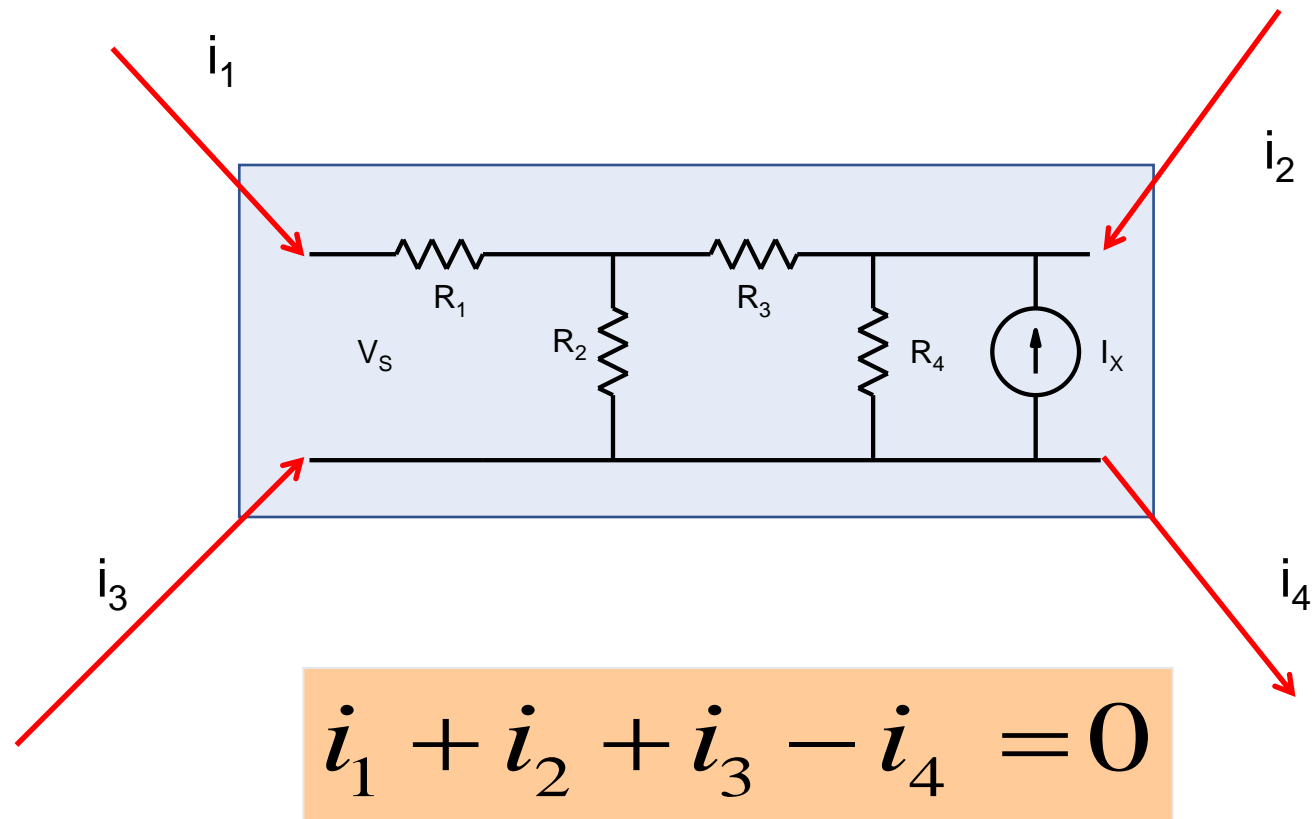

Series Circuit

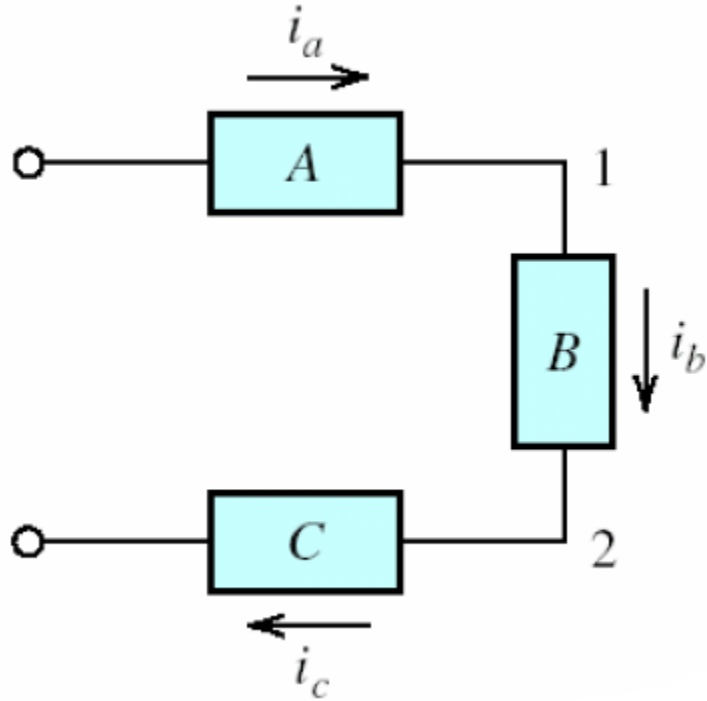Two elements are connected in series if there is no other element connected to the node joining them




A, B and C are in series

The elements have the same current going through them

$$i_a = i_b = i_c$$

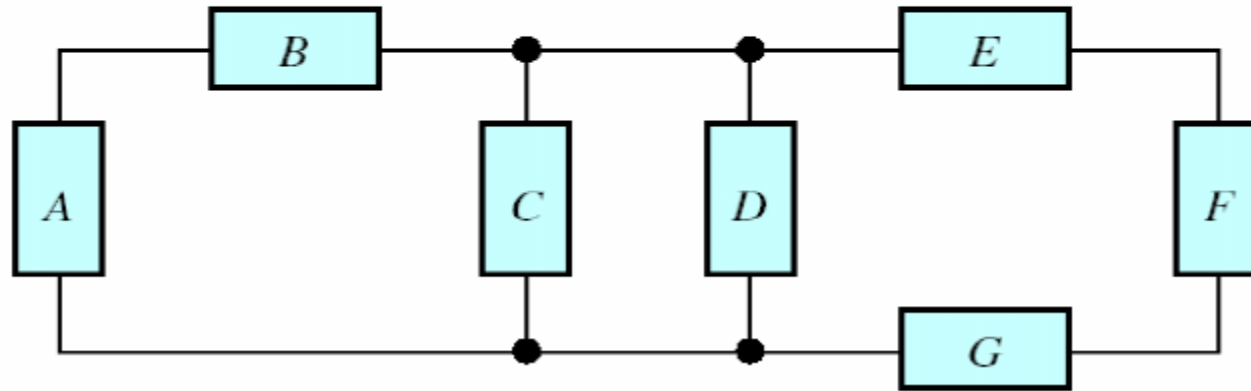Example:

Identify the groups of elements connected in series



A and B are in series

E, F and G are in series


Kirchhoff's Voltage Law (KVL)

The algebraic sum of the voltages equals zero for any closed path (loop) in an electrical circuit.

In applying KVL to a Loop


voltages are added (or subtracted)

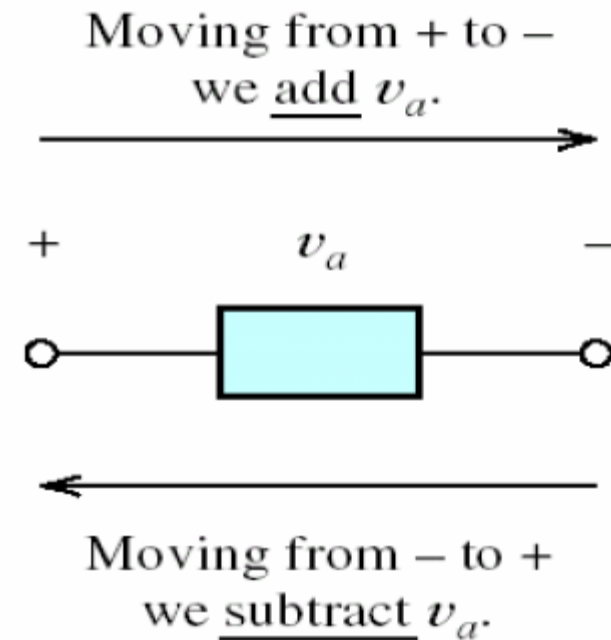depending on their polarities relative to the direction of travel around the loop



Conservation of energy!

KVL: example

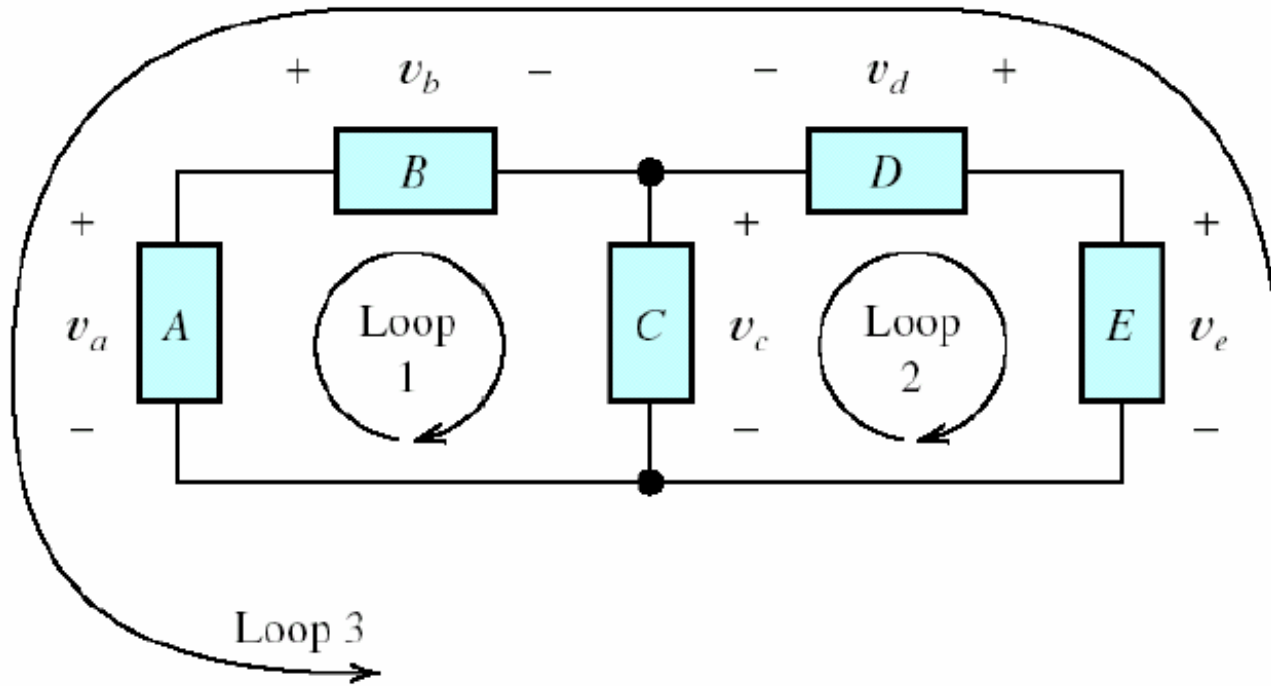


$$\text{Loop1: } -v_a + v_b + v_c = 0$$

$$\text{Loop2: } -v_c - v_d + v_e = 0$$

$$\text{Loop3: } -v_e + v_d - v_b + v_a = 0$$

Parallel Circuits

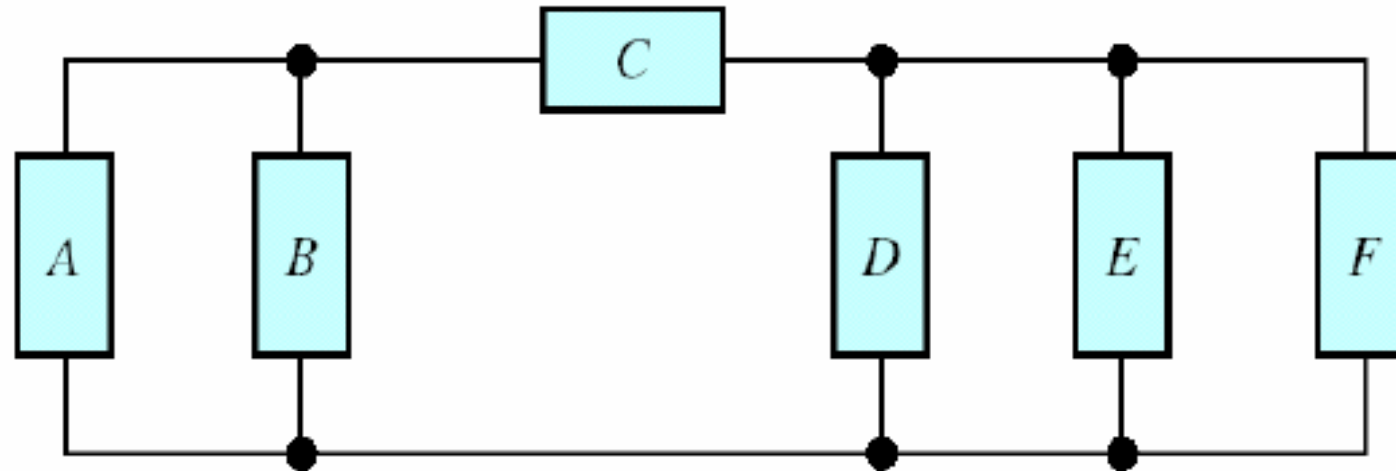
Two elements are connected in parallel if both ends of one element are connected directly to corresponding ends of the other



A and B are connected in parallel

D, E and F are connected in parallel

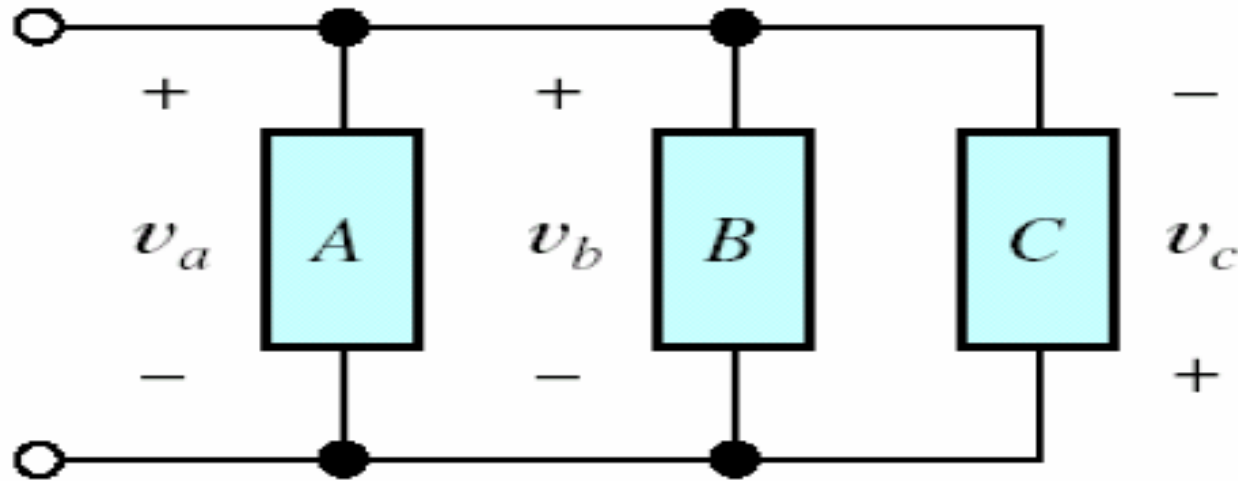
The voltage across parallel elements are equal (both **magnitude and polarity**)



$$v_a = v_b = -v_c$$

Example


Use KVL to find v_c and v_e

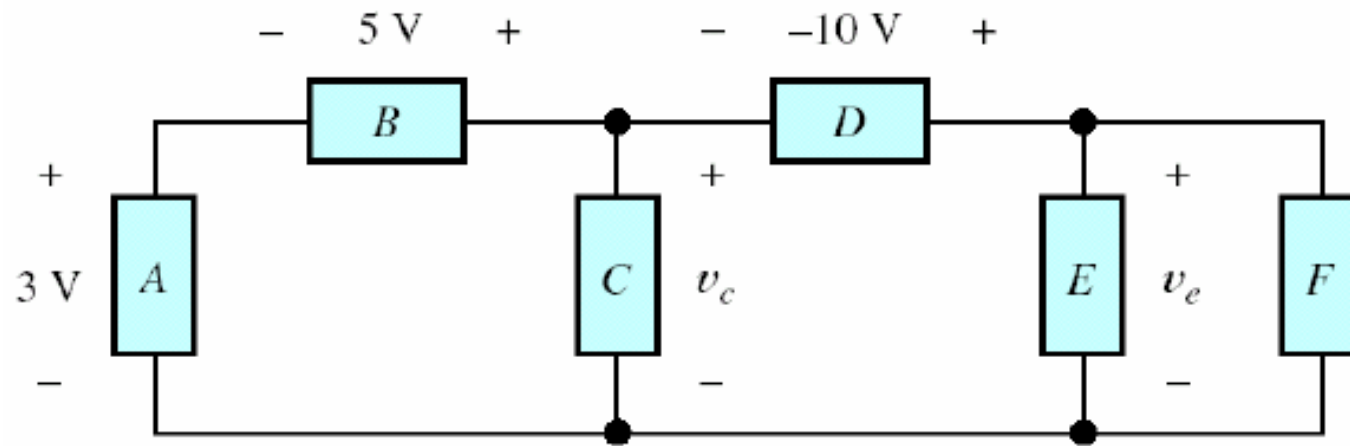

$$-3 - 5 + v_c = 0 \Rightarrow v_c = 8V$$

$$-v_c - (-10) + v_e = 0 \Rightarrow v_e = -2V$$

Ready to use KCL-KVL?

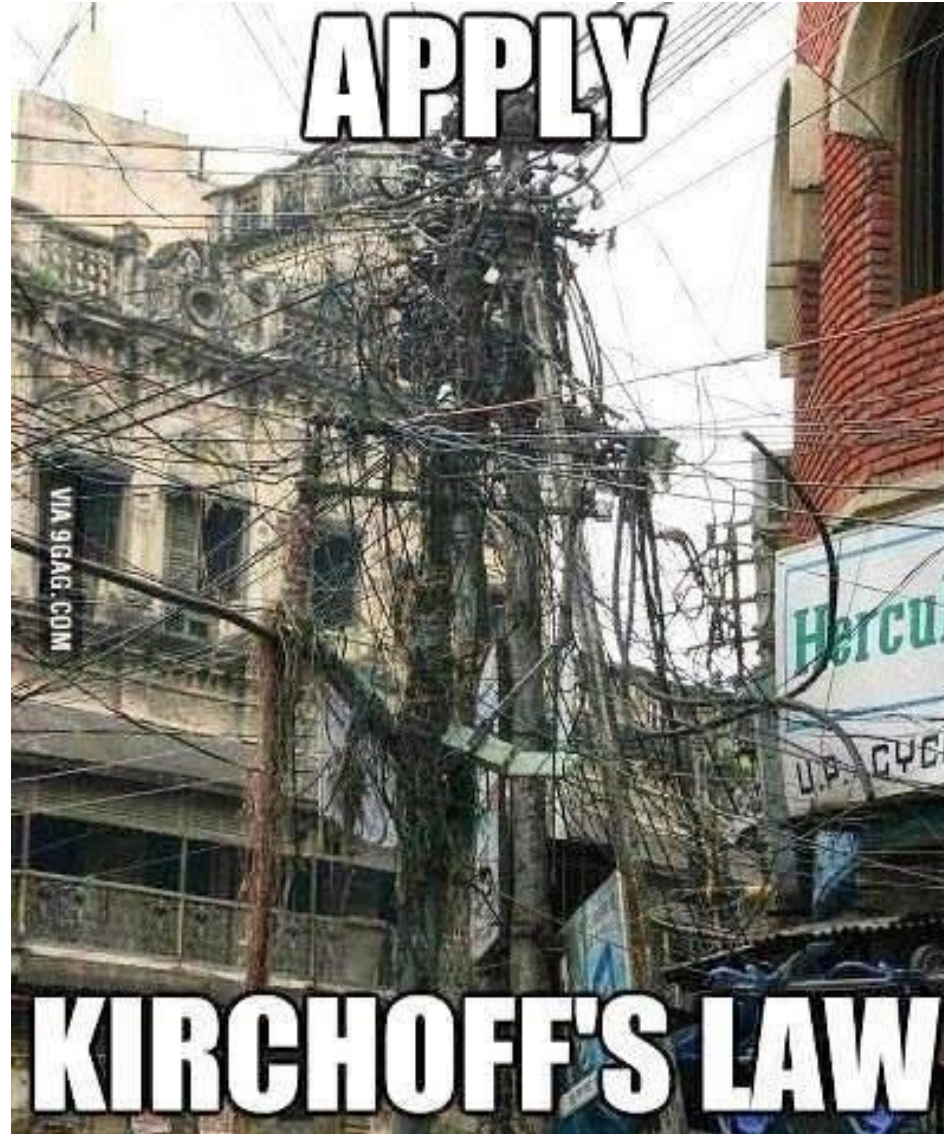

Tidy circuits are easier to understand

