

# ESC201: INTRODUCTION TO ELECTRONICS

## MODULE 1: CIRCUIT ANALYSIS



Dr. Shubham Sahay,  
Assistant Professor,  
Department of Electrical Engineering,  
IIT Kanpur

# Recap: Techniques of Circuit Analysis

## Nodal Analysis

1. Identify and number the nodes
2. Pick Ground node/Reference node wisely, if it is not already specified
3. Writing KCL Equations in Terms of the Node Voltages

## Mesh Analysis


1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
2. Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

## Superposition Method for Linear Circuits

The superposition principle states that the total response is the sum of the responses to each of the **independent sources** acting individually.


Linear circuit: linear elements, independent voltage/current

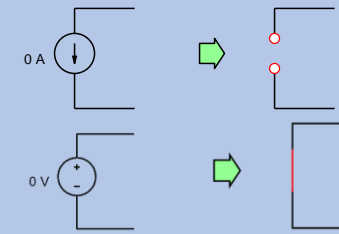Sources, and **linear dependent sources**



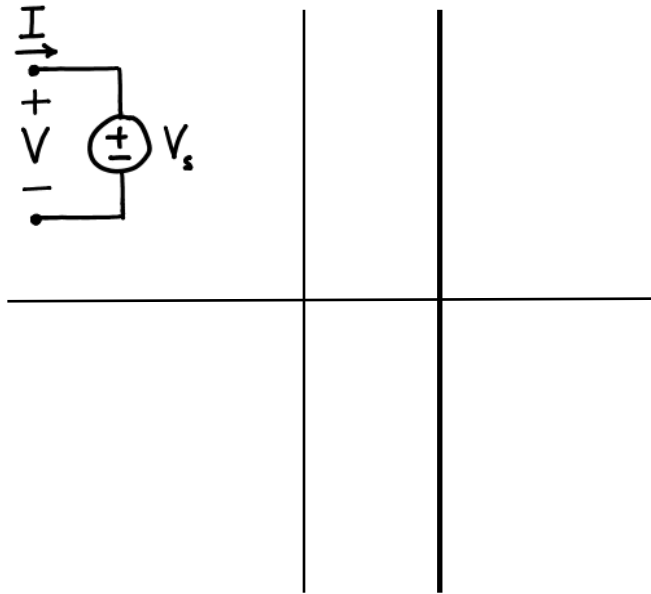
# Non-ideal sources

- How to model non-ideal batteries?
- Draw intuition from the VI characteristic





Ideal battery

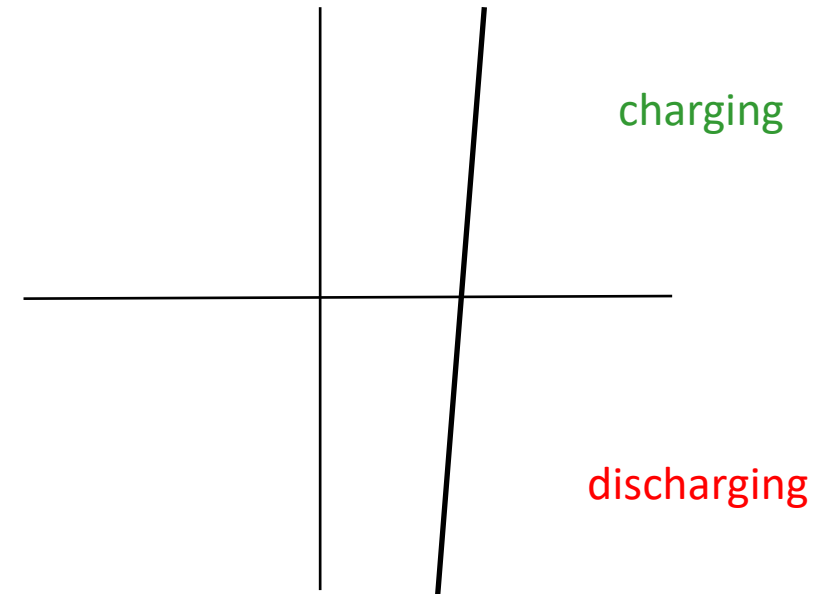

Real battery

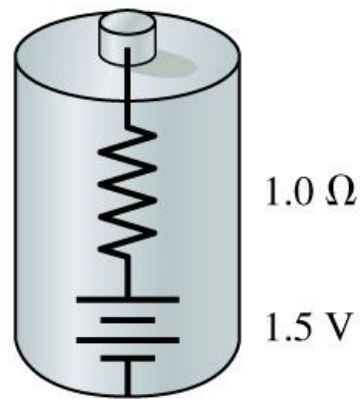
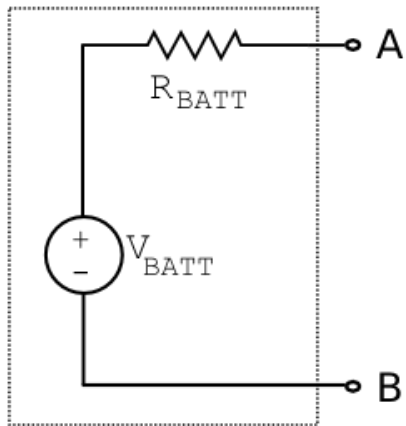
# Non-ideal battery

- The non-ideal battery consists of linear elements inside it
- Thevenin equivalent of a battery!



**Validity:** only when current magnitude is not too large and voltage is around  $V_{\text{BATT}}$

# General Case

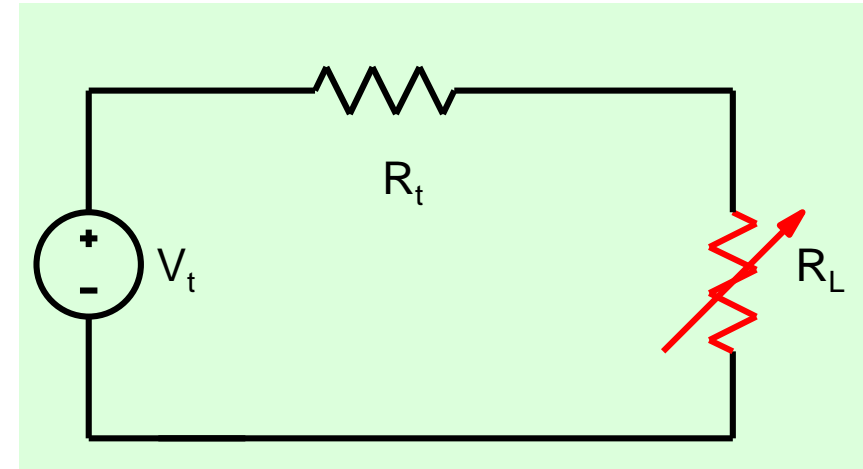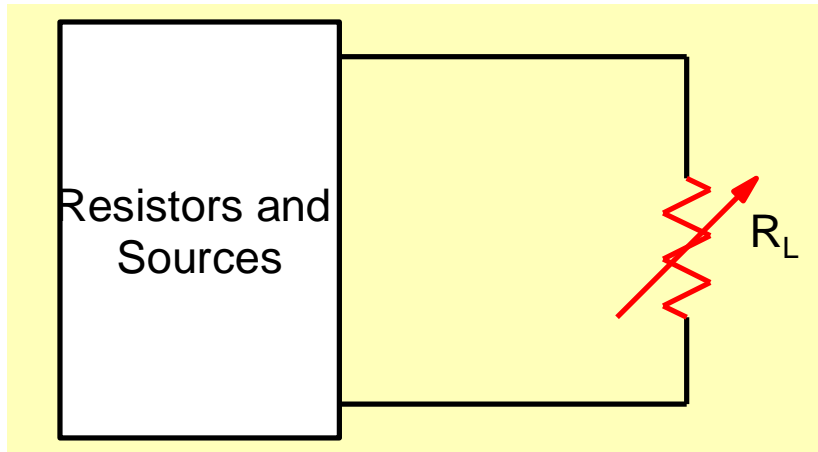




Maximum power is delivered to the load when  $R_L = R_t$

# Thévenin's Theorem







"Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load"

Any linear circuit with power supplies (voltage sources and/or current sources) and resistances can be replaced by a single resistance connected in series with a voltage source to make it equivalent to the original circuit.

# Thévenin Equivalent Circuits

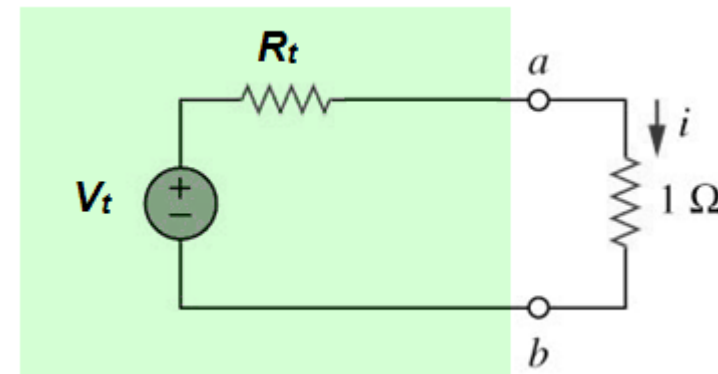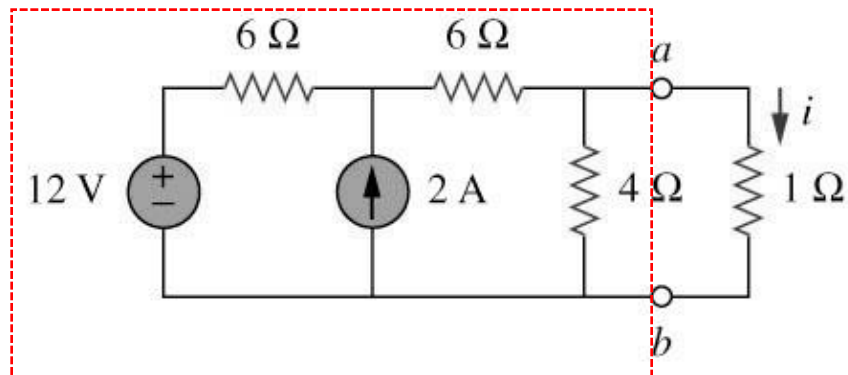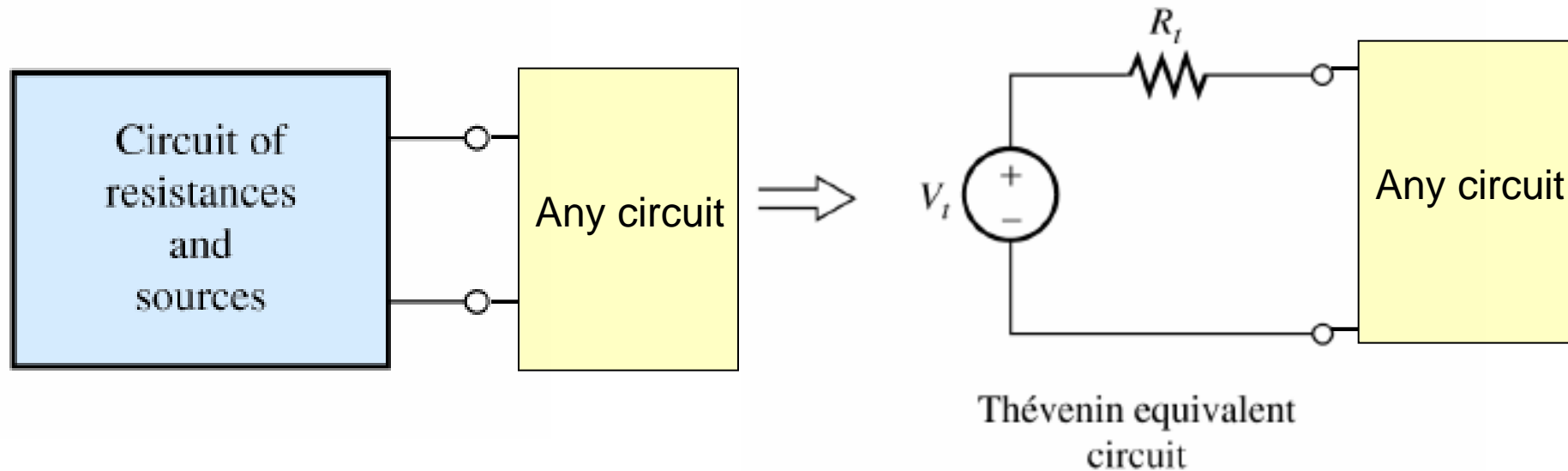

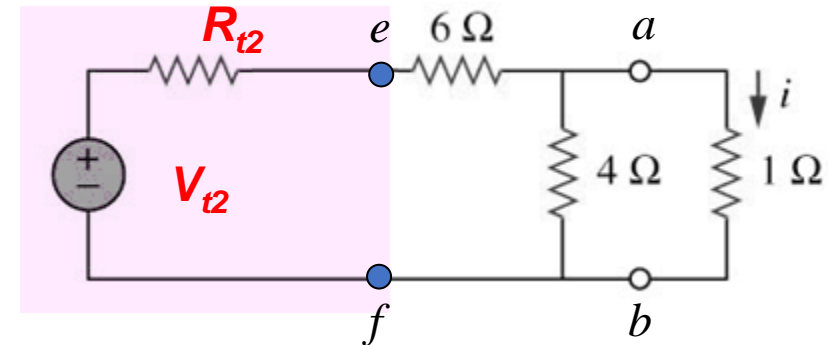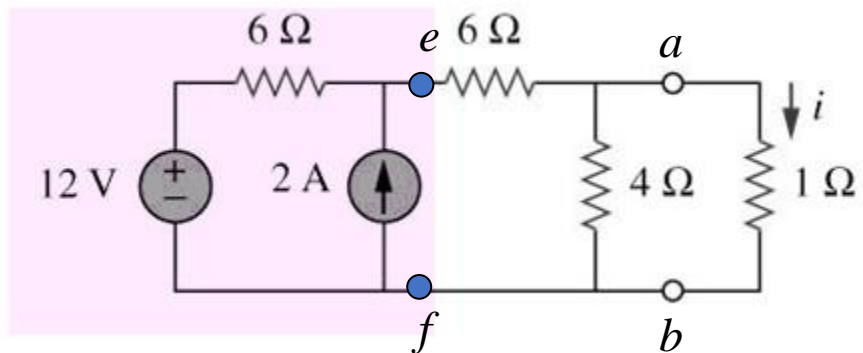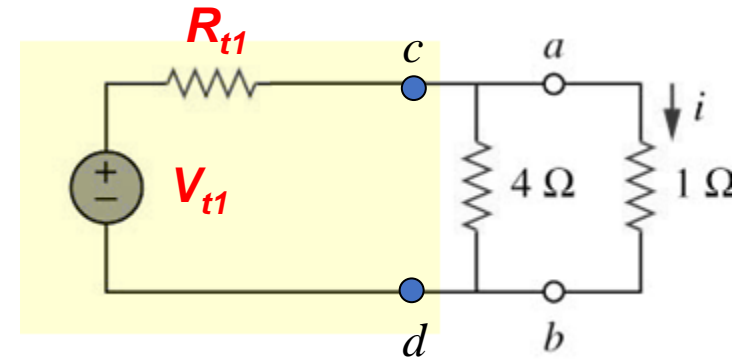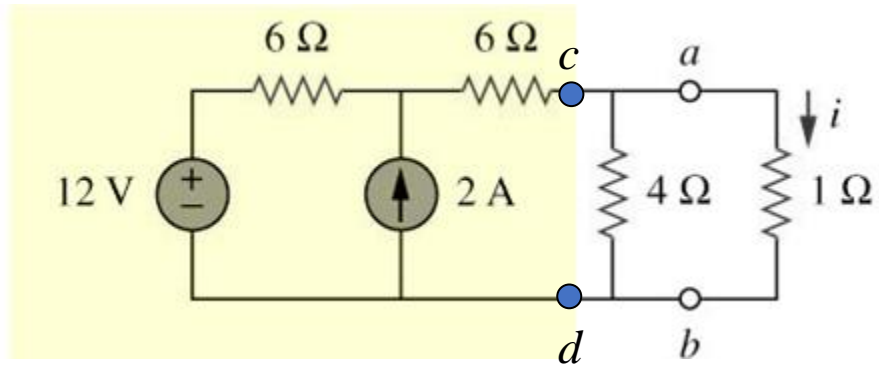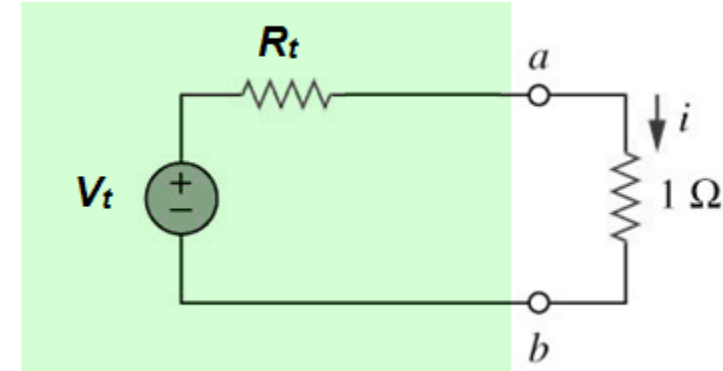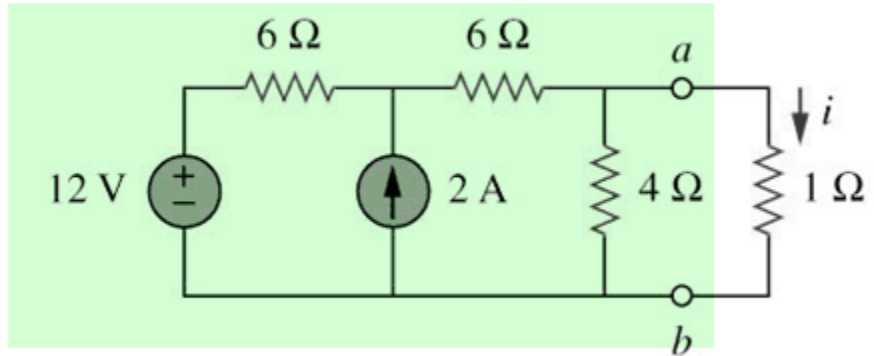
## Thévenin's Theorem Applies to Any Part of the Circuit







# Thévenin Voltage

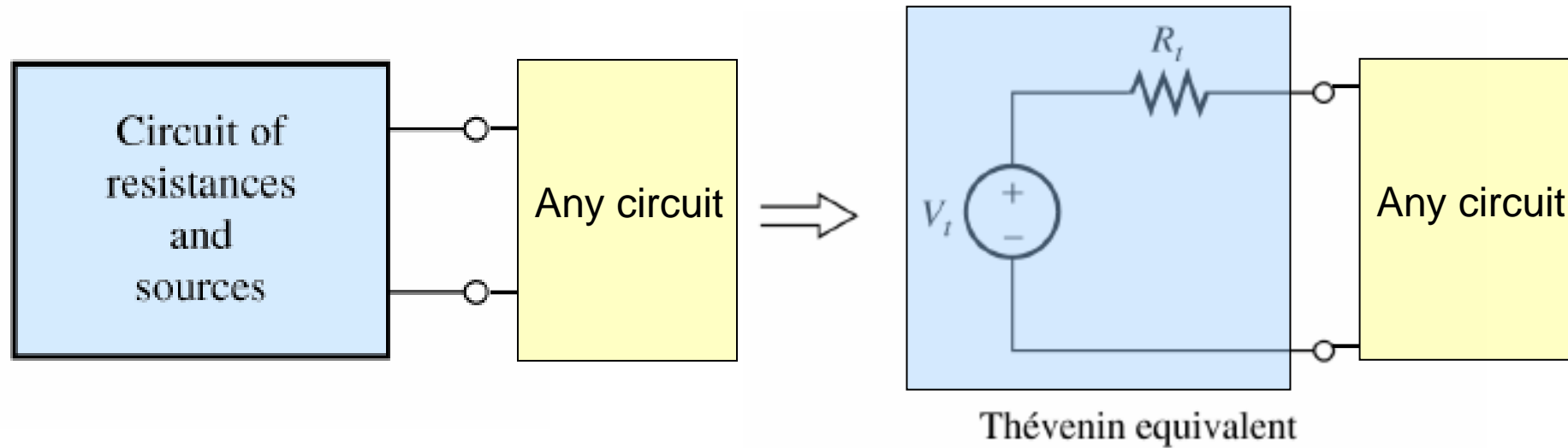

What is Thévenin Voltage  $V_t$  ?

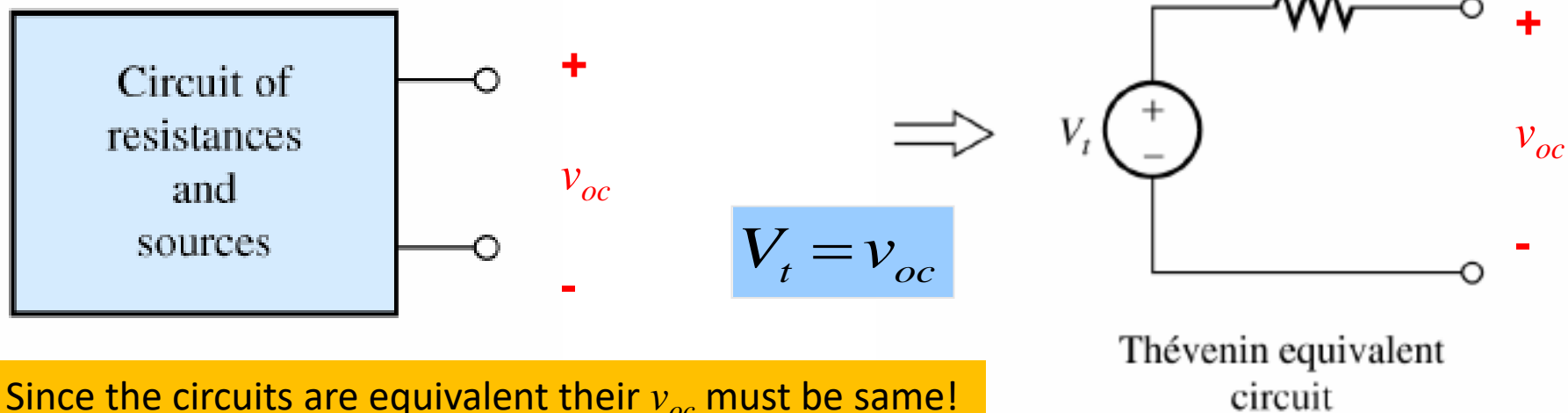


# Thévenin Resistance

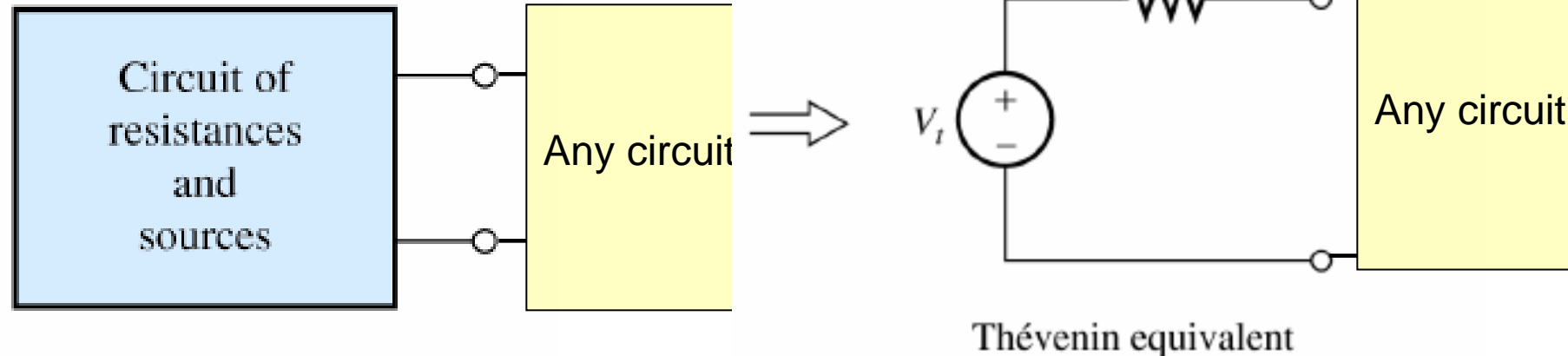


What is  $R_t$  ?

The first level solution:

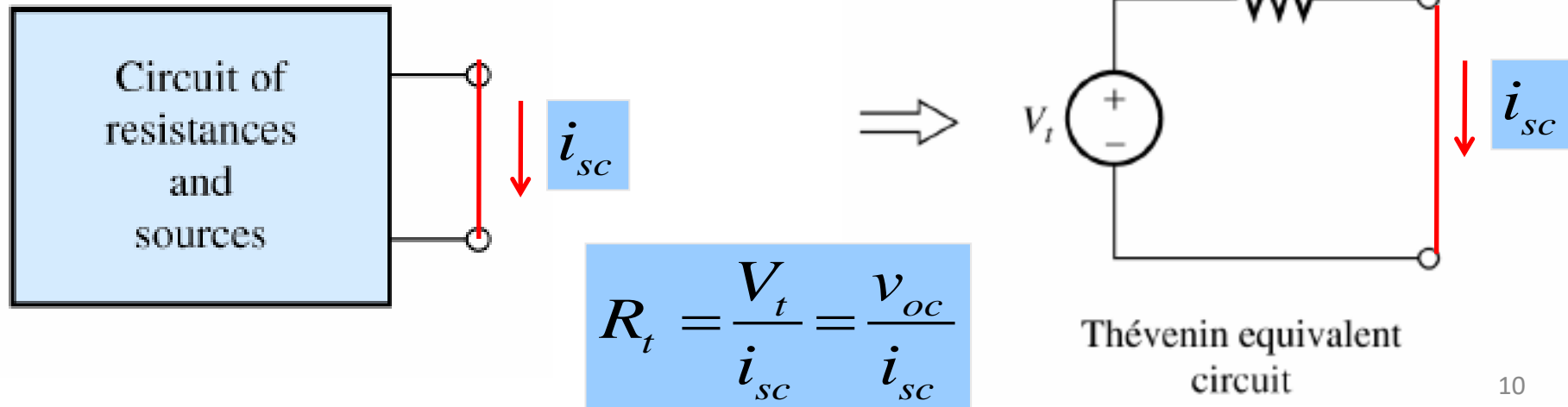

Since the circuits are equivalent their  $i_{sc}$  must be same!



# Thévenin Parameters

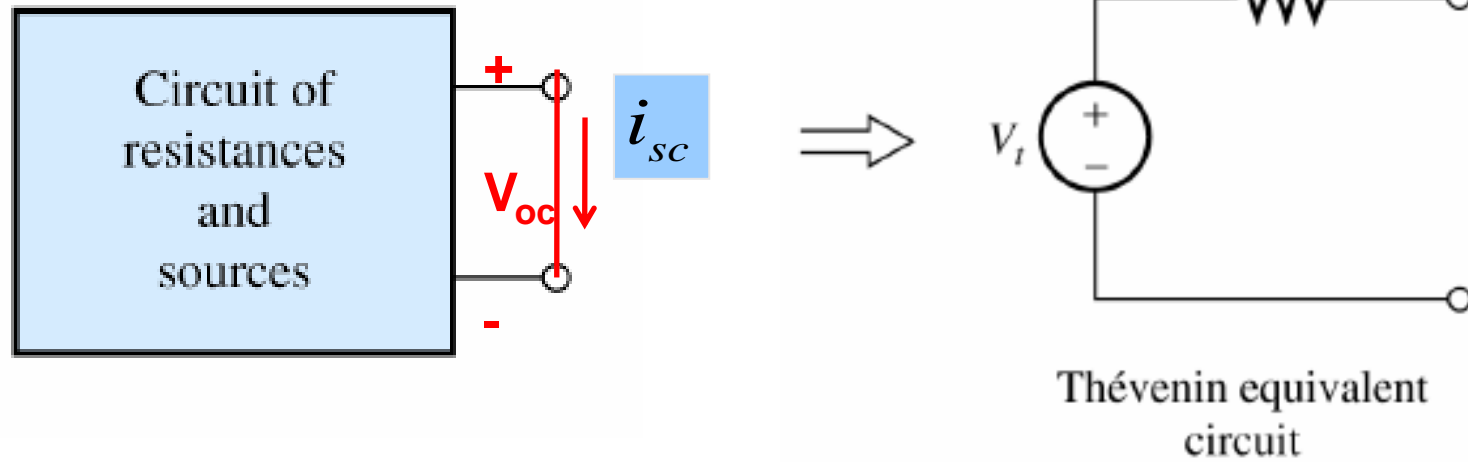

$$V_t = v_{oc}$$


$$R_t = \frac{v_{oc}}{i_{sc}}$$
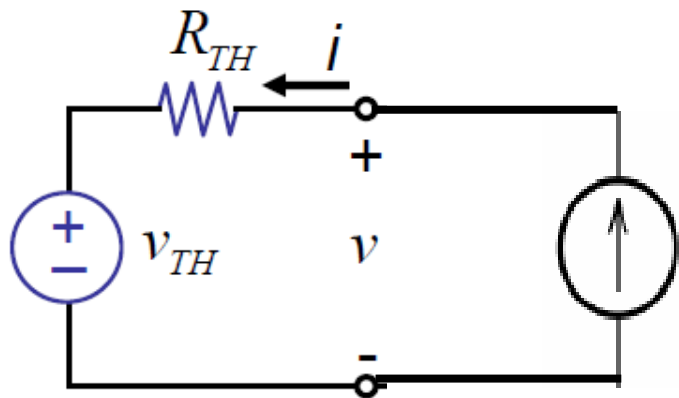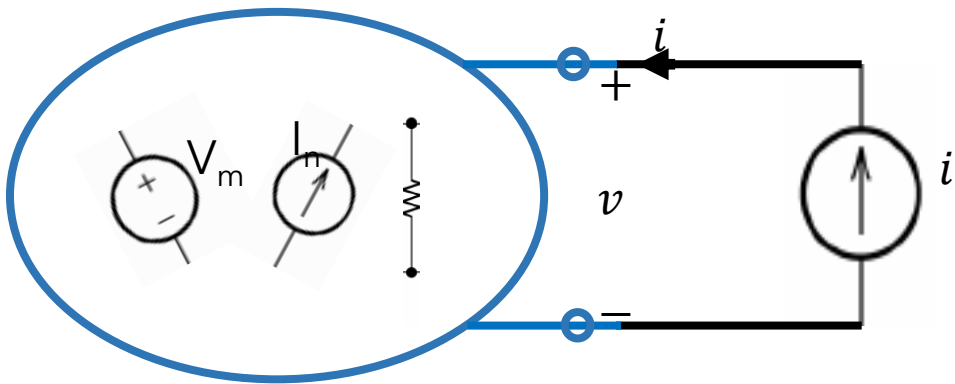
# $V_{TH}$ and $R_{TH}$ from V-I Characteristics



Equal  
Characteristics

$$v = v_{TH} + R_{TH}i$$

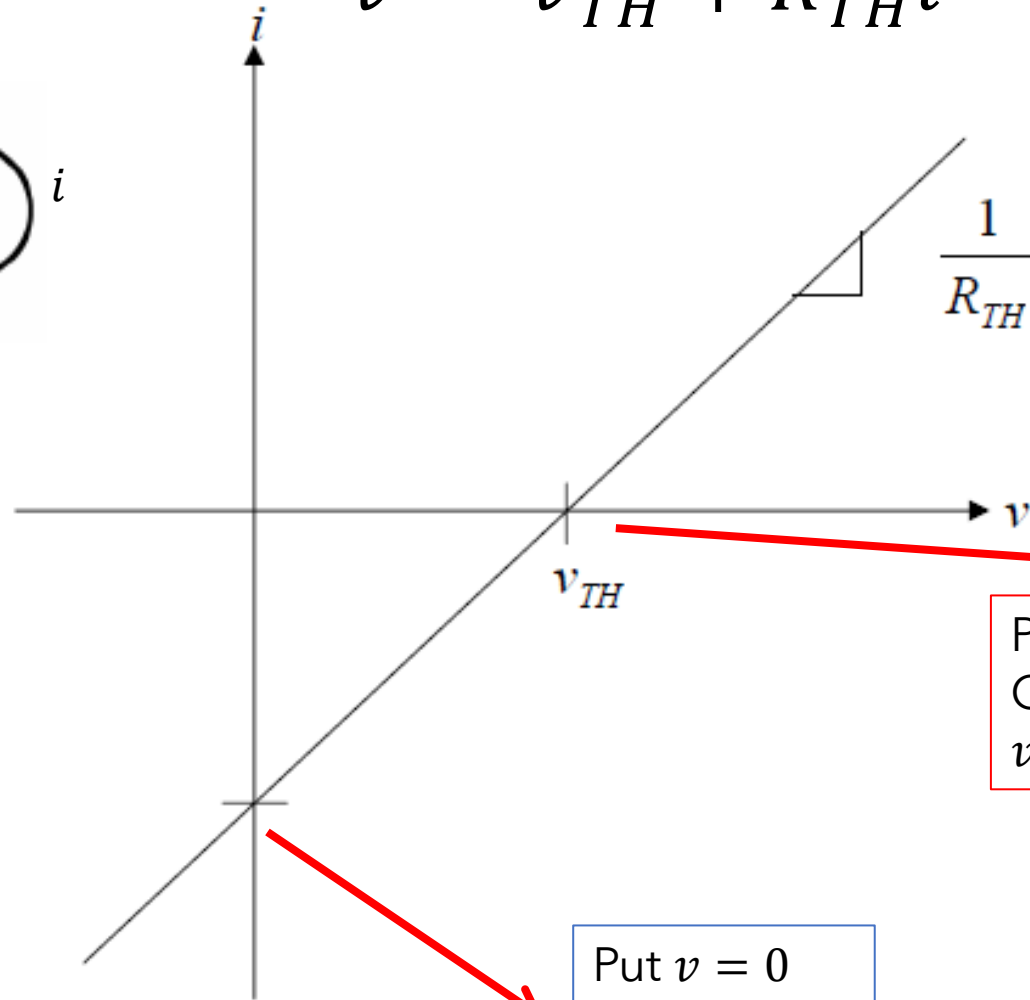


Put  $i = 0$   
Open circuit  
 $v_{OC}$

Put  $v = 0$   
Short circuit  
 $i_{SC}$

$$0 = v_{TH} + R_{TH}i_{SC}$$
$$-v_{TH} = R_{TH}i_{SC}$$


$$R_{TH} = \frac{v_{TH}}{-i_{SC}} = \frac{v_{OC}}{-i_{SC}}$$

## Examples

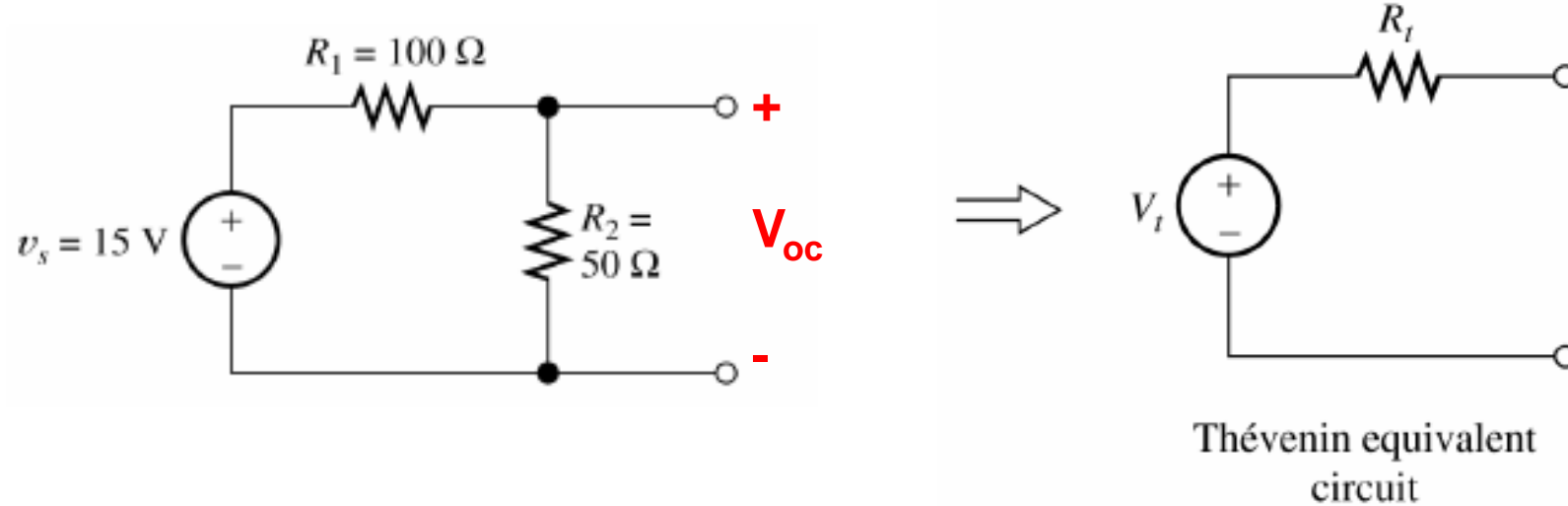

$$V_t = v_{oc}$$

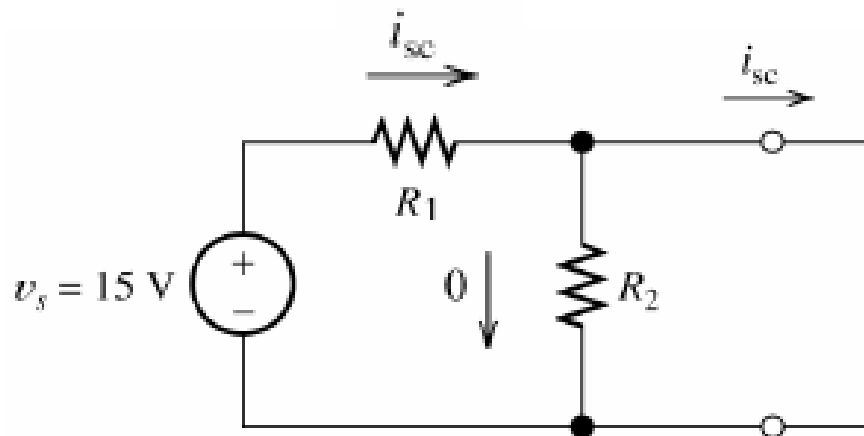
$$V_t = \frac{R_2}{R_2 + R_1} \times 15 = 5 \text{ V}$$




$$i_{sc} = \frac{v_s}{R_1} = 0.15 \text{ A}$$

$$R_t = \frac{v_{oc}}{i_{sc}} = 33.3 \Omega$$
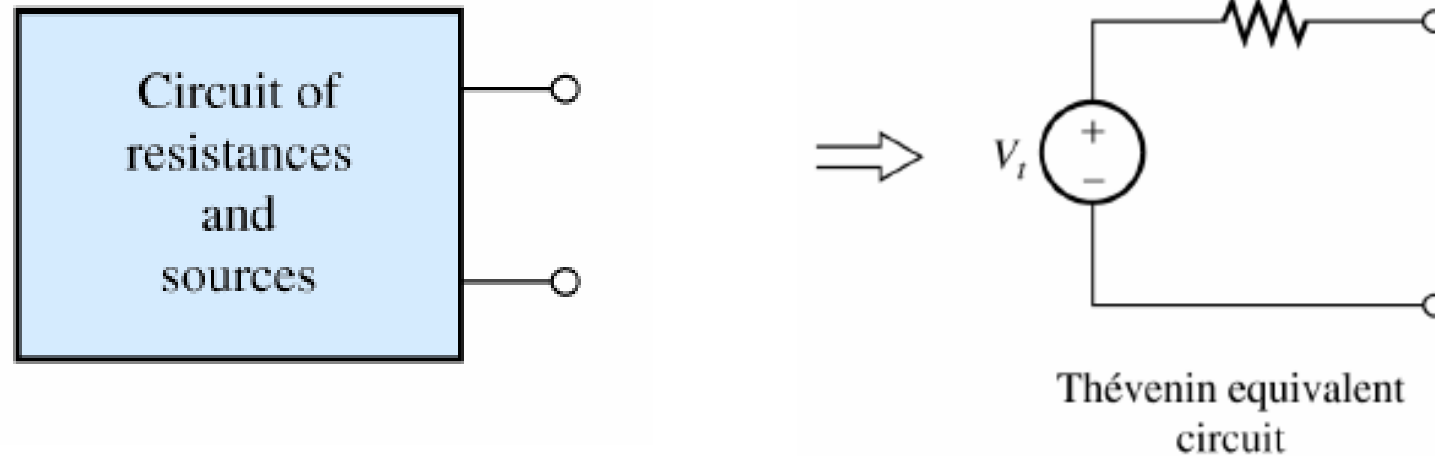
## For Circuits with Only Independent Sources



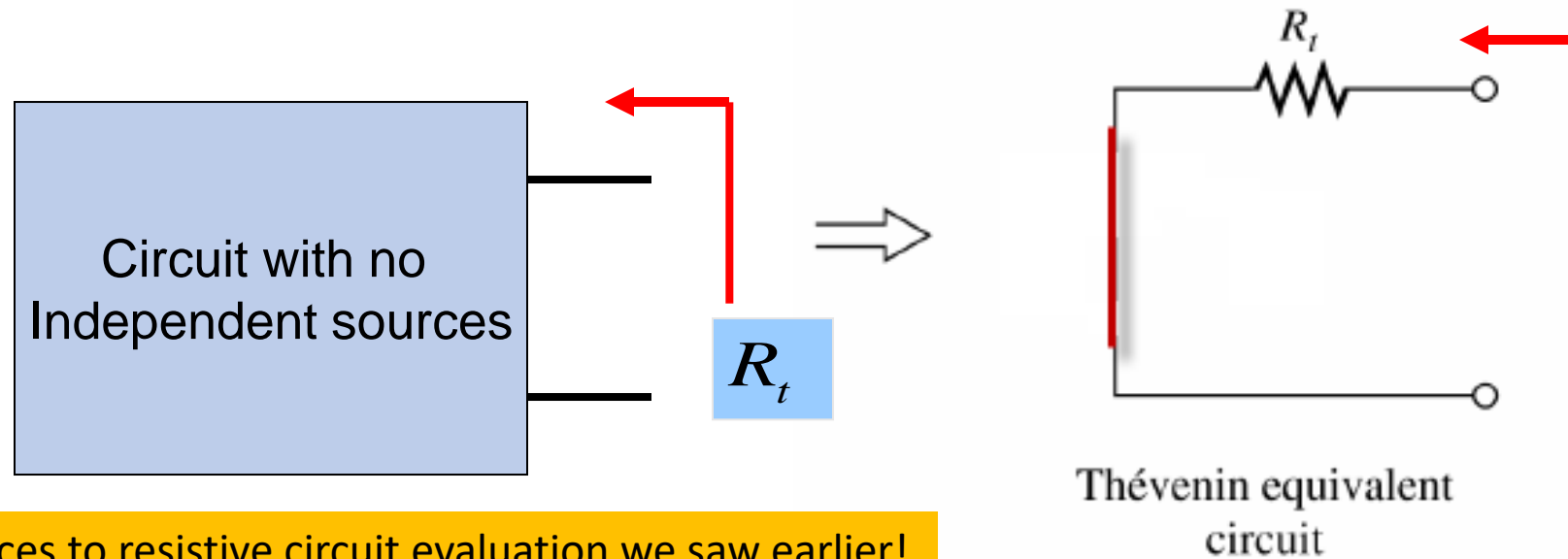Suppose we make all independent sources zero in the circuit





Reduces to resistive circuit evaluation we saw earlier!

# Evaluation of $R_t$


- Turn off independent sources in the original network:

- Replace a voltage source with a short circuit
- Replace a current source with an open circuit

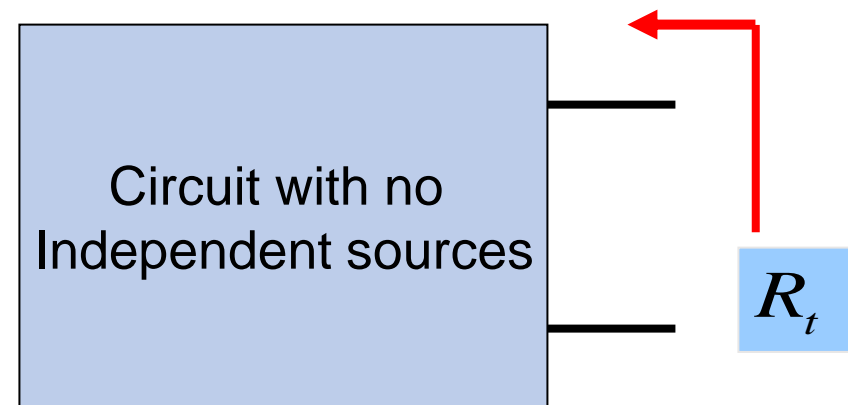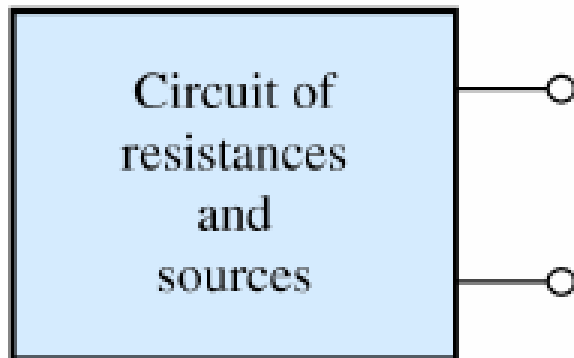- 2. Compute the resistance between the terminals





# Procedure to Directly Evaluate $R_t$

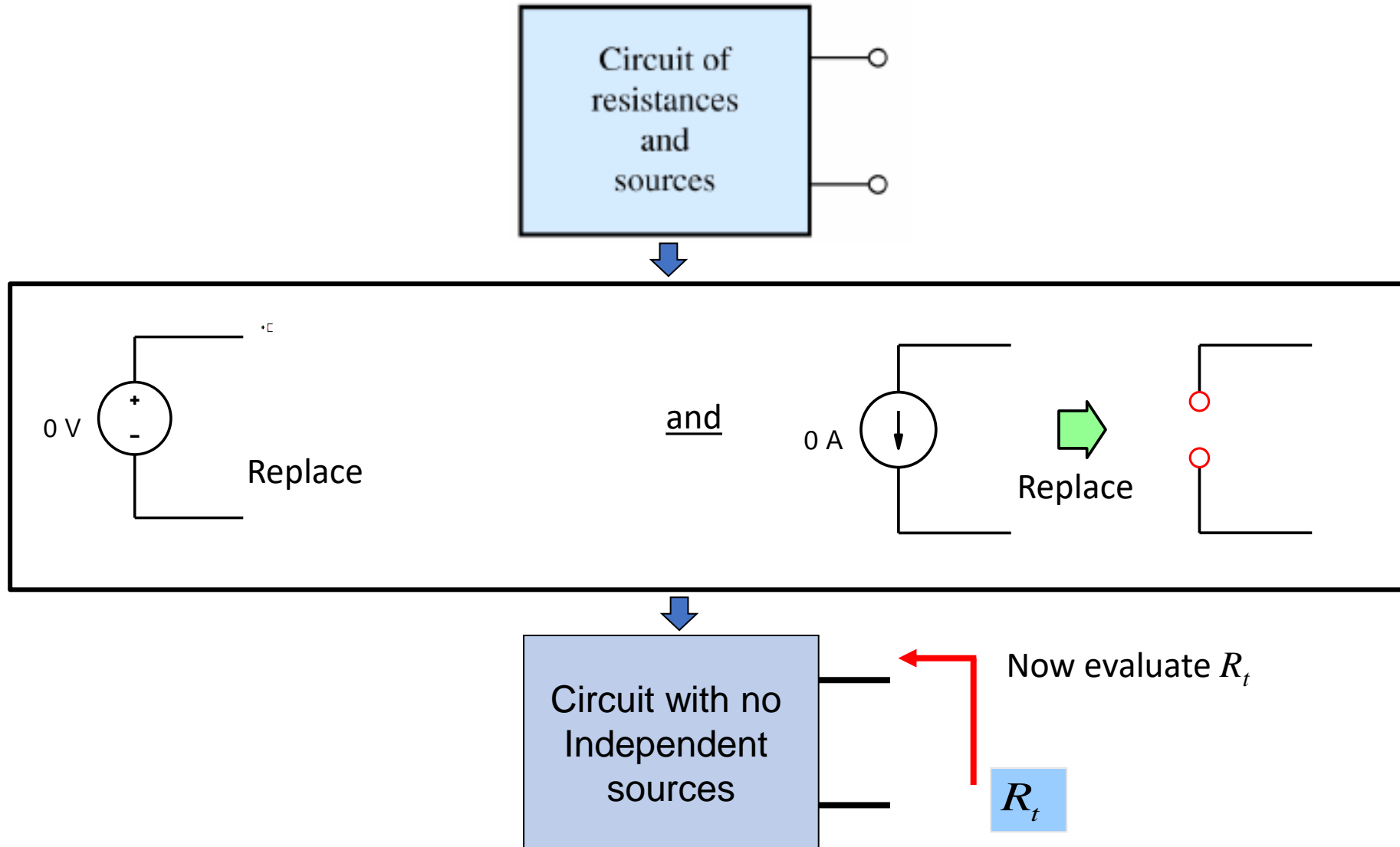





# Thevenin Equivalent: Example

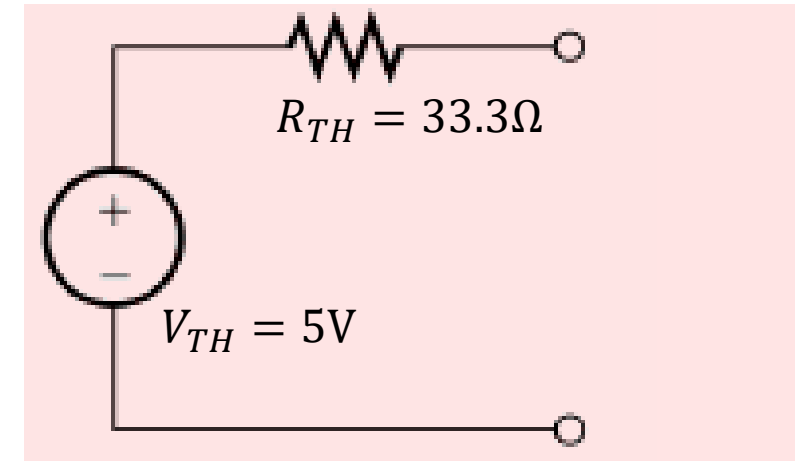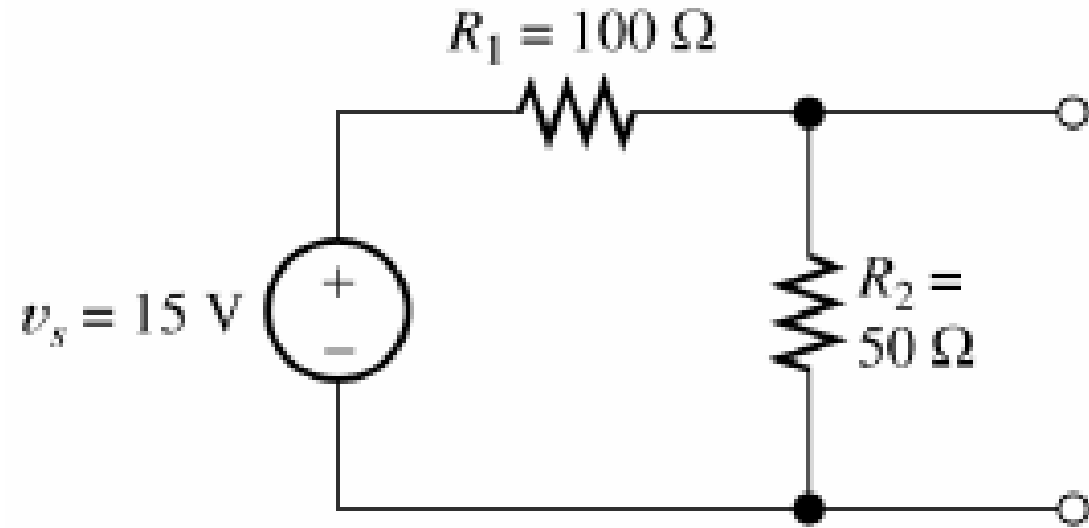
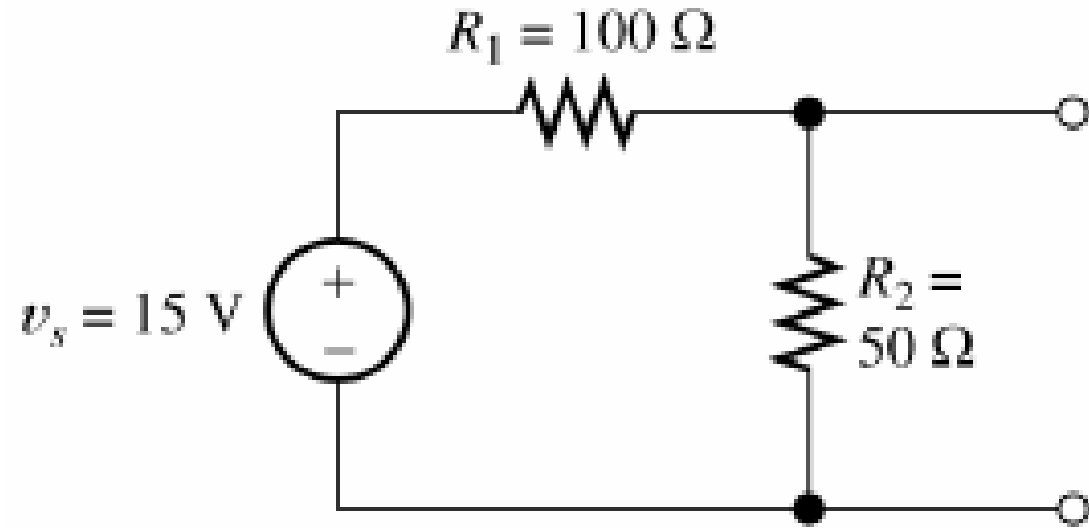
# Thevenin Equivalent: Example: Direct $R_{TH}$




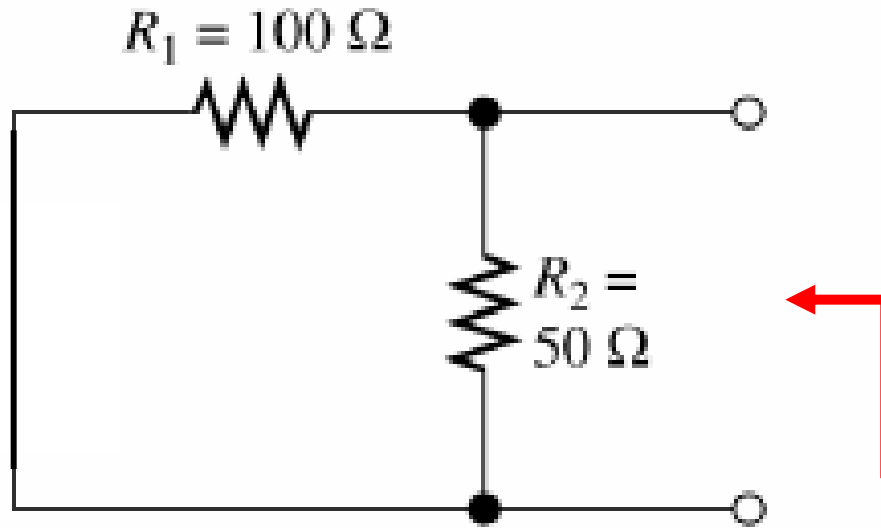
# Thevenin Equivalent: Example : Direct $R_{TH}$



$$R_{TH} = 100 || 50 = 33.3\ \Omega$$



# How to Use Thevenin Equivalent

Compute Current in R

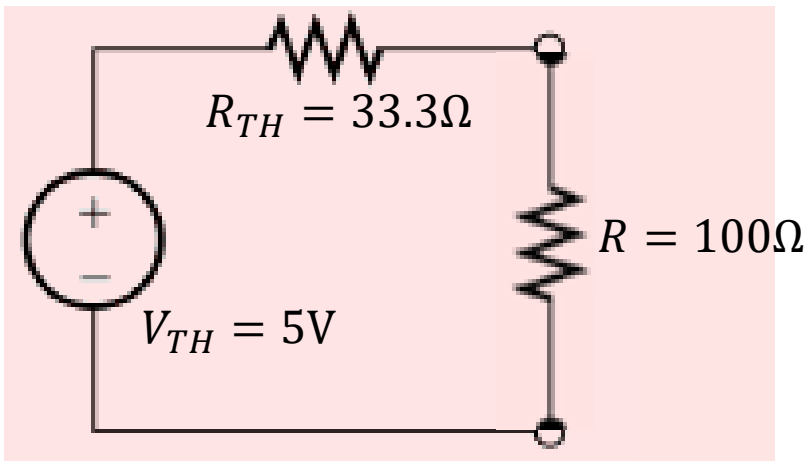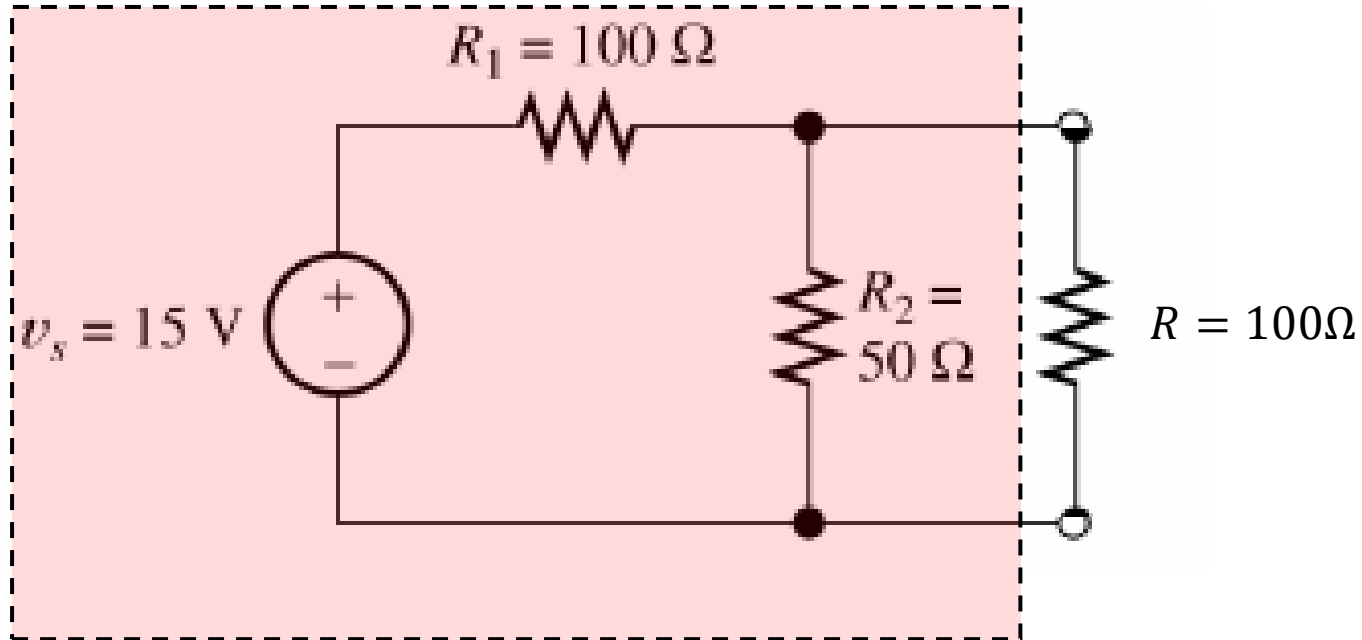

$$i = \frac{5}{33.3 + 100} \text{ A}$$


## Example

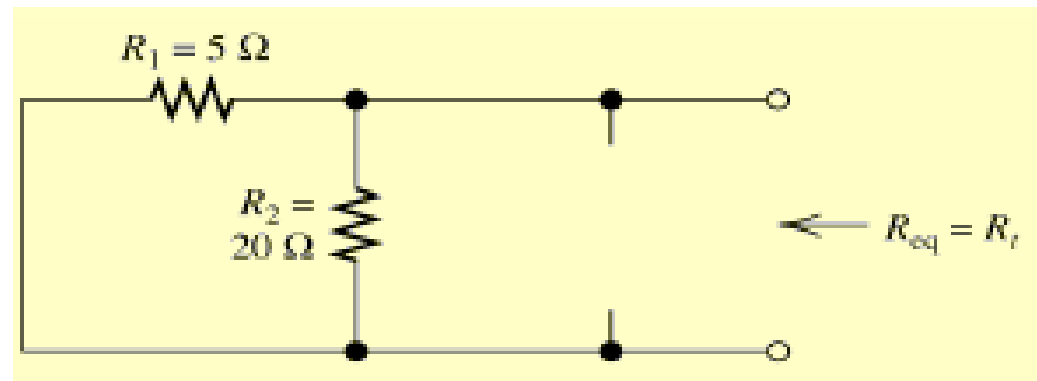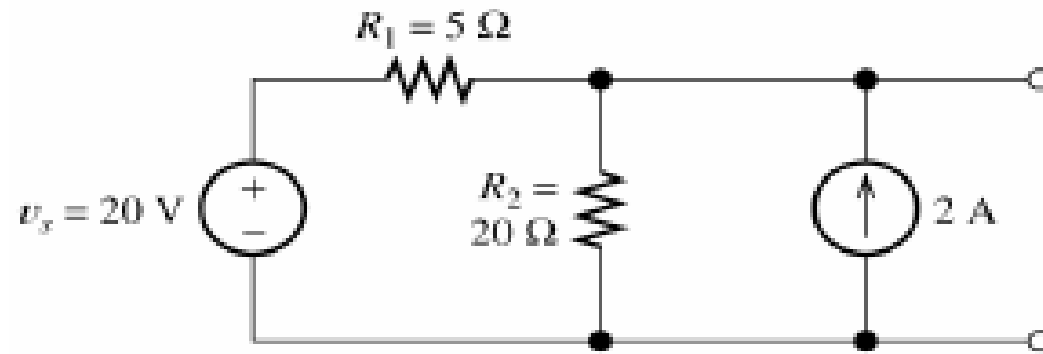


$$R_{eq} = \frac{5 \times 20}{5 + 20} = 4 \Omega$$
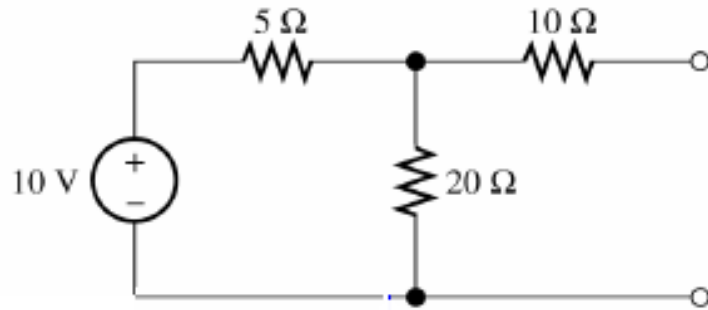
### Example


Find Thévenin resistance  $R_t$  for each of the circuits shown below


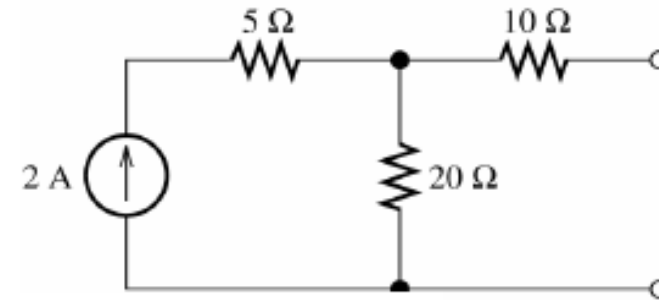
$$R_t = 10 + (5 \parallel 20) = 14 \, \Omega$$





$$R_t = 10 + 20 = 30 \, \Omega$$

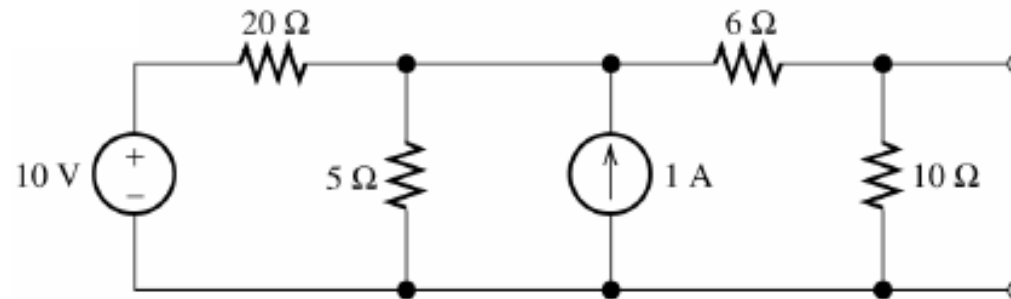


$$R_t = ((20 \parallel 5) + 6) \parallel 10 = 5 \, \Omega$$
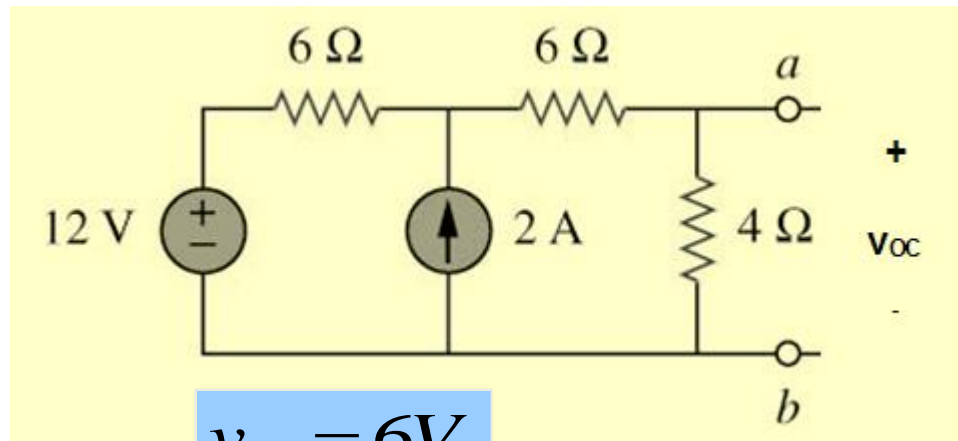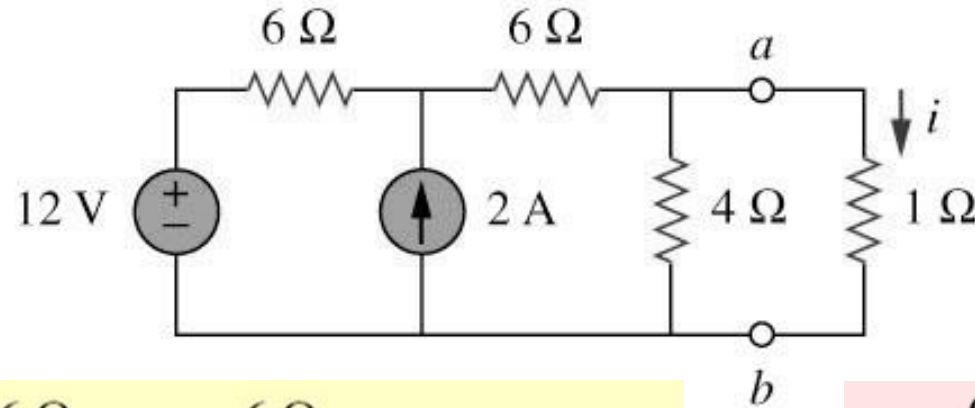
### Example


Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Hence find  $i$ .



$$v_{oc} = 6V$$

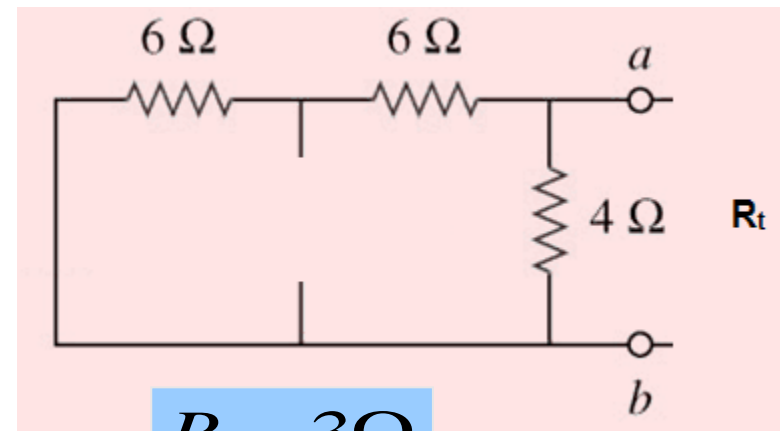


$$R_t = 3\Omega$$

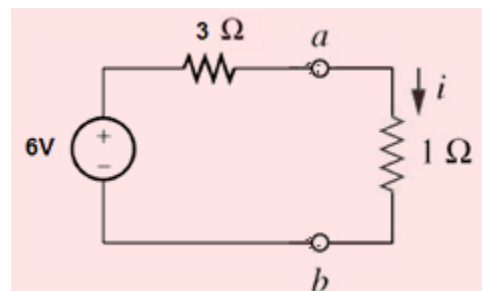


$$i = 1.5A$$

Use Superposition


$$v_{oc} = 6V$$

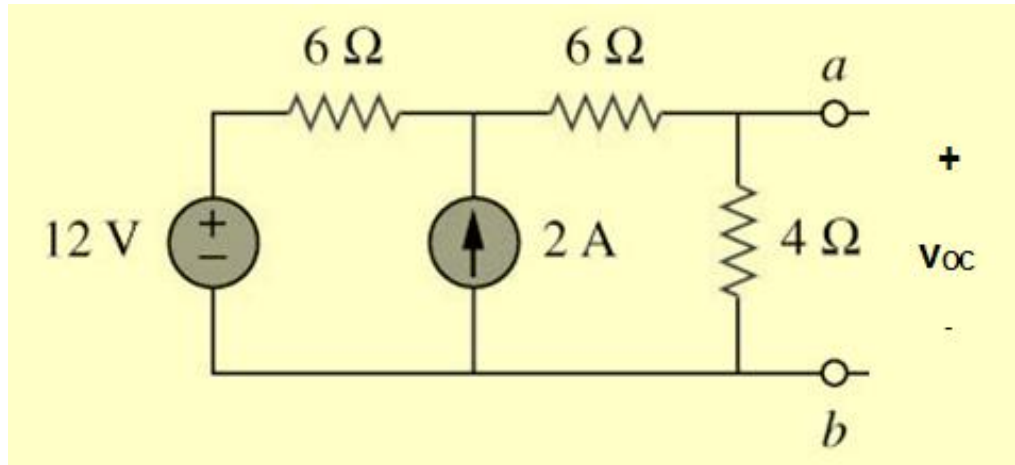

$$V_{oc} = V_{oc1} + V_{oc2} = 6$$

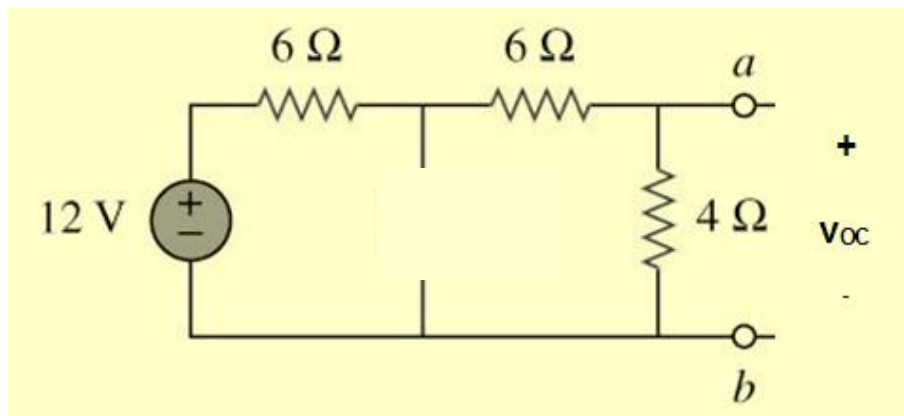


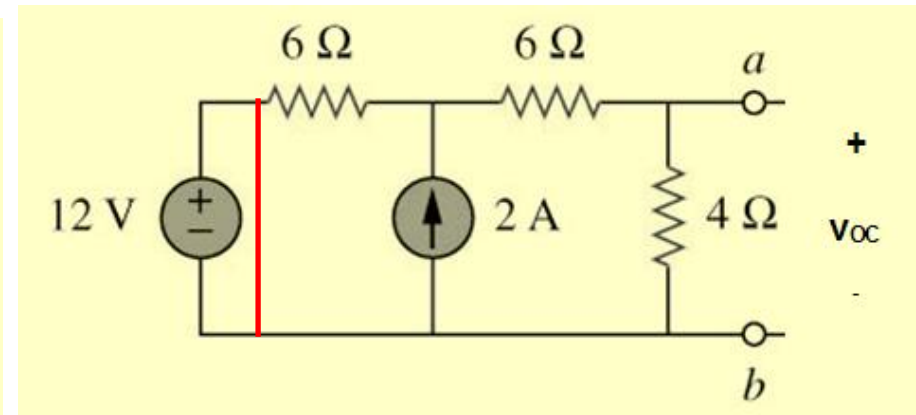
$$V_{oc1} = \frac{4}{4 + 12} \times 12 = 3$$




$$V_{oc2} = 4 \times \left( 2 \times \frac{6}{6 + 10} \right) = 3$$


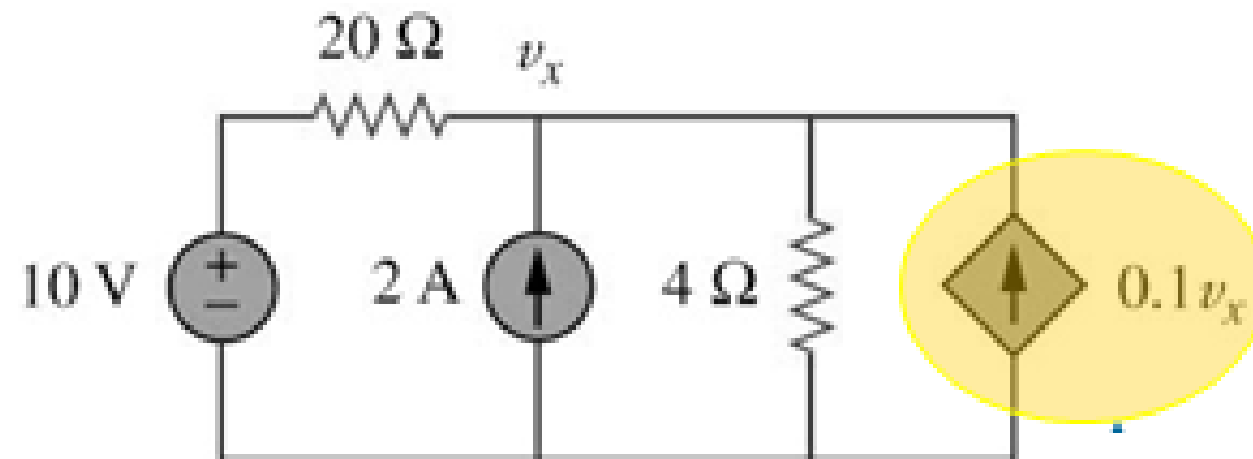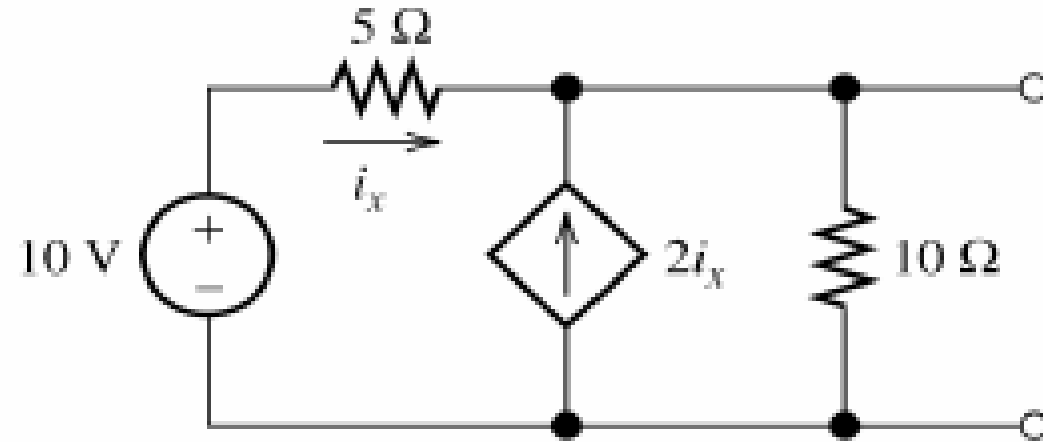
## What If There Are Dependent Power Supplies?



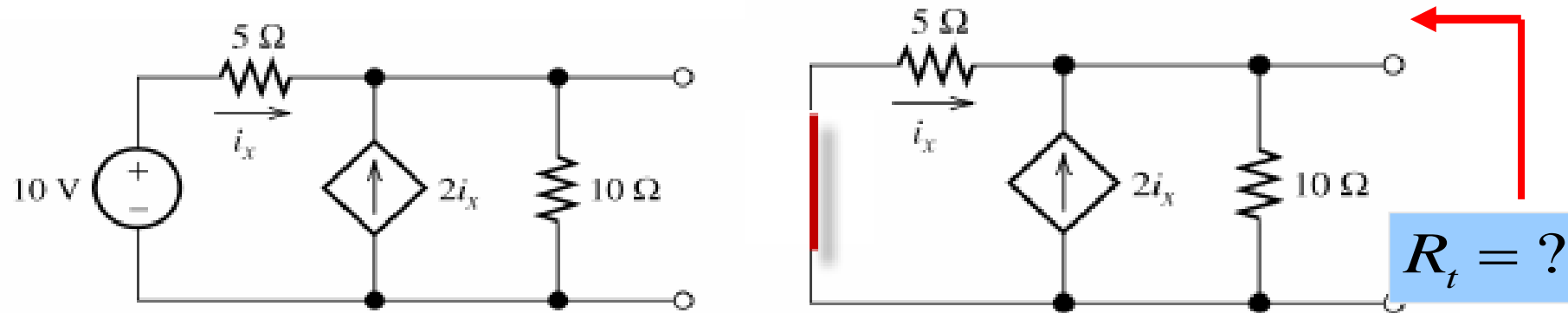
## Thévenin Resistance for Circuit with Dependent Sources



Not easy to evaluate!


Procedure:

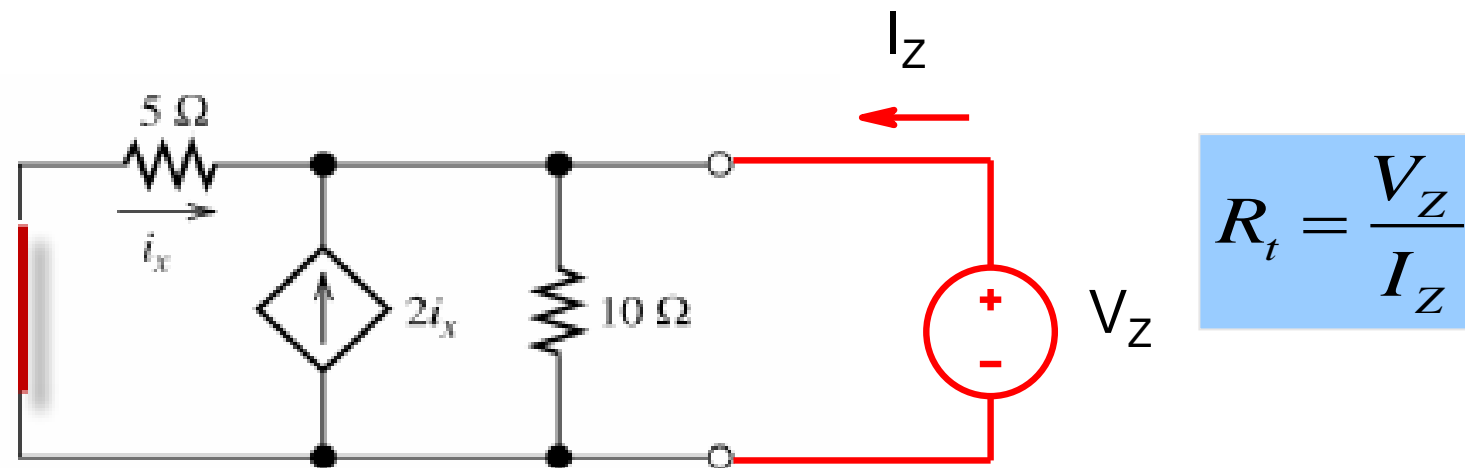Add a power sources at evaluation nodes and then evaluate  $R_t$



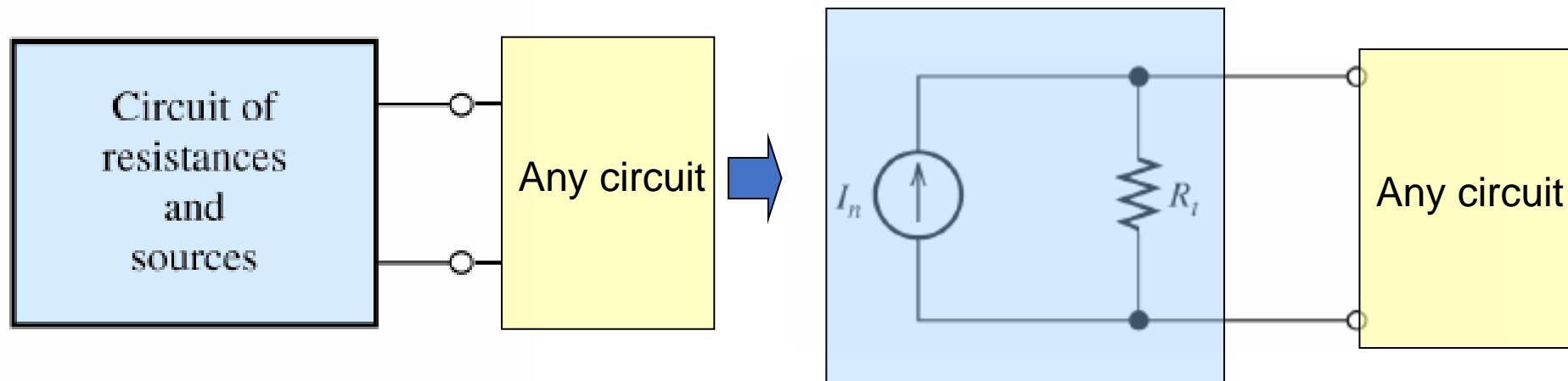
# Norton's Theorem


*"Any linear circuit containing several energy sources and resistances can be replaced by a single Constant Current generator in parallel with a Single Resistor"*




# Norton Current

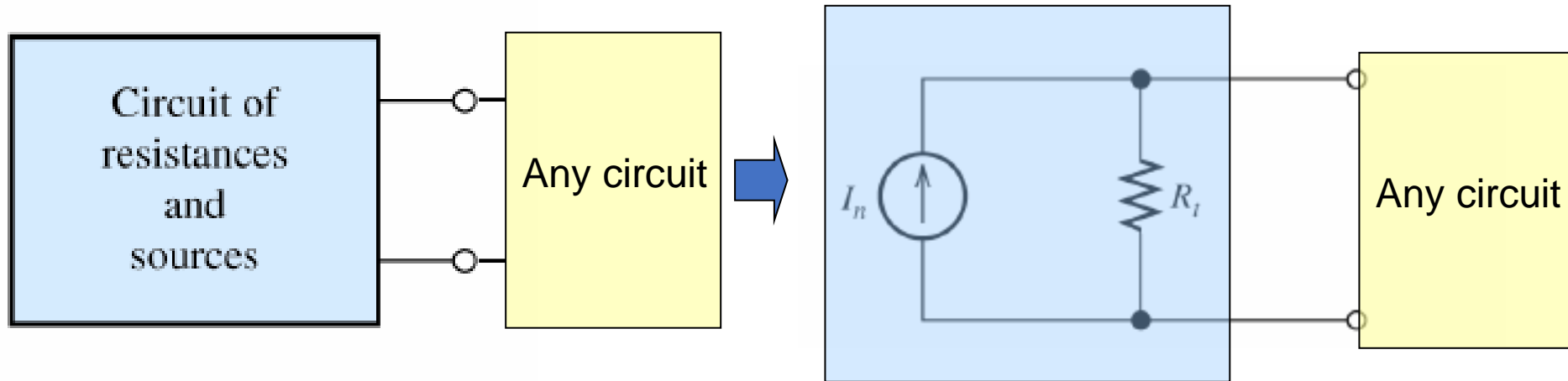



How do we find  $I_n$  ?

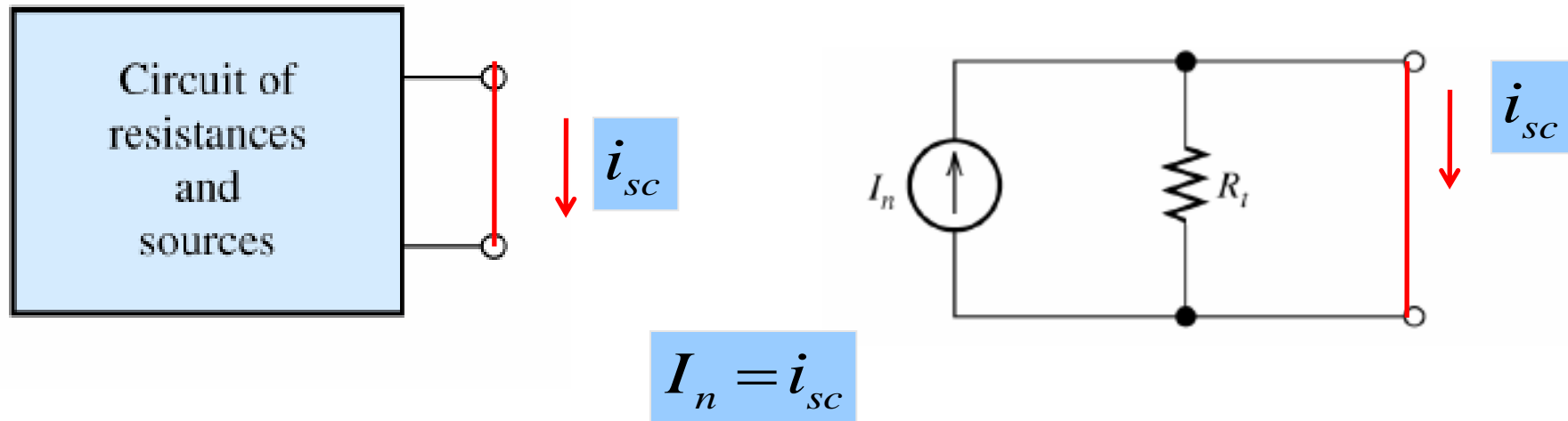

# Norton Resistance

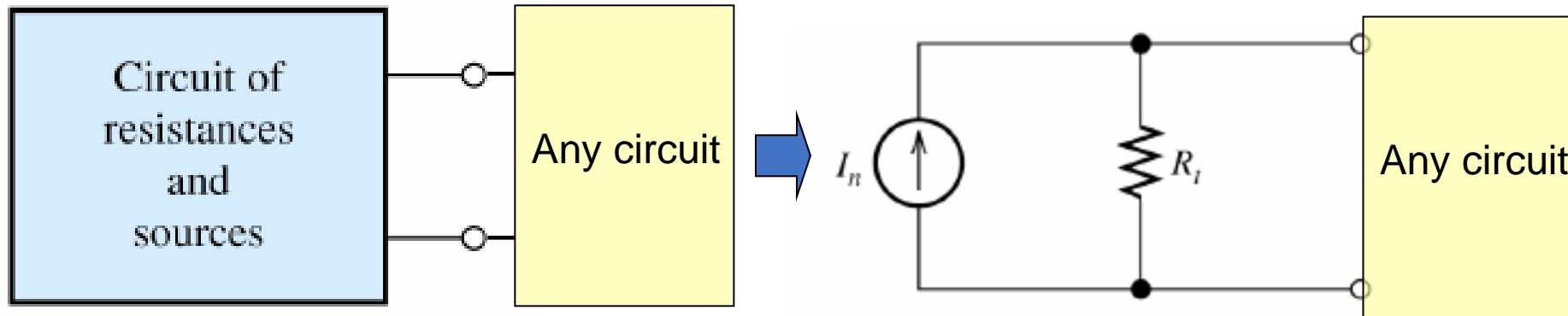



How do we find  $R_t$  ?

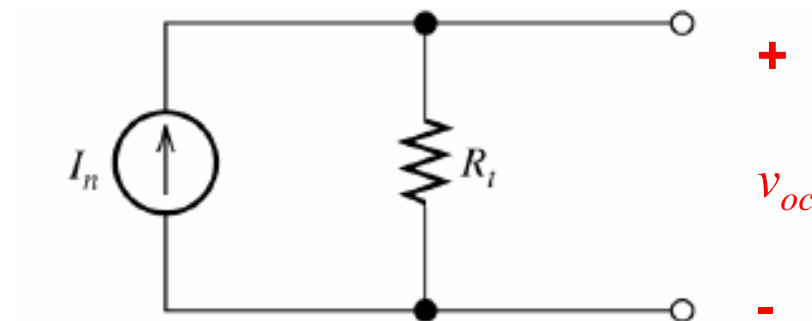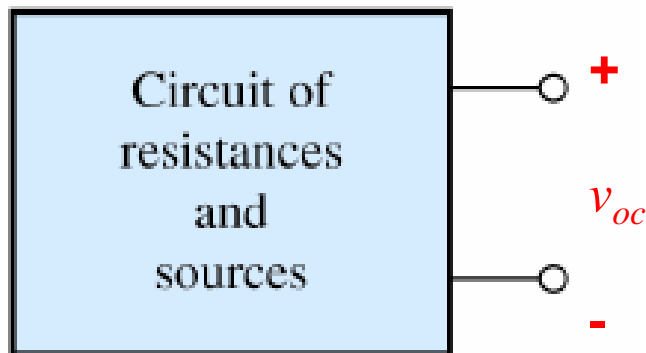

$$R_t = \frac{v_{oc}}{i_{sc}}$$

$$v_{oc} = I_n \times R_t$$

# Norton Parameters

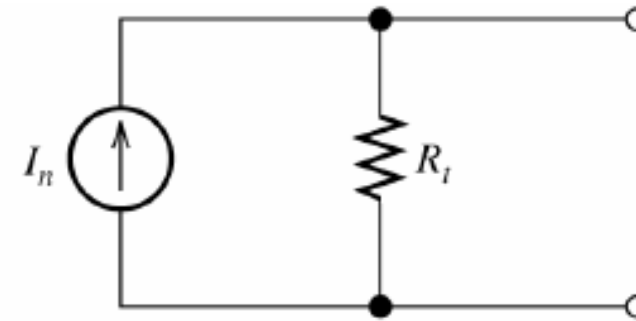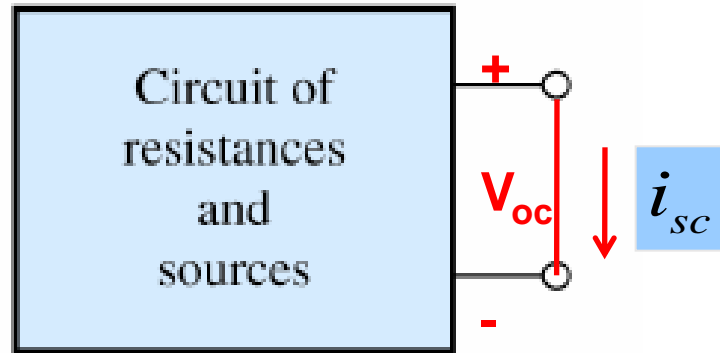


$$I_n = i_{sc}$$

$$R_t = \frac{V_{oc}}{i_{sc}}$$

Norton resistance is the same as Thévenin Resistance

# Norton Equivalent: example


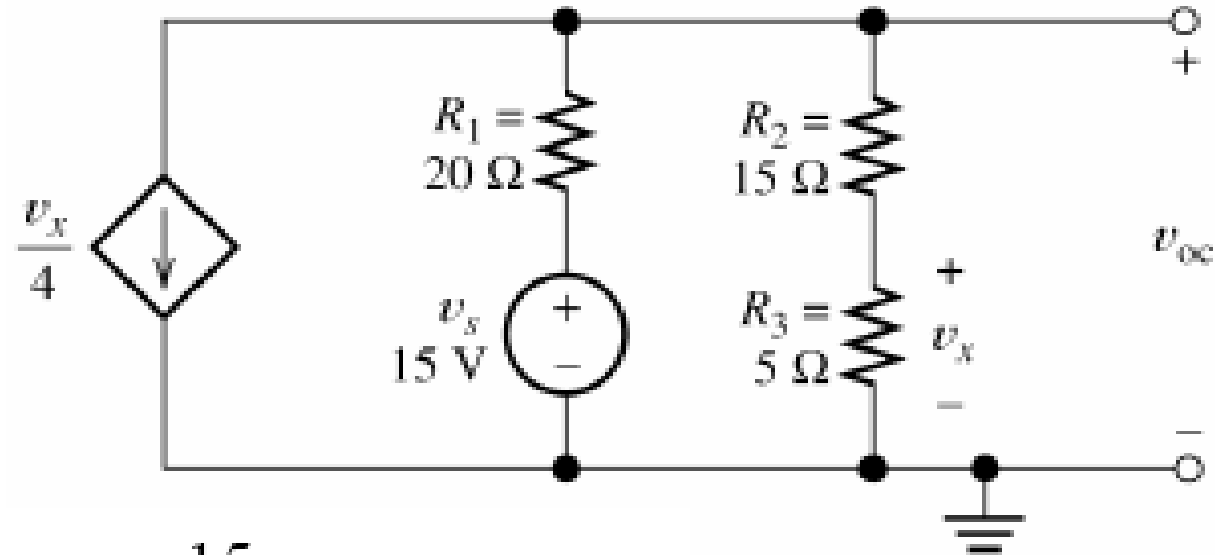


$$\frac{v_x}{4} + \frac{v_{oc} - 15}{R_1} + \frac{v_{oc}}{R_2 + R_3} = 0$$



$$v_x = \frac{R_3}{R_2 + R_3} v_{oc} = 0.25 v_{oc}$$

$$v_{oc} = 4.62\text{V}$$

# Source Transformation

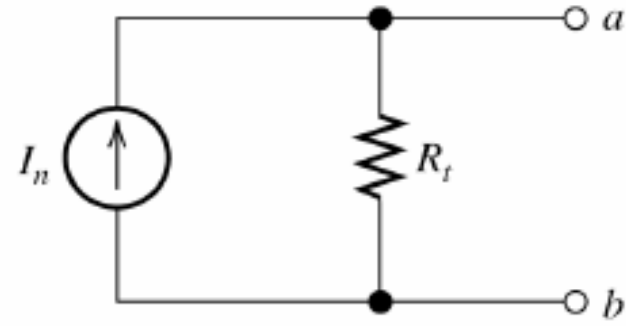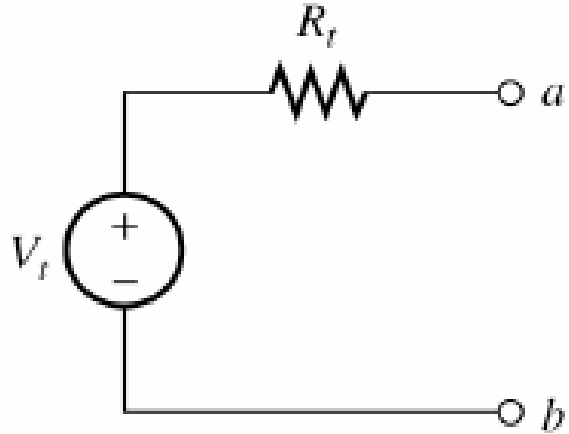




$$I_n = \frac{V_t}{R_t}$$

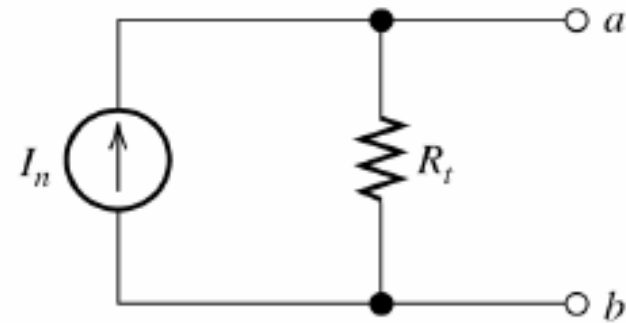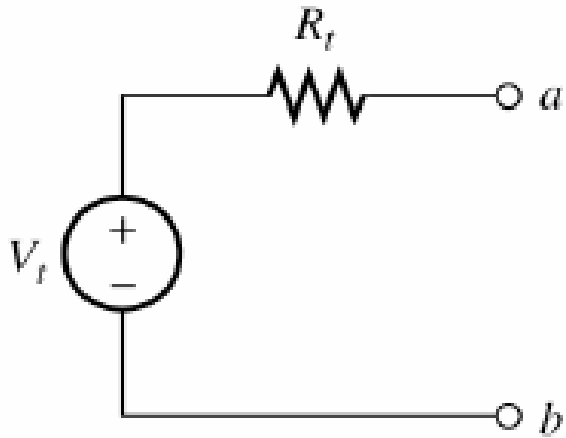

$$V_t = I_n \times R_t$$





## Example

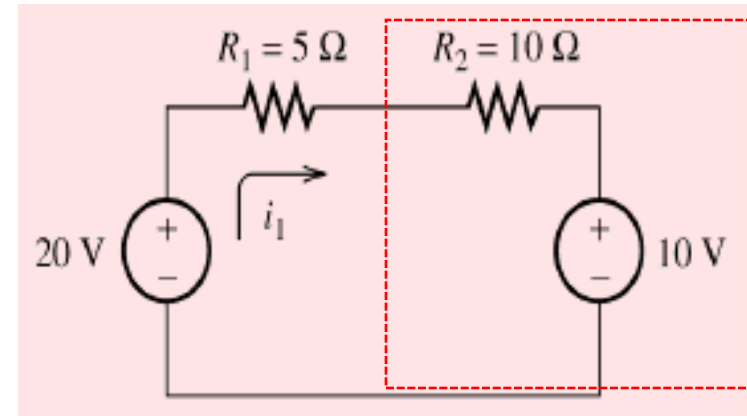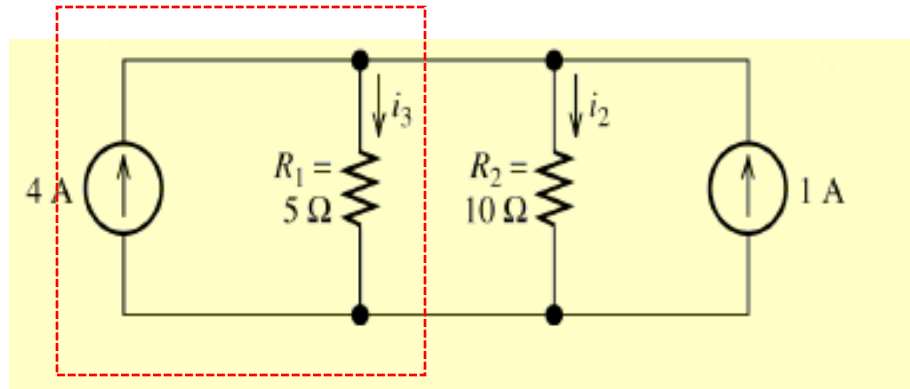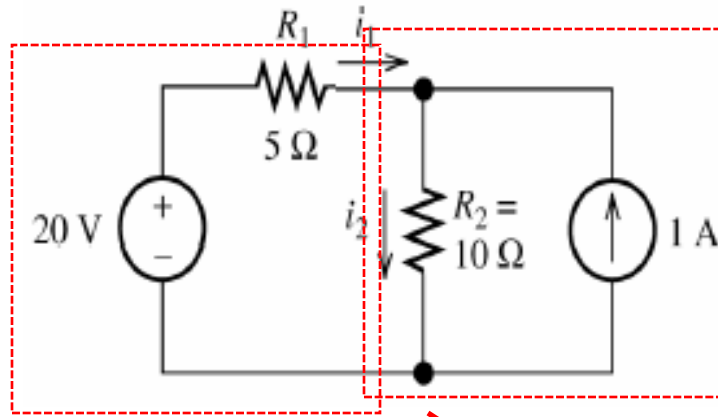


# Summary

## Series/Parallel resistances

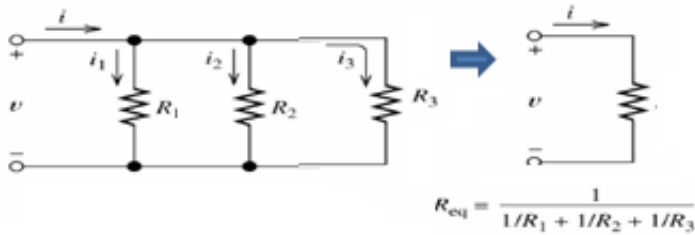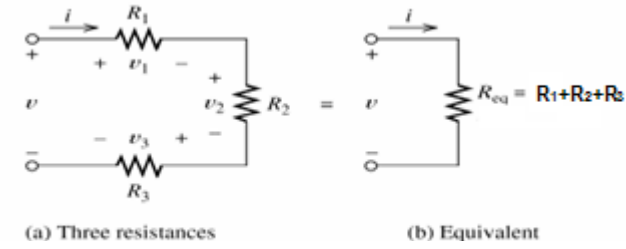

## Nodal Analysis:

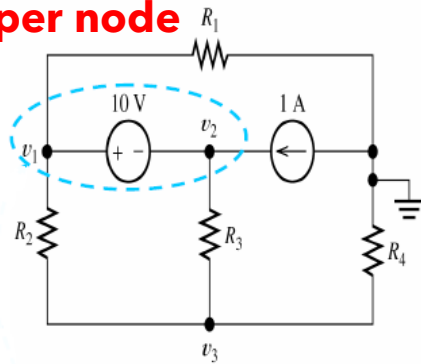
1. Identify and number the nodes
2. Choose a reference node
3. Write KCL for each node such that Sum of currents leaving a node is zero



## Mesh Analysis



1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
2. Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

## Voltage division

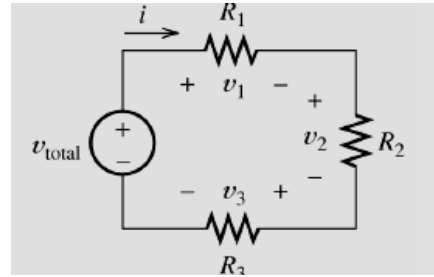


$$v_2 = R_2 i = \frac{R_2}{R_1 + R_2 + R_3} v_{total}$$

## Current division

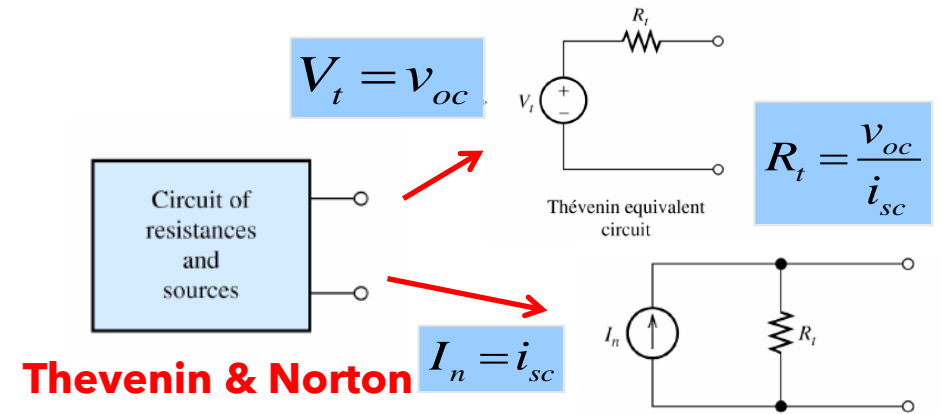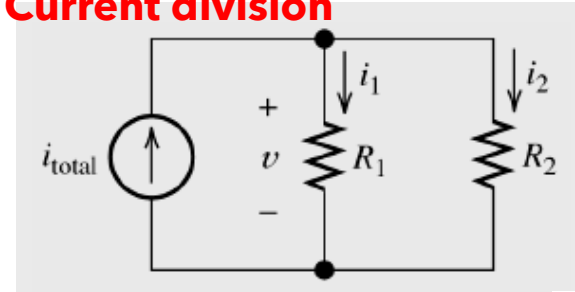

## Thevenin & Norton

## Source Transformation

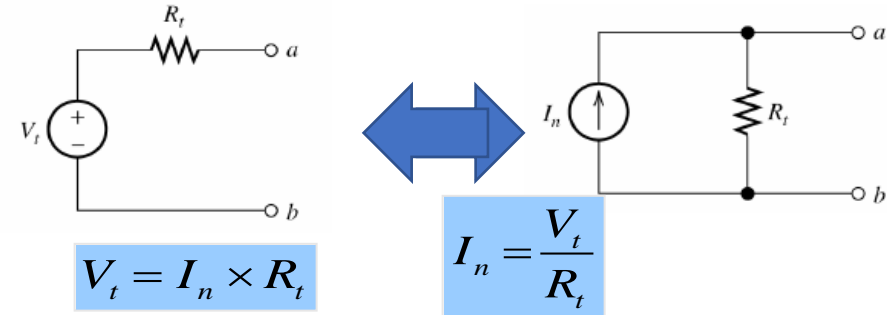

The **superposition principle** states that the total response is the sum of the responses to each of the independent sources acting individually.