

Name: Shubham Sahay Roll. No.

Department of Electrical Engineering,
Indian Institute of Technology, Kanpur

ESC201
Total Marks: 5

Mini-Quiz III


04/02/2025
Time: 10 minutes

Instructions

- Please write your name and roll number first.
- Read the question carefully and answer it in the question paper itself.

- 1) For sinusoidal input sources, use the superposition principle and find the current through the inductor in the steady state. (4 marks)
- 2) Can you still apply the superposition principle if the inputs are no longer sinusoidal but replaced by triangular pulses? If yes, why? If not, why? (1 mark)

$\omega = 10^6 \text{ rad/s}$

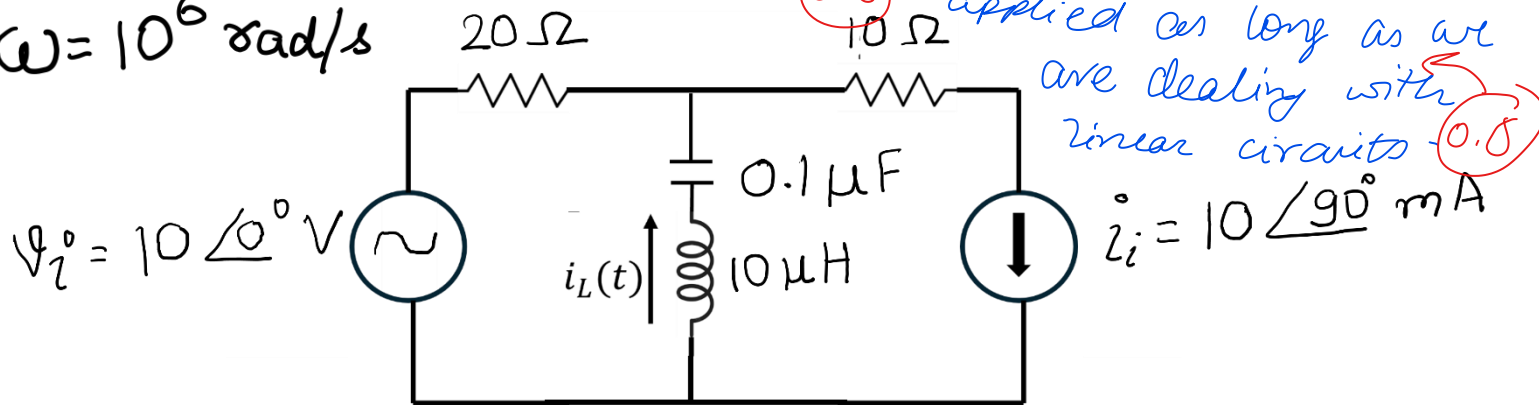

0.5 → Yes, superposition can be applied as long as we are dealing with linear circuits. 0.5

→ Considering only V_1 ; i_1 can be open circuited.

Eq. ckt. \Rightarrow




$Z_C = \frac{-j}{\omega C} = -j10$

$Z_L = j\omega L = j10$

$i_L(t) = \frac{10 \angle 0^\circ}{j10 + 20 \Omega - j10} = -0.5 \angle 0^\circ \text{ A}$

This -ve sign is important since it tells about initial phase of current through inductor in the given direction.

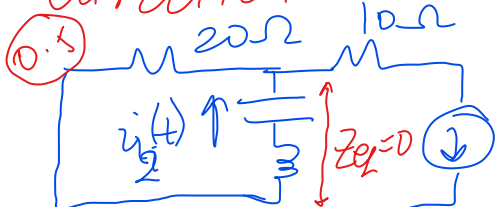→ Eq. ckt only considering i_1 (shorting V_1)



→ "0" impedance means a short circuit $\therefore i_1$ flows entirely through inductor $\Rightarrow i_L(t) = i_1 = 10 \angle 90^\circ \text{ mA}$

$\therefore i_L(t) = i_{L1} + i_{L2} = -0.5 \angle 0^\circ + 0.01 \angle 90^\circ \text{ A}$