

→ Give full credits if students have used the formula :  $\text{Max. power transferred} = \frac{V_{Th}^2}{4R_{Th}}$

Name: Shubham Sanay Roll. No. ....

Department of Electrical Engineering,  
Indian Institute of Technology, Kanpur

ESC201  
Total Marks: 5


Mini-Quiz I

21/01/2025  
Time: 10 minutes

Instructions

- Please write your name and roll number first.
- Read the question carefully and answer it in the question paper itself.

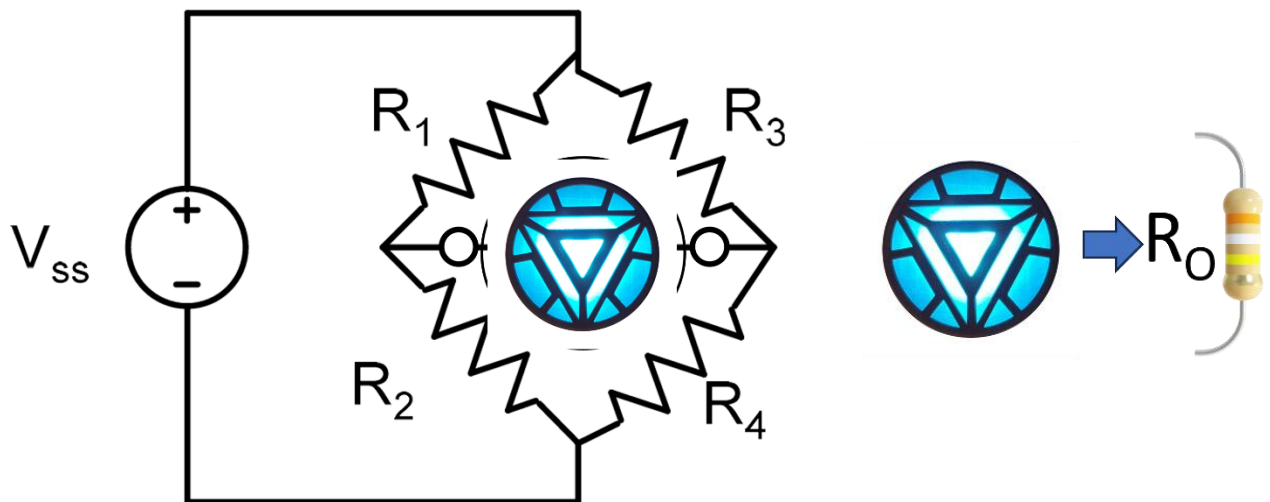- 1) Tony Stark wants to design his arc reactor, represented by a lumped load resistor  $R_0$ , such that it gets maximum power delivered from the following circuit:
  - (a) Help the Iron man by finding out the appropriate value of  $R_0$  so that maximum power is delivered to his arc reactor. (2 marks)
  - (b) What is the value of the maximum power delivered to the arc reactor? (3 marks)



→ To find out the maximum power transfer, Let us construct the Thevenin equivalent ckt. →

→ For maximum power transfer from the source;  $R_0 = R_{Th}$  ①

→ Let us find  $R_{Th}$  first. ∴ short  $V_{ss}$  & then find equivalent resistance

→  $R_1$  &  $R_2$  are connected b/w a & c  $R_1 || R_2$   
 $R_3$  &  $R_4$  " " " b & c  $R_3 || R_4$

$$\therefore R_{Th} = R_{a-b} = (R_1 || R_2) + (R_3 || R_4) = R_0$$

→ Let us find out  $V_{Th} = V_{oc} = V_a - V_b$

→ By voltage division ∴  $V_{Th} = V_{ss} \left[ \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right] = V_a - V_b$

$V_a = V_{ss} \left[ \frac{R_2}{R_1 + R_2} \right]$  → Current through  $R_0 = i_{R_0} = \frac{V_{Th}}{R_{Th} + R_0}$  ①  
 $V_b = V_{ss} \left[ \frac{R_4}{R_3 + R_4} \right]$  → Max. Power delivered =  $i_{R_0}^2 \cdot R_0$  ①