


## ESC201 Lab Quiz Sample Questions

- Each question is a multiple-choice type question. More than one options may be correct for a question.
- You will get either full marks or zero marks in each question. There will be no partial marking.
- To get the full marks in a question, you have to select all the correct options and only the correct options.

1. To measure the output resistance  $R_S$  of a function generator (FG) producing a 10 kHz 5 V pk-pk sine wave, one measures the open circuit voltage to be  $V_{OC}$ , and then connects a known resistance  $R_L$  across the terminals of the FG and measures the voltage across  $R_L$  to be  $V_L$ . The output resistance  $R_S$  is given by
- ☐  $R_S = R_L * (V_{OC} + V_L) / V_L$ .
  - ☐  $R_S = R_L * (V_{OC} - V_L) / V_L$ .
  - ☐  $R_S = R_L * (V_{OC} / V_L)$ .
  - ☐ None of the above.

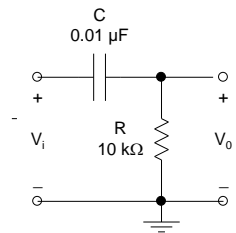
2. The circuit shown on right is a good integrator for a square wave of time period  $T$ , when (where  $\tau$  is the associated time constant)

- ☐  $T \gg \tau$ .
- ☐  $T \approx \tau$ .
- ☐  $T \ll \tau$ .
- ☐ None of the above.



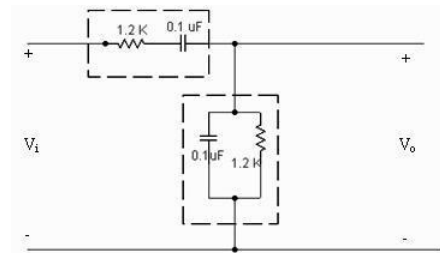3. The circuit shown in the figure on right will work as a

- ☐ low pass filter.
- ☐ high pass filter.
- ☐ band pass filter.
- ☐ band stop filter.



4. Consider the experiment in which the I-V characteristics of normal diode and Zener diode are measured with the help of a difference amplifier circuit. The output of the difference amplifier used in the diode I-V characterization experiment represents the current in mA with 1:1 scaling setting for the oscilloscope probe, because

- ☐ a difference amplifier always measures the current in mA for the 1:1 scaling setting for the probe.
- ☐ the difference amplifier is actually measuring the current through the 1 kΩ resistor.
- ☐ the difference amplifier is actually measuring the voltage difference across the 1 kΩ resistor.
- ☐ none of the above.

5. Which of the following statements are true for an ideal op-amp?

- ☐ The op-amp has infinite input impedance.
- ☐ The op-amp has infinite output impedance.
- ☐ The op-amp is infinite open-loop voltage gain.
- ☐ The op-amp has infinite bandwidth.

6. Consider the op-amp circuit shown on right. Without the feedback resistor  $R'$ ,

- ☐ the circuit will behave like a differentiator if input offset voltage is zero.
- ☐ the circuit will behave like an integrator if input offset voltage is zero.
- ☐ the output may saturate to either  $+V_{SAT}$  or  $-V_{SAT}$  if input offset voltage is nonzero.
- ☐ the output may oscillate between  $+V_{SAT}$  and  $-V_{SAT}$  if input offset voltage is nonzero.

