


# ESC201 Assignment 2

## Topics


Superposition, Nodal/Mesh analysis, Thevenin/Norton equivalent, Power, Transient analysis, Steady state.

## Questions

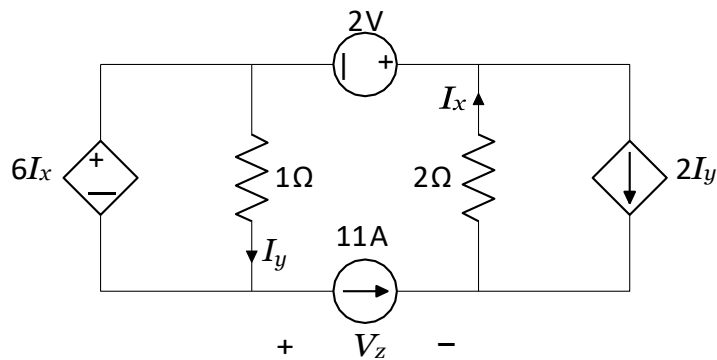
1. Determine  $I_x$ ,  $I_y$  and  $V_z$  using superposition:



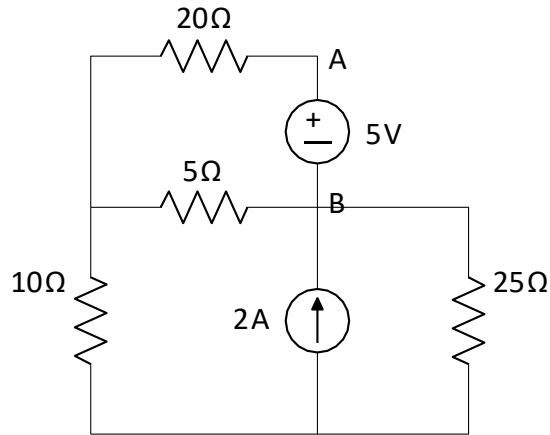
2. Determine the power supplied by the 5V source using
  - (a) Mesh analysis
  - (b) Nodal analysis
  - (c) Superposition principle
  - (d) Thevenin's equivalent circuit between terminals A and B.



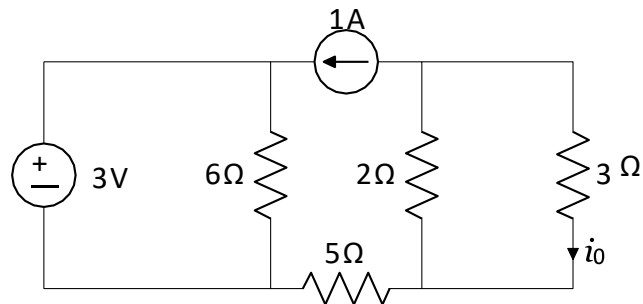
3. Use Thevenin's theorem to determine  $i_o$ .



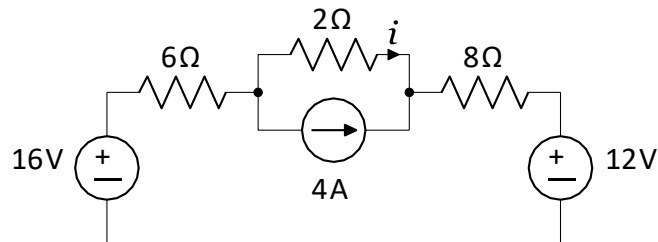
4. Determine current  $i$  through  $2\Omega$  resistor by building Thevenin's equivalent for the rest of the circuit.



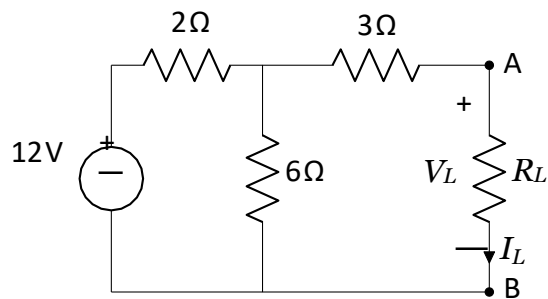
5. Find Voltage  $V_L$  across the load resistor  $R_L$ , and the current  $I_L$  flowing through the load resistor  $R_L$ , in the below circuit, by using Norton's Theorem. Where  $R_L = 1.5\Omega$ .



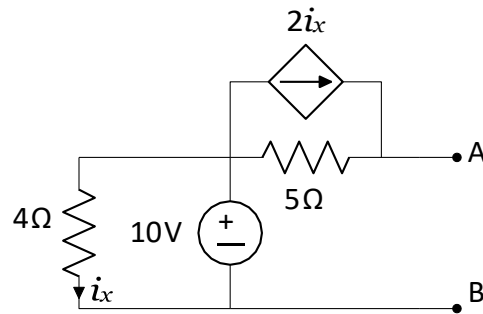
6. Find the Norton resistance  $R_N$ , and the Norton current  $I_N$ , at the terminals  $A - B$ .



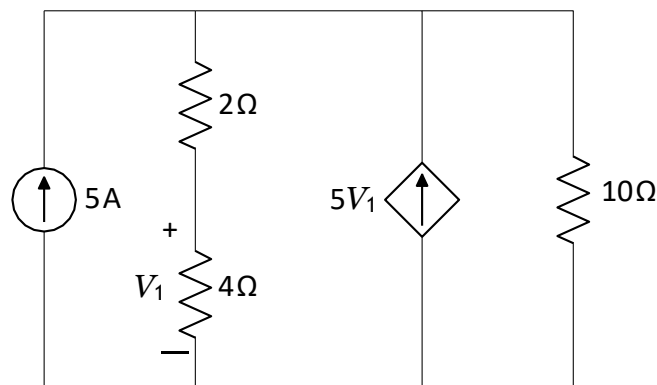
7. Determine the power dissipated in the  $10\Omega$  resistor in the following circuit



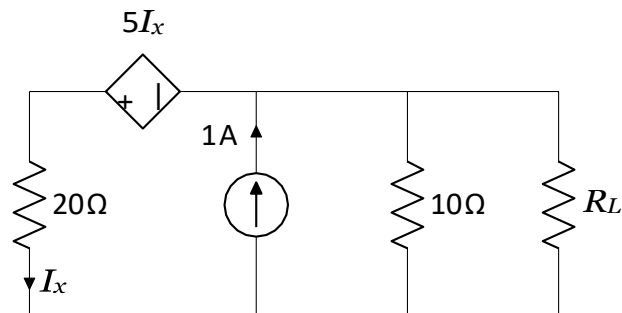
8. A practical current source provides  $10W$  to  $250\Omega$  load and,  $20W$  to  $80\Omega$  load. A resistance  $R_L$  with voltage  $v_L$  across it, and with current  $i_L$  through it, is connected to the source. Find the values of  $R_L$ ,  $v_L$ , and  $i_L$  if,
- $v_L \cdot i_L$  is maximum.
  - $v_L$  is maximum.
  - $i_L$  is maximum.
9. Determine the value of  $R_L$  in the below circuit, such that maximum power is delivered into  $R_L$ . Calculate the value of the maximum power.



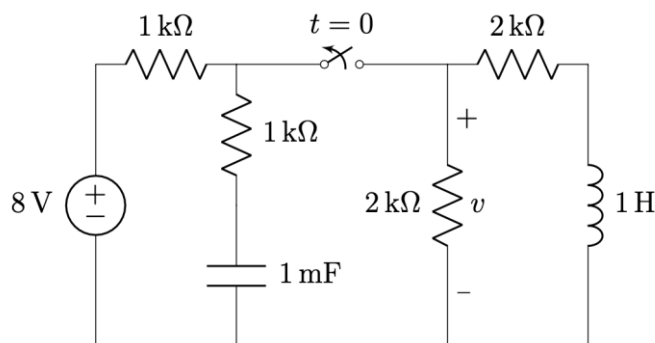
10. For the circuit shown below, determine the voltage across the 2K resistor (vertical) as a function of time after the switch is opened at  $t = 0$ .



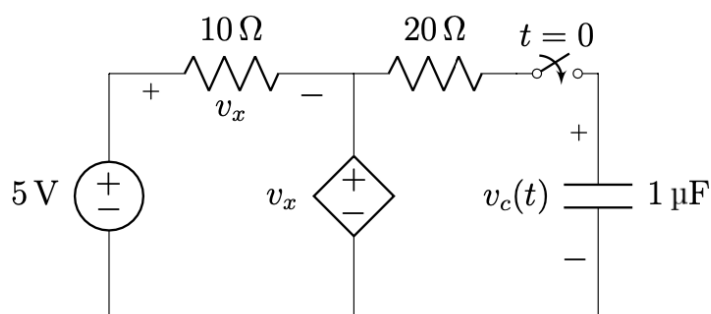11. Find  $v_c(t)$  for  $t > 0$  in the following circuit if the capacitor voltage is zero for  $t < 0$ .



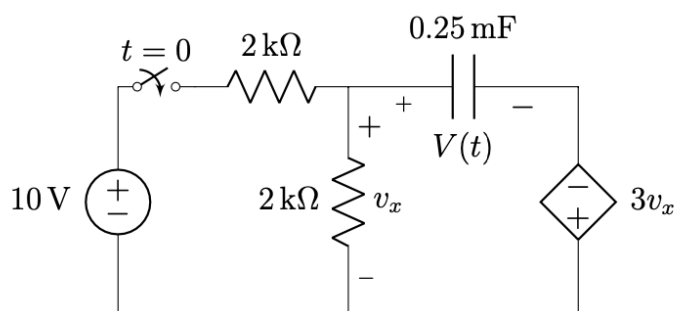12. Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor  $V(t)$  as a function of time after the switch is closed at  $t = 0$ .



13. In the following circuit the switch S1 is closed and S2 is left open for a long time. At  $t=0$ , S1 is opened and S2 is closed. Determine the current,  $i_5$ , through the 5Ω resistor for all time

