

ESC201: INTRODUCTION TO ELECTRONICS


MODULE 4: NON-LINEAR ELEMENTS




Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur

Summary: approximations


Simplicity

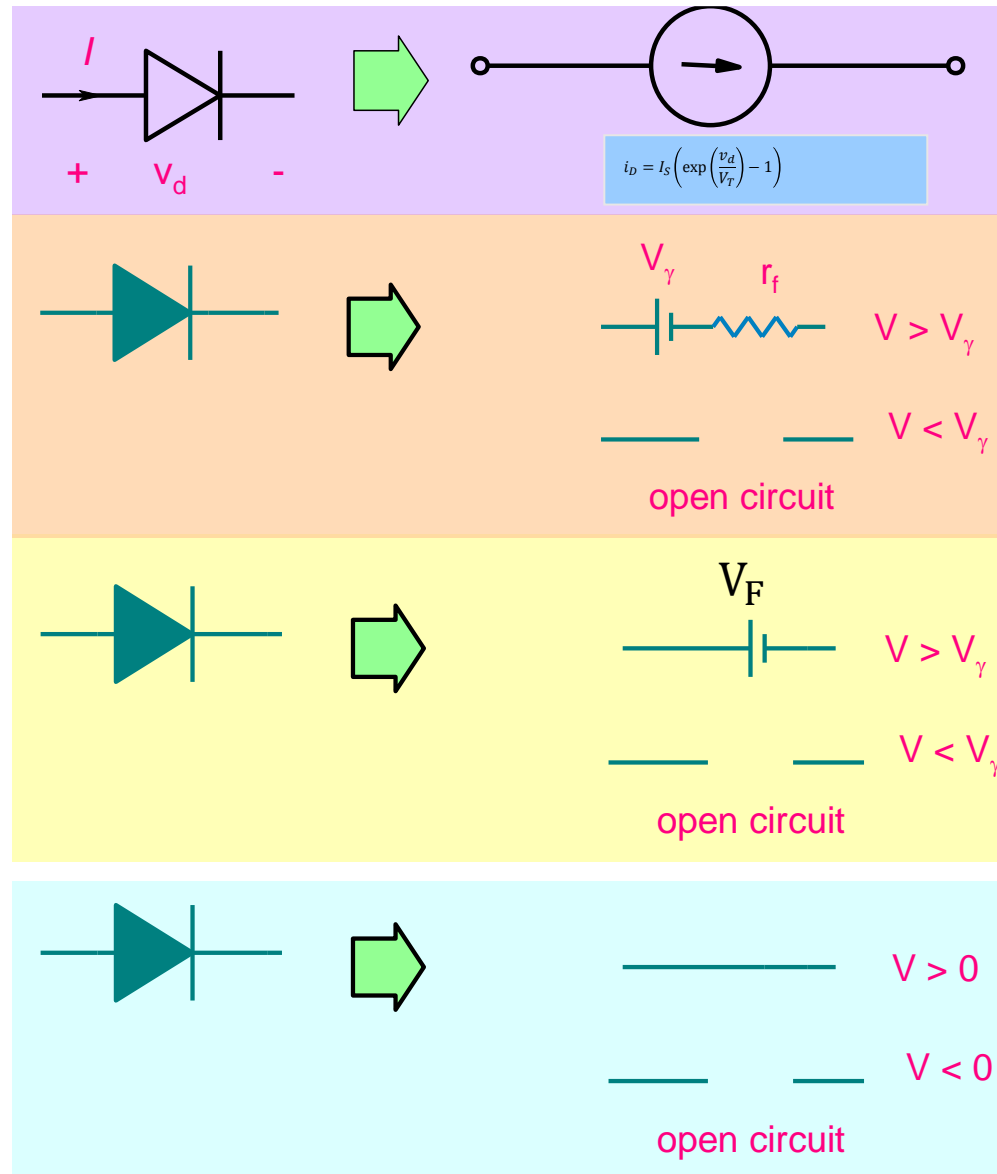


Accuracy

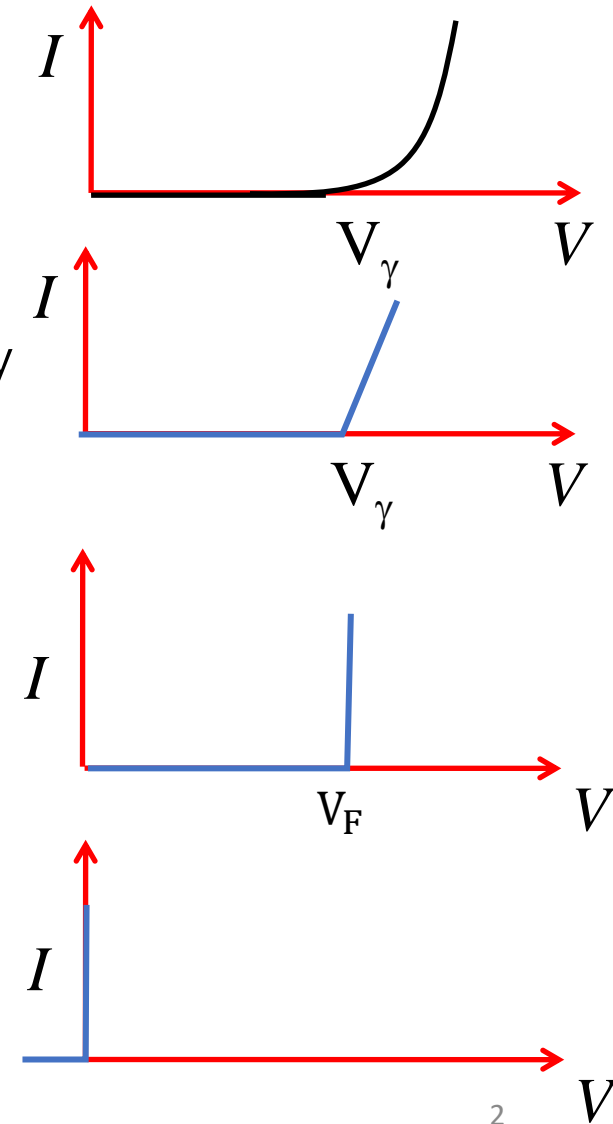


Power supply: block diagram

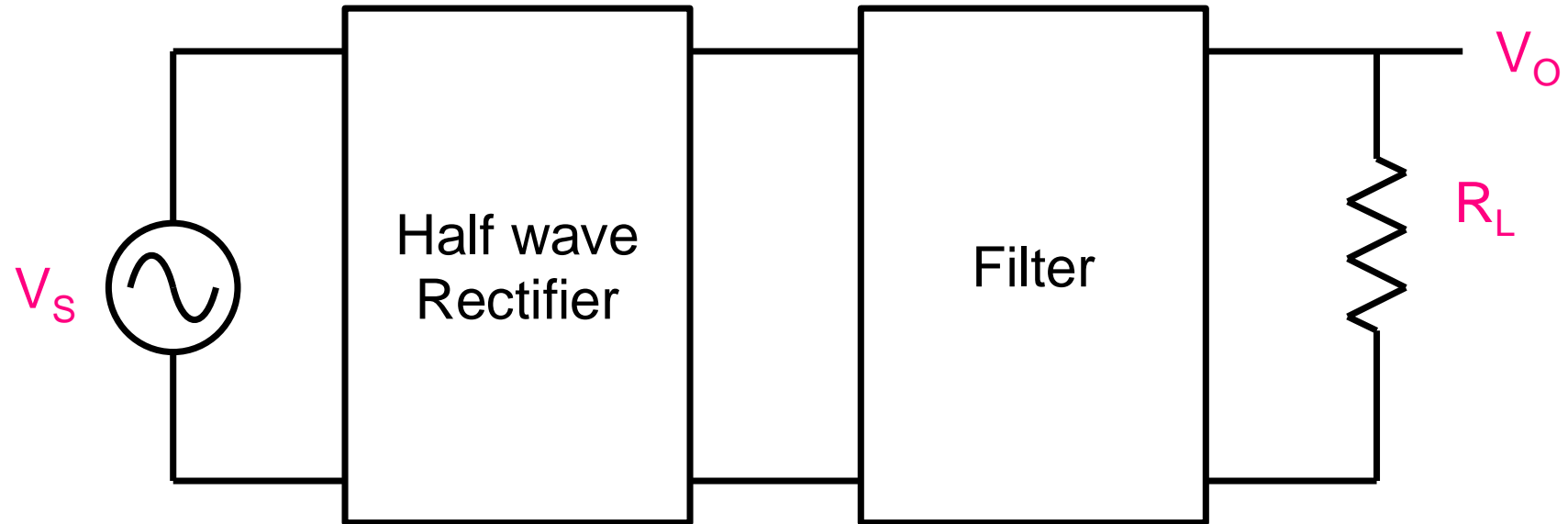


Filtered output

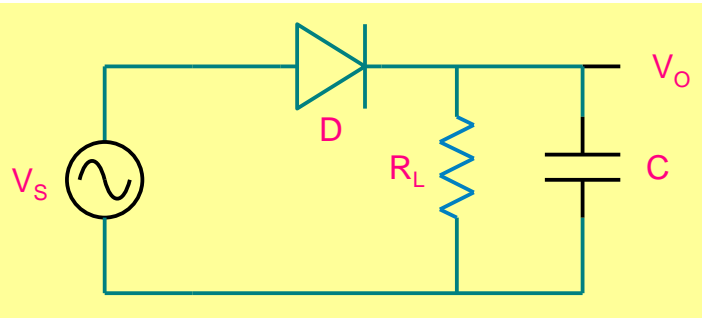


Diode is forward biased

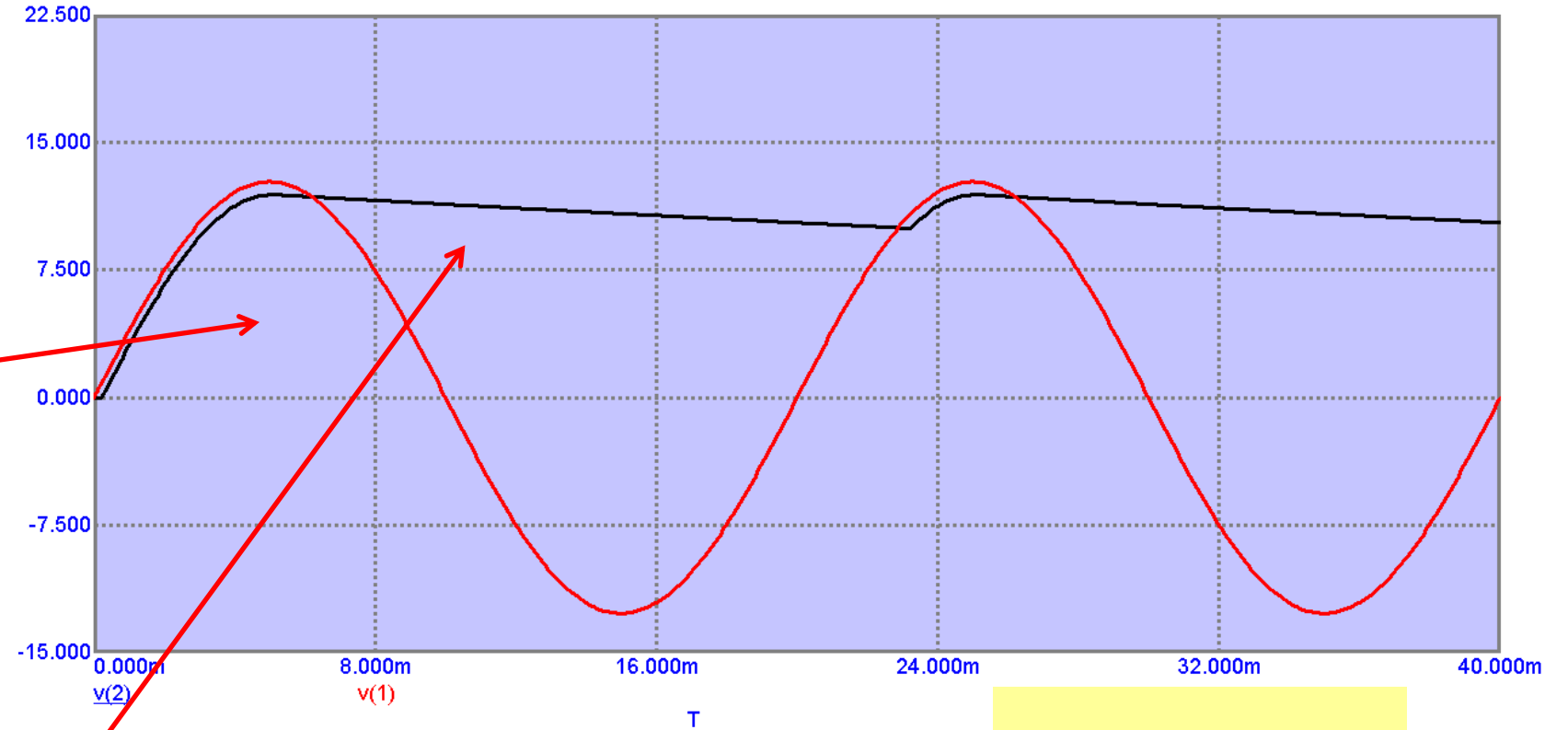

Diode is reverse biased

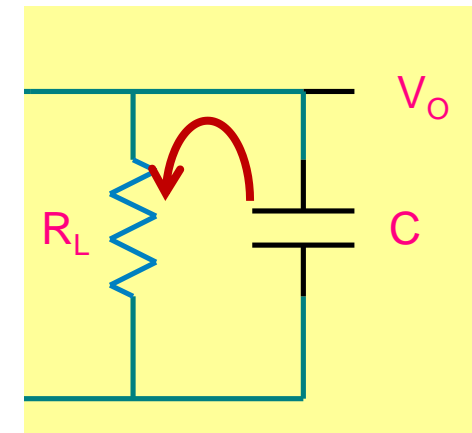

Output has a ripple

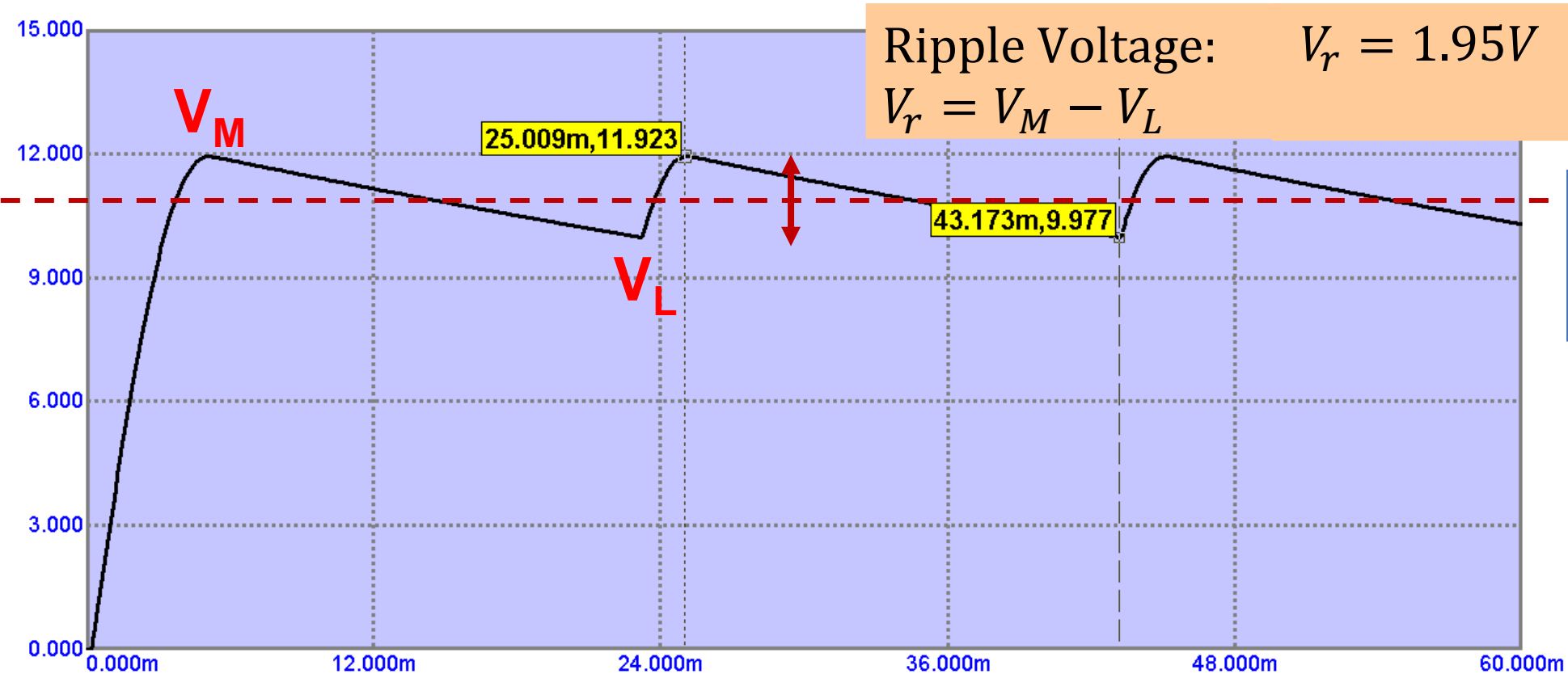

Average Output Voltage :

$$V_O(avg) \cong V_M - \frac{V_R}{2}$$


Diode inverse voltage

In practice, we must also look at diode specifications: can the diode tolerate the current and voltage?

Let the input voltage after step-down transformer is

$$V_m = 12.7 \text{ V}$$

$$V_{\gamma} = 0.7 \text{ V}$$

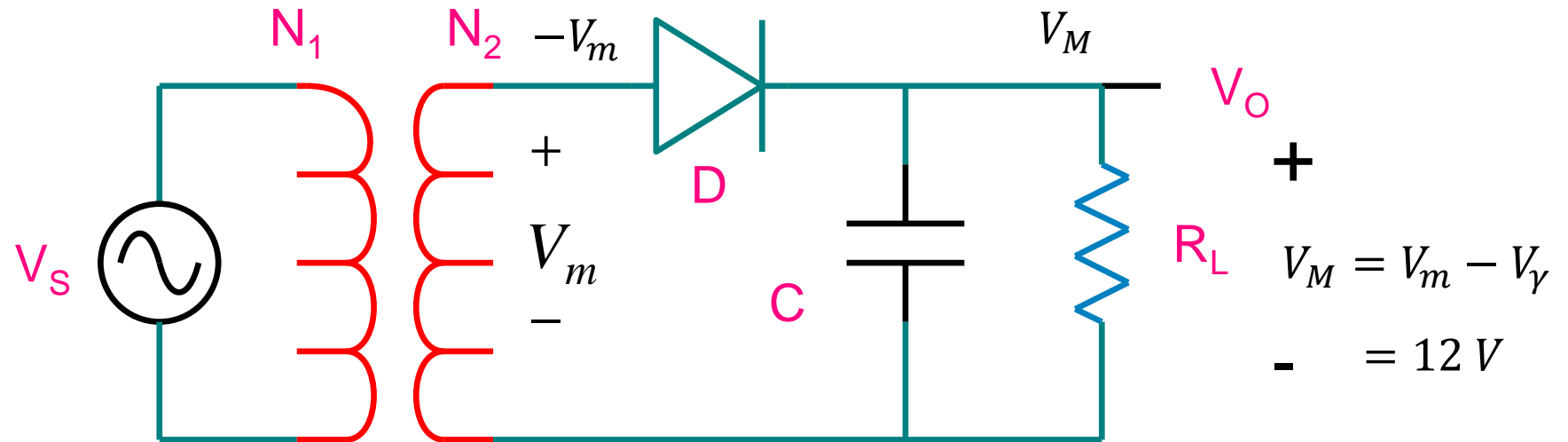


$$\text{PIV} = V_M + V_m$$


$$= 2V_M + V_\gamma$$

$$= 12 + 12.7 = 24.7 \text{ V}$$

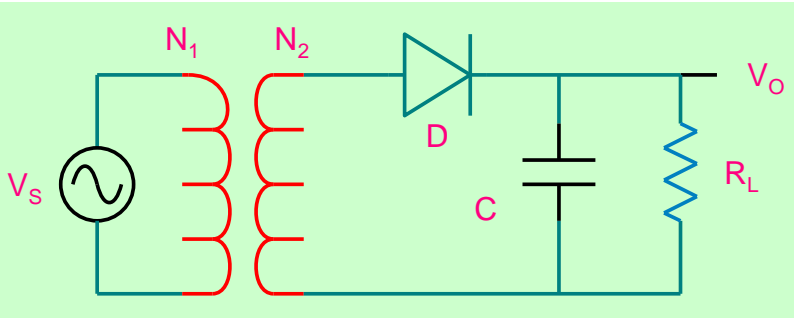
DC Power Supply using Half Wave Rectifier



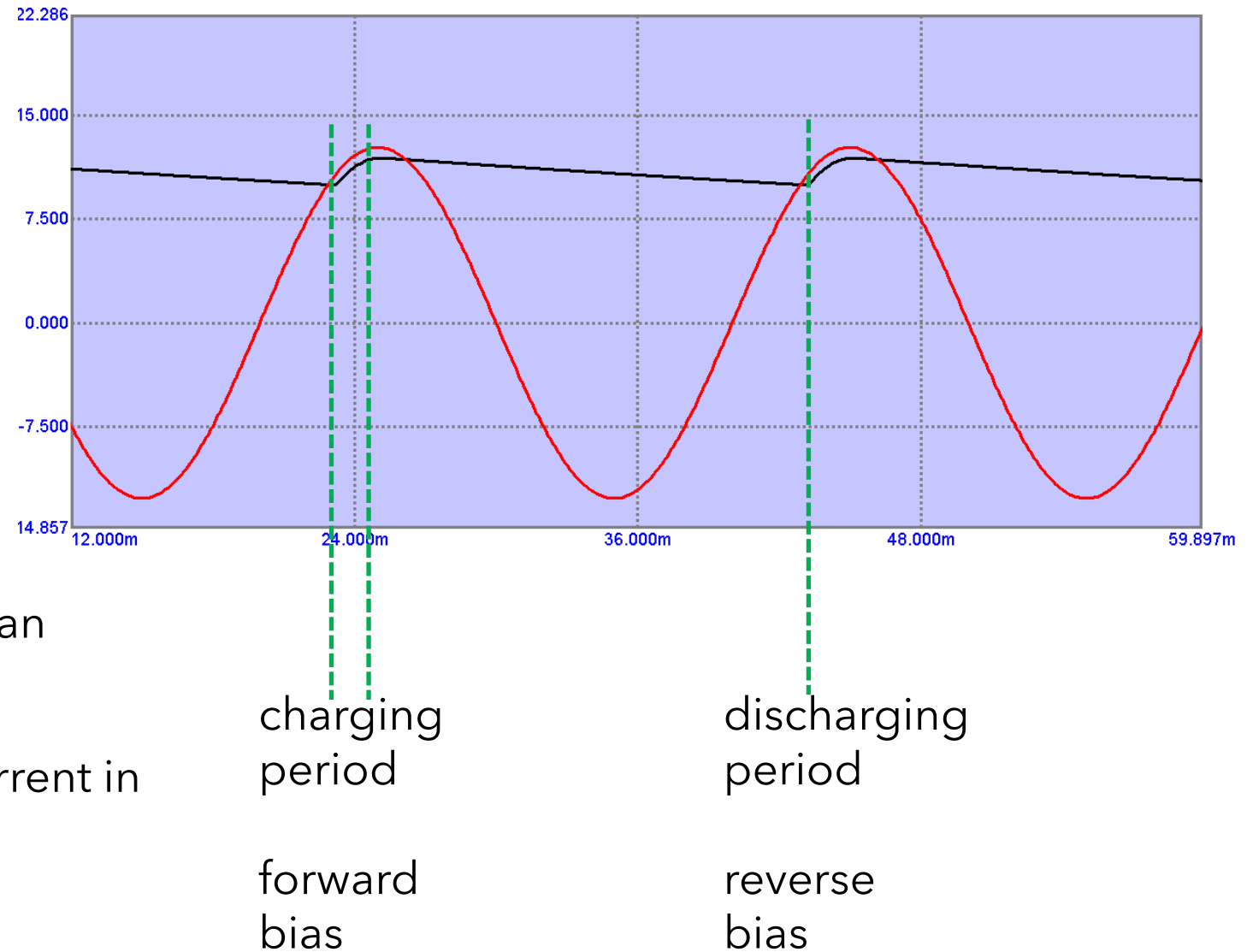
- How much current and voltage diode can handle?
- Let us calculate the maximum diode current in forward bias



Step 1

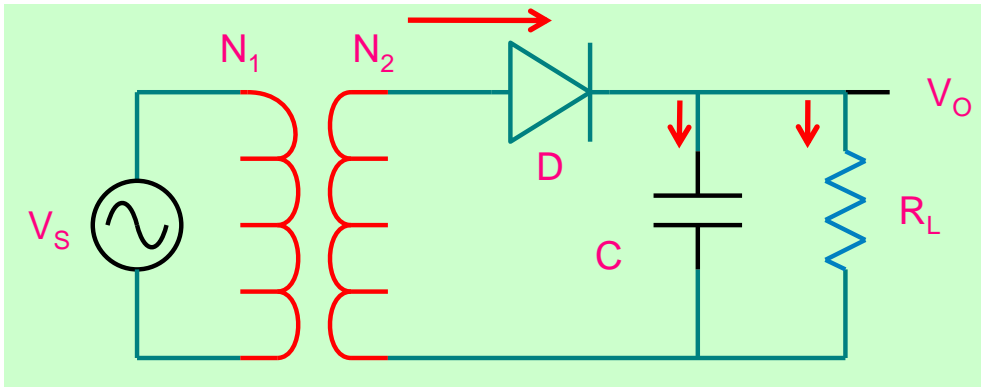
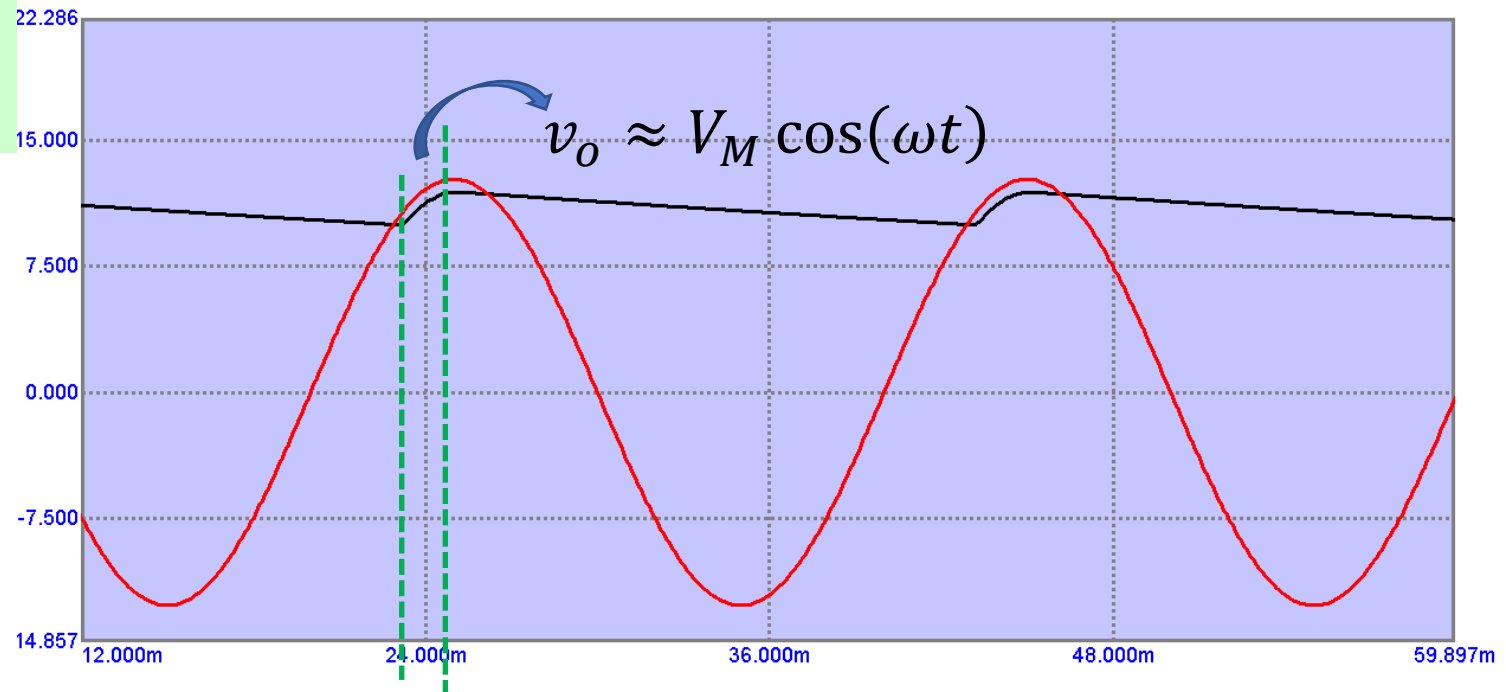
$$i_D = C \times \frac{dv_o}{dt} + \frac{v_o}{R_L}$$



$$t = -\Delta t \quad t = 0$$

Charging period
Forward Bias

Approximation:
 v_o follows input voltage when D is forward biased

Step 2

Substituting: $v_o \approx V_M \cos(\omega t)$

$$i_D = C \times \frac{dv_o}{dt} + \frac{v_o}{R_L}$$


$$i_D(t) \approx -CV_M\omega \sin(\omega t) + \frac{V_M \cos(\omega t)}{R_L}$$

Assuming a short ripple,

the charging interval $(-\Delta t, 0)$ is a small interval near $t = 0$.

In this interval, $\sin(\omega t) \approx \omega t$, and $\cos(\omega t) \approx 1 - \frac{(\omega t)^2}{2}$
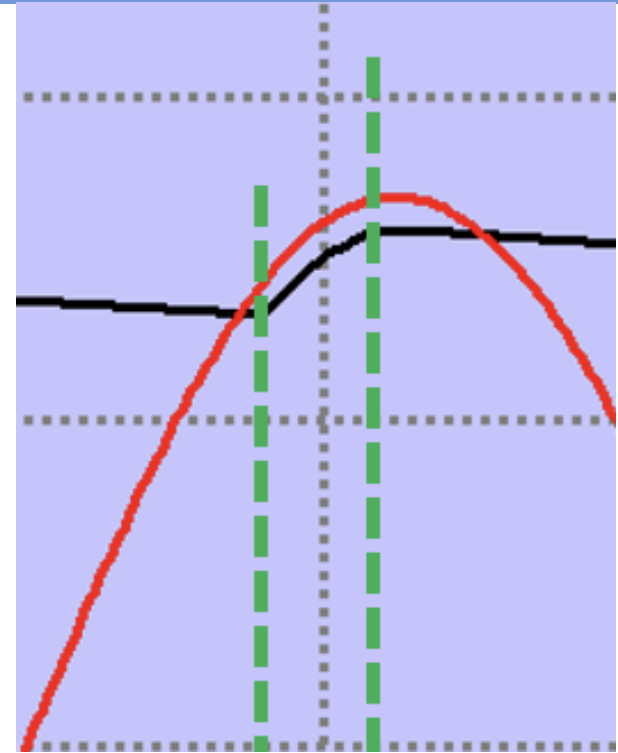
$$i_D(t) \approx -CV_M\omega^2 t + \frac{V_M}{R_L} \left(1 - \frac{(\omega t)^2}{2} \right) \approx -CV_M\omega^2 t + \frac{V_M}{R_L}$$



$t = -\Delta t$ $t = 0$

Step 2

$$i_D(t) \approx -CV_M\omega^2 t + \frac{V_M}{R_L}$$

Diode current is maximum near $t = -\Delta t$


$$i_{D,\max} \approx CV_M\omega^2 \Delta t + \frac{V_M}{R_L}$$

$$i_{D,\max} \approx CV_M\omega \sqrt{\frac{2V_r}{V_M}} + \frac{V_M}{R_L}$$

Recall $v_o \approx V_M \cos(\omega t)$

$$V_L \approx V_M \cos(\omega \Delta t) \approx V_M \left(1 - \frac{(\omega \Delta t)^2}{2}\right)$$
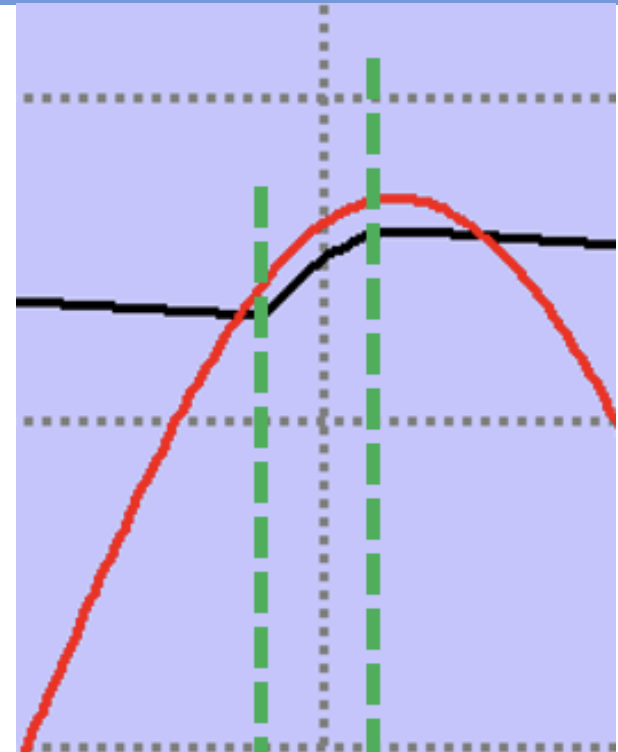
$$\Rightarrow \omega \Delta t = \sqrt{\frac{2(V_M - V_L)}{V_M}} = \sqrt{\frac{2V_r}{V_M}}$$



$t = -\Delta t$ $t = 0$

Step 3

$$i_{D,\max} \approx CV_M \omega \sqrt{\frac{2V_r}{V_M}} + \frac{V_M}{R_L}$$



- Recall that $V_r \approx \frac{V_M}{fR_L C}$

$$i_{D,\max} \approx \frac{V_M}{R_L} \left(1 + 2\pi \sqrt{2fCR_L} \right)$$


$$i_{D,\max} \approx \frac{V_M}{R_L} \left(1 + 2\pi \sqrt{\frac{2V_M}{V_r}} \right)$$

	Ripple Voltage	Max diode current
High Cap	low	high
Low Cap	high	low


Full-wave rectifier

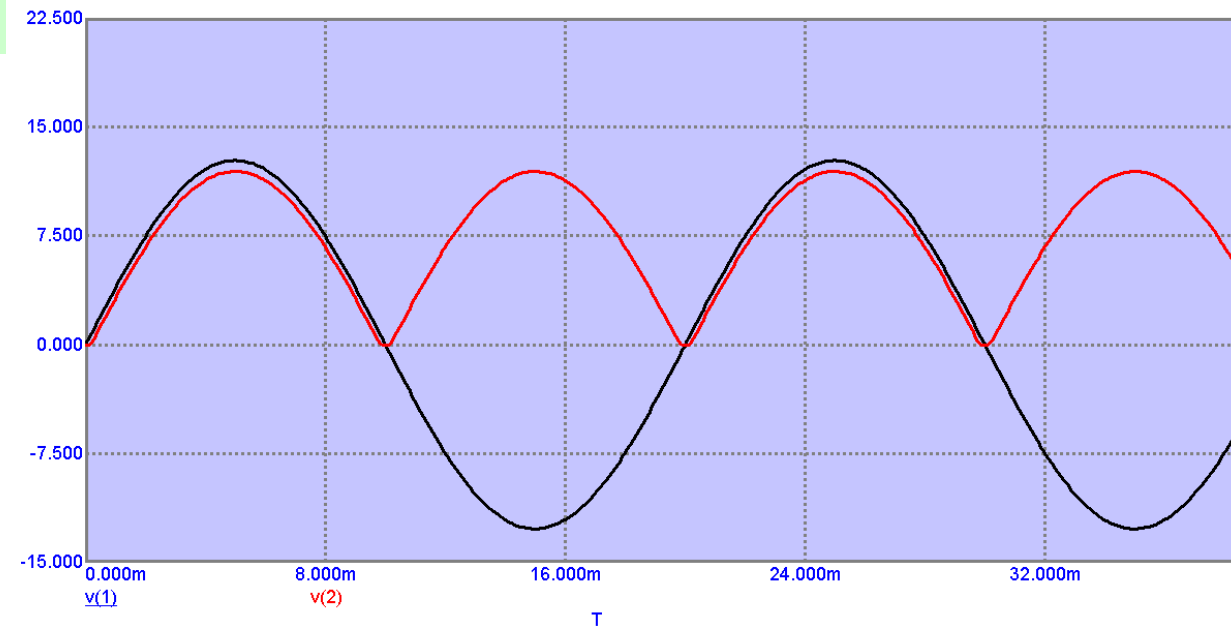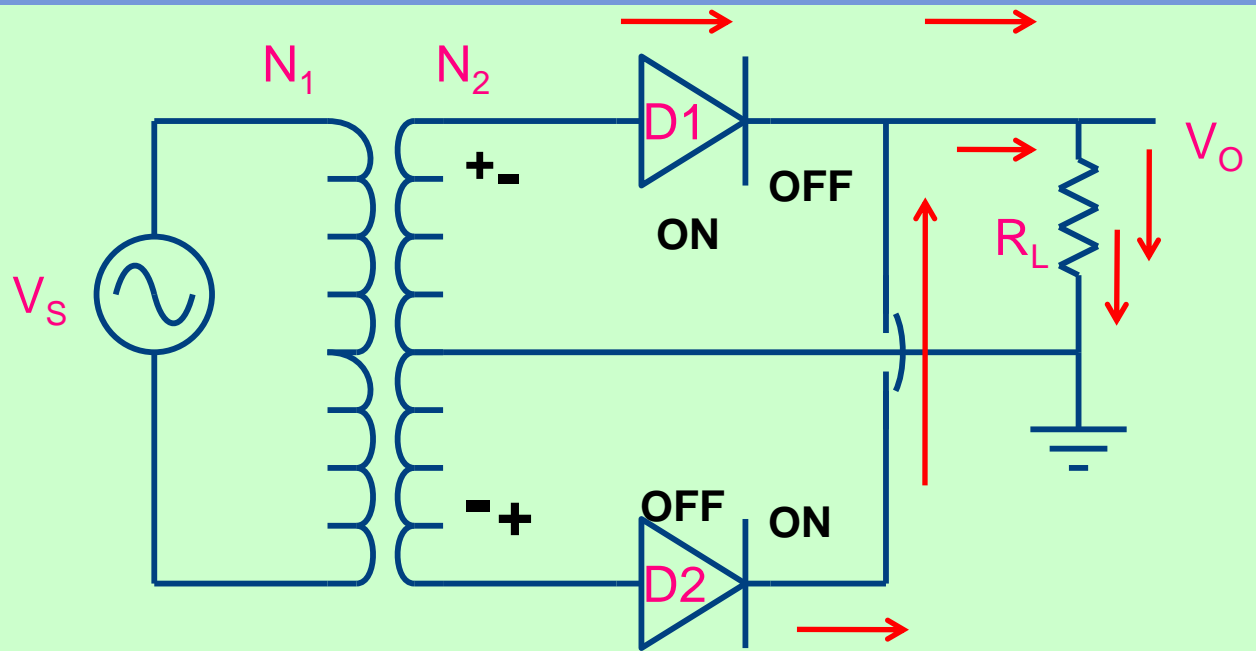

Strategy 2

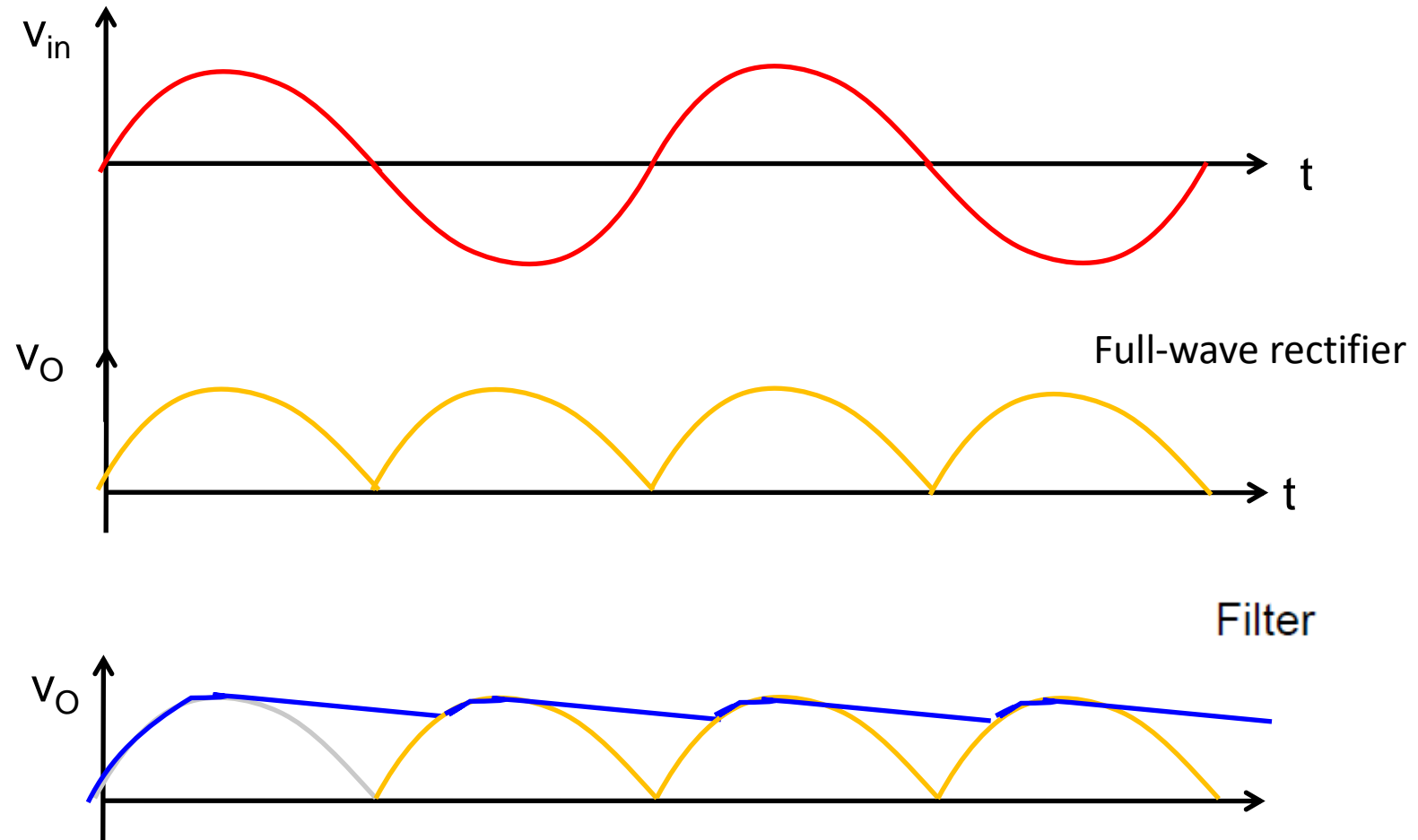

Ripple Voltage

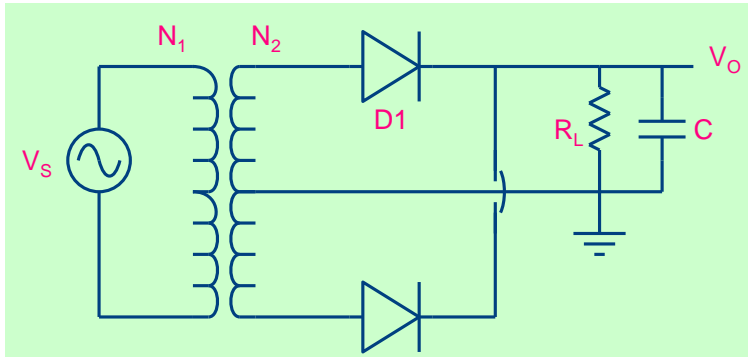

Recall the ripple voltage is


$$V_r = V_M - V_L = V_M \times \left(1 - e^{-\frac{t_1}{R_L C}}\right)$$

$$V_r \cong V_M \times \left(1 - \left(1 - \frac{t_1}{R_L C}\right)\right) = \frac{V_M t_1}{R_L C}$$


t_1 is the discharging time

$$t_1 \approx \frac{T}{2}$$

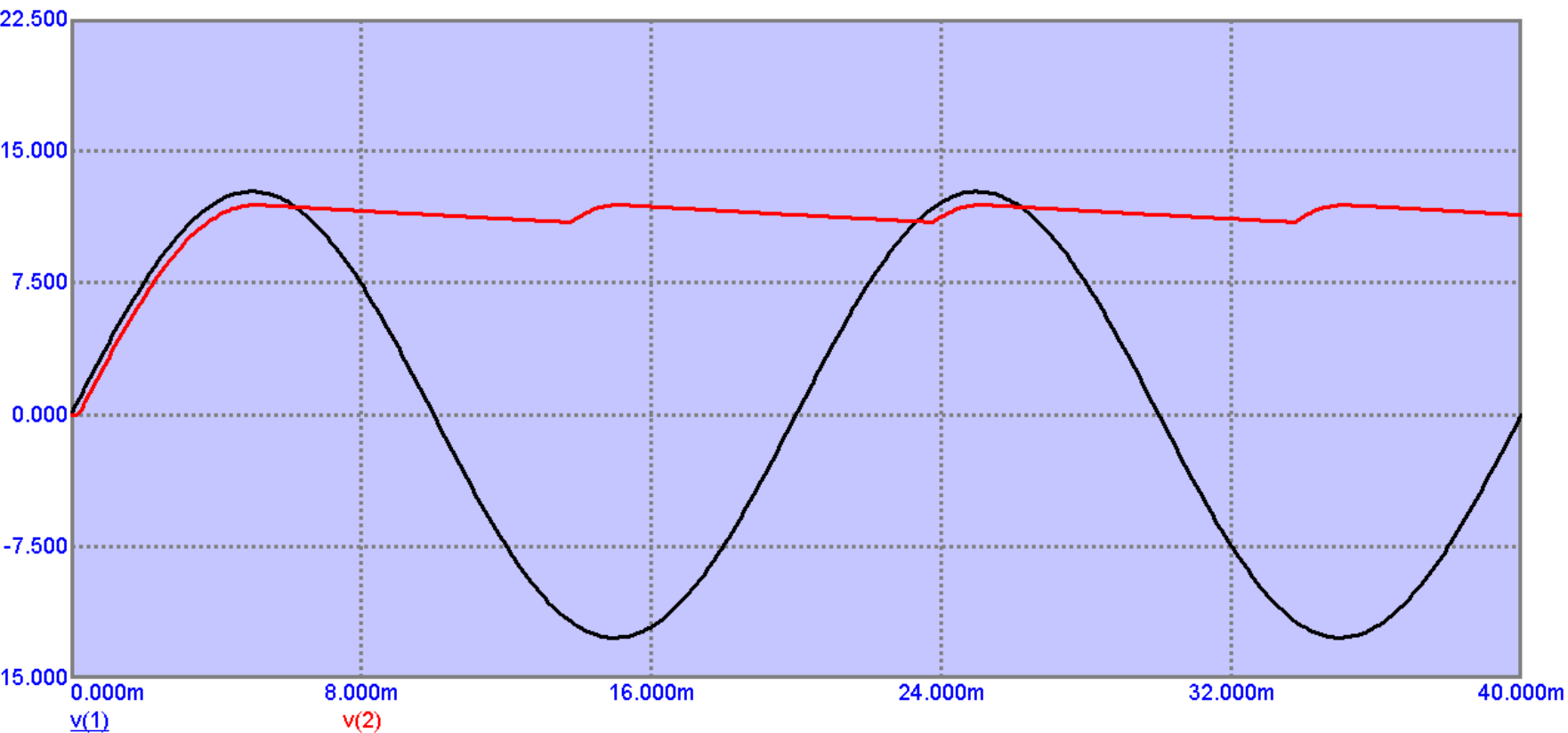
$$V_r = \frac{V_M t_1}{R_L C} \cong \frac{V_M T}{2 R_L C}$$




Comparison

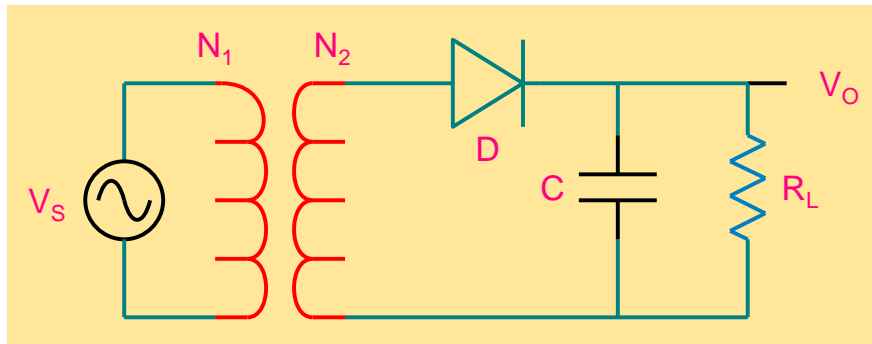

$$V_r \cong \frac{V_M}{fR_L C}$$

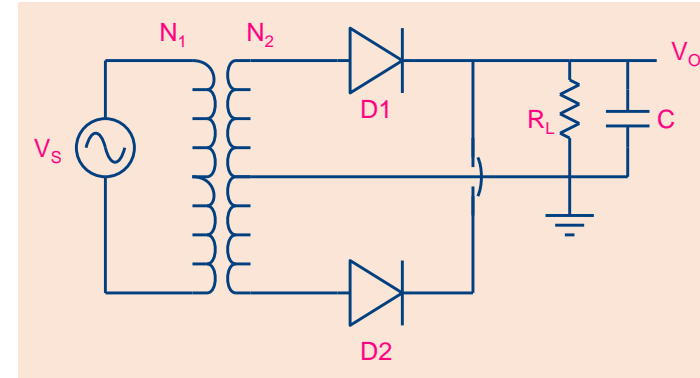

$$V_r \cong \frac{V_M}{2fR_L C}$$

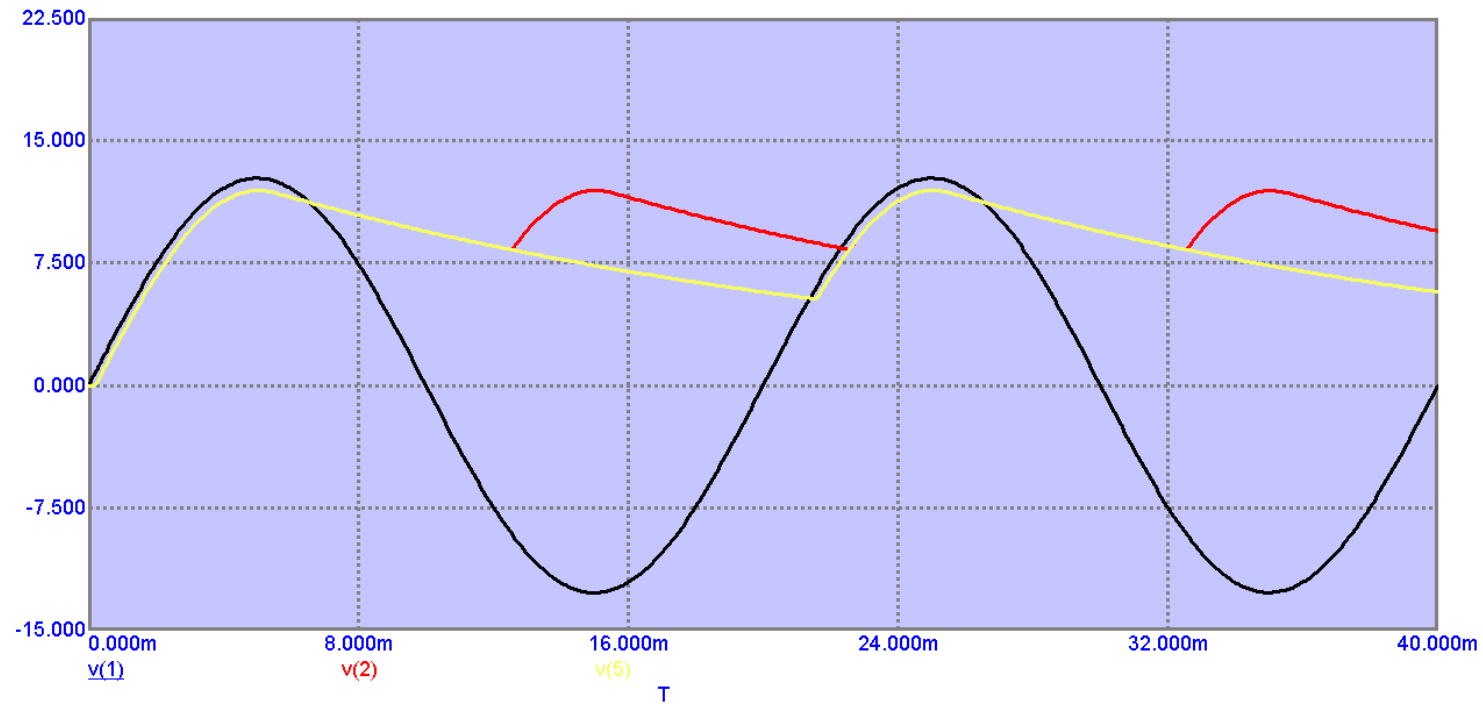

Max. diode current

- All steps of the earlier derivation remain the same


$$\omega\Delta t \approx \sqrt{\frac{2V_r}{V_M}} \qquad i_D(\Delta t) \approx -CV_M\omega^2\Delta t + \frac{V_M}{R_L}$$

- Except the value of V_r is halved

$$i_{D,\max} \approx \frac{V_M}{R_L} (1 + 2\pi\sqrt{fCR_L})$$

- Therefore a reduction in $i_{D,\max}$


Peak inverse voltage

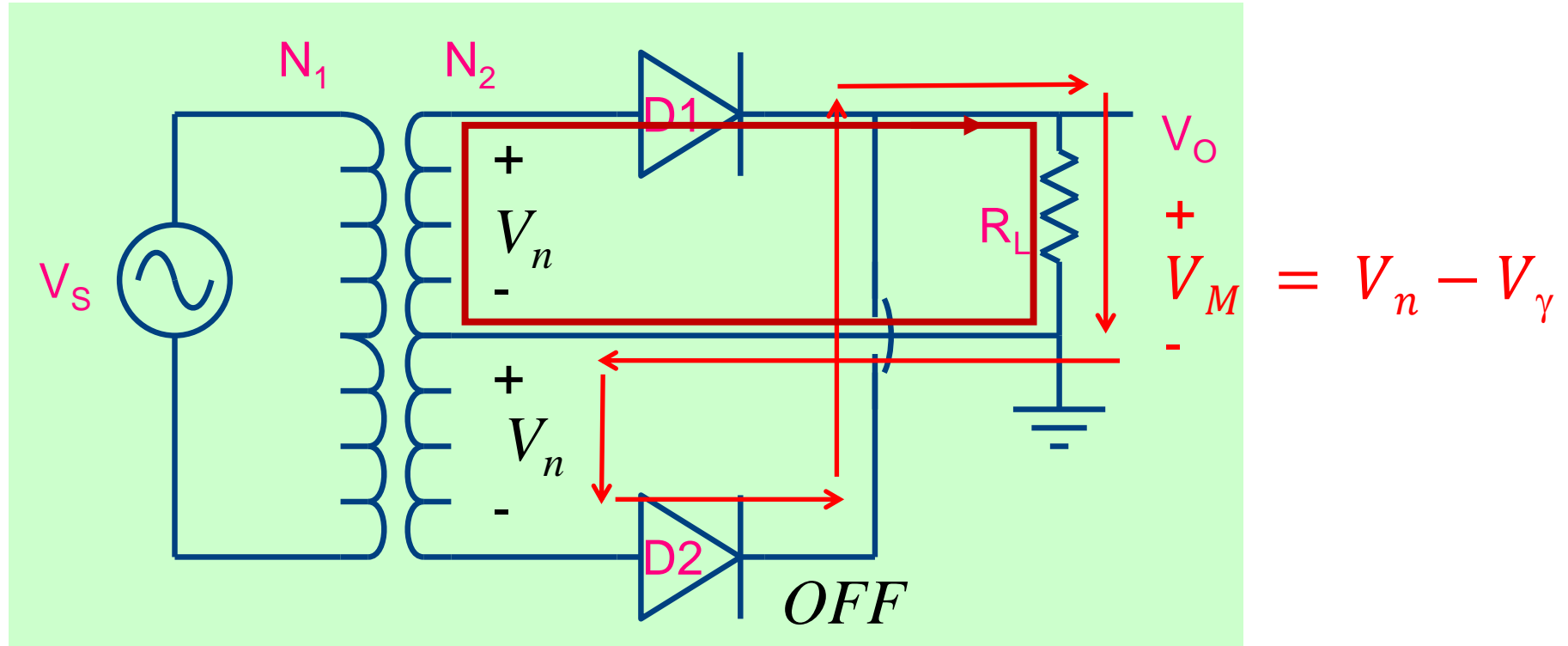


$$V_n + V_D + V_n - V_\gamma = 0$$

$$PIV = 2V_n - V_\gamma$$






Bridge rectifier

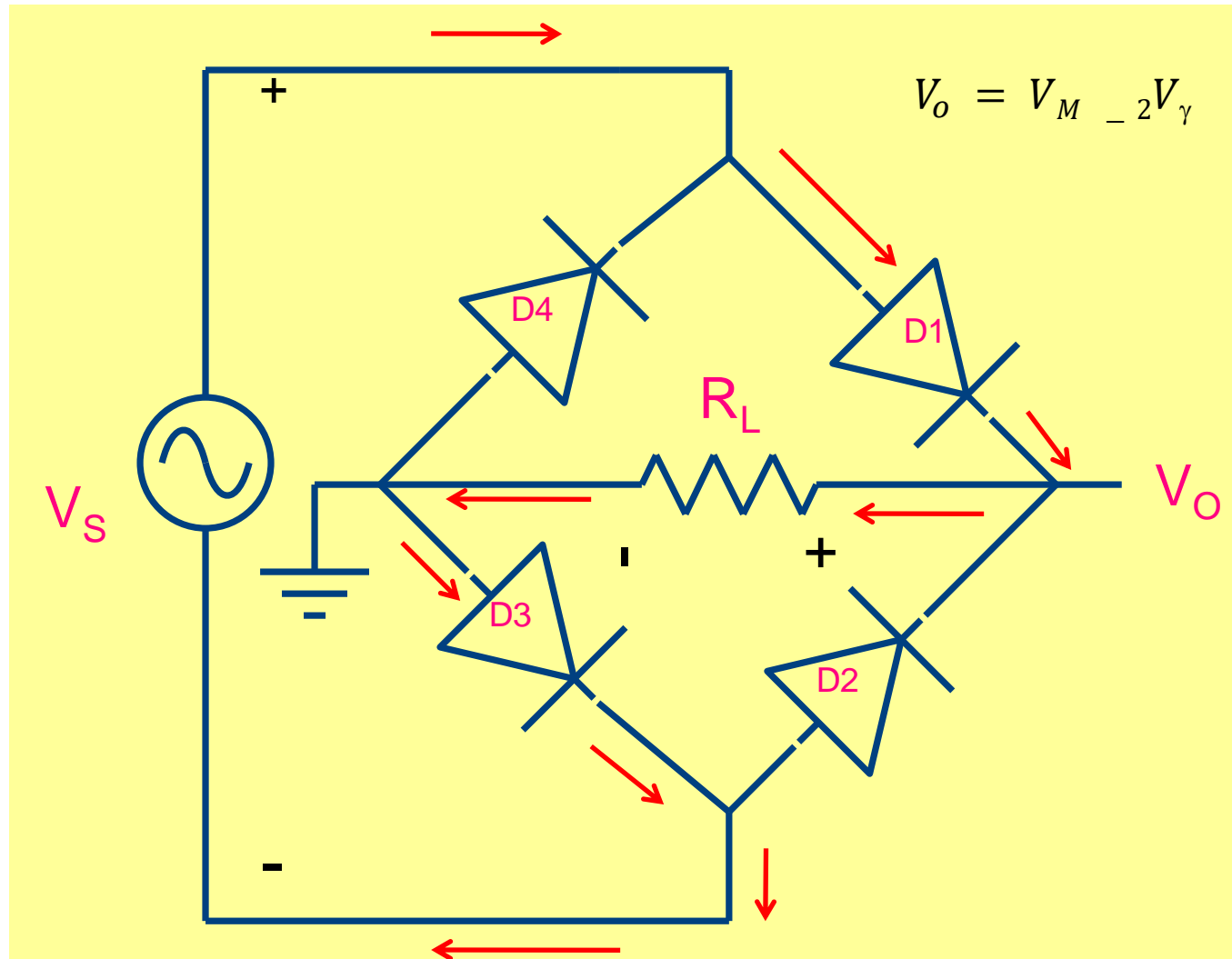

Bridge rectifier

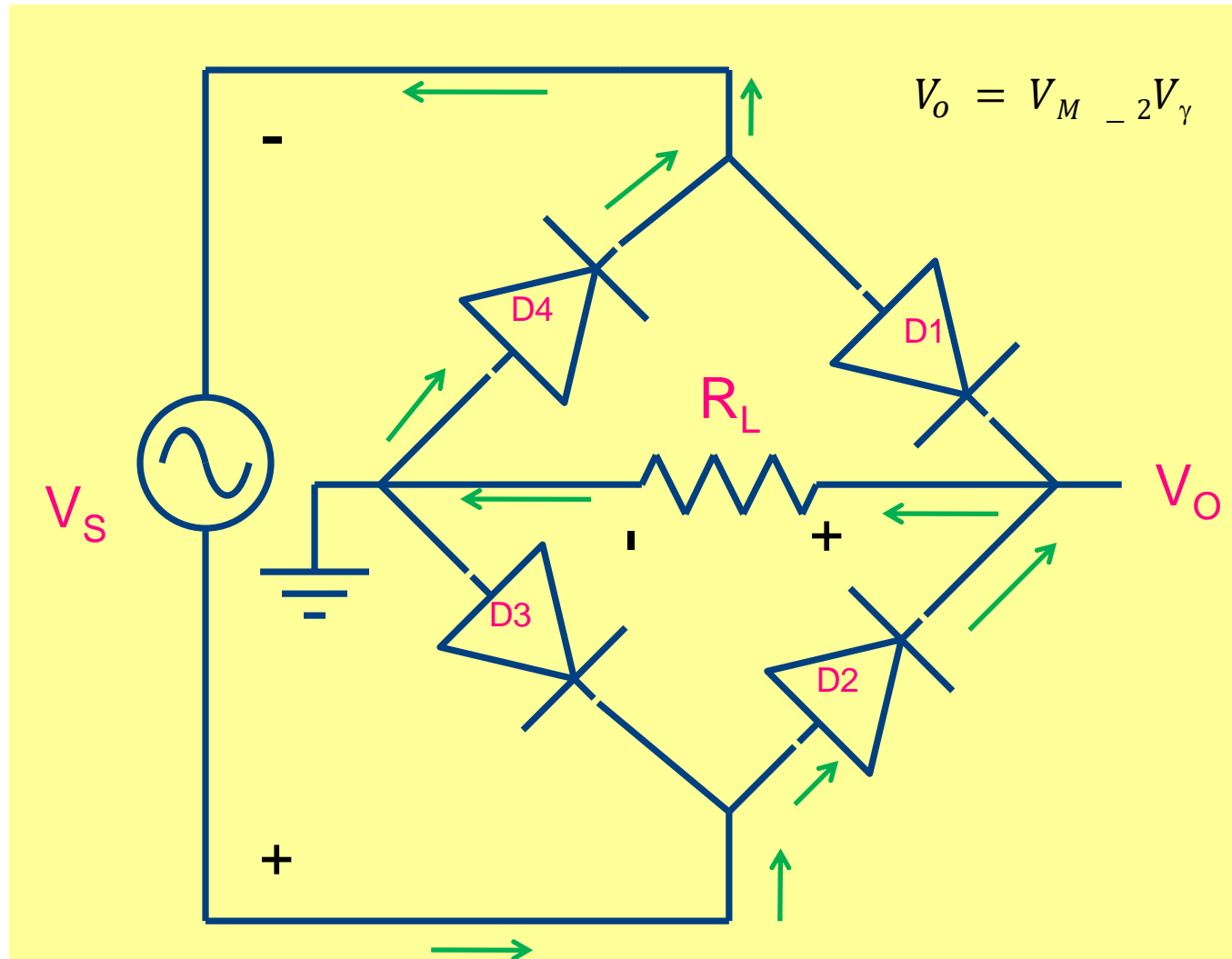


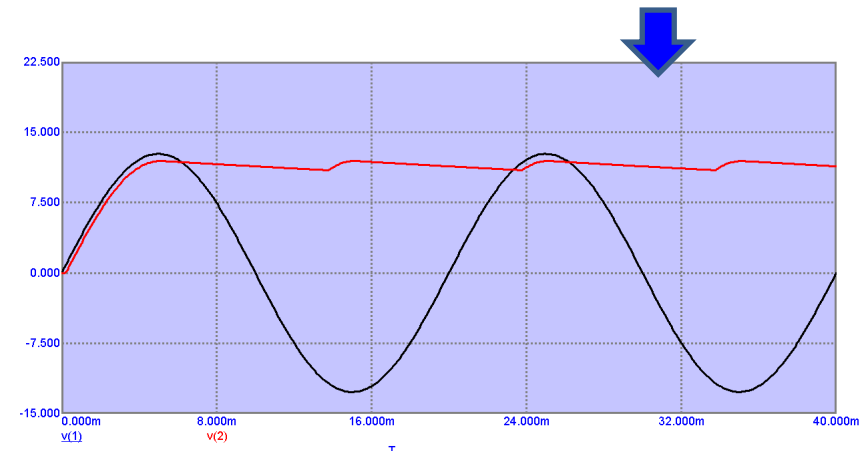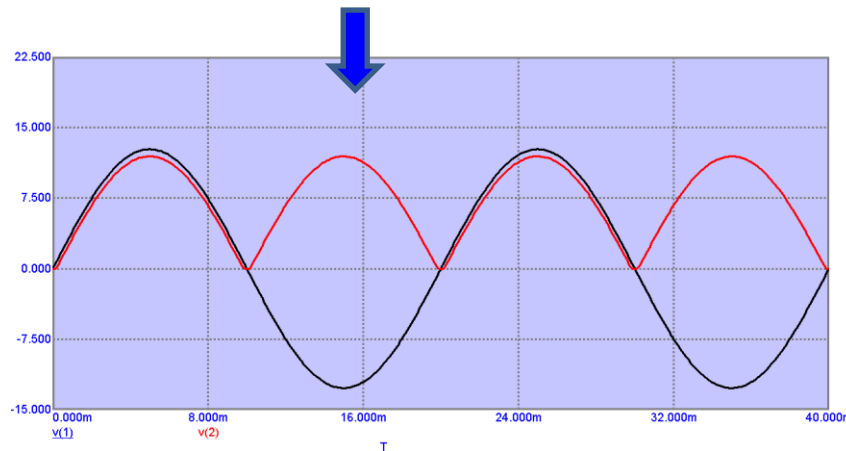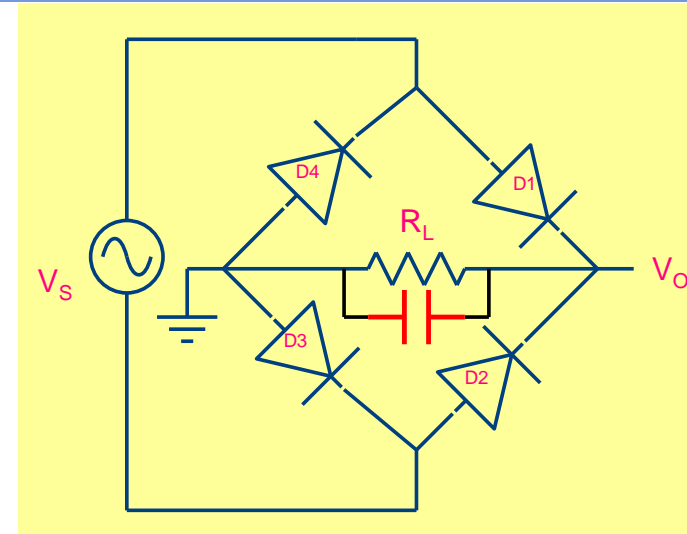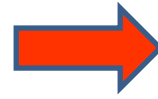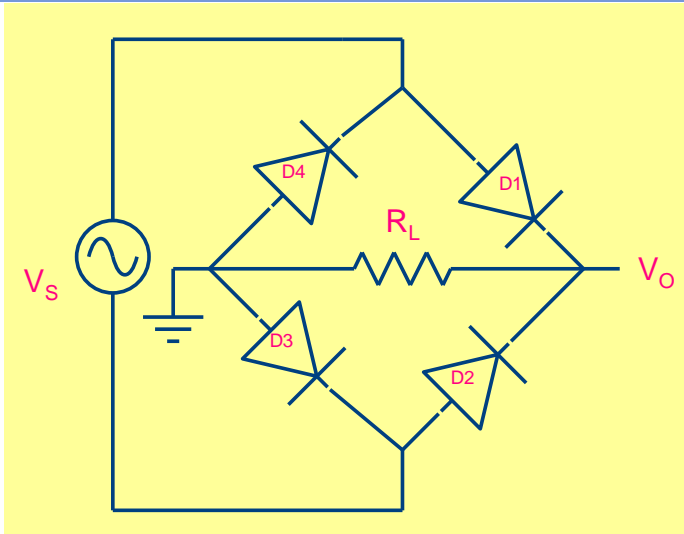Power supply using full wave Bridge Rectifier




$$V_r \cong \frac{V_M}{2fR_L C}$$


Peak Inverse Voltage

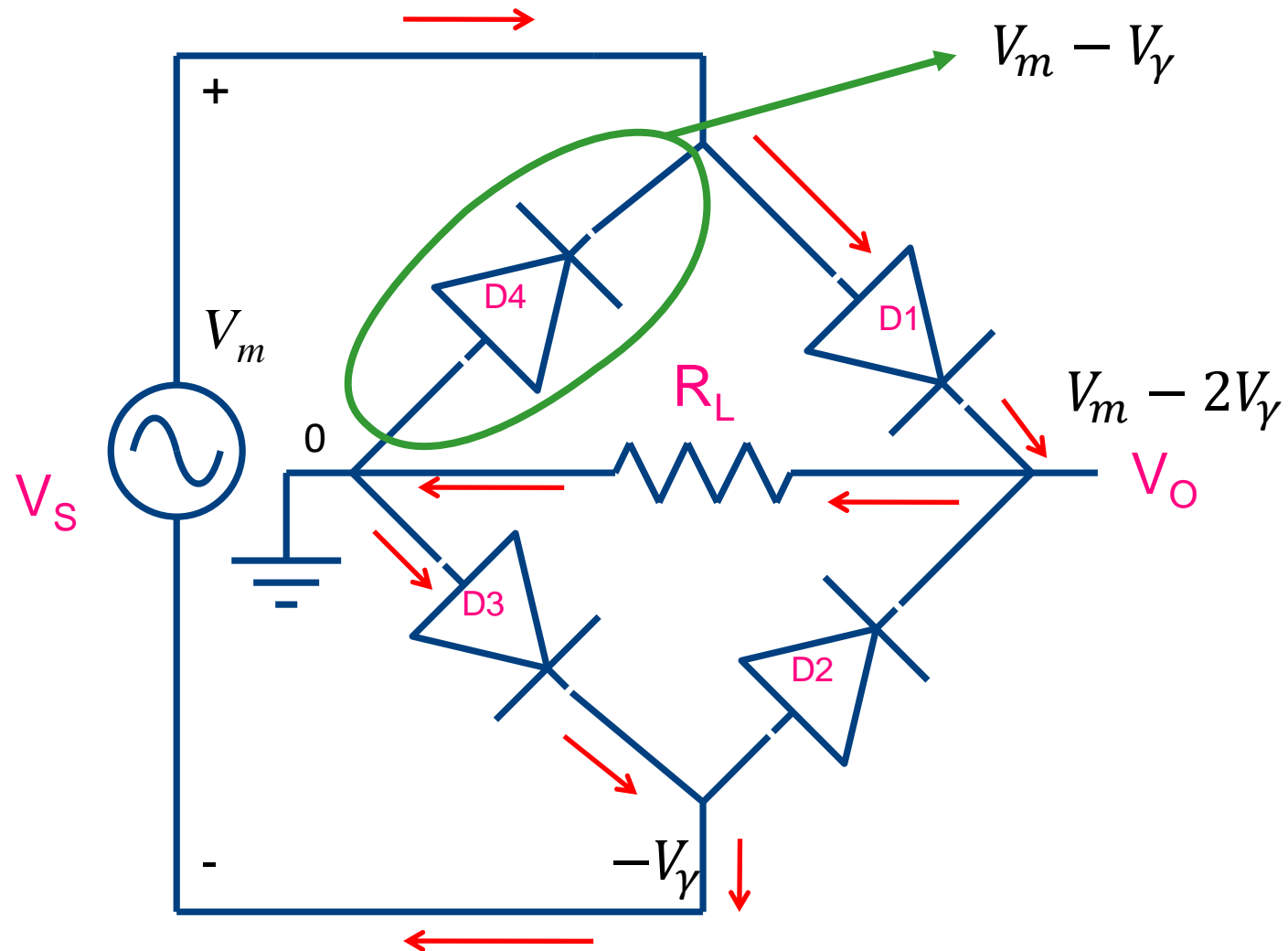

Advantage: lower PIV

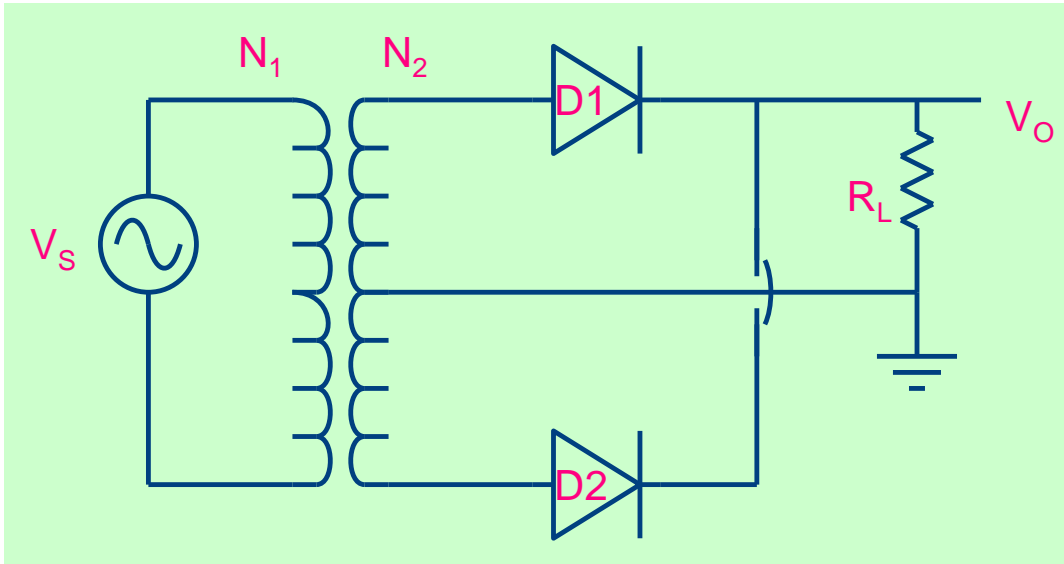


$$\text{PIV} = 2V_m - V_\gamma$$

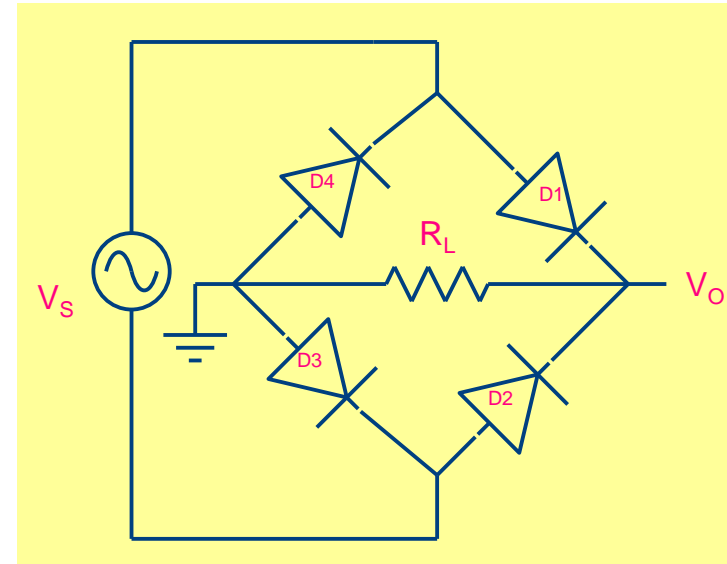


$$\text{PIV} = V_m - V_\gamma$$

Zener Diode


Off State

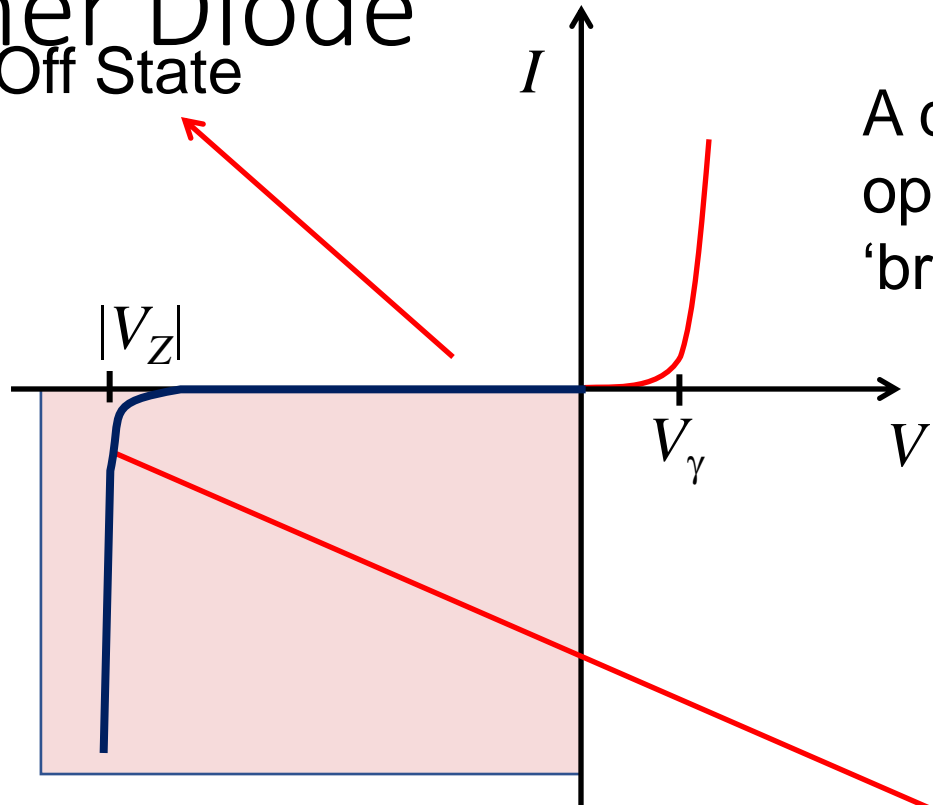

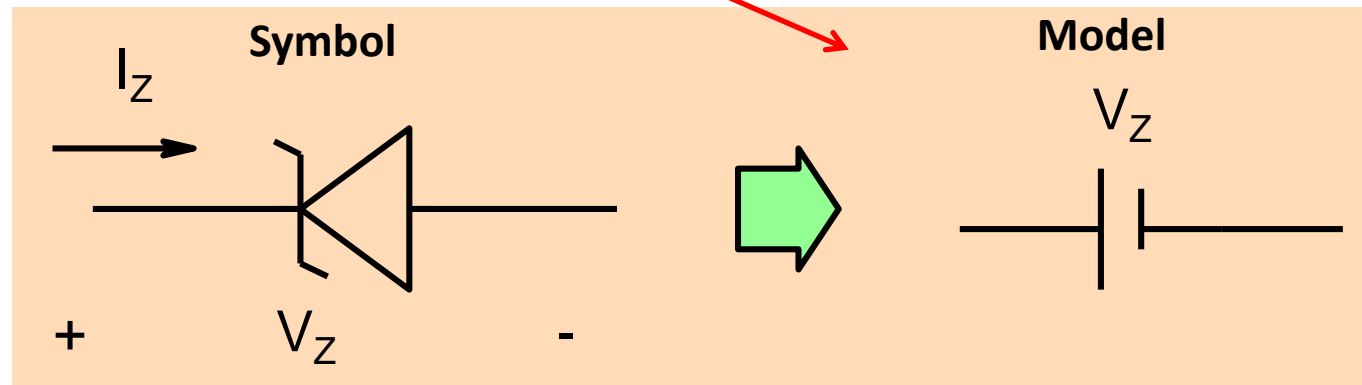A diode specially designed to operate in reverse bias and in 'breakdown' region



Example




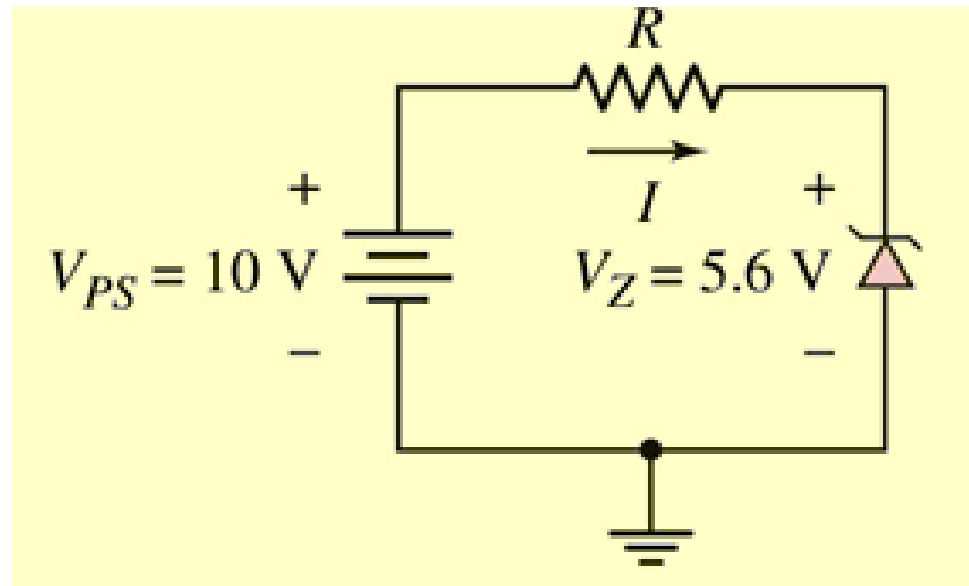


Given $V_Z = 5.6\text{ V}$

$$r_Z = 0\Omega$$

Find a value for R such
that the current through the
diode is limited to 3 mA


Example (continued)

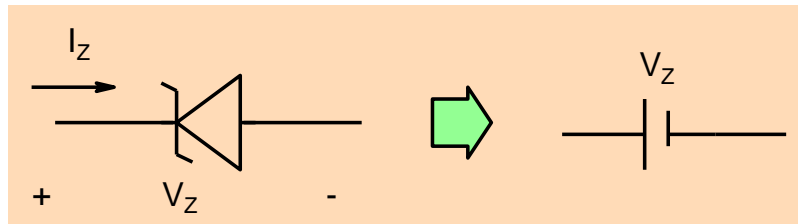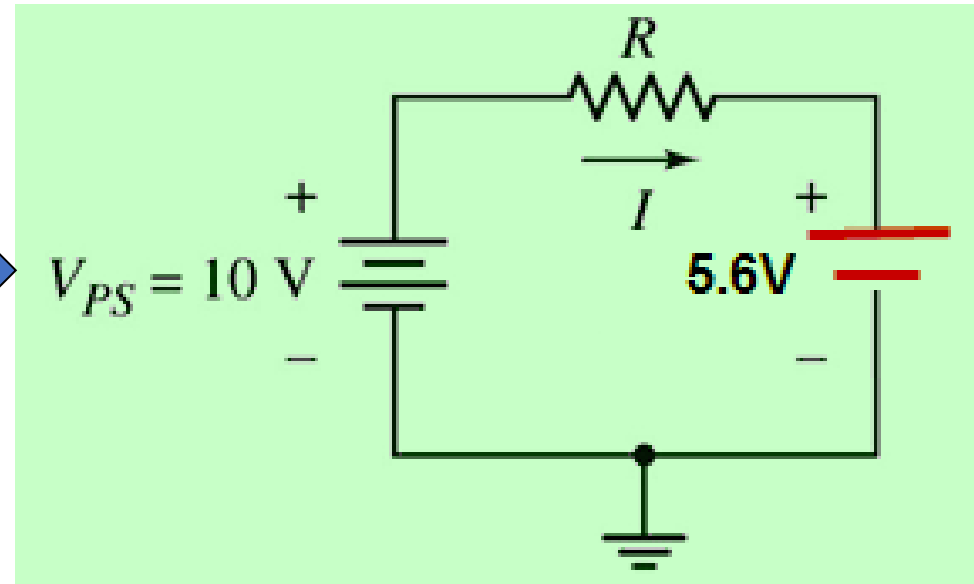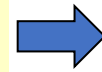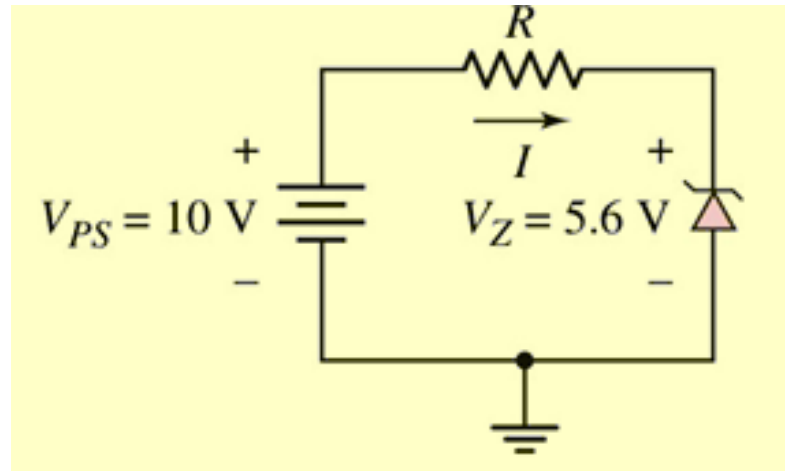

$$I = \frac{V_{PS} - V_Z}{R}$$

$$R = \frac{V_{PS} - V_Z}{I} = \frac{10\text{V} - 5.6\text{V}}{3\text{mA}} = 1.47\text{k}\Omega$$

Zener diode: Important Characteristics

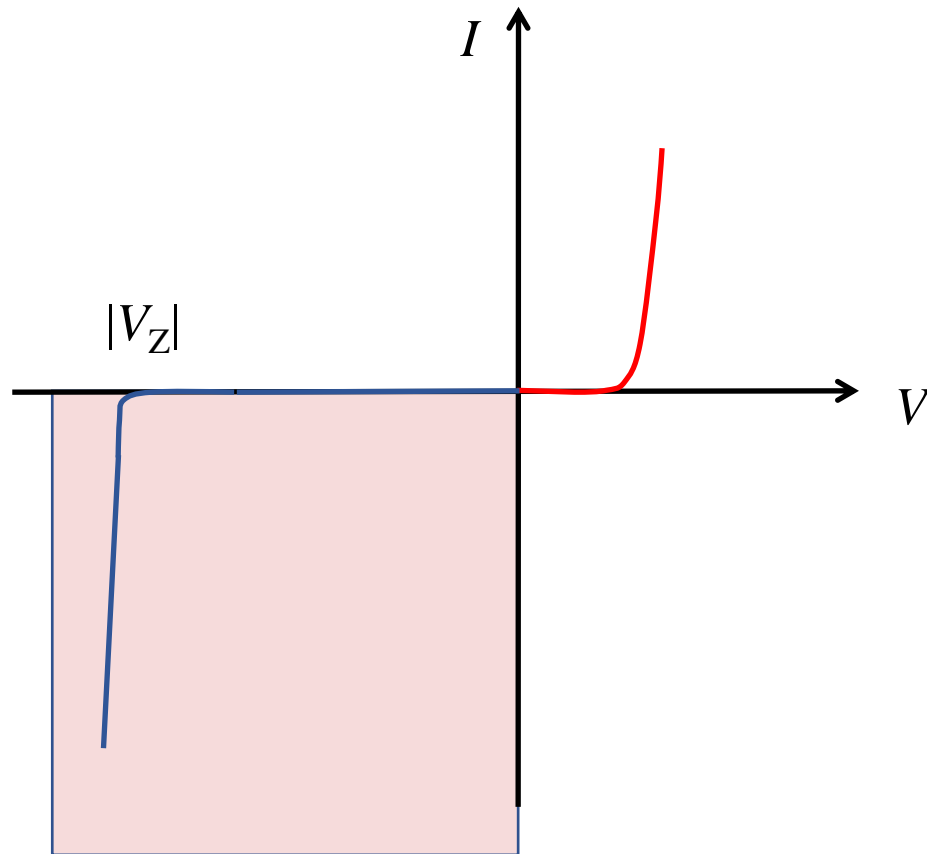

$$V_Z$$

Zener voltage
→ a good reference

$$I_Z(\text{max.})$$

Maximum current
→ to safeguard diode




$$I_Z(\text{min.})$$

Minimum current
→ to ensure V_Z




$$P_Z$$

Maximum Power
→ to safeguard diode


Voltage Reference Circuit

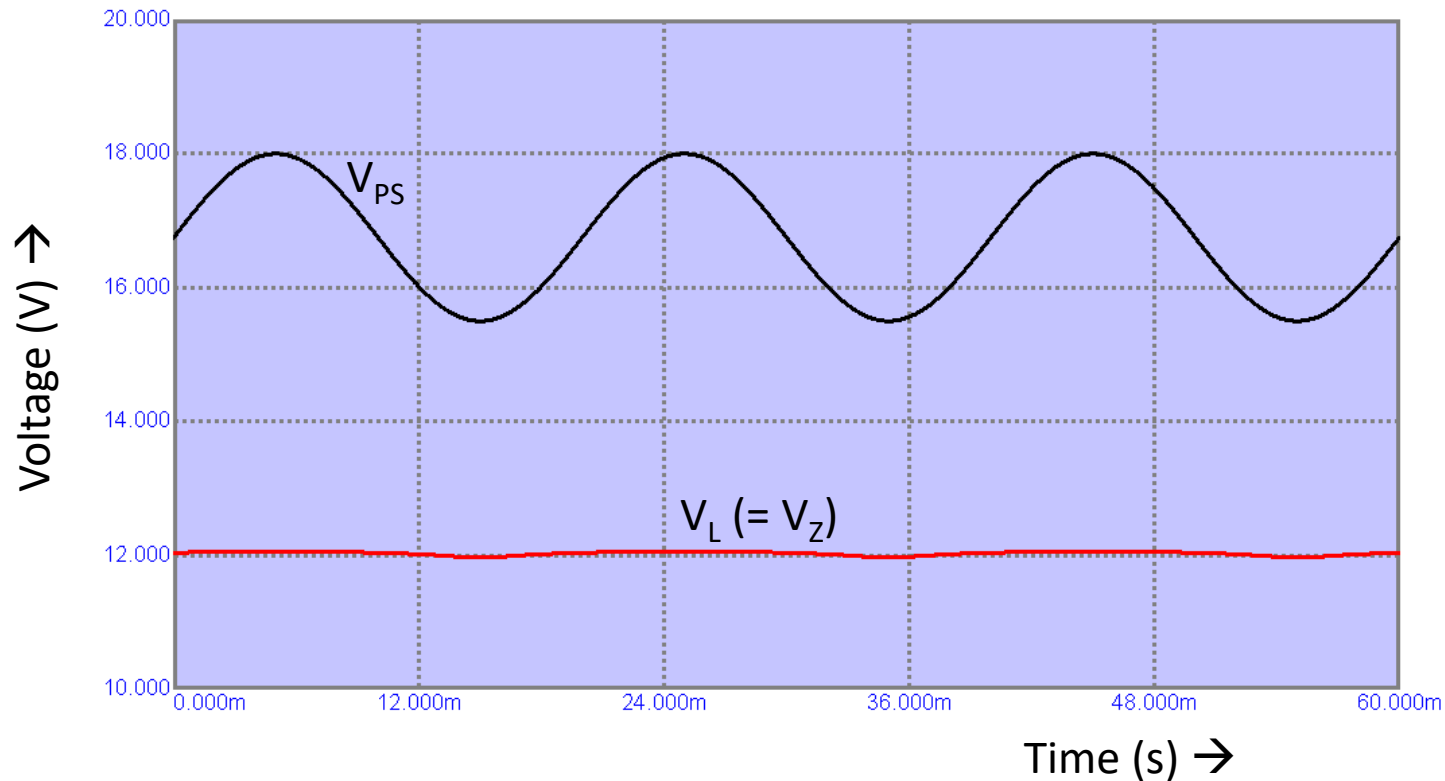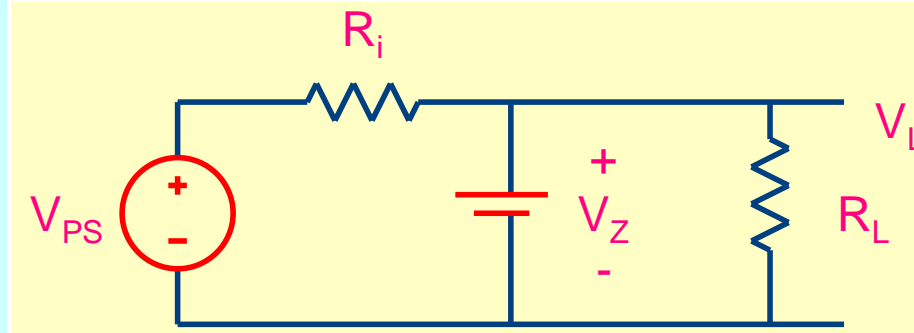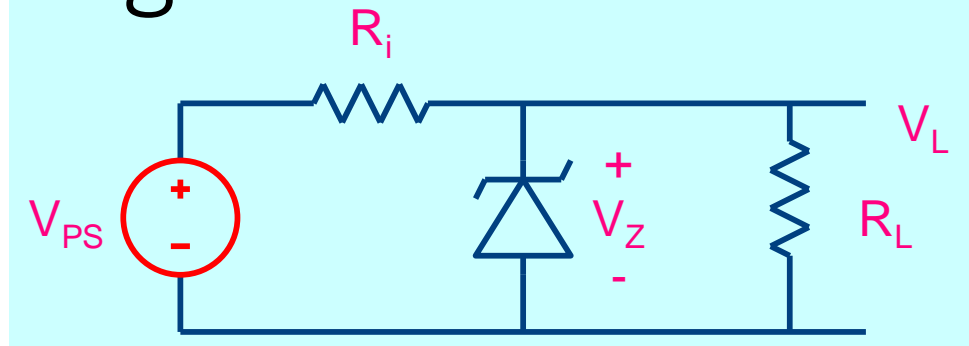


Power Supply with Regulator

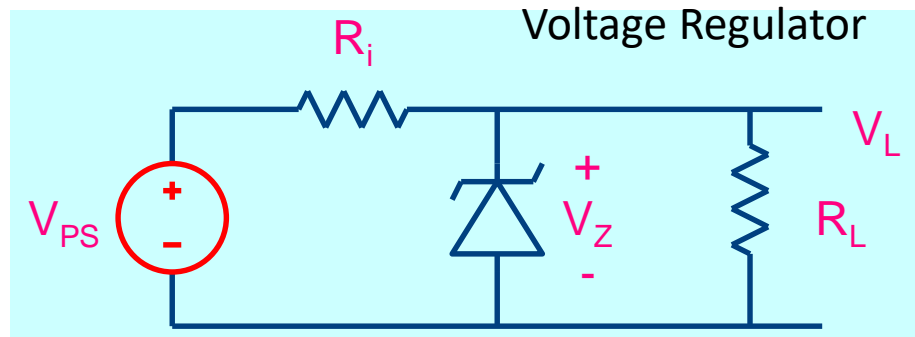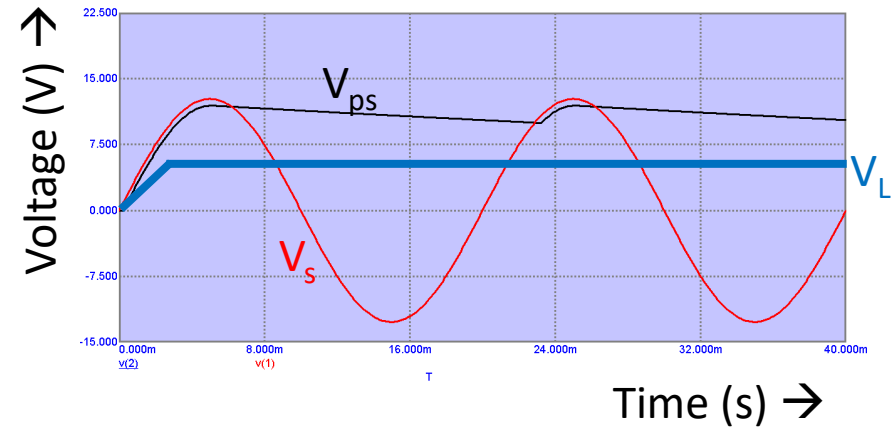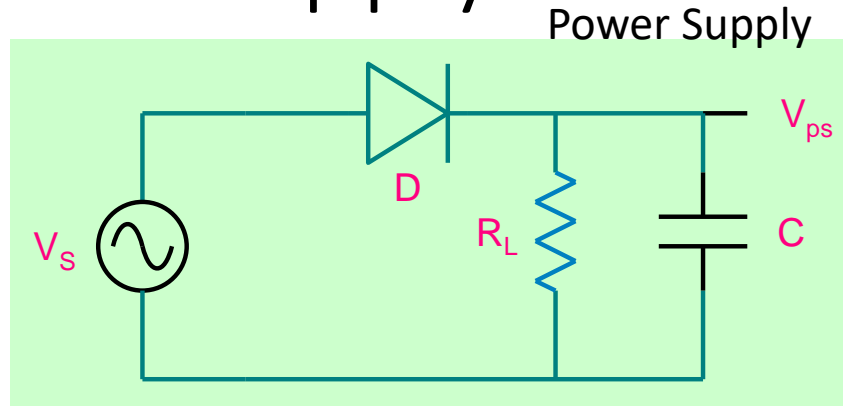

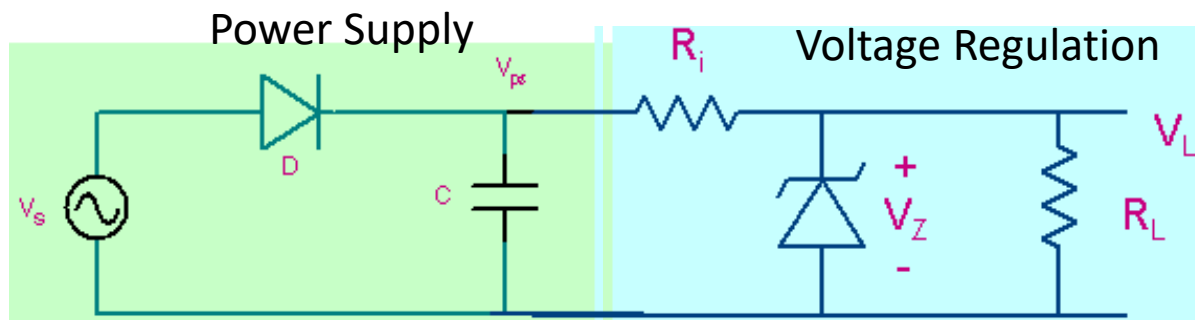
Combine:
Power Supply and Voltage Regulator



Zener Diode as Voltage Regulator

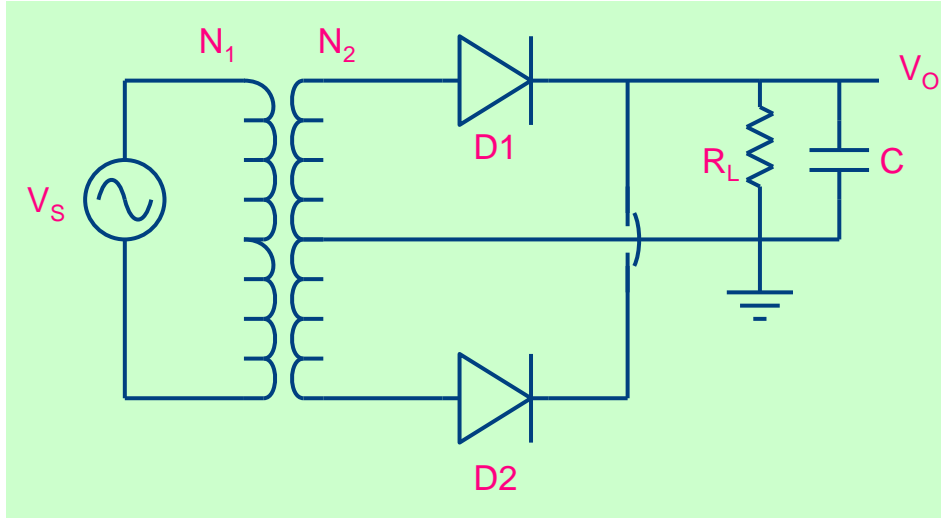

Earlier circuit without Zener

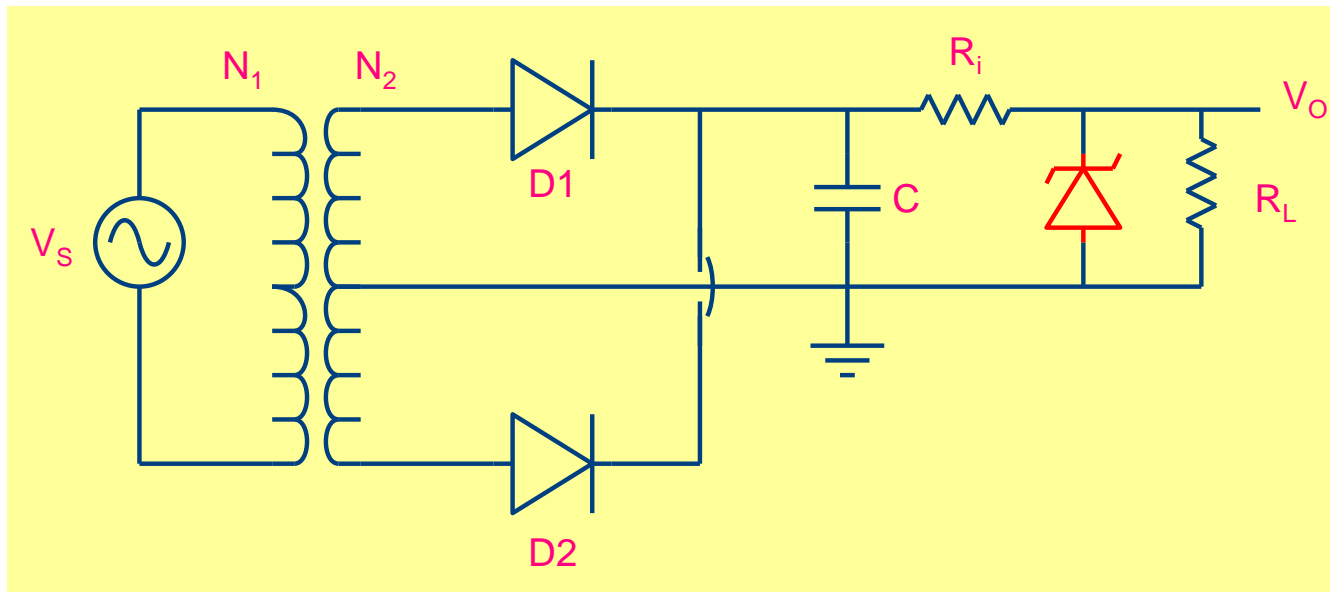

Regulated supply

Zener diode
regulates supply

