




ESC201: INTRODUCTION TO ELECTRONICS

MODULE 4: NON-LINEAR ELEMENTS



Dr. Shubham Sahay,
Assistant Professor,
Department of Electrical Engineering,
IIT Kanpur

Recap

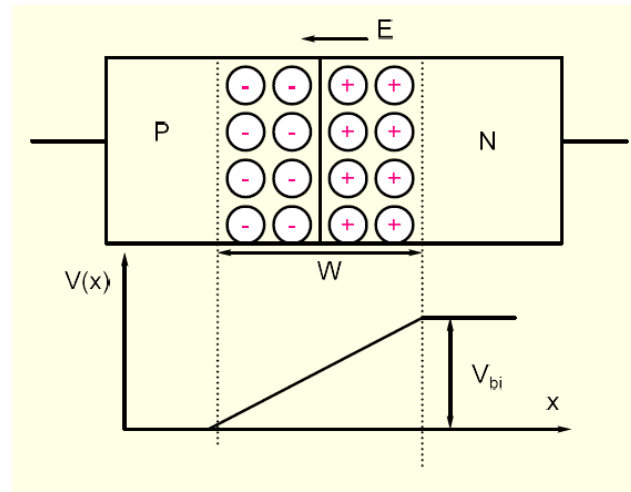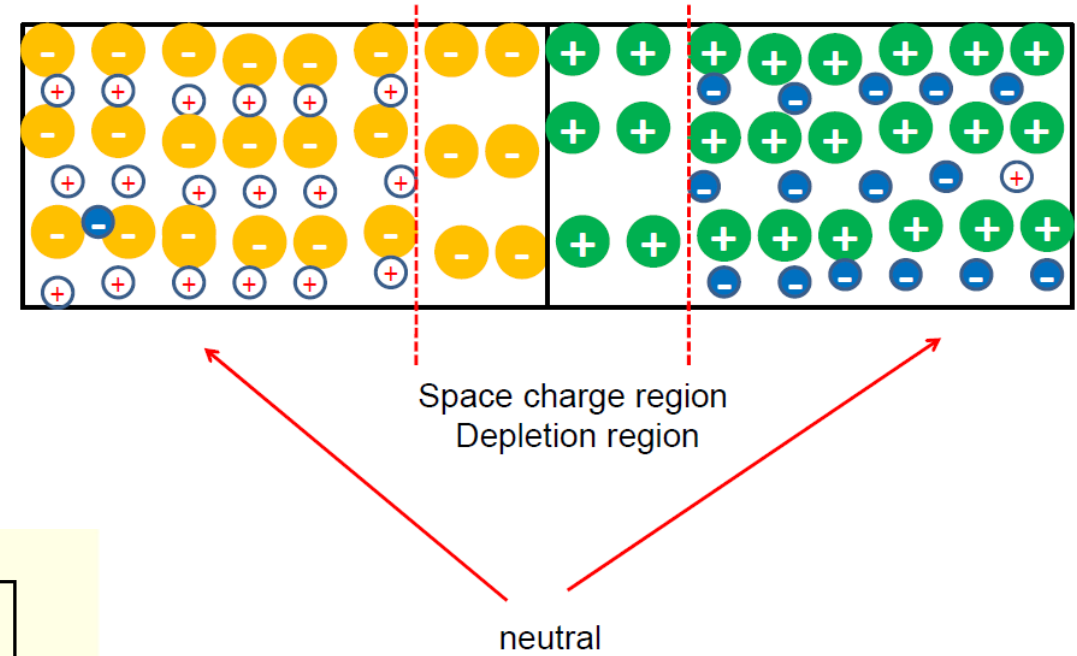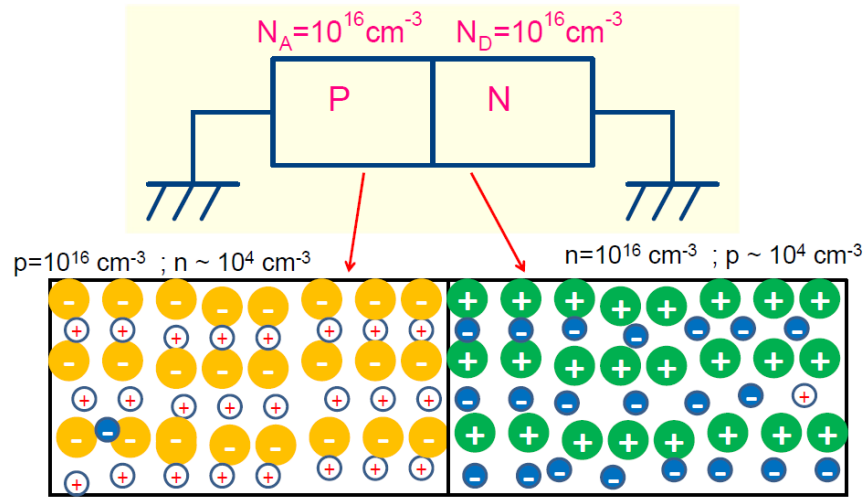

$$V_{bi} = \frac{k T}{q} \ln \left[\frac{N_A N_D}{n_i^2} \right]$$

$$N_A = N_D = 10^{16} \text{ cm}^{-3}, \quad T = 300^\circ \text{K}$$

$$V_{bi} = 0.86 \text{ V}$$

I-V Characteristics- Nonlinear Behavior

Let us ignore breakdown region, assuming that our circuit does not generate large negative voltages

applied voltage = v_D



diode current:

$$i_D = I_S \left(\exp \left(\frac{v_D}{nV_T} \right) - 1 \right)$$

I_S : Reverse saturation current

n : ideality factor (= 1 for ideal diodes)
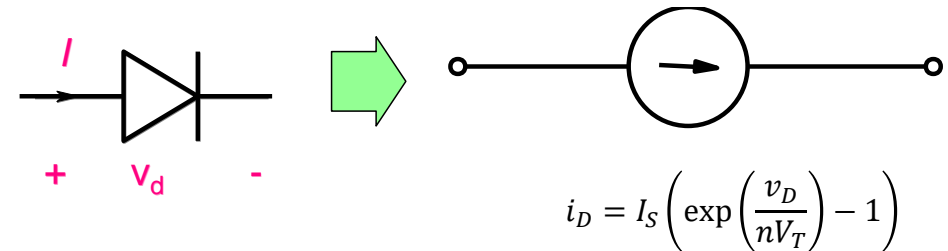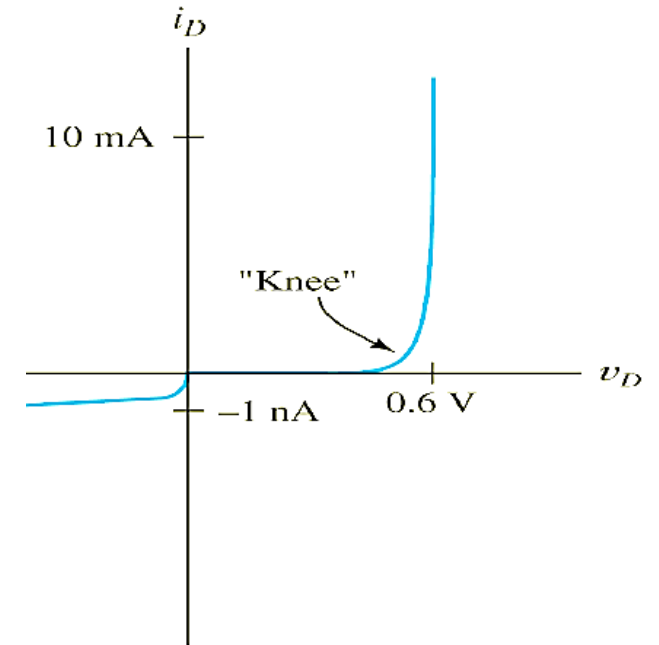
$$V_T = \frac{kT}{q} \approx 26\text{mV at } T = 300\text{K}$$




Forward Bias

$$I_D = I_S \left(\exp \left(\frac{v_D}{V_T} \right) - 1 \right)$$


$$v_d \gg V_T = 26mV$$
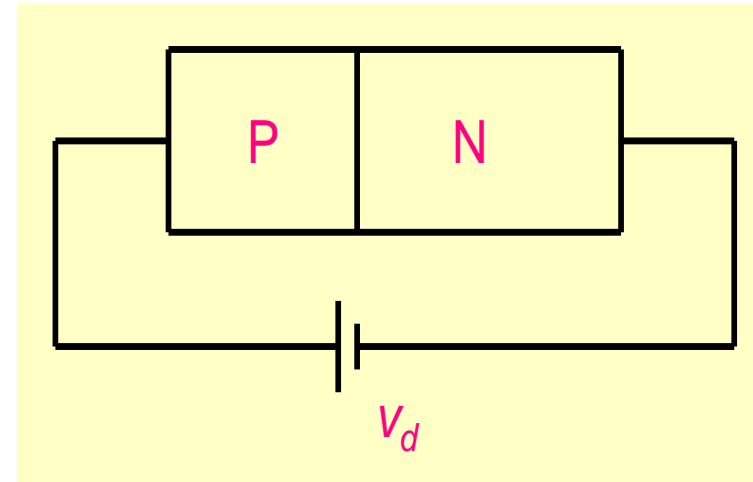
$$i_D \approx I_S \times \exp \left(\frac{v_d}{V_T} \right)$$



Reverse Bias
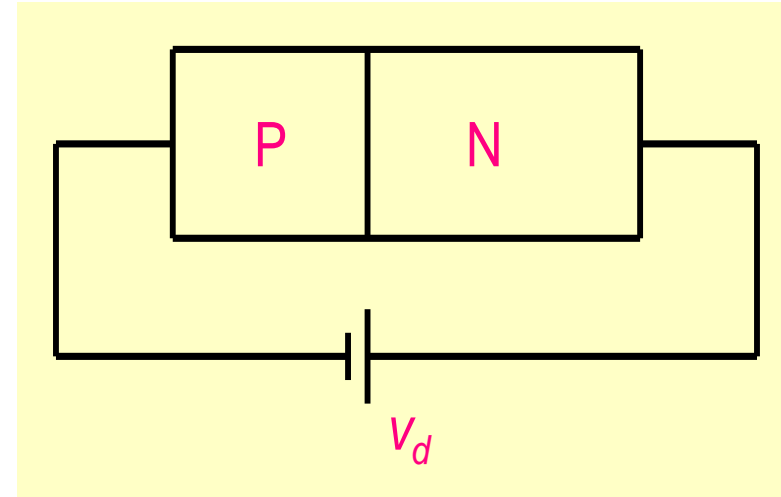
$$I_D = I_S \left(\exp \left(\frac{v_D}{V_T} \right) - 1 \right)$$




$$v_d = -v_R$$

$$|v_R| \gg V_T$$

$$i_D = I_S \left(\exp \left(-\frac{v_R}{V_T} \right) - 1 \right) \approx -I_S$$

Analysis

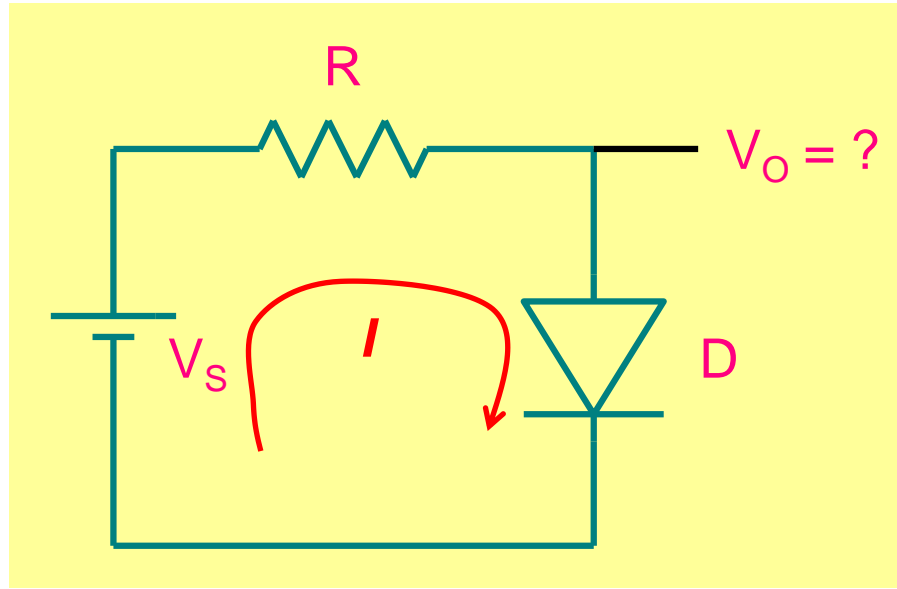

$$V_S = IR + V_D$$

$$I = I_S \left(\exp \left(\frac{V_D}{V_T} \right) - 1 \right)$$

2 equations, 2 variables

Numerical methods, graphical method, etc.

- Analysis using a non-linear diode model is relatively difficult and time consuming.
- It also does not give a symbolic expression that can provide insight and help in the design of the circuit.



Need SIMPLER and LINEAR Device Models

Piecewise Linear Approximation

- Diode is clearly a non-linear device
- We can however approximate its behavior with that of a piecewise linear system
- IV graph is made by joining two or more straight lines




Model A: Ideal

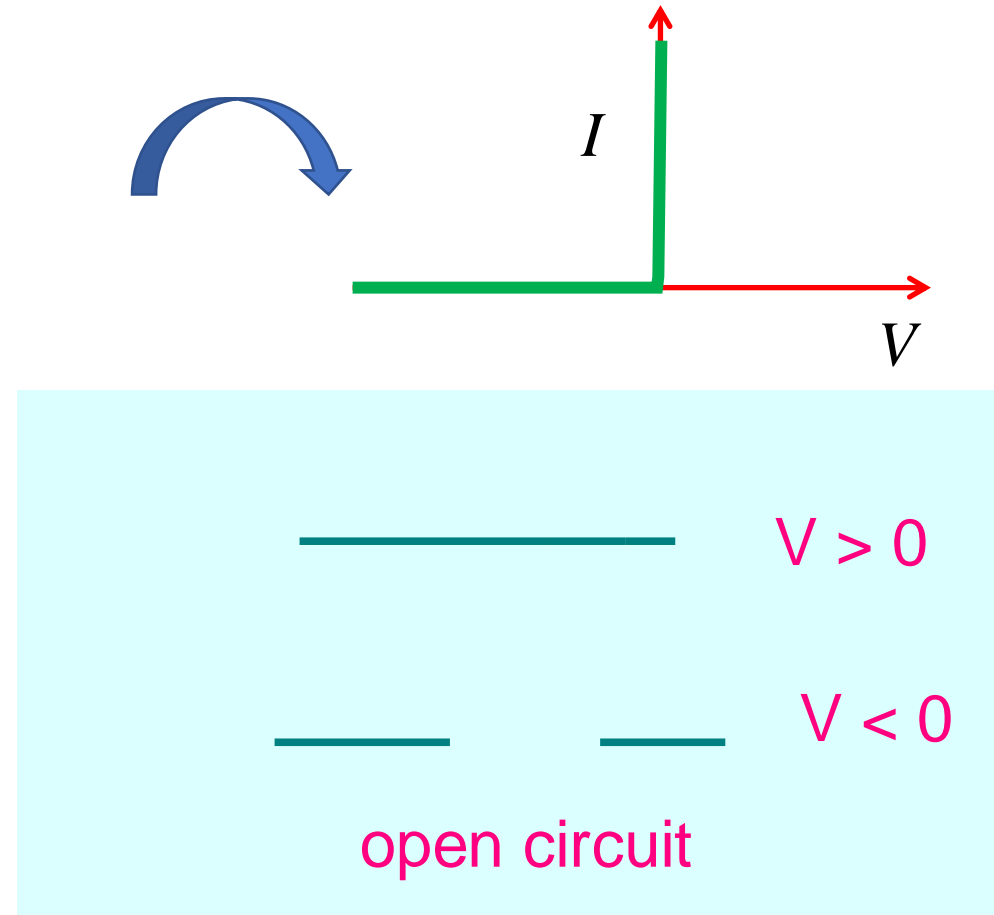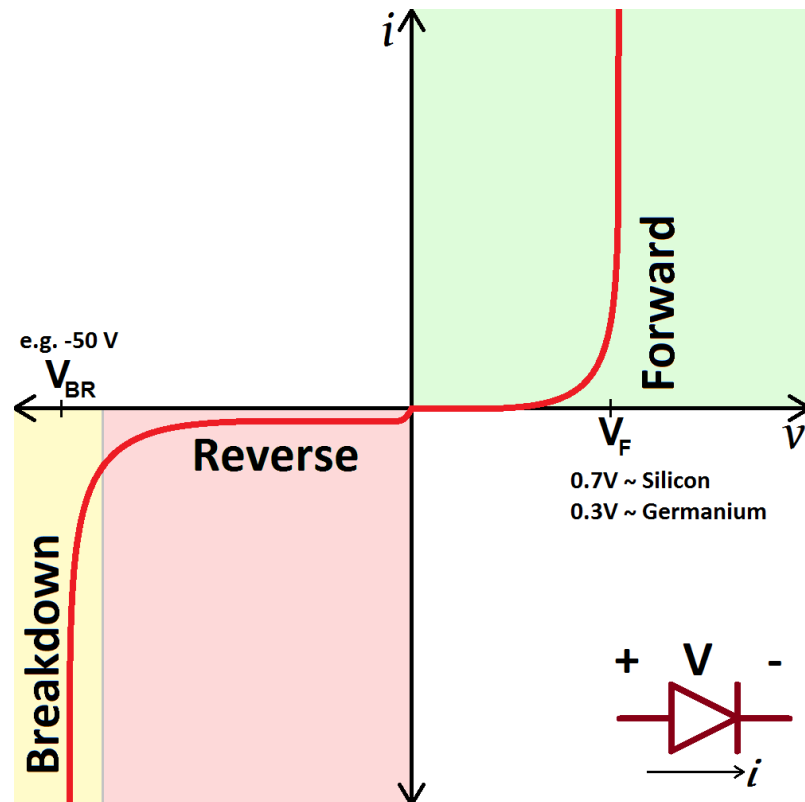- Simplest possible approximation: acts as an ideal valve
- ignore breakdown



Model B: Constant Voltage Drop

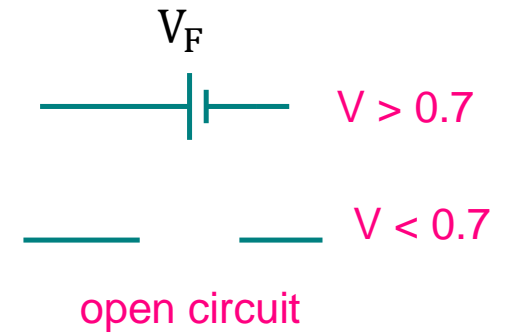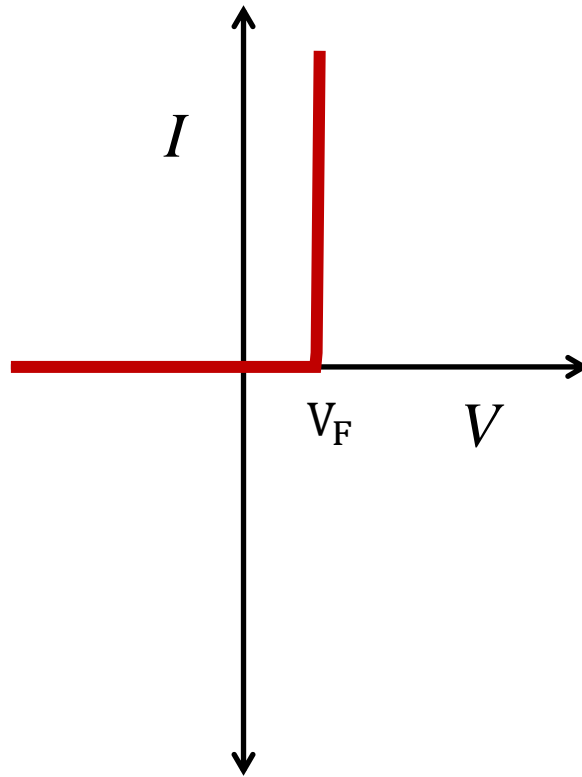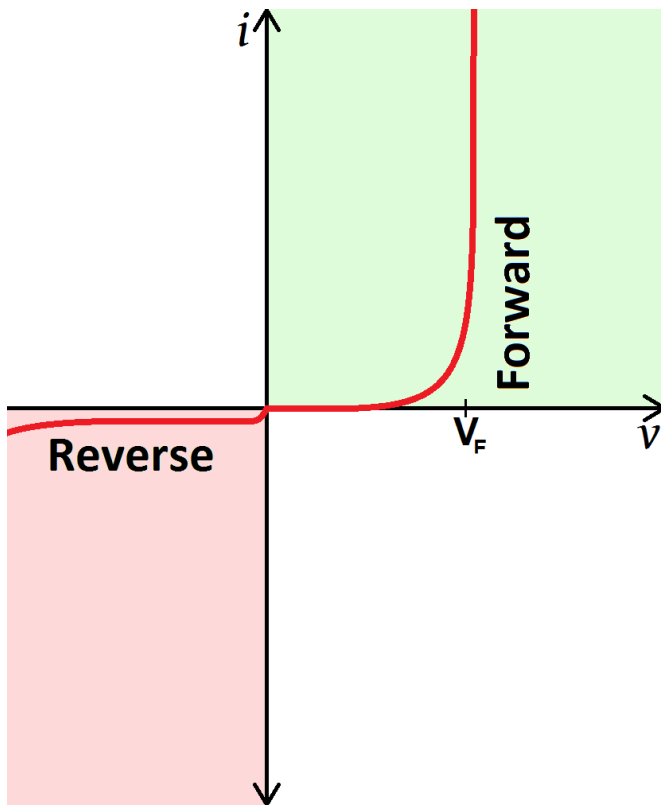- Simplest possible approximation: acts as an ideal valve with a drop in voltage




Model C: Piecewise Linear

$$V = V_\gamma + I r_f$$

V_γ is called cut-in or turn-on voltage and depends on nature of diode and range of current considered


For example:
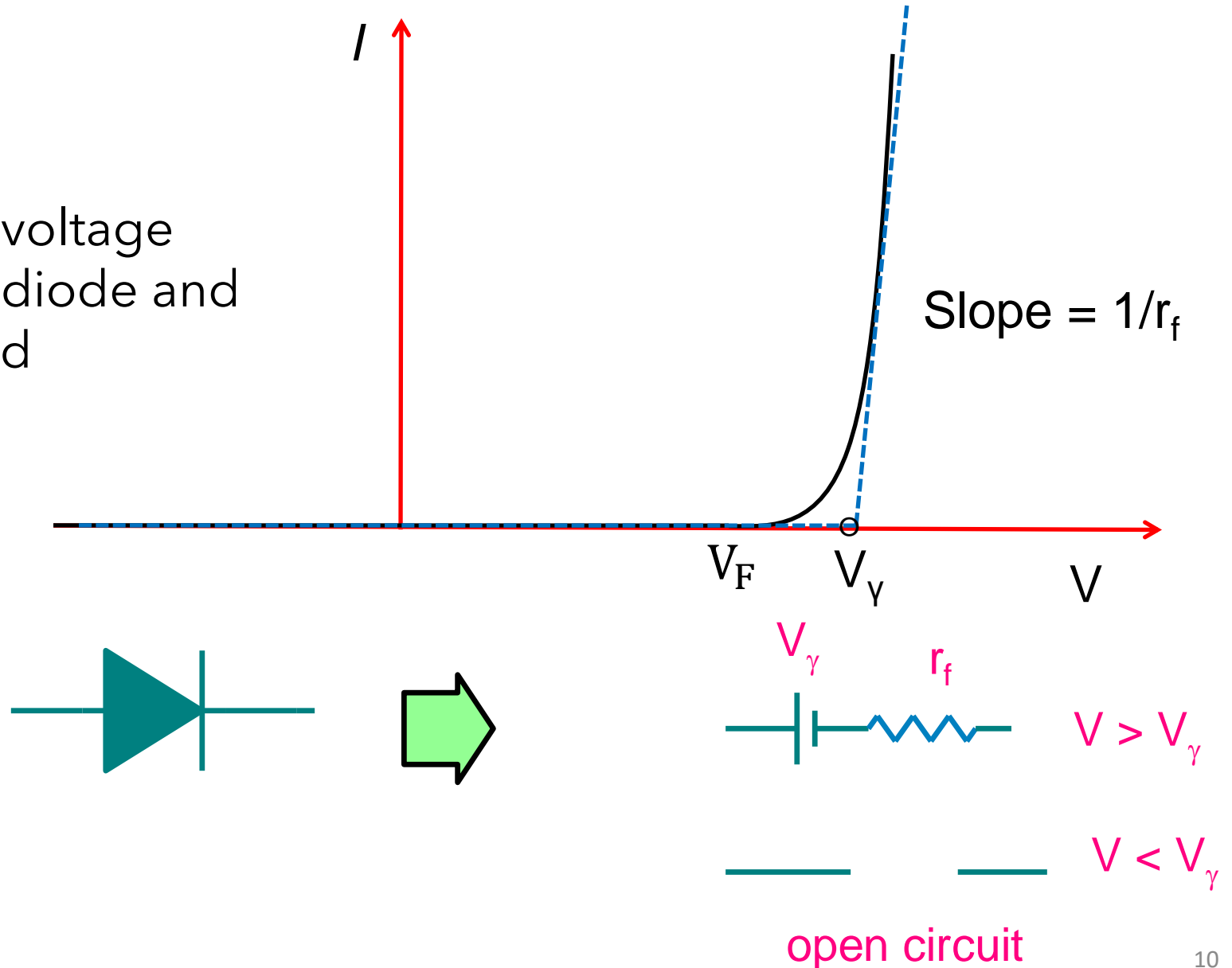
$$V_\gamma = 0.7V \text{ and } r_f \sim 10\Omega$$




Summary: approximations

Simplicity

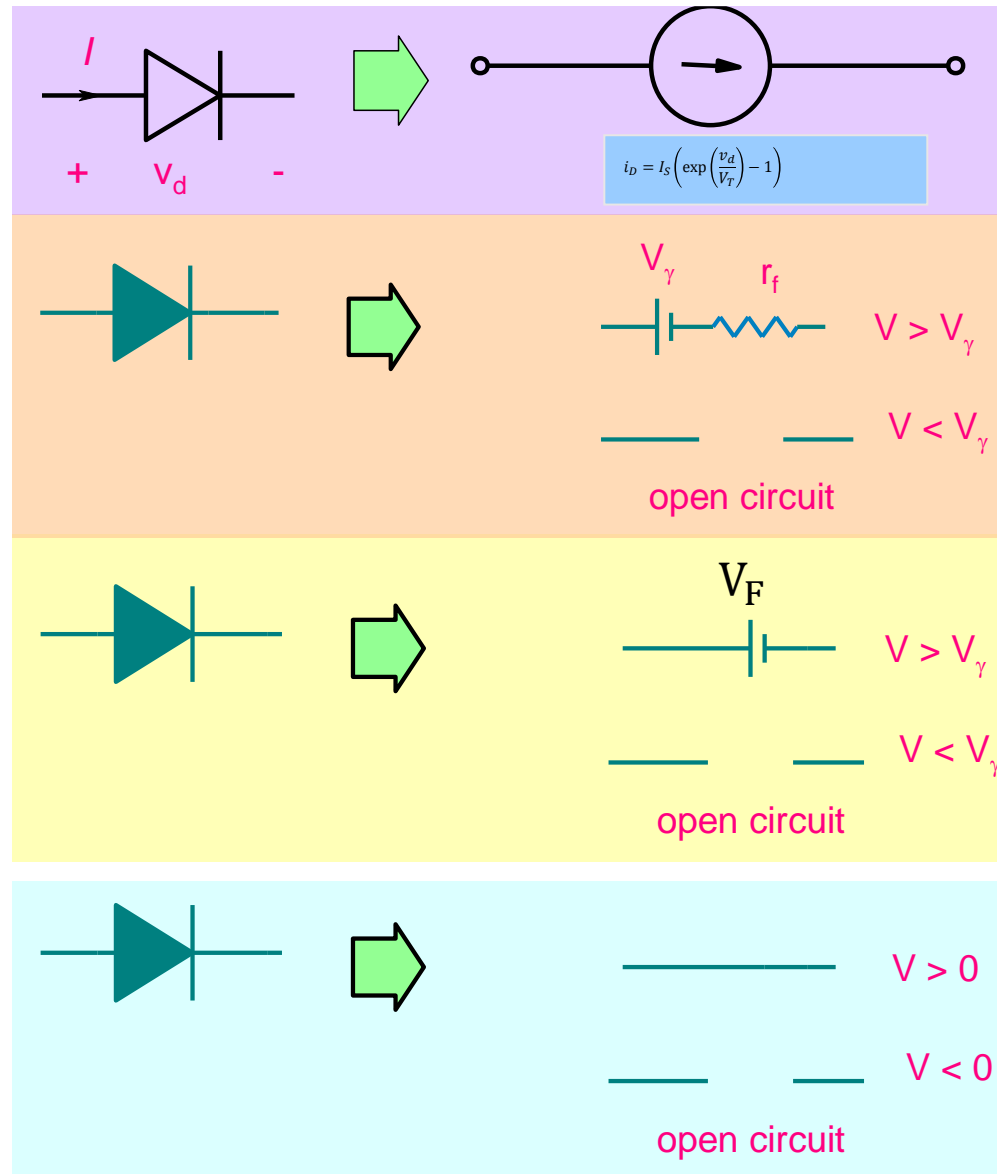


Accuracy


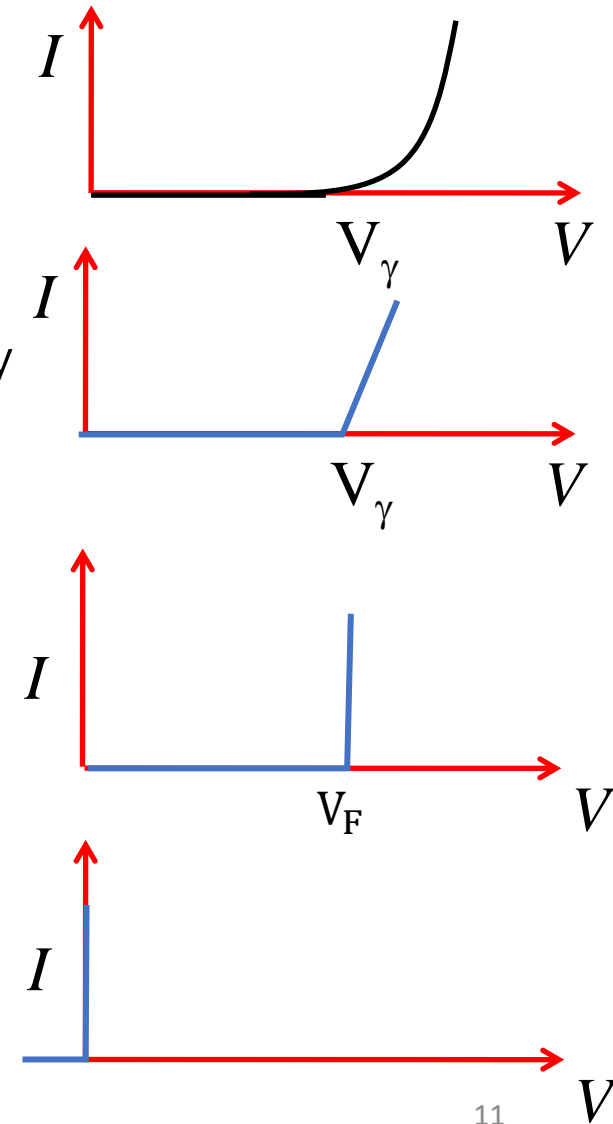


Example 1

Analysis using ideal diode model

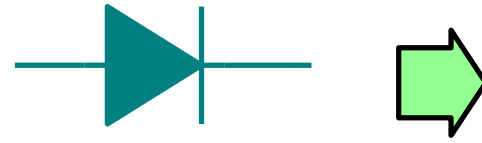





_____ $V > 0$
_____ $V < 0$
open circuit

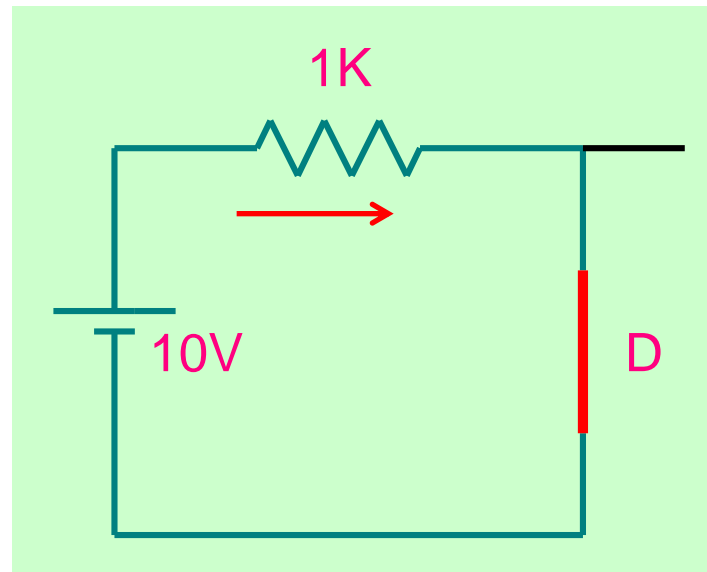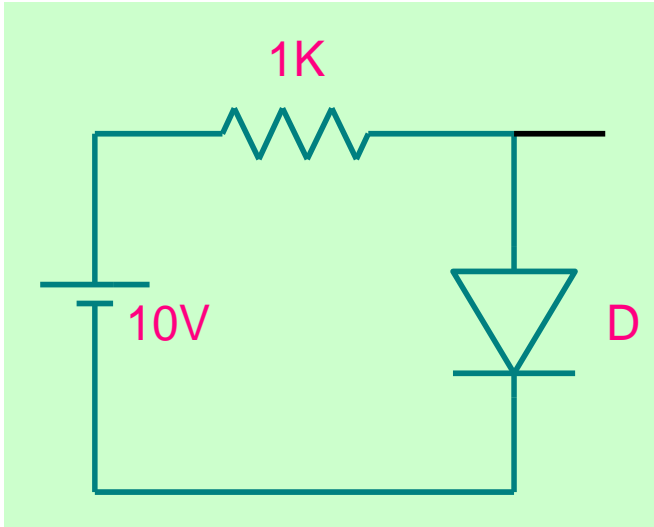

$$I = \frac{10}{1k} = 10mA$$

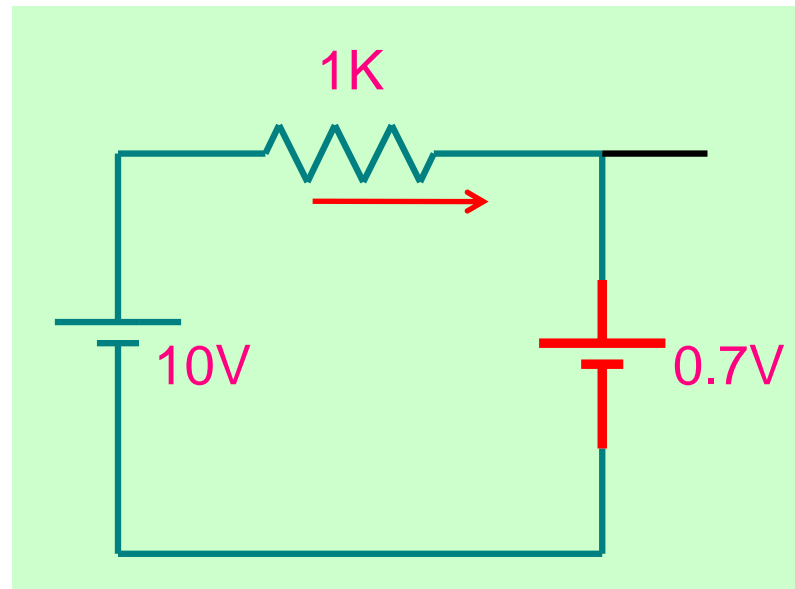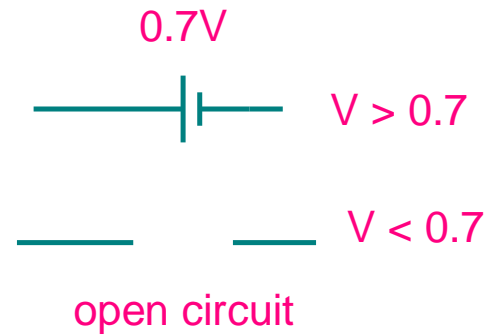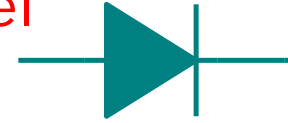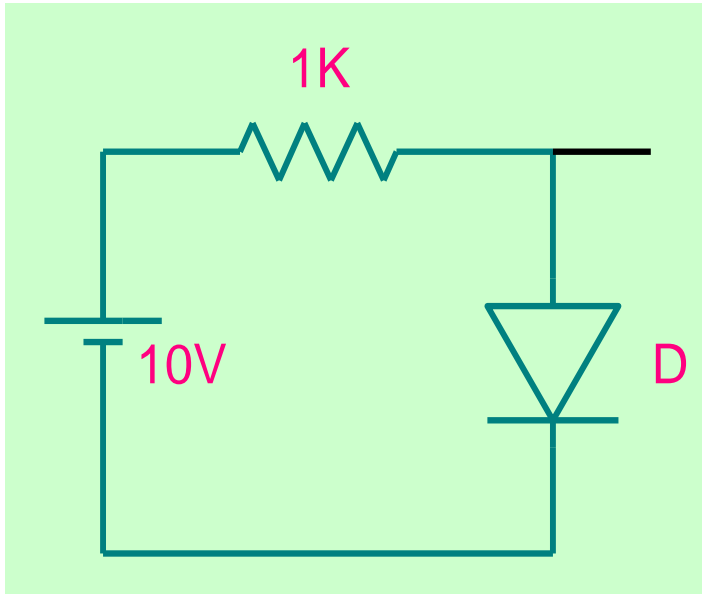Example





Analysis with a constant voltage diode model



$$I = \frac{10 - 0.7}{1k} = 9.3mA$$

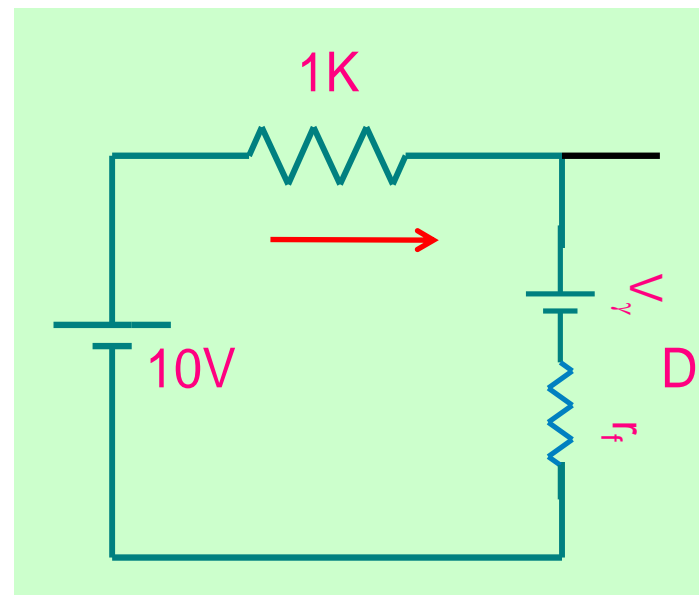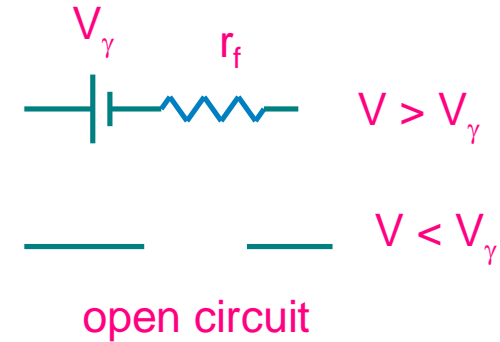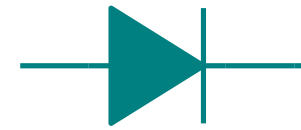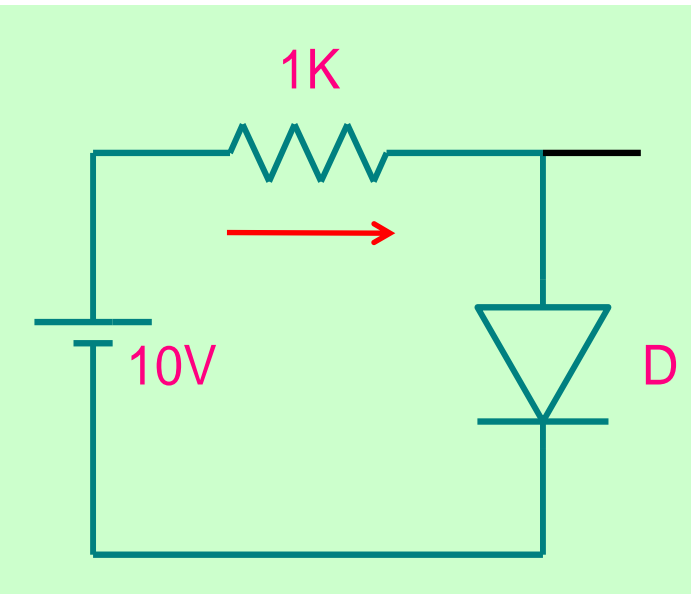Example

Analysis with a constant voltage
plus resistor diode model



$$I = \frac{10 - 0.7}{1000 + 10} = 9.208mA$$

Analysis: 'assumed' states

- How to know in which state diode is?
 - Easier if the voltage is known.
 - Otherwise
 - Analyze circuit assuming diode is forward biased
 - Check assumption ($I > 0$?)
 - Analyze circuit assuming diode is reverse biased
 - Check assumption ($V < 0$?)
 - Select the consistent one.
- What if 2 diodes: 4 possible circuits, only 1 will be valid
- N diodes $\Rightarrow 2^N$ circuits, only one will be valid

Example 2


Find the current through the 5k resistor using ideal diode model

Is the diode forward biased? – Not Sure!!

Assume that it is forward biased

Carry out analysis and then check if current through the diode is in **appropriate** direction.

If not, diode is reverse biased and we carry out the analysis again!!

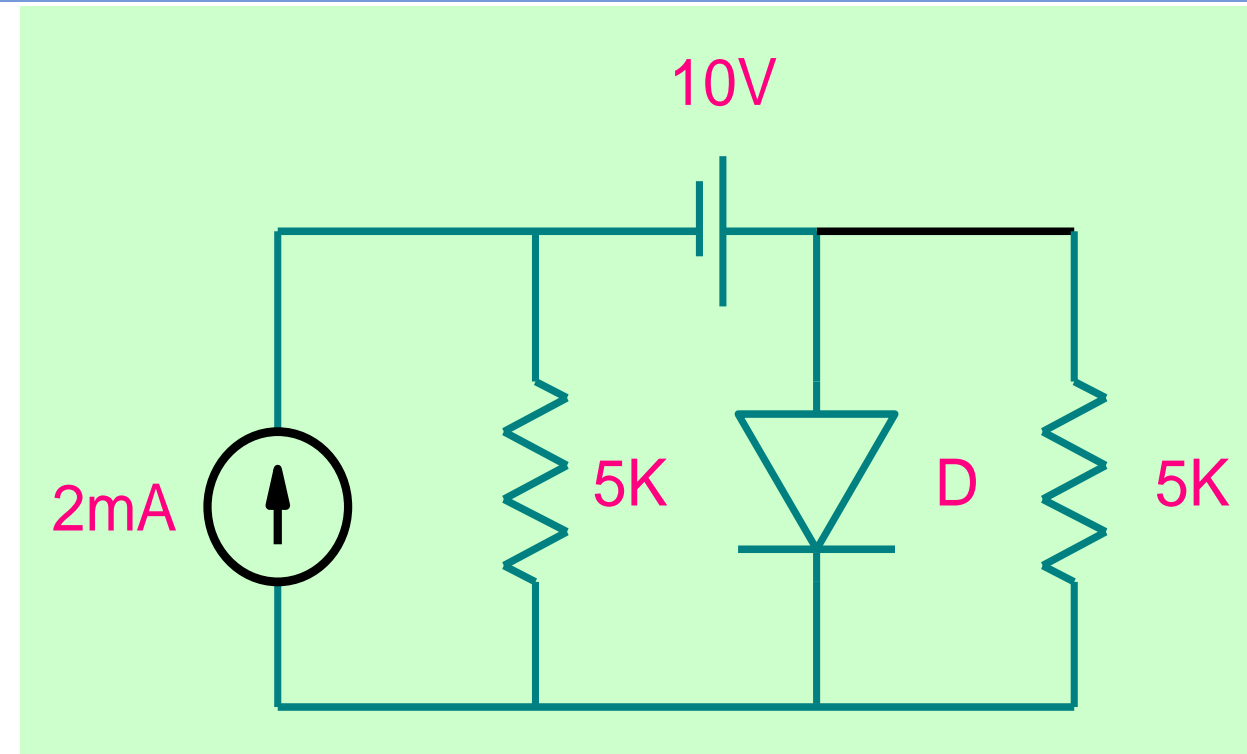



Example 2

Assume forward bias

$$-2mA + \frac{-10}{5K} + i_D = 0$$


$$i_D = 4mA$$

Current is positive, so our assumption is correct

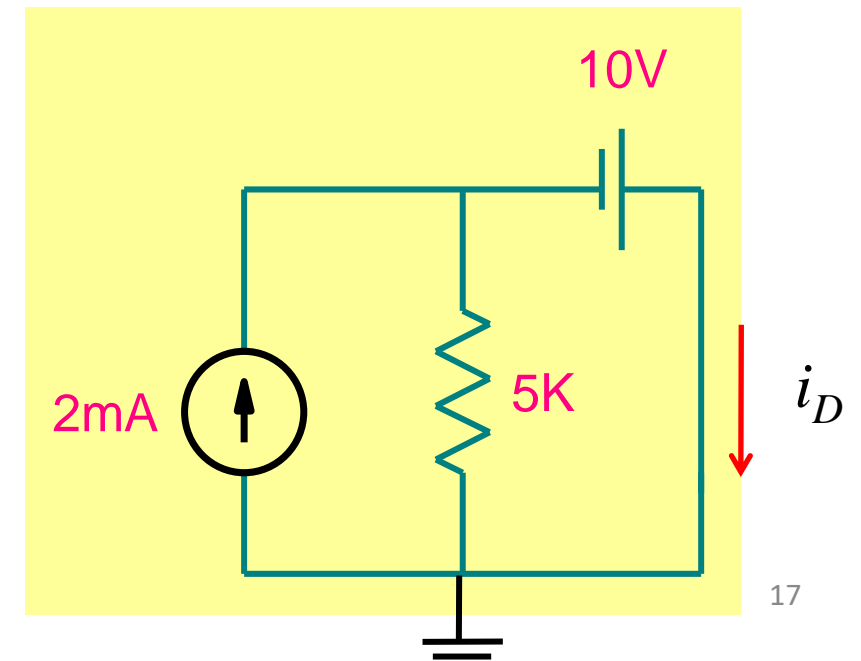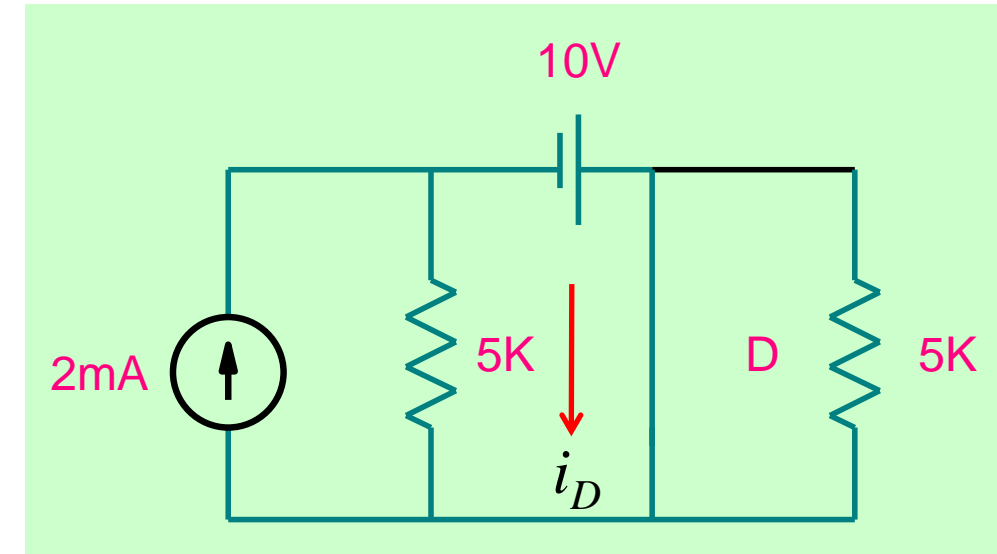


Example 3

Find the current through the 5k resistor using ideal diode model

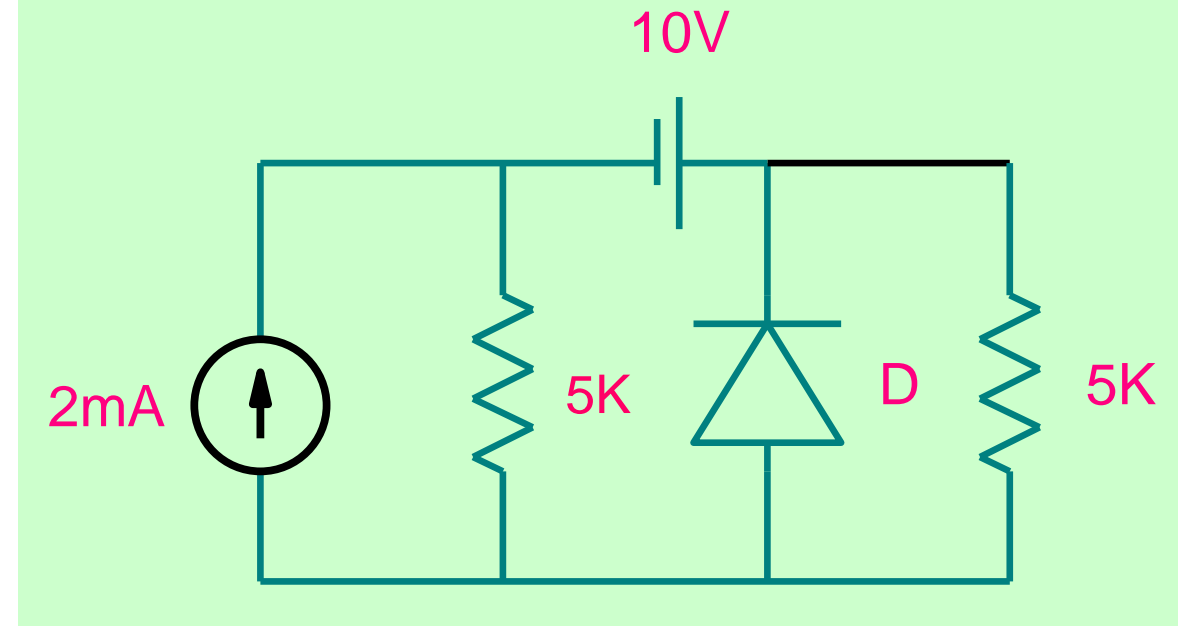


Example 3

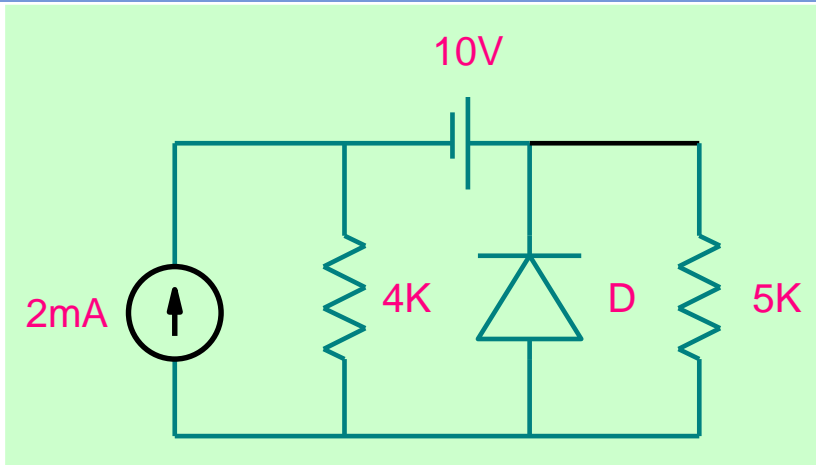

Assume forward bias


$$-2mA + \frac{-10}{5K} - i_D = 0$$

$$i_D = -4 \text{ mA}$$

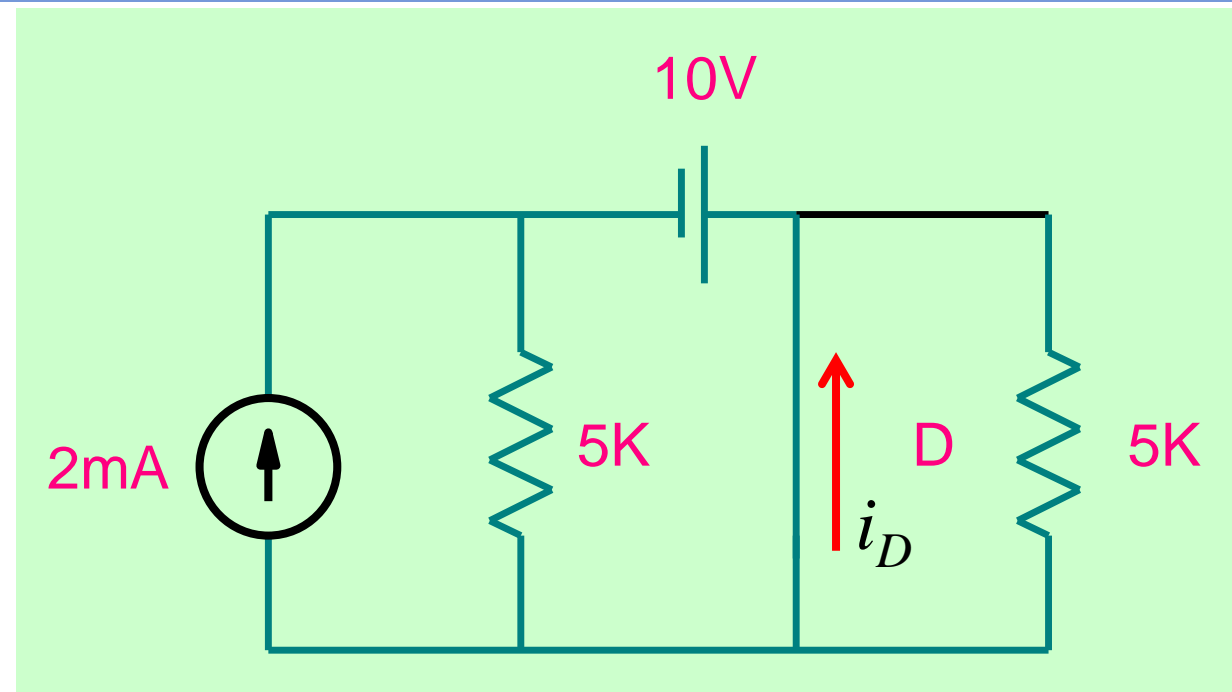

Therefore, our assumption is incorrect

Example

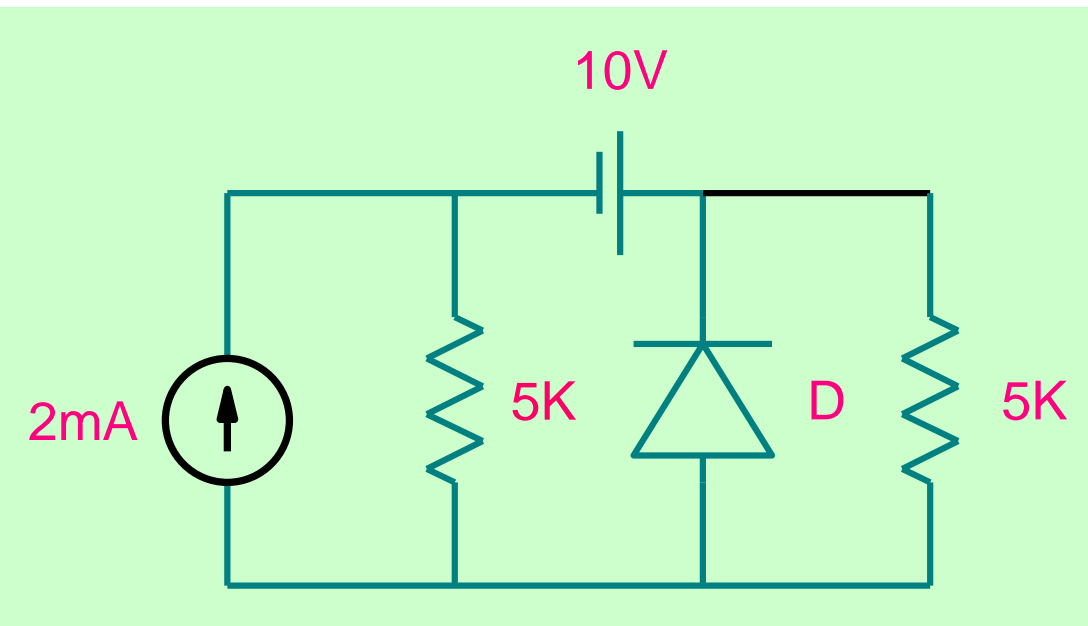


Assume reverse bias

$$-2mA + \frac{V_1}{5k} + \frac{V_1 + 10}{5k} = 0$$

$$V_1 = 0$$



$$V_2 = 10V$$

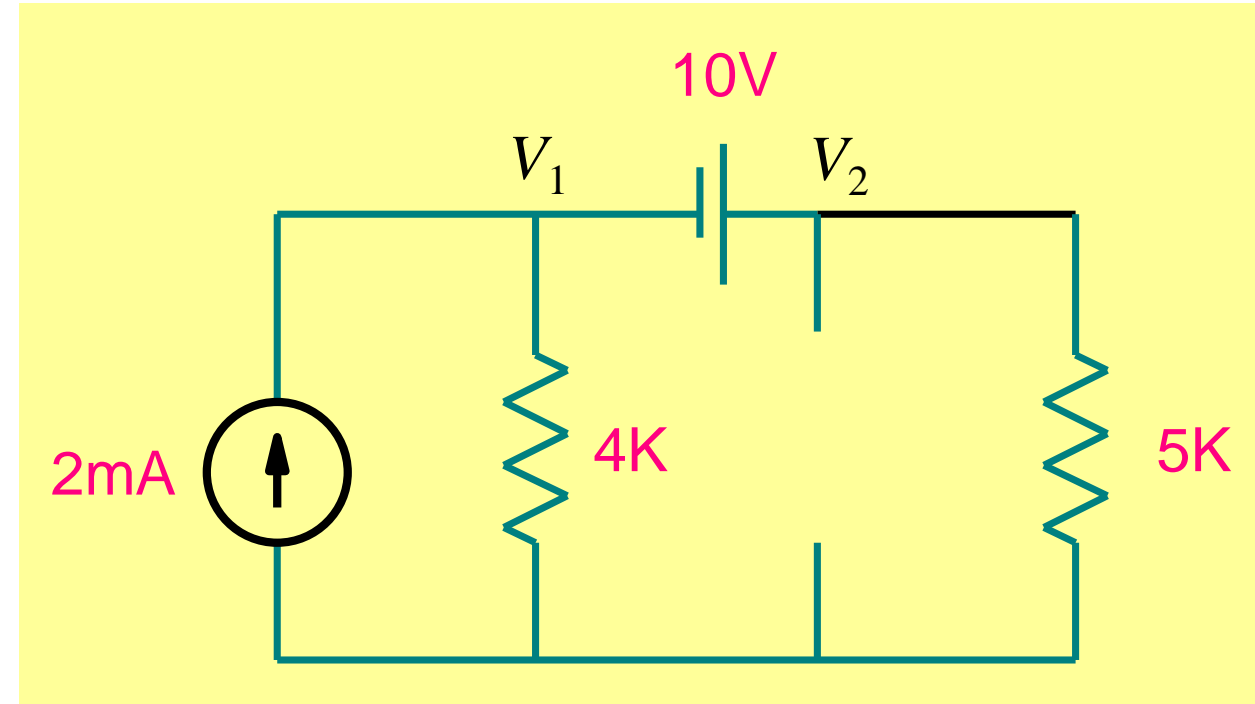


Therefore, our assumption is correct,

$$I_{5K} = 2A$$


DC power supply

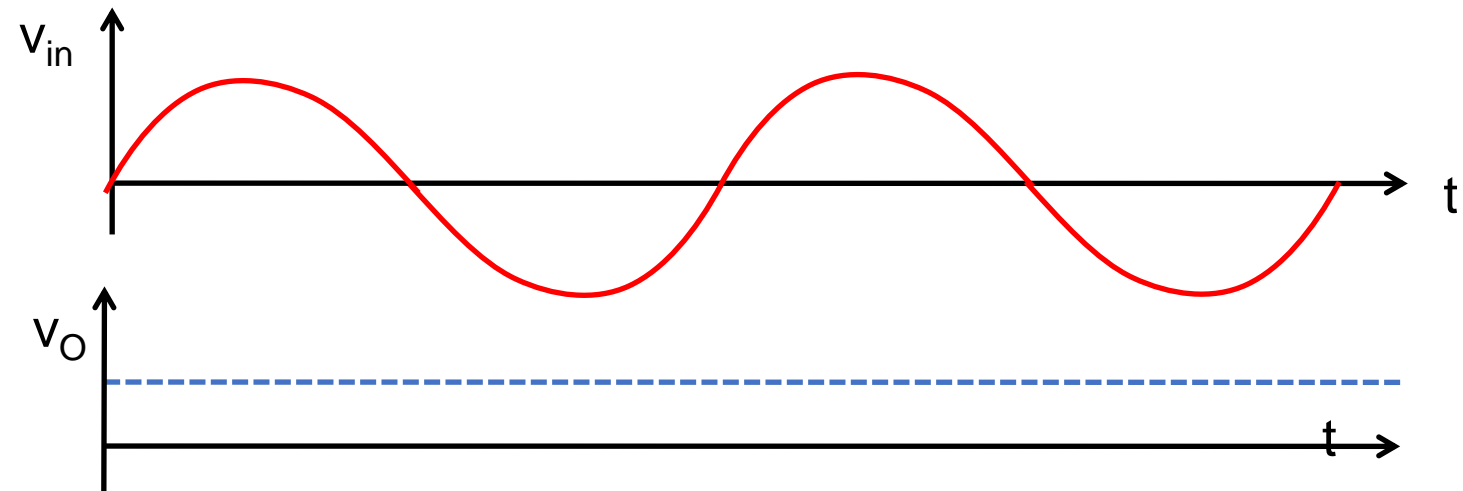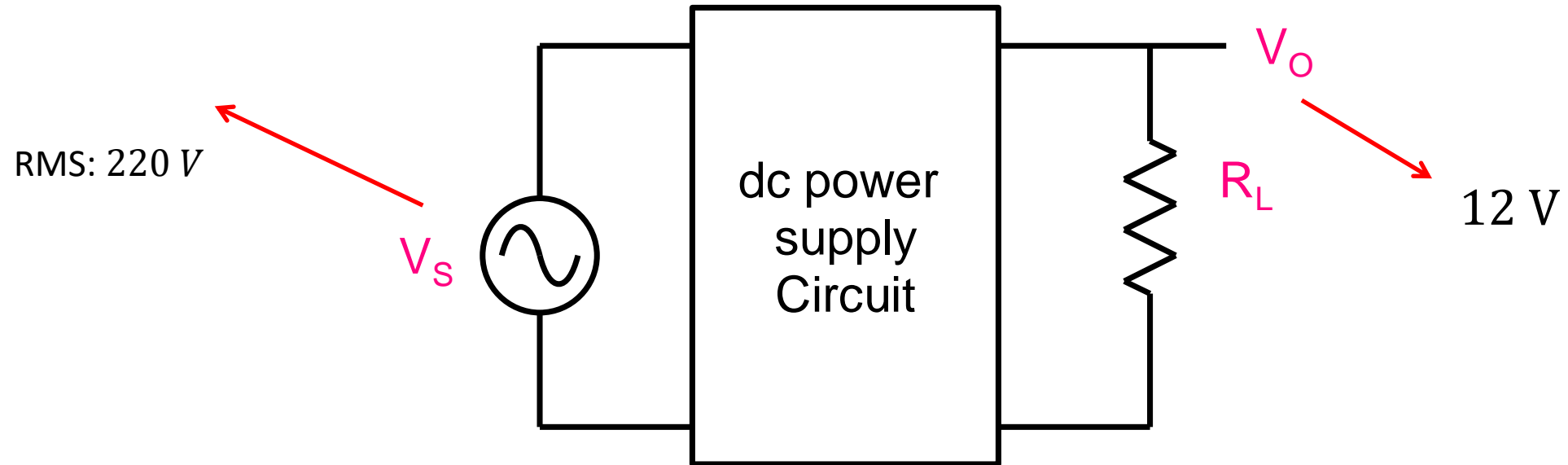


Strategy 1

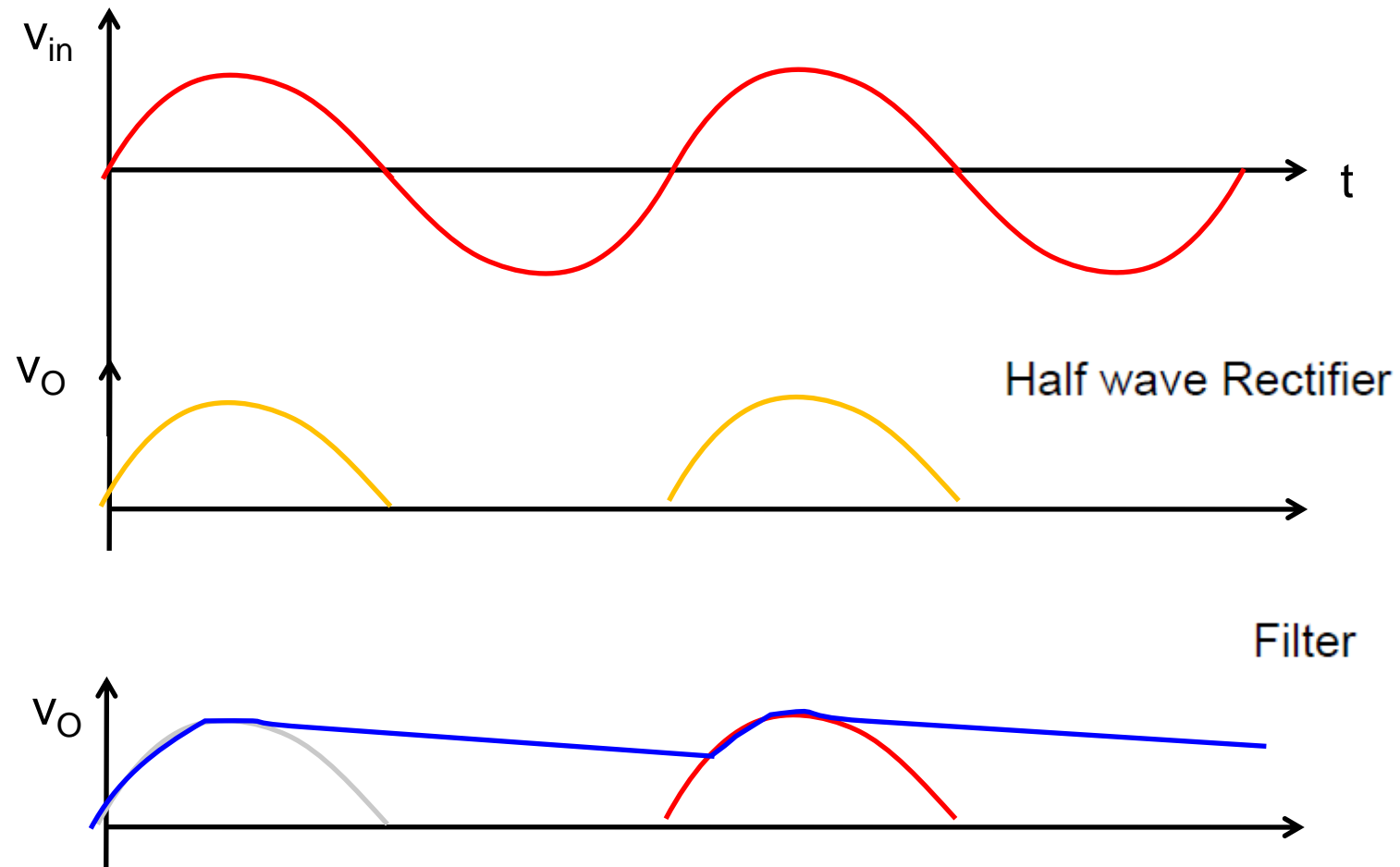

Power supply: block diagram

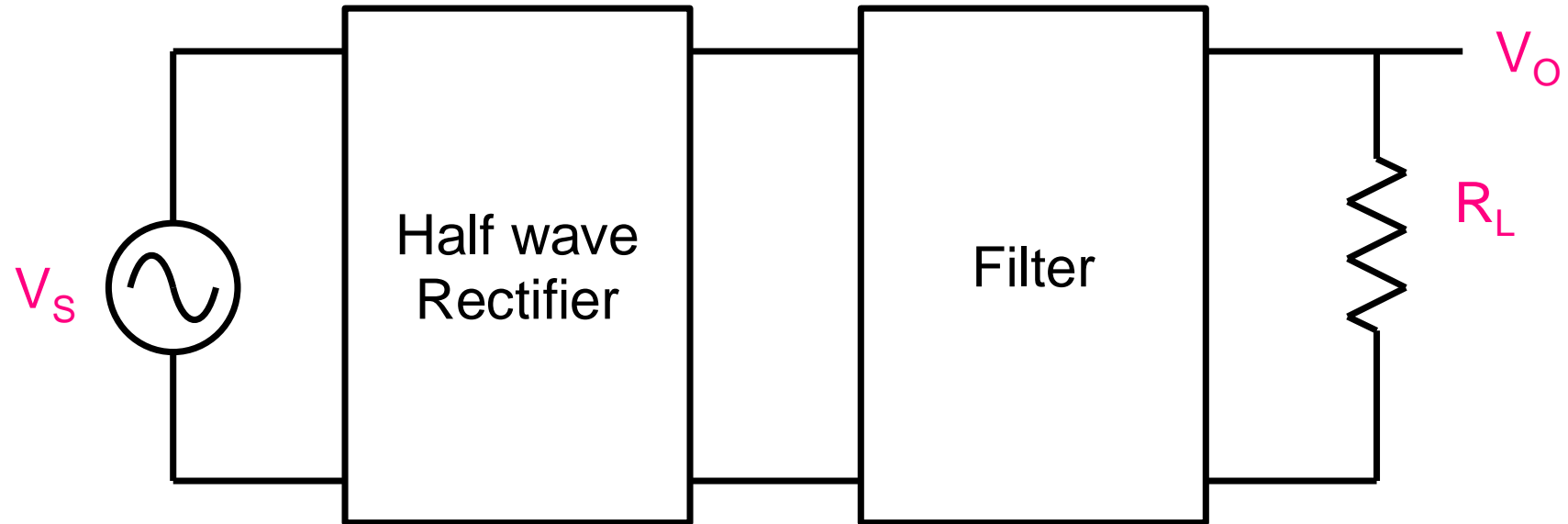


Half-wave rectifier

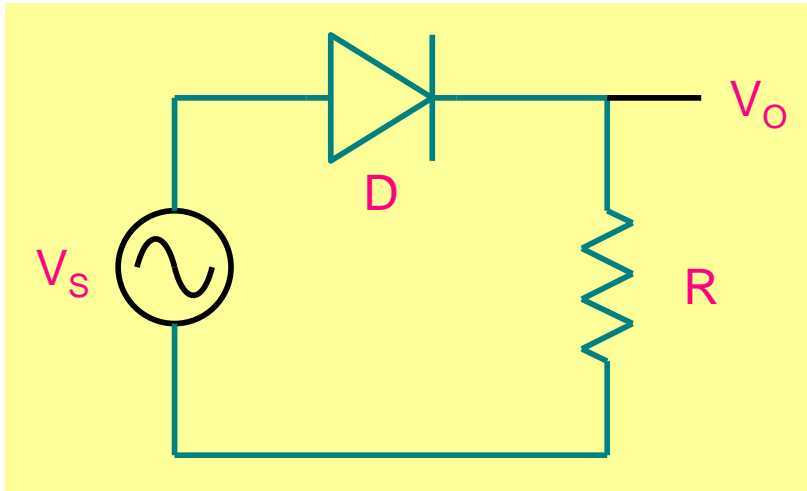

RMS: 220 V




Peak value: 311.13

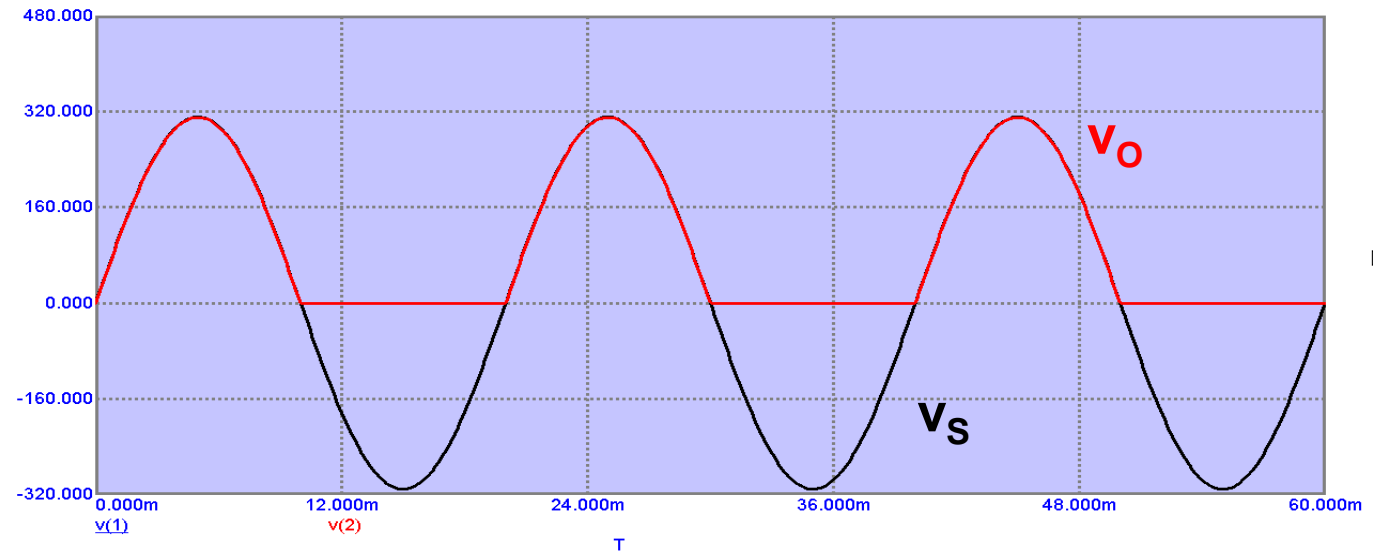

Peak value: $311.1 - 0.7 = 310.4 \text{ V}$

Voltage too high!



Half-wave rectifier

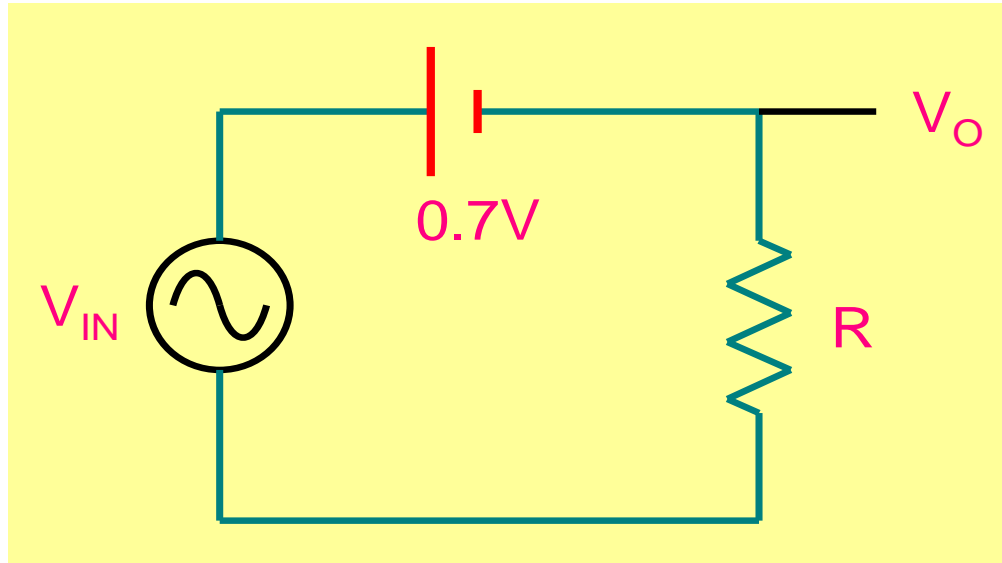

For V_O to be $12V$,
the input V_{IN} should be $\sim 12.7V$

$$\begin{aligned} V_s &= 220V \times \sqrt{2} \\ &= 311.127V \text{ peak value} \end{aligned}$$



Step-down transformer

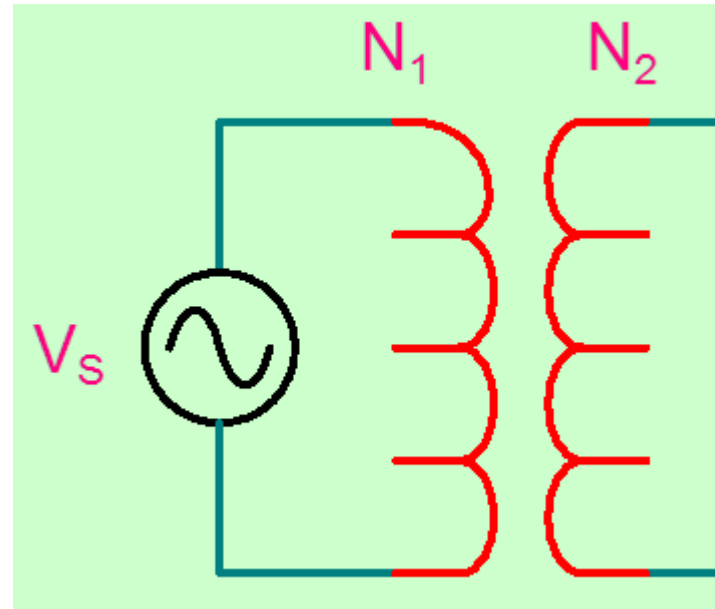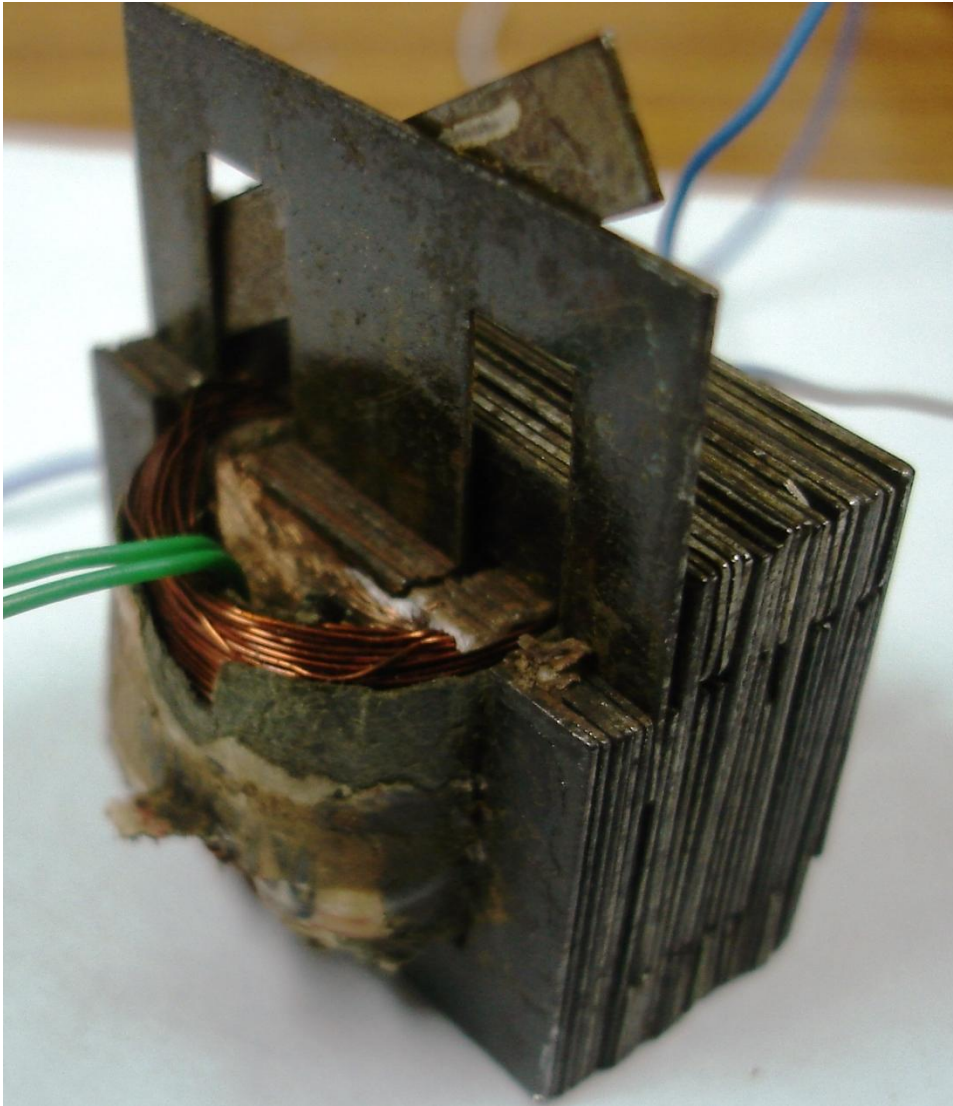

$$\frac{N_1}{N_2} = \frac{311}{12.7} = 24.5$$



$$\frac{V_s}{V_{IN}} = \frac{N_1}{N_2}$$

Step 1

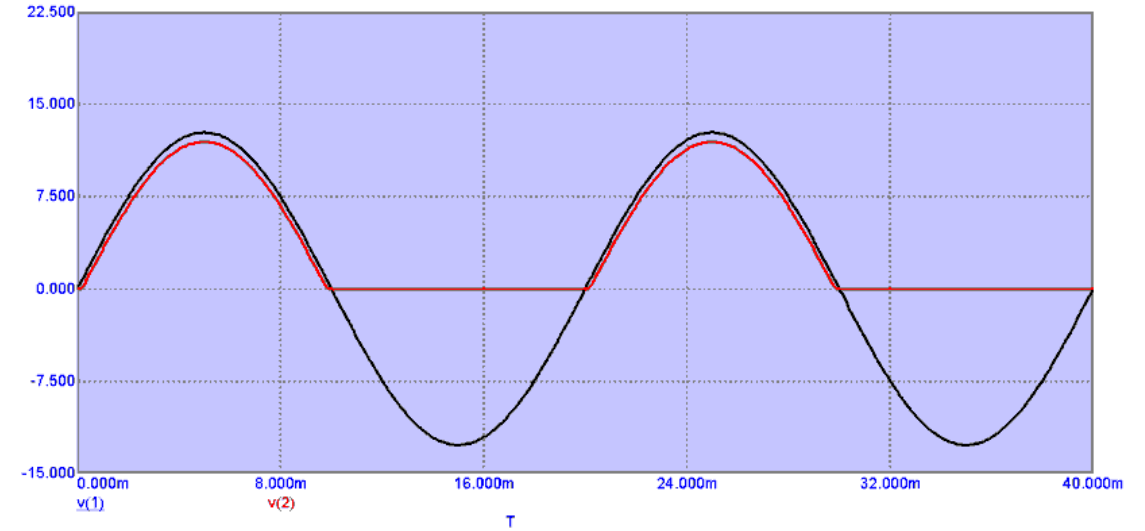
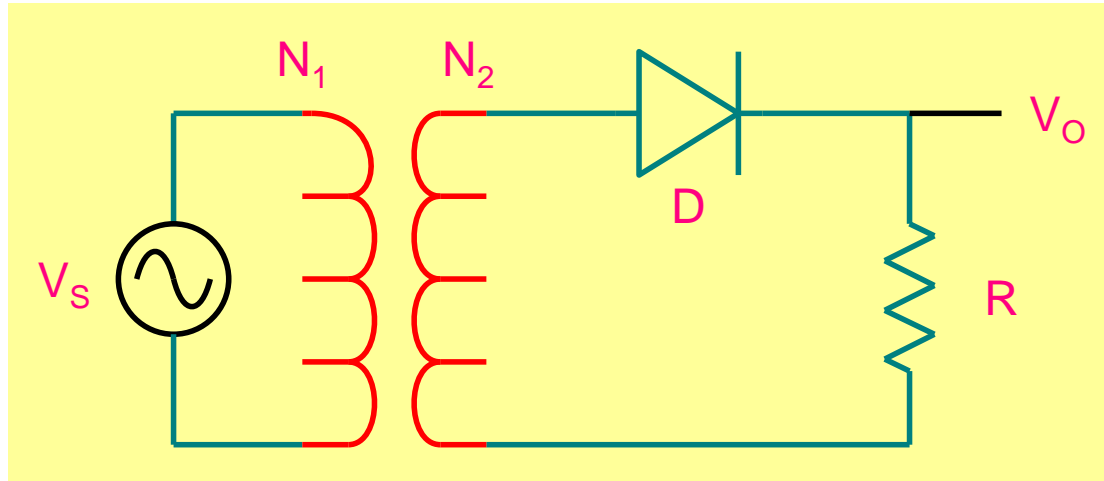


Want to hold that voltage during negative half cycle


Filtering

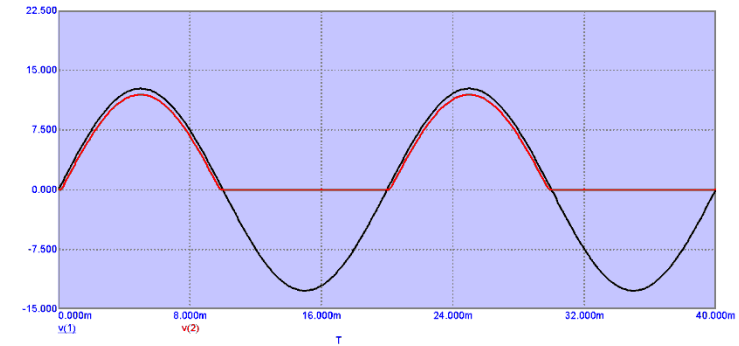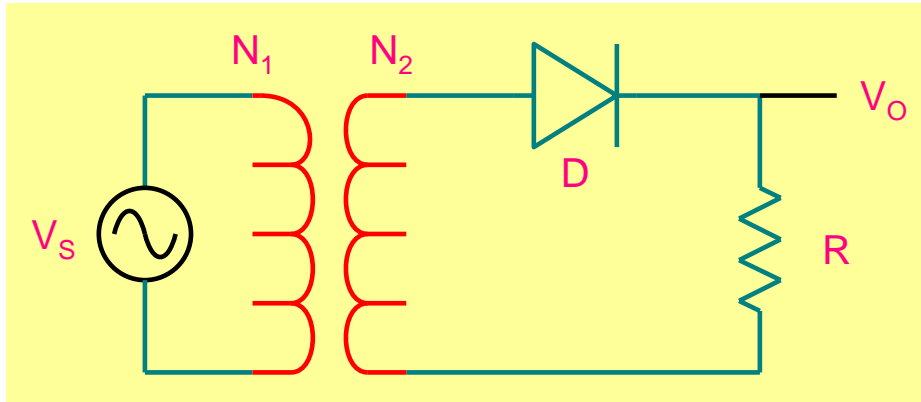

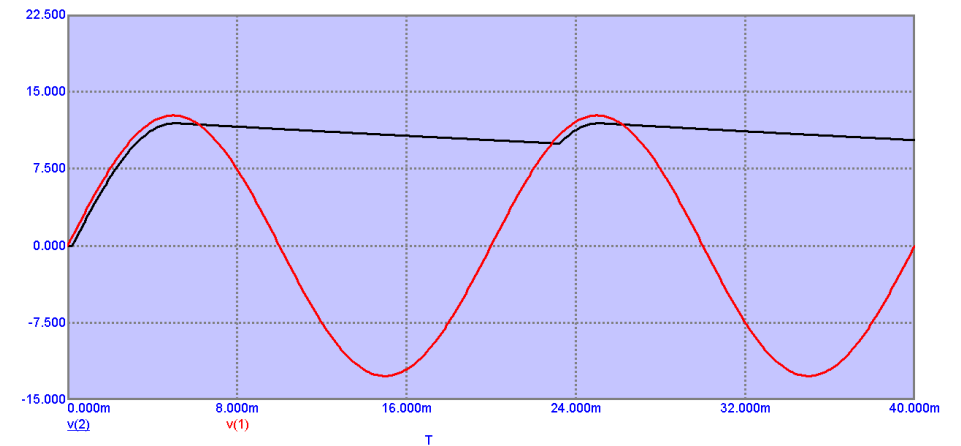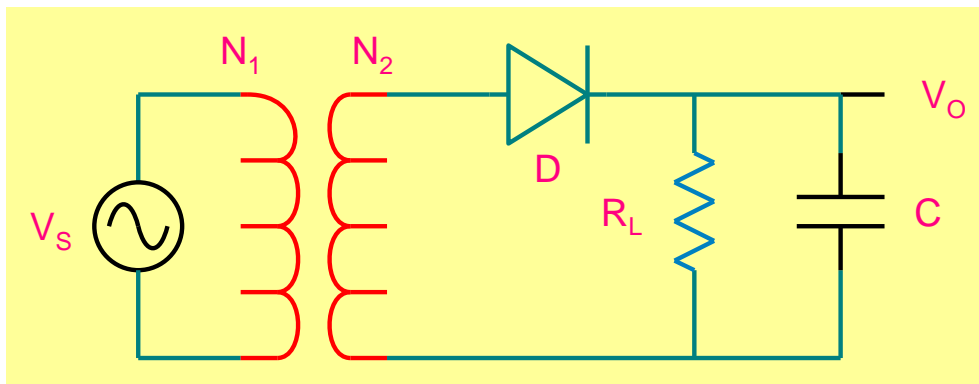
Want to hold that voltage during negative half cycle




Filtered output

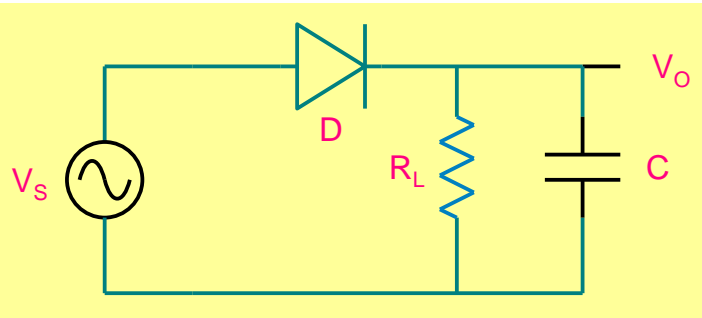


Diode is forward biased

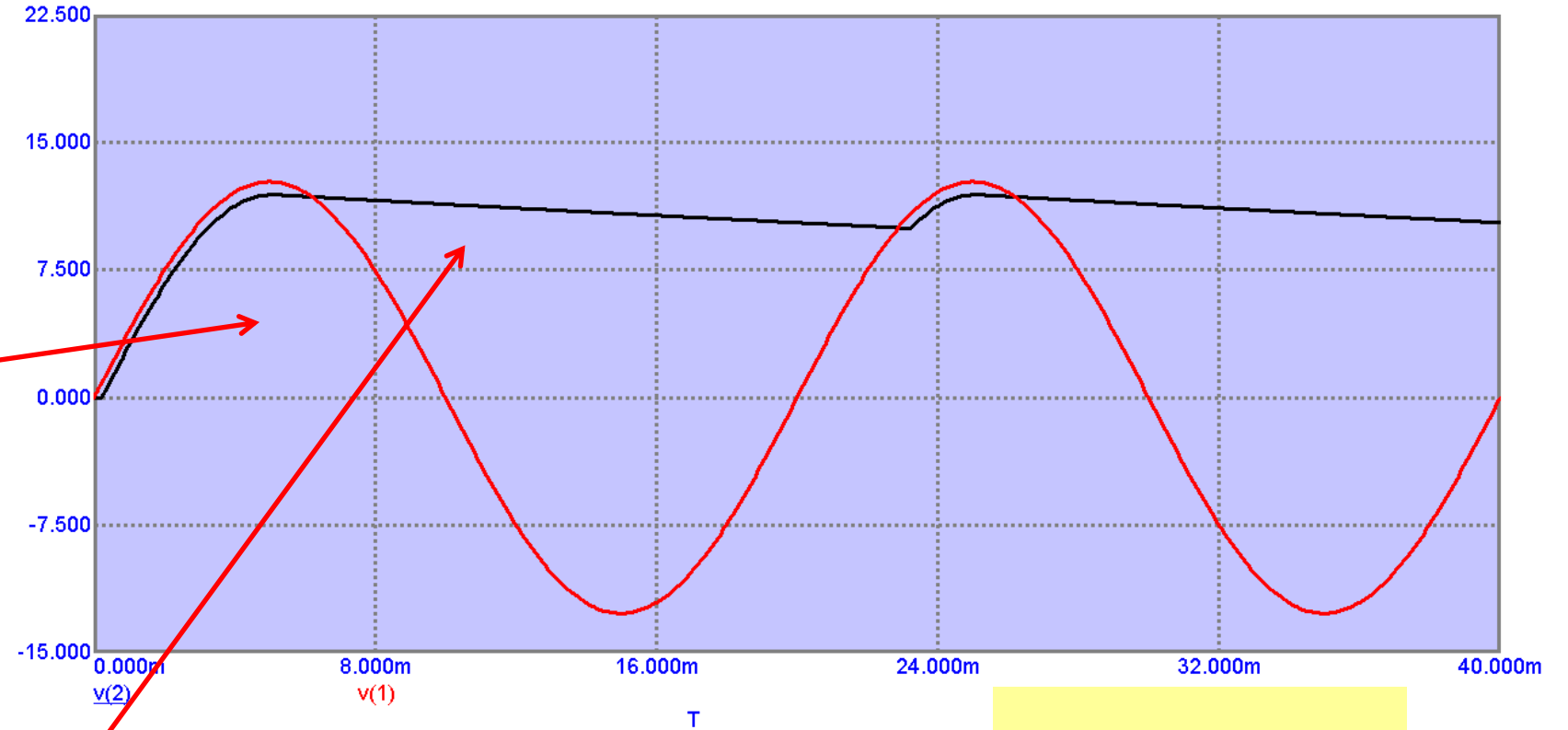

Diode is reverse biased

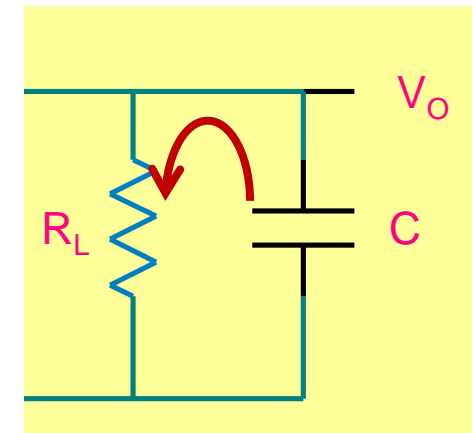



Output has a ripple

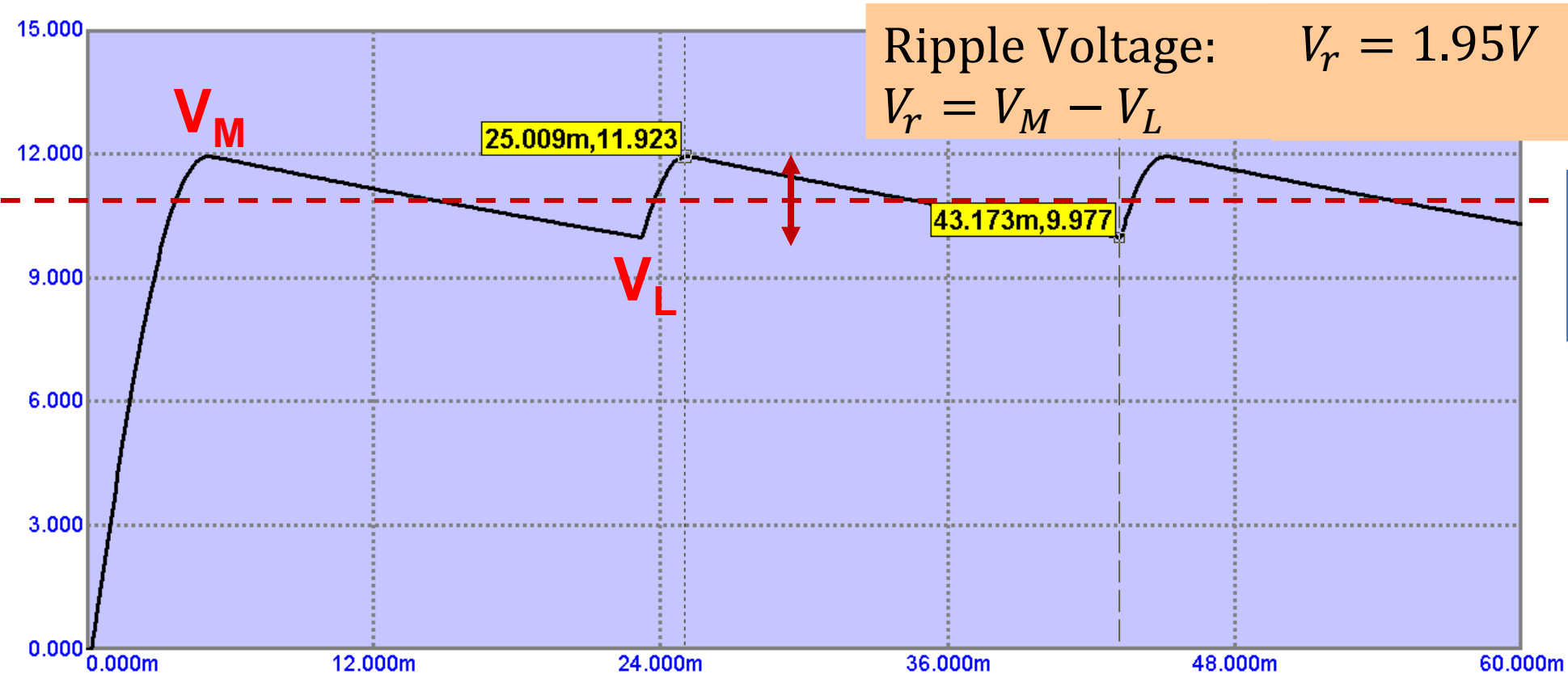

Average Output Voltage :

$$V_O(avg) \cong V_M - \frac{V_R}{2}$$

Approximate ripple calculation

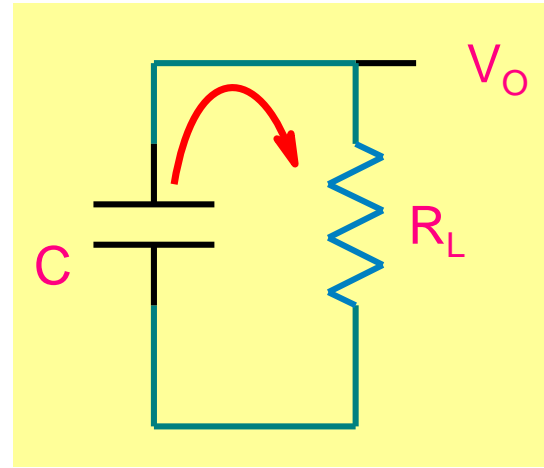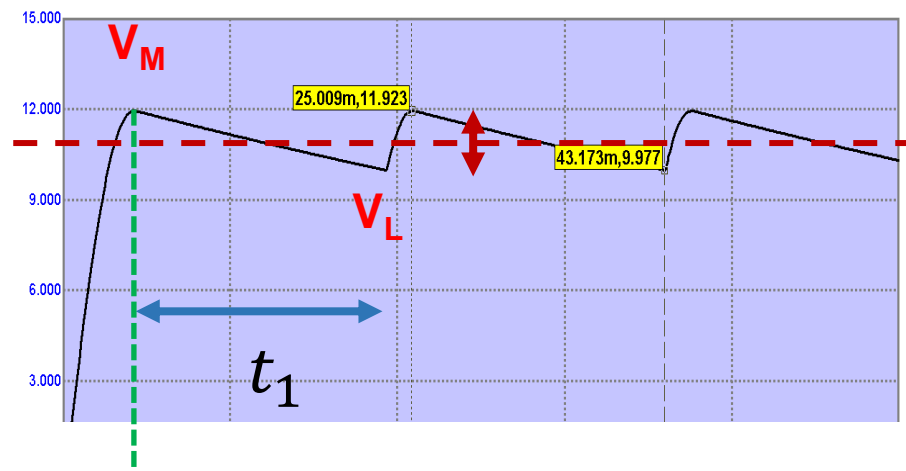

Ripple Voltage:
 $V_r = V_M - V_L$

$$V_r = V_M \times \left(1 - e^{-\frac{t_1}{R_L C}}\right)$$

Design circuit such
 that $t_1 \ll R_L C$

$$\begin{aligned} V_r &\cong V_M \times \left\{1 - \left(1 - \frac{t_1}{R_L C}\right)\right\} \\ &= \frac{V_M t_1}{R_L C} \end{aligned}$$

$$t_1 \approx T$$

$$V_r \approx \frac{V_M T}{R_L C}$$

- Capacitor discharges from V_M to V_L
- Recall: $v_C(t) = v_C(\infty) + (v_C(0^+) - v_C(\infty))e^{-\frac{t}{RC}}$

$$v_C(t) = V_M e^{-\frac{t}{RC}}$$

- Suppose it discharges for time t_1

$$V_L = V_M \times e^{-\frac{t_1}{R_L C}}$$