

ESC201: INTRODUCTION TO ELECTRONICS



MODULE 6: DIGITAL CIRCUITS





Dr. Shubham Sahay,
Associate Professor,
Department of Electrical Engineering,
IIT Kanpur

Combining Switches


N-MOSFET (positive) switches

  



P-MOSFET (negative) switches

  


Inverters or NOT Gate

 

$$F = A^{-}$$

  

A popular solution:
CMOS inverter

 


V_{in} and V_{out} are analogue values of input and output voltage

A and B are Boolean values of input and output.

Popular Two Input Universal Gates


NAND

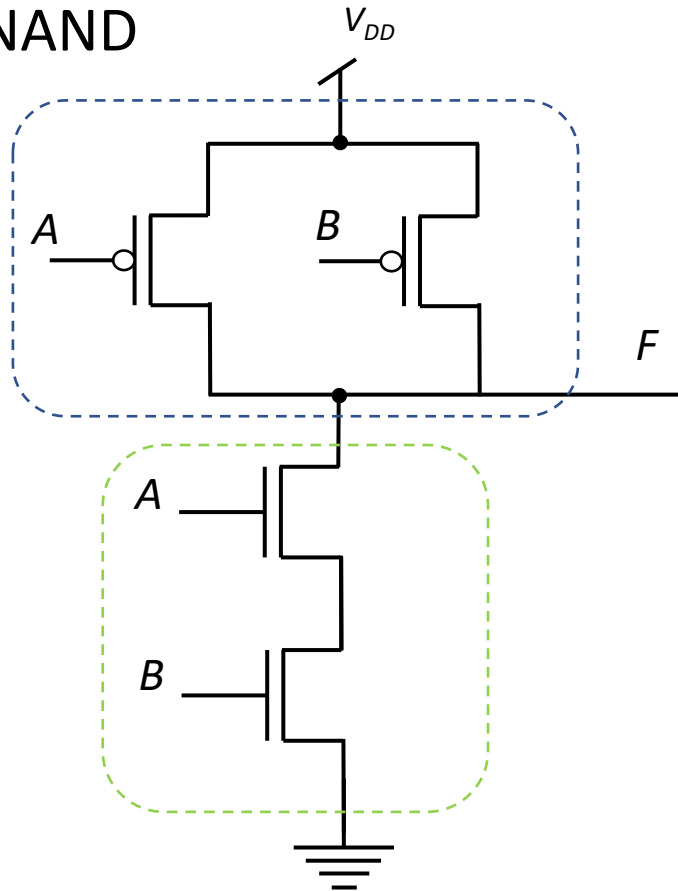

Two input NAND Gate

$$F = \overline{A \cdot B} = \overline{A} + \overline{B}$$


NOR

 

Two input NOR Gate

$$F = \overline{A + B} = \overline{A} \cdot \overline{B}$$

Combinational Logic

 

$$v_{outi} = f_i(v_{in1}, v_{in2}, \dots, v_{inN}) \text{ for } i = 1 \text{ to } M$$

Here the f_i 's are Boolean functions


The functions are typically built with logic gates

Any circuit that implements a combinational logic is a combinational circuit.


There are many popular methods to implement Combinational circuits

- Complementary CMOS design
- Pseudo n-MOS or Pseudo p-MOS design
- Pass-transistor logic design
- Dynamic circuit design
- ...
- Spintronic circuits
- Neuromorphic Computing

CMOS Inverter

 

Complementary CMOS Circuit

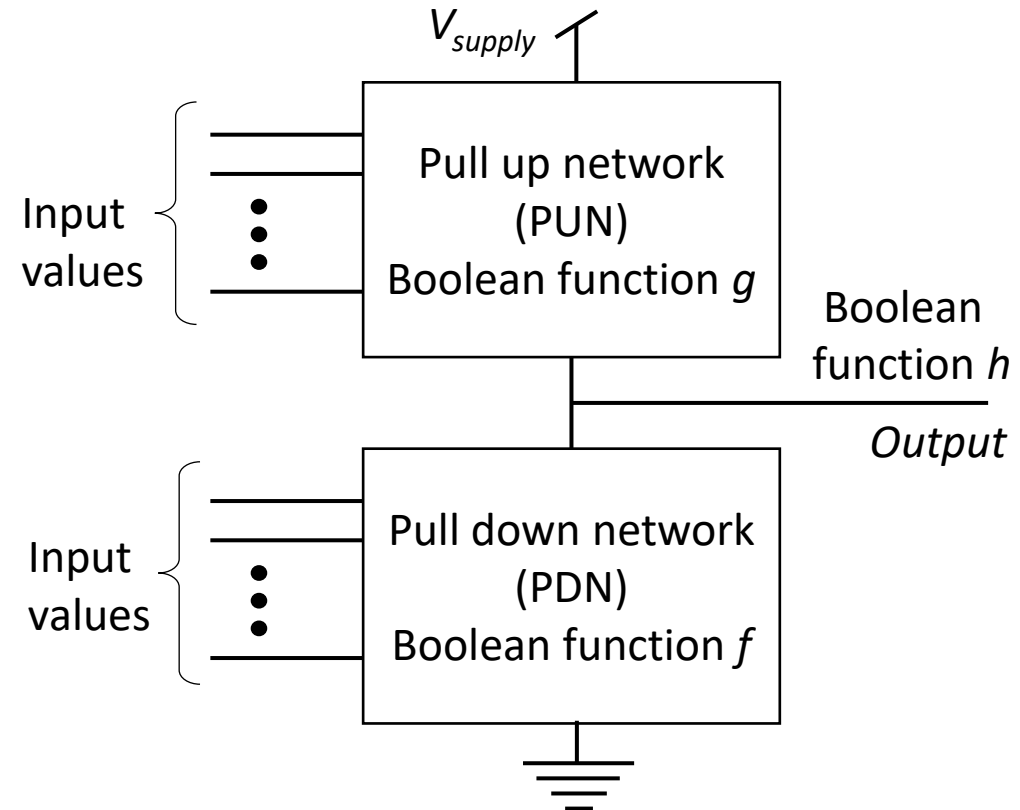


Boolean functions g and f are complements of each other for all input combinations.
Why? Because you don't want V_{DD} and GND to 'fight' over the output node.

Boolean function $h = g = f$ $\overline{}$


Multi Input NAND or NOR

N input NAND Gate

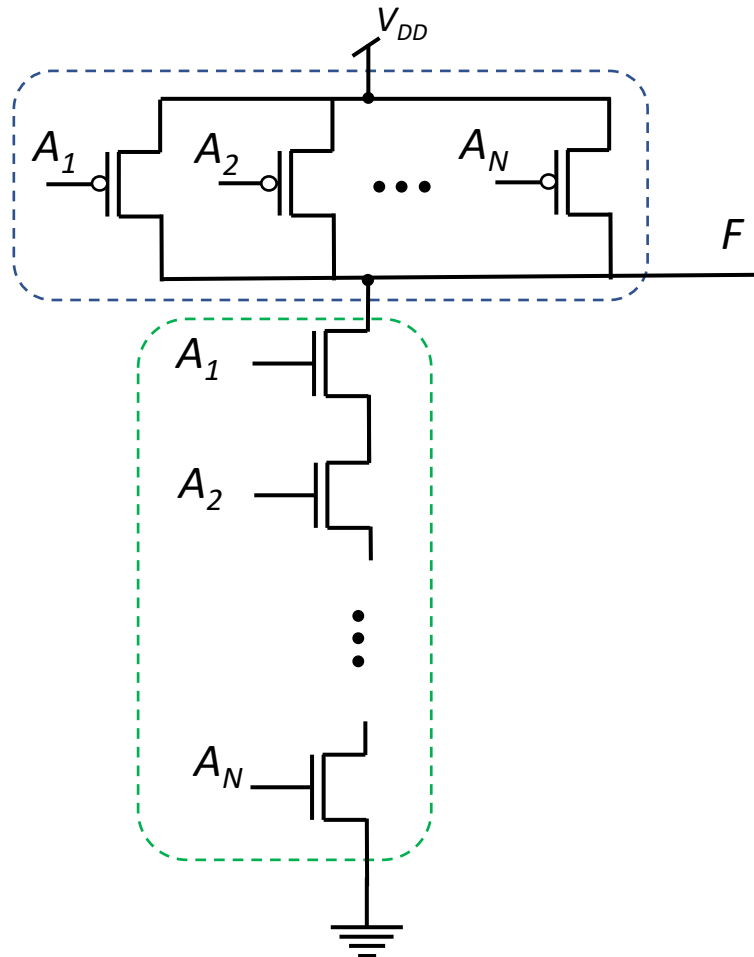

$$F = \overline{A_1 \cdot A_2 \cdot \dots \cdot A_N} = \overline{A_1} + \overline{A_2} + \dots + \overline{A_N}$$


N input NOR Gate

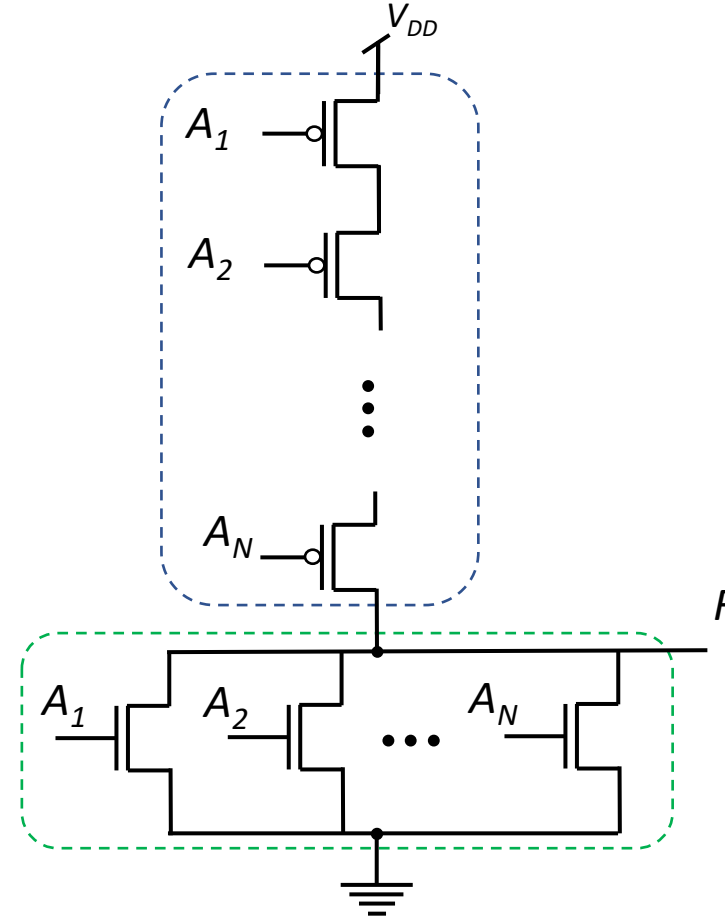

$$F = \overline{A_1 + A_2 + \dots + A_N} = \overline{A_1} \cdot \overline{A_2} \cdot \dots \cdot \overline{A_N}$$

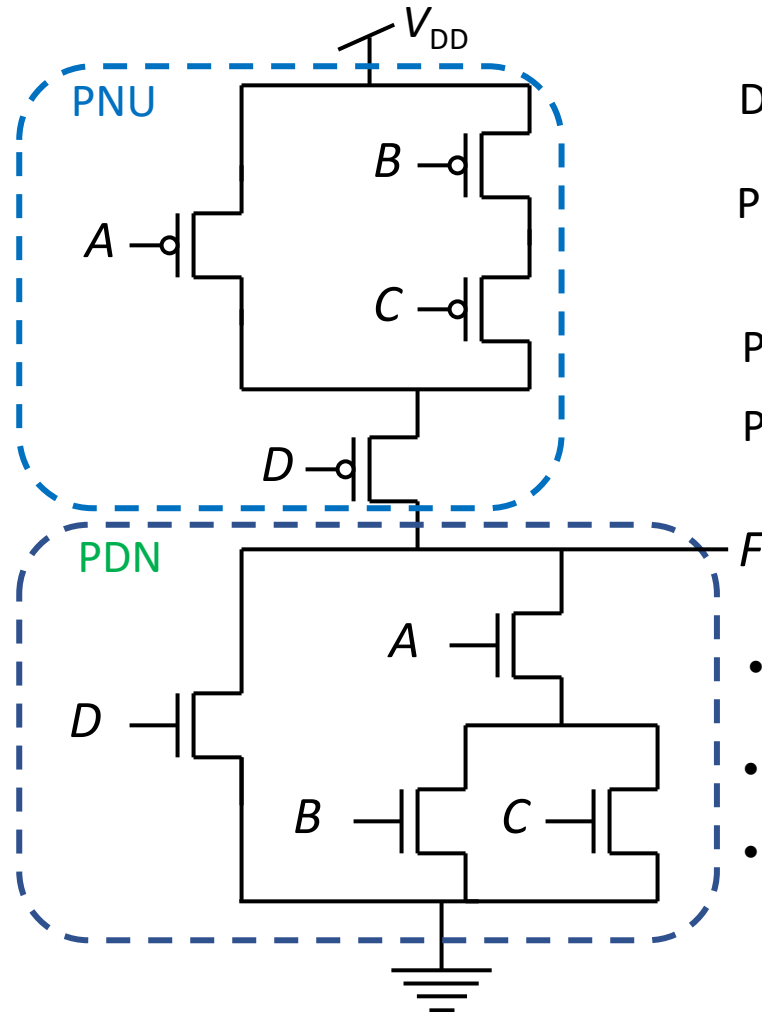Example

Implement the function $F = \overline{D + A \cdot (B + C)}$ as a complementary CMOS circuit



Design PDN function $g = F = \overline{D + A \cdot (B + C)}$


PUN function $h = F = D \cdot (\overline{A} + \overline{B} \cdot \overline{C})$

PDN are nMOSFET → Positive switches

PUN are pMOSFET → Negative switches

- PUN function is complement of PDN function
- What is in series in PDN is in parallel in PUN.
- What is in parallel in PDN is in series in PUN.

Useful Circuit Blocks

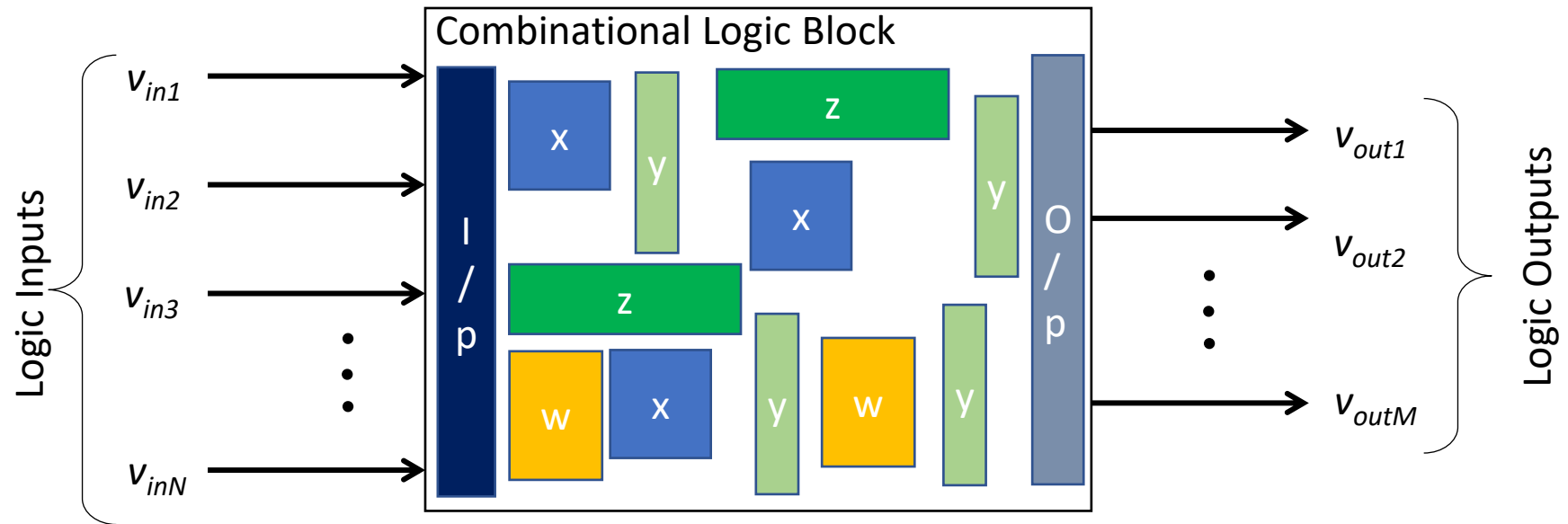


Build the larger circuit by using many smaller combinational logic functional blocks.


MUX, DeMUX, Encoder, Decoder, ... adder, subtractor, multiplier, ... and so on.

Only in special situations will one want to re-design to optimise the integrated block.


Decoder

 


Encoder

 

Multiplexer (MUX)

 


Demultiplexer (DeMUX)

 

Decoder


2-to-4 Line Decoder

 Maps a smaller number of inputs to a larger set of outputs in general



B	A	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Active High


 


b	a	Y_0	Y_1	Y_2	Y_3
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Active Low


Decoder

Decoder Interprets Coded Data

  


Decoder

Decoder with Enable Input

 


E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
1	x	x	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1


Decoder

Decoder Gate Implementation

 

E	B	A	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
 
$$Y_0 = E \cdot \bar{B} \cdot \bar{A} ; Y_1 = E \cdot \bar{B} \cdot A ; Y_2 = E \cdot B \cdot \bar{A} ; Y_3 = E \cdot B \cdot A$$



A n to 2^n decoder is a minterm generator

By selecting the min-terms, one may implement a truth table function!