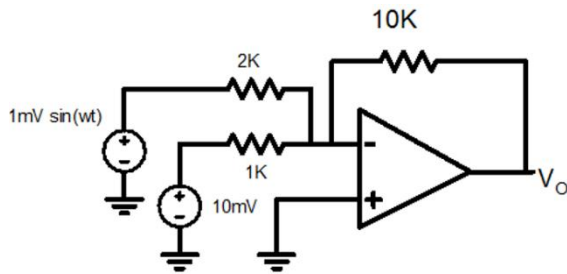


1. Determine the output of the ideal op-amp circuits shown below.


i.



$$v_o = -\left\{\frac{10K}{1K} \times 10mV + \frac{10K}{2K} \times 1mV \sin(\omega t)\right\}$$

$$= -\{0.1 + 5 \times 10^{-3} \sin(\omega t)\}$$


ii.

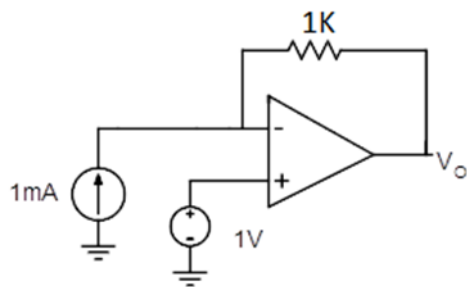

$$v_+ = v_- = 1V$$


$$\frac{1 - v_o}{1K} = 1mA \quad v_o = 0V$$

iii.

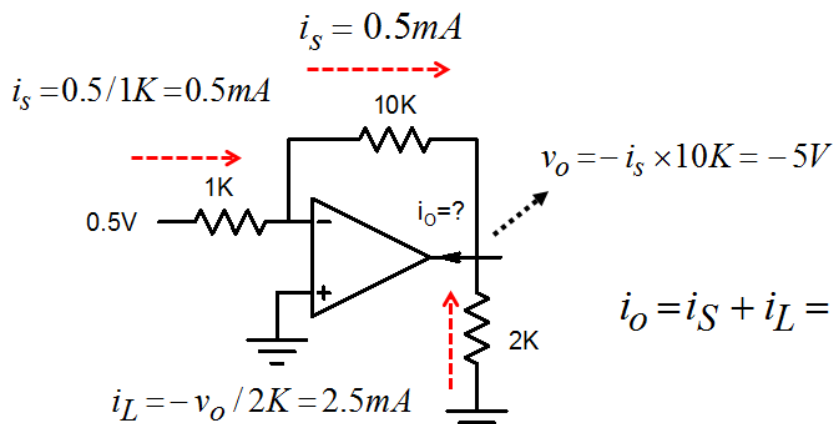


$$i_o = i_s + i_L = 3mA$$

iv.

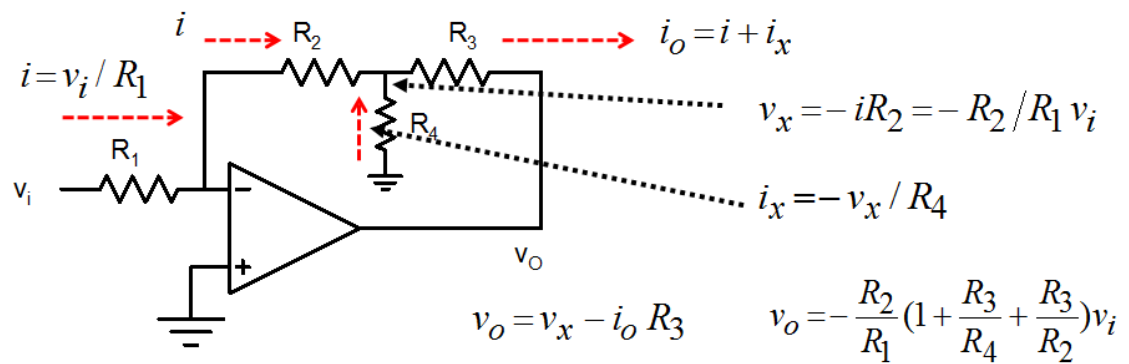

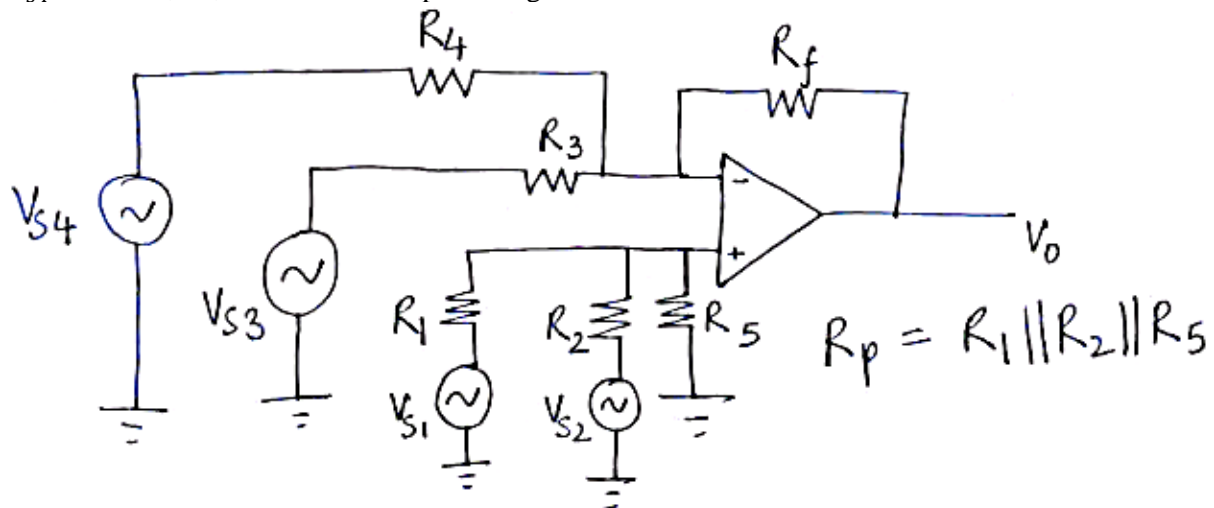2. Design an op-amp circuit that would generate the following output voltage $V_o = 2v_{s1} + 4v_{s2} - 8v_{s3} - 10v_{s4}$ where v_{s1} , v_{s2} , v_{s3} and v_{s4} are input voltages.



$$V_0 = -\left(\frac{R_f}{R_3}\right)V_{S3} - \left(\frac{R_f}{R_4}\right)V_{S4} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_p}{R_1} V_{S1} \\ + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_p}{R_2} V_{S2}$$

$$V_0 = 2V_{S1} + 4V_{S2} - 8V_{S3} - 10V_{S4}$$

$$\text{Let } R_f = 10K$$

$$\therefore \frac{R_f}{R_3} = 8$$

$$\frac{10K}{R_3} = 8 \Rightarrow R_3 = 1.25k\Omega$$

$$\frac{R_f}{R_4} = 10$$

$$\therefore \frac{10K}{R_4} = 10 \Rightarrow R_4 = 1k\Omega$$

$$\frac{R_f}{R_3 \parallel R_4} \times \frac{R_p}{R_1} = 2 \Rightarrow \frac{10K}{(1.25k \parallel 1k)} \times \frac{R_p}{R_1} = 2$$

$$\Rightarrow \frac{R_p}{R_1} = 0.105$$


$$\frac{R_f}{R_3 \parallel R_4} \times \frac{R_p}{R_2} = 4 \Rightarrow \frac{10K}{(1.25k \parallel 1k)} \times \frac{R_p}{R_2} = 4$$

$$\Rightarrow \frac{R_p}{R_2} = 0.211$$


$$\frac{R_1}{R_p} \times \frac{R_p}{R_2} = \frac{1}{0.105} \times 0.211 \Rightarrow \frac{R_1}{R_2} = 2$$

$$\text{Let } R_2 = 1k\Omega \Rightarrow R_1 = 2k\Omega \Rightarrow R_p = 0.211k\Omega \\ \therefore R_5 = 0.308k\Omega$$

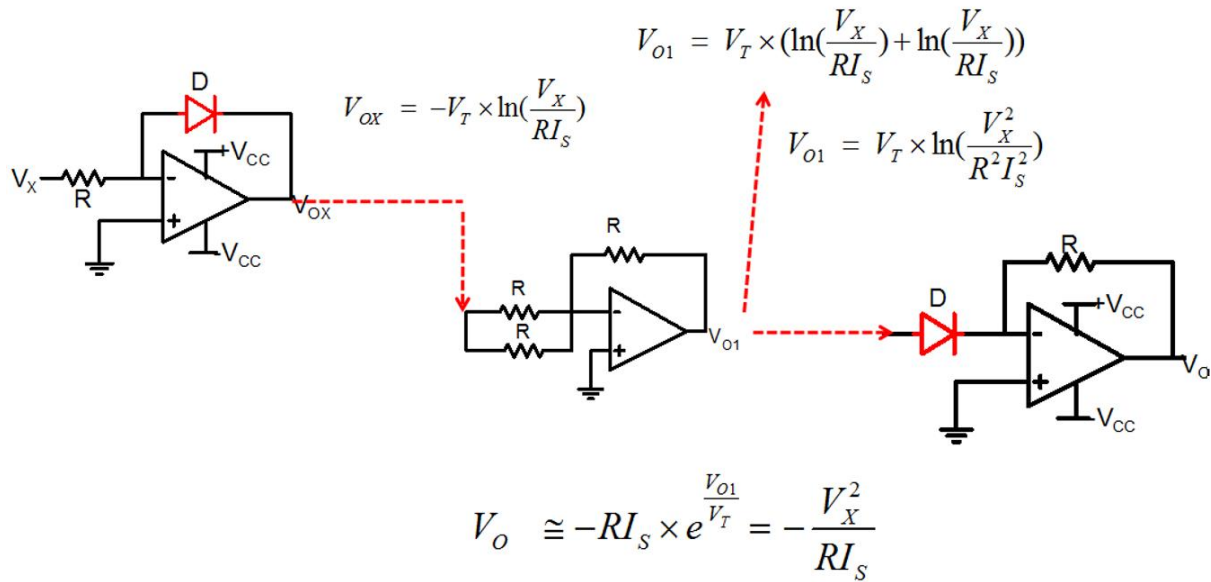3. Design an op-amp circuit that can produce $V_O = K \times V_{IN}^2$ where V_{in} is the input voltage.




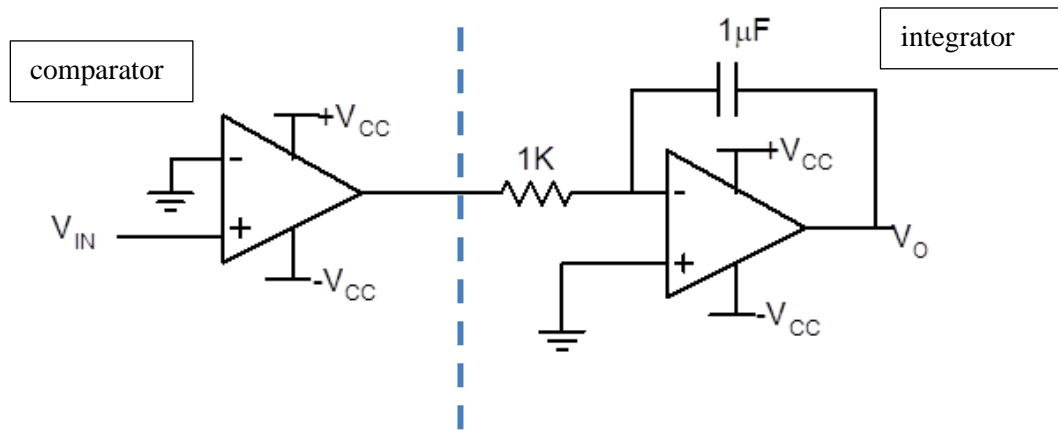4. Sketch the output voltage of the circuit shown below for $V_{in} = 1V \sin(2\pi ft)$; $f = 1KHz$ and supply voltages of $\pm 5V$



for the comparator,
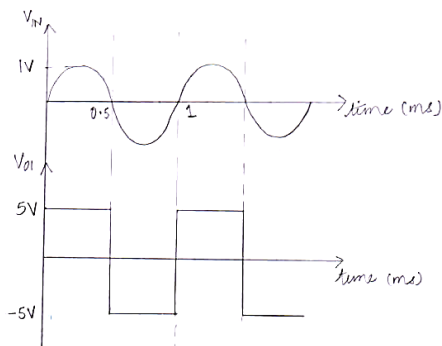
$$\begin{aligned}
 V_{O1} &= +5V \text{ if } V_{IN} > 0 \\
 &= -5V \text{ if } V_{IN} < 0
 \end{aligned}$$




for the integrator, $V_O(t) = -\frac{1}{RC} \int V_{O1} dt = -10^3 \int V_{O1} dt$


$$\text{for } V_{IN} > 0, V_O = -5 \times 10^3 \times t$$

$$\text{for } V_{IN} < 0, V_O = -2.5 + 5 \times 10^3 (t - 0.5 \text{ ms})$$
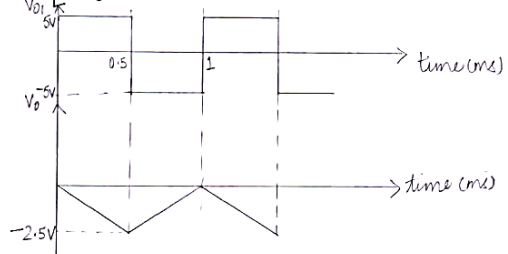
$$[\because V_O(t = 0.5 \text{ ms}) = -2.5 \text{ V}]$$



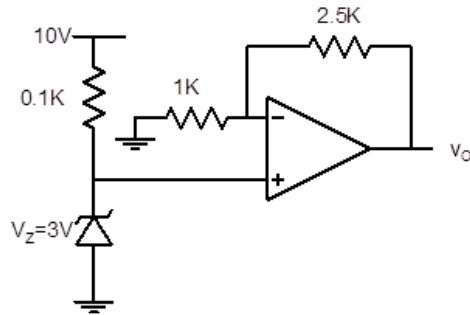5. Determine the output for the ideal op-amp circuit shown below.



this is a non-inverting amplifier with V_Z as input.


$$V_O = V_Z \left(1 + \frac{R_2}{R_1} \right)$$

$$\therefore V_O = 3 \left(1 + \frac{2.5}{1} \right) V$$

$$\Rightarrow V_O = 3(3.5) V$$

$$\Rightarrow V_O = 10.5 V$$

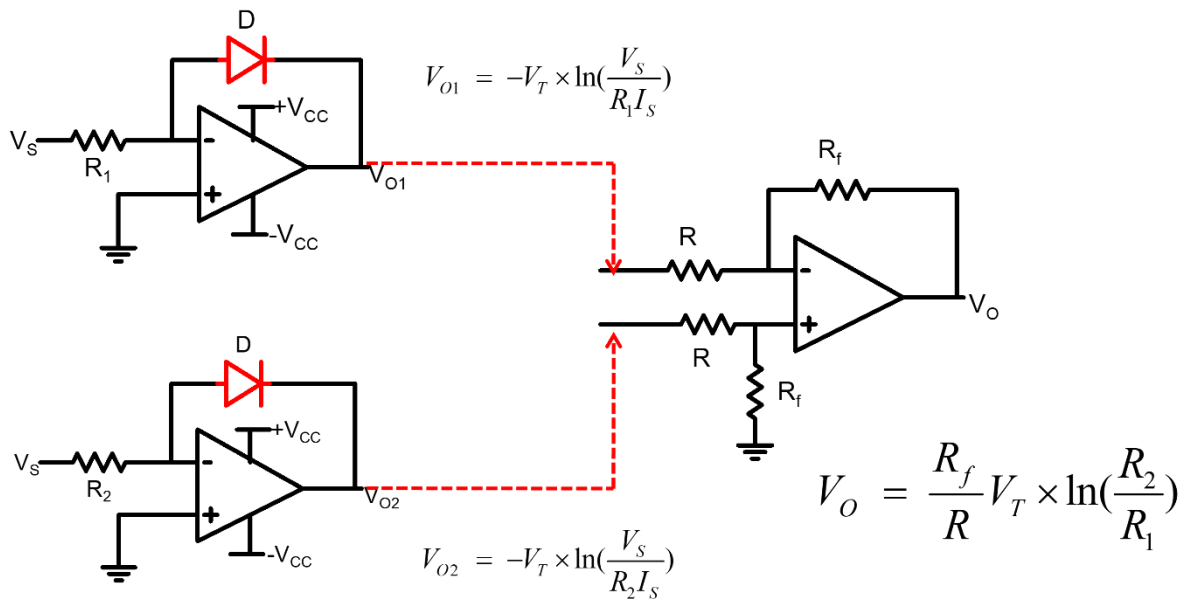6. Design a temperature sensor using a couple of OP-Amps and resistors.



Output voltage is directly proportional to temperature